

FULL LIST: NEW RADIO AND TV FREQUENCIES



## Just for the record The Little River Band tapes with **Ampex**

In top recording studios throughout the world, the professionals entrust original master recordings to Ampex tape.

Equally at home with our uncompromising artists is this same performance in studio quality cassettes and tapes, now available from selected hi-fi stores and retailers. If it's worth taping—it's worth Ampex.





Ampex Australia Pty Limited,

4 Carlotta Street, Artarmon. Phone (02) 439 4077

541 King Street, West Melbourne 3003 Phone (03) 329 0388

MPEX the professionals

# ELECTROMICS

Austrolio

VOL. 40 No. 10

**JANUARY, 1979** 

Australia's largest selling electronics & hi-fi magazine



Car stereo system lacking in power? This new booster amplifier is easy to build and will deliver 12 watts per channel. Full details on p38.

Our final article on the Playmaster AM-FM Tuner this month gives tips on reception, and includes a useful troubleshooting procedure. See p49.

#### On the cover



Our cover this month (and above) illustrates the growing uses of solar cells — from charging batteries on a yacht to powering an electric toothbrush! This month, our Reader Service Department is offering the solar panel shown in these pictures at an attractive price. See p19 & p61 for the details. (Pictures courtesy lan Carter Photography, Sydney.)

#### **FEATURES**

FUSION REACTORS: IN OUR FUTURE? A look at some of the problems	10
TV AUDIENCE TALKS BACK Watching viewers' reactions	14
TELECOM OPENS \$10m RESEARCH COMPLEX Updating our communication links	16
CONTROLLER RUNS 16 TRAINS ON ONE TRACK Bringing realism to model trains	18
SENSOR TECH'S SOLAR ARRAYS NOW IN AUSTRALIA Special offer to EA readers.	61
AUSTRALIAN AND NZ BROADCASTING SERVICES List of radio and TV stations	92
The state of the s	32
HIFI NEWS AND REVIEWS	
THE THE MENTERO	
20,000 MASTERS: PORTRAIT OF A DISC RECORDING ENGINEER	27
REFURBISHING A BRAND IMAGE Portrait of a hifi executive	30
REVIEW: TECHNICS SA-400 STEREO RECEIVER 3-page in-depth review	
PROJECTS AND CIRCUITS	
POWER BOOSTER FOR CAR STEREOS Easy to build, 12 watts per channel	38
UNIVERSAL TACHO USES HT PICKUP For all kinds of ignition systems	44
PLAYMASTER AM-FM STEREO TUNER PT.3 Useful troubleshooting guide	49
DIRECT READING CAPACITANCE METER Measures values from 1 pF to 5 uF	- 56
AUDIO IMPEDANCE METER PT.2 Second article gives the construction details	66
A LOW COST PRINTER FOR YOUR 2650 How to use the Matsushita modules	74
CALCULATOR CHART FOR HEX DISPLACEMENTS Easy-to-use lookup table	
EXIDY'S SORCERER MICROCOMPUTER 8k BASIC, user-programmed graphics	82
AMATEUR RADIO OR COTHE DV	
AMATEUR RADIO, CB SCENE, DX	
OR COPNE, ORVOTALO OVNITUEOICERO & THE RHACE LOOVER LOOP BTO	00
CB SCENE: CRYSTALS, SYNTHESISERS & THE PHASE-LOCKED LOOP PT.2	96
AMATEUR RADIO Wireless Institute educational service report	
SHORTWAVE SCENE More frequencies and restricted power predicted	
SHORT VANE SCENE More frequencies and restricted power predicted	107
COLUMNS	
EDITORIAL We'll get what we accept	3
FORUM Peter O'Neill and the metric system: we stand accused and plead guilty	22

#### **DEPARTMENTS**

NEWS HIGHLIGHTS 4 — CIRCUIT & DESIGN IDEAS 63 — MICROCOMPUTER NEWS & PRODUCTS 84 — LETTERS TO THE EDITOR 109 — NEW PRODUCTS 110 — BOOKS & LITERATURE 114 — INFORMATION CENTRE 117 — MARKETPLACE 118 — INDEX TO ADVERTISERS 120 — NOTES & ERRATA 116

RECORD REVIEWS Classical .....

RECORD REVIEWS Devotional, popular and jazz .....

70

87

89

## REAL POWER LINE UP


sanwa

#### N-501

2<sub>µ</sub>A suspension move-0.05mA/1mV ment resolution.

Double protection - fuse & Si diode

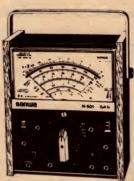Constant 1MΩ input impedance (ACV) - RF-diode rectified current direct to movement.



#### **U-60D**

44 M movement - quality performance, diode protected.

Temperature measurement of -30°C to +150°C with extra scale.



#### **AX-303TR**

44 A meter movement -Si diode protection against pulse input.

Measures hFE (0-1000) by using the extra connector.



#### BX-505

Fast-response, 24µA movement - fuse & diode protected with high resolution factor. (0.4µA/scale division) Revised scale marking intermediate readings readily determined

#### **CAM-250D**

Clamp meter Economical and multi-function. Single motion core

Compact yet provides 4 ranges on ACA and 2 ranges on ACV.



#### PDM-500/C

Performs as low resistance ohmmeter besides insulation

Measurement, scale calibration and battery check are all operated by pushbutton

Has constant voltage impressed irrespective of the value of resistance checked.

#### N-501

• ± DCV 0-60m 0-0.3-1.2-3-12-30 0-120-300-1.2k-30k (w/HV probe) ● ±DCA 0-2µ 0-0.3-0.3-1.2-3-12-30m 0-0.12-0.3-1.2-12A • ACV 0-3-12-30-120-300-

1.2k ± 2.5% Freq. 20Hz to 50kHz • ACA 0-1.2-12 • Ω x 1-x10- x 100-x 1k-x 10k-x 100k(max. 200M)Batt. 1.5V 50-250 -1k-25k (w/HV x1&9Vx1 • dB -20 to +63

#### **AX-303TR**

• ± DCV 0-0.3-3-12-30-120-300-1200 · ACV 0-6-30-120-300-1200 • ± DCV 0.60µ -3m-30m-0.3-12 €  $\Omega \times 1 - \times 10 - \times 1k - \times 10k$ (max. 20M)

#### **U-60D**

• DCV 0-0.1-0.5-2.5-10probe) • DCA 0-50µ -2.550-500m • ACV 0-2.5-10-50-250-1k ● Ω x 1-x 10-x 100-x1k(max.5M)

#### BX-505

• ± DCV 0-0.12-3-12-30-120-300-1200-30k (w/HV probe) •  $\pm$  DCA 0-30 $\mu$ -3m-30m-0.3-12 • ACV 0-6-30-120-300-1200 • ACA 0-12 • Ω x 1-x 10x 1k-x 10k (max. 20M)

#### **CAM-250D**

 ACA 6-30-60-300 ● ACV 300-600 • kΩ 0-50k • Batt. 1.5V x 1

#### PDM-500/C

- V/Ω rated 500V/100M
- Scale range 0-0.1-100-200m (1st effective scale range underlined)  $\bullet \Omega$ 0-100Ω • Power source AM or UM-2 x 3



WARBURTON FRANKI

• ADELAIDE 356-7333 • BRISBANE 52-7255 • HOBART 23-1841 MELBOURNE 699-4999 • PERTH 277-7000 • SYDNEY 648-1711

AUCKLAND N.Z. 79-7781 • WELLINGTON N.Z. 698-272



## **Editorial Viewpoint**

#### **EDITOR-IN-CHIEF** Neville Williams

M.I.R.E.E. (Aust.) (VK2XV)

Jamieson Rowe B.A. (Sydney), B.Sc (Technology, NSW) M.I.R.E.E. (Aust.) (VK2ZLO/T)

#### ASSISTANT EDITOR

Philip Watson A.M.I.R.E.E. (Aust.) (VK2ZPW)

#### SCIENCE FEATURES

Greg Swain, B.Sc. (Hons, Sydney)

#### PRODUCT REVIEWS

Leo Simpson

#### TECHNICAL PROJECTS

David Edwards, B.E. (Hons, Tasmania) Ian Pogson (VK2AZN/T)

#### GRAPHICS Robert Flynn

**PRODUCTION** Danny Hooper

#### **ADVERTISING MANAGER**

Selwyn Sayers

#### CIRCULATION MANAGER

Alan Parker

#### We'll get what we accept!

Recent inquiries into the tenure of radio and television licences, conducted by the Australian Broadcasting Tribunal, have raised a great many social issues, without obviously resolving any of them. The views expressed by witnesses have been diverse and conflicting — so much so that the extremes have tended to cancel, adding to the appeal and the seeming inevitability the median view.

If one chose to be cynical, one might conclude that, after the huff and the puff have died down, nothing will really have changed. That, while paying lip service to their social obligations, station managements will simply revert to the old programming patterns for as many years as it takes to stir the pot again! It need not be so, however.

For perhaps the first time, station executives have been put on the spot — under the full glare of publicity — and subjected to some highly uncomfortable periods of question and challenge. Right now, they are very conscious of the force and breadth of the new industry in-word: "accountability".

They are fully aware that, in the future, accountability may not be simply to a

board and to shareholders. Rather, along with the board, they may be answerable to the Tribunal, the Government and, through them, to listeners and viewers.

At risk: the very licence by which the station operates.

But why did I say "may" be answerable? For the simple reason that the spirit of examination and challenge, which has recently emerged, could as easily subside.

Once the current series of inquiries are over, the Government could back off, the Broadcasting Tribunal could become an administrative formality and the public could go back to sleep. That would indeed be the signal for station executives to pass up the whole 78/79 thing as a bad dream, and to fall back into their old value judgements.

While we may look to the Tribunal and to the Government to maintain the pressure on programming standards and practices, the plain fact is that, in the ultimate, the pressure must come from the public at large: from the listeners and viewers themselves. If we sense that what is being served up on radio and television is repressive or mindless or inappropriate or anti-social or obscene — or anything — then we should continue to protest publicly and, in particular, to our Federal member.

That way, we will keep alive the spirit of question and challenge and emphasise to the Government and to the Tribunal that there is an on-going job to be done. If I can repeat the words of the heading: In terms of radio and TV programs "we'll get what we accept!"

Some might even say: "We'll get what we deserve!"

- Neville Williams

#### Registered for posting as a publication -Category B.

Printed by Magazine Printers Pty Ltd, of Regent Street, Sydney and Masterprint Pty Ltd of Dubbo, NSW, for Sungravure Pty Ltd, of Regent St, Sydney.

#### **Editorial Office**

57 Regent St, Sydney 2008. Phone (02) 699 3622 Postal Address: PO Box 163, Beaconsfield 2014.

#### **Advertising Offices**

Sydney - 57 Regent St, Sydney 2008 Phone (02) 699 3622 Representative: Narcisco Pimental.

Melbourne - 392 Little Collins St. Melbourne 3000. Phone (03) 602 3033 Representative: Keith Watts

Adelaide - Charles F. Brown & Associates Ltd, 254 Melbourne St, North Adelaide 5006 Representative: Tom Duffy, (08) 267 4433. Perth — 454 Murray Street, Perth 6000

Representative: Ashley Croft, (09) 21 8217. Subscriptions

## Subscription Dept, John Fairfax & Sons Ltd, GPO Box 506, Sydney 2001. Enquiries: Phone (02) 20944, ext 2589.

Circulation Office

#### 21 Morley Ave, Rosebery, Sydney 2018 Phone (02) 663 3911.

#### Distribution

Distributed in NSW by Sungravure Pty Ltd, 57 Regent St, Sydney; in Victoria by Sungravure Pty Ltd, 392 Little Collins Street, Melbourne; in South Australia by Sungravure Pty Ltd, 101-105 Weymouth St, Adelaide; in Western Australia by

Sungravure Pty Ltd, 454 Murray Street, Perth; in Queensland by Gordon and Gotch (A'asia) Ltd; in Tasmania by Ingle Distributors, 93 Macquarie St, Hobart; in New Zealand by Gordon and Gotch (NZ) Ltd, Adelaide Rd, Wellington.

#### Copyright. All rights reserved

Devices or arrangements shown or described herein may embody patents. Information is furnished without responsibility for its use and without prejudice for patent rights. All manuscripts, photographs and other material submitted to Electronics Australia for publication must be accompanied by a stamped, addressed envelope. Contributions are submitted at the sender's risk, and responsibility for loss cannot be accepted by Electronics Australia. \*Recommended and maximum price only



## **News Highlights**

## NS sets sights on European auto manufacturers

National Semiconductor Corporation, well on its way to becoming a major supplier of semiconductor devices for use in advanced electronic systems in US autos, is now planning a major effort in Europe.

"European automobile manufacturers are a major factor in the worldwide automarket with 41% of the worldwide automobile production facilities," says Thomas Anthony, industry director for automotive electronics at National Semiconductor. NS is committed to becoming the major

supplier of auto electronics worldwide, he says, and Europe is a key to that effort.

NS has identified five key areas in the automobile, says Anthony, which can be enhanced through the use of advanced semiconductor technology:

- Engine the area of most growth to meet fuel economy and emission demands;
- Entertainment the next generation of equipment will be in the area of electronic tuning and AM stereo:
- Instrument Panel electronic

clocks, speedometers, tachometers, displays and trip computers;

• Body — illuminated entry, temperature, lighting and antiskid controls:

• Sensors and Transducers — This is the key to the all-electronic auto and an area in which National Semiconductor has been a pioneer.

According to Anthony, the semiconductor impact in the automotive industry will be close to half a billion dollars by model year 1981. "That is about \$39.50 of semiconductors in every car," he says, "with about \$30 of this just to meet US legislated engine controls." It is National Semiconductor's plan over the next several years to experience strong, yet controlled growth in the auto industry.

Webster Spectrum II minicomputer goes double density

Computex Data Product's, a division of D.D. Webster Electronics Pty Ltd, has released double-density floppy-disc versions of its LSI11-based Spectrum-11 minicomputer.

The new minicomputer can provide over 2.5 megabytes on-line, four times the disc capacity of the previous model released by the company just over a year ago. It is available in single or double sided versions from \$7000, hardware only, and has been designed for sale to original equipment manufacturers or experienced end users who can create their own application packages.

The computer is ideal for small businesses and in Australia has been sold with appropriate software to doctors, lawyers, accountants, wholesalers and retailers. Its designer, Mr David Webster, visied the United States and Canada in October, seeking a North American market for his computer.

Spectrum II can provide up to 2.5 megabytes online, and is ideal for small business applications and in hospitals. Overseas markets are sought by its Australian manufacturer, D. D. Webster Electronics Pty Ltd.



#### Big defence contract to Racal

Racal Electronics Pty Ltd has won the largest defence communications contract ever awarded by the Australian Government, and will supply transportable HF radio communications stations to the Army and the RAAF. The contract is worth over \$15 million.

# Australian designed FM transceiver

A new mobile two-way radio, the "Movar FM," has been launched onto the local market.

The radio, designed entirely by Australian engineers, is now coming off the assembly line at the Motorola Australia plant at Mulgrave in Victoria. Motorola claim it has already attracted wide interest overseas, with inquiries coming from Germany, Britain and South East Asian countries.

With Movar, only the control head, microphone and speaker need be inside the driving compartment of the vehicle. The main component of the radio can be mounted in the boot or engine compartment of a car or truck;



or under the chassis, for example, of a tractor or low loader.

Motorola says that Movar has been

specially designed for Australian conditions, and is highly resistant to heat, dust and humidity.

## Magazine on computer fraud

Computer crime is on the increase in advanced countries, so much so that Elsevier International Bulletins of the UK has commenced publication of a new monthly bulletin called "Computer Fraud and Security".

According to the publisher, "Computer Fraud and Security" will strive to alert management to the risks of computer abuse. Most cases of fraud have so far been discovered only by accident. The bulletin aims to supplement this accidental discovery factor by helping subscribers implement systems and policies based on informed understanding of the problems.

The editorial scope of the new bulletin will cover: reviews of computer crime; products and programs; auditing; people problems; legislation; pre-employment screening; investigation of fraud; industrial espionage; terrorism; and fraud detection techniques.

For information on subscription rates write to Elsevier International Bulletins, Mayfield House, 256 Banbury Rd, Oxford OX2 7DH, England.

#### 64K RAM chip

US semiconductor giant Texas Instruments will start production this year of the world's first commercial 64K dynamic RAM — a silicon "random access" memory with 65,536 logic elements crammed on a single chip. First production samples of the 64K device have already been produced. TI expects the 64K RAM market to be viable only to 1984, after which increasing levels of integration should mean memories in standard use are 256K at least.

## Fibre optic communication link

A new, complete fibre optic link for data communications applications that requires no expertise in optical design, calibration or adjustment has been introduced by Hewlett-Packard.

The new HFBR-0010 low error rate fibre optic link system makes the use of fibre optics simple and practical for a broad range of customers. It comes ready to hook up, and consists of a digital transmitter, a digital receiver, a single fibre, 10 metre connector/cable assembly and complete technical literature.

Using fibre optic techniques, digital information is carried via light waves instead of electronic signals using traditional methods. Benefits include immunity to electro-magnetic interference; lack of radiated signal; absence of electrical path between terminals; lightweight and flexibility; and broad bandwidth over long distances.

Typical applications of the new link



include: large computer installations; distributed processing systems; hospital computer systems; power plant communications and control; and process control etc.

For further information contact Hewlett-Packard's official component distributor: Amtron Tyree Holding Pty Ltd, 176 Botany St, Waterloo 2017.

#### IT'S THE 100 MILLIONTH FOR MATSUSHITA ELECTRIC

The Matsushita Electric Company of Japan, makers of National Panasonic and Technics sound equipment, has become the first organisation in Japan to achieve a production record of 100 million radios, according to Mr J. Ukita, Managing Director of National Panasonic (Aust.) Pty Ltd.

Mr Ukita said that the 100 millionth set, one of the National range of ultrathin types, came off the line last August. He said that while it took 40 years from 1931 to achieve the 50 million mark, production of the next 50 million radios

Ultra-thin AM-FM radio from National Panasonic. Features of the unit include a quartz-crystal clock, alarm, and liquid crystal readout.



had taken only 7 years.

Out of the 100 million sets produced, 31 million were sold in Japan and the remainder in more than 130 countries throughout the world.

#### **NEWS HIGHLIGHTS**

#### New IC obsoletes TV hold controls

National Semiconductor Corporation engineers have developed an integrated circuit that could make both horizontal and vertical hold controls (including factory presets) in television sets obsolete. What's more, no adjustments would be required for the life of the receiver.

Designated the LM1880, the IC chip is designed to operate with a new ceramic resonator made by MuRata Corporation of America, Rockmart, Georgia. This gives a more accurate initial frequency reference than the LC and RC voltage controlled scanning oscillators now used in most television

receivers on the market. According to product marketing manager Charles Smaltz, the LM1880 will deliver a phase locked loop horizontal scanning frequency and, counting down from that, obtain an injection locked vertical output pulse.

Heart of the LM1880 is a precision 32 times horizontal frequency VCO, designed to use the MuRata resonator, and accurate to within plus or minus 2kHz of a 503.5kHz centre frequency.

The VCO signal is then divided down in the horizontal section to produce a pre-driver output, which is locked to negative sync by means of an on-chip

phase detector. The vertical output ramp is injection locked by a vertical sync signal subject to a sync window derived from a 542 element countdown section. Should no sync pulse arrive in the time period following the 510 count, the counter will continue to 542 when an automatic reset will occur, generating a vertical output pulse. If the horizontal output is locked to 15,734kHz (US NTSC standards) then the vertical output can be "injection locked" from 58.1 to 61.7Hz.

The linear portions of the chip about 60 percent - include the VCO and phase detector and are implemented using a standard linear process. The rest of the chip — the countdown circuitry — is implemented with integrated injection logic (I<sup>2</sup>L).

The LM1880 also generates a burst gate pulse centred on the chroma burst. It will be available on the US market for \$1.50 each in 100-up quantities.

#### English as she is spelt!

National Semiconductor has announced a new product that applies electronic technology to the problem of teaching children to spell.


Looking somewhat like an electronic calculator, the "Quiz Kid Speller" has three modes of operation: the "Learn" mode, which can be mastered by children as young as three; and the "Spell" and "Game" modes which can hold the attention of children up to 12 years and older.

Included with the unit is a completely illustrated game book which pictures 99 different words that have been selected from six different levels of word difficulty.

In the Learn or Spell mode, the display shows a series of ten randomly selected game book page numbers. The child spells the name of the picture on that page by pressing the alphabet keys. The green light glows on correct spelling, and the red light glows for incorrect spelling. The score, five points for correct answers on the first try, three points on the second try, and one point on the third try, is accumulated and displayed at the end

The Quiz Kid Speller — taking the boredom out of learning to spell. Other Quiz Kid products teach the basics

of mathematics. of each series.

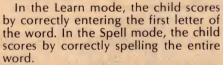


The Game mode can be used to play many different word guessing games, or any word up to nine letters long can be keyed in. The display then shows the number of letters in the word, and the number of times a guessed letter appears in that word. The score is displayed on completion of the word.

The Quiz Kid Speller will be available in Australia in February, and will cost around the \$30 mark without batteries.



## Super magnet

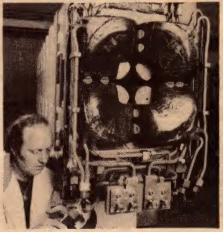

Twenty tonnes of magnet is checked at a British factory before despatch to the Centre for European Nuclear Research (CERN) in Geneva, Switzerland.

The magnet is of the quadrupole type and will form part of the new North experimental area at CERN. The North area is linked to the giant Super Proton Synchrotron (SPS) particle accelerator.

The quadrupole magnets will be used to accelerate sub-atomic particles called protons away from the main accelerator ring and into the new experimental area where further research can be conducted. Other magnets control the centralisation of the beam of particles as it hurtles along within a vacuum tube reaching a terminal velocity of 99,9997 per cent of the speed of light!

#### **High power MOSFET**

Originally developed for low power signal handling, the field effect transistor (FET) has now moved into the high power switching market with the announcement by International Rectifier (UK) of a device capable of handling over one kilowatt in switching power supply applications.
International Rectifier says that, in

the next few years, the power MOSFET

will secure a major share of the power transistor market. The company claims that the power levels achieved in its new device are more than double those of any comparable units previously available.

The new devices should make possible a significant reduction in equipment size and give high reliability and efficiency in applications such as power supplies, motor controllers and lighting controllers.

Dick Smith says: Just look at this INCREDIBLE HOME ENTERTAINMENT COMPUTER!



BE ONE OF THE FIRST TO ENJOY THIS AMAZING COLOUR COMPUTER - CONNECTS TO ANY TV SET.

\* EDUCATIONAL!

Your children can actually learn or improve mathematics:

addition, subtraction, multiplication and division right there on the TV screen. It even tells you when you're wrong or right!

You can play incredibly complex games like BLACKJACK!

Imagine: it actually draws your cards, raises the bet, 'pays' you for a win . . . you won't believe it!

Over twenty thousand sold in the USA since its release a short time

now available in limited quantity here in Australia. Don't miss out!

Imagine! For only-\$259 you get a real computer - the heart of this unit is an incredibly powerful Fairchild microcomputer containing thousands of transistors. No, this is not just another TV game this incredible machine has a mind of its own, giving versatility and performance not even thought possible just a few months ago!

Basic price includes the computer console with two inbuilt games (tennis and football), the two 8-way hand control units, an AC power supply plus a BONUS 'noughts & crosses' game cartridge.

today for a demonstra

SPECIAL 7 DAY TRIAL OFFER Purchase this Fairchild Video Home Entertainment Computer with two or more cartridges and try it in your own home for 7 days. If you're not completely satisfied, return it to us in the condition you received it and we'll refund your money in full!

A pleasure. To approved personal shoppers, terms are available from \$29.00 deposit and \$2.90 p.w.

#### MAIL ORDERS:

Yes. We'll send this unit anywhere in Australia for \$5.00 extra - game cartridges post FREE with unit. (If purchased separately p&p \$2.00)

ADD MORE **EXCITEMENT!** ALL OF THESE **FULL COLOUR** CARTRIDGES **ARE NOW** AVAILABLE!

Cat X-1200

ONLY <sup>\$</sup>24<sup>50</sup> EACH.

BLACKJACK Cat X-1201
You can play the TV (the bank) by yourself or with a partner
Try to break the bank at your home without losing a cent!

**DESERT FOX Cat X-1203** 

Try and destroy the desert fox without being blown up yourself (tank game) — or try the shooting gallery game on this cartridge. MAZE Cat X-1204

Four great games: Maze, Jailbreak, Blind-man's-bluff and Trail-blazer. Games that will test your skill and give you feal fun.

BASEBALL Cat X-1205
All the skills and thrills of the real game — played in the comfort of your own home. For two players.

SPITFIRE Cat X-1206
Two games: Solo the red baron is hot on your tail, or for two players you try to shoot each other out of the sky.

SPACE WAR Cat X-1207

Can you escape the piercing laser beams? The aliens from outer space are out to get you. Just how good are you? MATH QUIZ 1 Cat X-1208

Teach the kids addition and subtraction — or brush up on your, own basic arithmetic skills.

MATH QUIZ 2 Cat X-1209 Multiplication and division on this cartridge. It poses the problems — it's up to you to come up with the answers PINBALL CHALLENGE Cat X-1217
Remove different coloured walls of bricks to become the pinball

BACKGAMMON Cat X-1213
All the rules of this exciting game are programmed on the cartridge.
No cheating! Also has Acey Ducey (a variation of Backgammon)

TORPEDO ALLEY Cat X-1211
Sink as many ships as possible. Or play Robot War — try and escape the robots by destroying them in a force field.

SONAR SEARCH Cat X-1214 Use your ears to try to sink the enemy's hidden fleet. Hours of fun for everyone.

DODGE IT Cat X-1216

Dodge a varying number of hidden balls to win this game. Tests your endurance!

MEMORY GAME Cat X-1215
Number come and go. But can you remember where they were?
A modern version of Kim's game.

MAGIC NUMBERS Cat X-1210
Guess the right digits in the right places to win. You can play the clock or play for points.

DRAG RACE Cat X-1212

Don't eat dust: stomp on your accelerator and beat your oppon ent in an exciting drag race.

DICK SMITH ELECTRONIC



147 Hume Hwy, CHULLORA. Ph. 642-8922

162 Pacific Hwy, GORE HILL: Ph. 439-5311 30 Grose Street, PARRAMATTA, Ph. 683 1133

399 Lonsdale Street, MELBOURNE Ph. 67 9834 656 Bridge Road, RICHMOND, Ph. 42 1614 166 Logan Road, BURANDA Ph 391 6233

ADFL AIDE 203 Wright Street, ADELAIDE Ph 212 1962

SHOPS OPEN 9AM to 5-30PM "Saturday 9AM = 12 megn" BRISBANE 1-2 Hory earlier

ANY TERMS OFFERED ARE TO APPROVED APPLICANTS ONLY

GRACE BROS

MAIL ORDERS P.O. Box 747, Crows Nest, N.S.W. 2065. Post and packing extra.

Dealers across Australia

### POWERSCOPE

A NEW CLASS OF OSCILLOSCOPE DEDICATED TO MEASUREMENT IN THE FIELD OF

#### **POWER CONTROL**



Safety engineered for DIRECT measurement of waveforms in AC and DC power lines

- 4 Channel differential input, 100mV to 200V/div. DC to 7.5 MHz.
- Common mode rejection 350V RMS (±500V)
- Maximum Input 660V RMS or ±1000V (3kV peak transient overload)
- 0° to 359° phase measurement with digital readout.
- 0°, 120°, 180° and 240° zero reference by push button selection.
- 100nSec to 10Sec/div. time base with phase delay trigger.
- Hazard-free operation with insulated controls, panel and probes.
- Powered-by single or two phase AC, DC, or optional battery pack.
- Supplied with 4 x 1:1 probes and 4 x 10:1 probes (3kV rating).

#### OSCILLOSCOPES made to measure

#### **ELECTRONICS PTY. LTD**

Miles St., Mulgrave, Vic. 3170 P.O. Box 325, Springvale, Vic. 3171 Phone (03) 561 2888 Cables: 'Oscilloscope Melb' Telex: 35115

PS 881

N.S.W: (02) 888 8111 N.T: (089) 85 2249 QLD: (07) 52 7255 S.A: (08) 42 6666 (08) 212 3111 TAS: (003) 23 1843 W.A: (092) 25 3144

DISTRIBUTORS

PROUDLY ANNOUNCE

Not in age, for our origins go back further than that, but in Transformer Voltage Taps.

#### Yes 21 Voltage Taps!

Just think of the advantages offered by a single transformer that provides a choice of 21 different output voltages including 3 centre tapped configurations.

FOR EXAMPLE: TRANSFORMER No. 2155A **VOLTAGES AVAILABLE** 1.0, 1.2, 2.0, 2.2, 2.4, 3.1, 3.2, 3.5, 4.1, 5.1, 5.5, 6.3, 7.5, 8.5, 8.7, 9.5, 12.6, 15.0 Volts 2.0V CT, 12.6V CT, 15V CT

#### But that's not all!

With 5 such transformers in our range there is a choice of output currents as well.

#### And just he the way of a bonus!

We are able to offer these new transformers for a price considerably lower than comparable single tapped units while still maintaining the high standards of quality for which we are renowned.

#### Like to know more?

Just ring your local Arlec branch.



What do we call them? ARLEC **MULTI-TAP TRANSFORMERS** 

of course!

A+R ELECTRONICS PTY, LTD. A MEMBER OF THE A+R-SOANAR ELECTRONICS GROUP

30 Lexton Road, Box Hitl, Vic., 3128, Australia. Telex: 32286.

VICTORIA: 89 0661 N.S.W.: 78 0281 S. AUST.: 51 6981 QUEENSLAND: 52 5421 W. AUST.: 81 5500

### **NEWS HIGHLIGHTS**

#### Microcomputer-controlled submersible



A small, unmanned and highly controllable submersible, armed with a battery of television cameras, has been developed in Britain for undersea inspection tasks.

Called "SMARTIE" (Submarine Automatic Remote Television Inspection Equipment), the craft has the shape of a thick disc, is about one metre in diameter, and is driven by directional water jets from an electrically powered pump. It can operate to a depth of 300 metres.

The craft is controlled by its own microcomputer, which interprets manual control signals from a console on the surface. It is supplied with power and control signals by an umbilical cable only 5mm in diameter,

with video signals sent over the same cable in the opposite direction. In low visibility, the on-board computer can accept input from the craft's magnetic compass and gyro and can project an artificial navigation "target" that the operator can follow on his screen, even though the craft may be passing through an area of zero visibility.

SMARTIE can be held automatically in any position in fast currents. The operator pushes a "hold" button and the computer compensates for disturbing forces, thus keeping the vehicle in the required position. A similar technique is used to maintain a steady course at speed.

The craft was developed by Martine Unit Technology Ltd, 3 Friars Lane, Richmond, Surrey, England.

#### Silicon ribbon solar cells

Westinghouse Electric Corporation scientists have announced the achievement of high efficiencies in solar photovoltaic cells made of low cost silicon.

Efficiencies of more than 15 per cent—the theoretical maximum is 22 per cent—have been achieved with silicon dendritic web, a single crystal form of silicon showing high potential for low-cost production, according to Dr. Daniel R. Muss, manager of solid state research and development at Westinghouse's Research and Development Centre in Pittsburgh.

Dr Muss said that the achievement of greater than 15 per cent efficiency is an

important milestone in the solar photovoltaic program, in that this is the highest efficiency yet reported for silicon ribbon.

The technique used by Westinghouse forms silicon into a ribbon by drawing the material out of a furnace in a thin strip. The ribbon, or web, is formed by the solidification of a liquid film supported between two silicon filaments called "dendrites".

This process yields a long, mirrors mooth ribbon free from contamination and essentially ready for solar cell fabrication. Thus, unlike other processes, costly slicing, lapping and polishing processes are not required.

## Satellite at liberation point

NASA, for the first time, has launched a spacecraft to the Sun-Earth liberation point — that point in space where the gravitational pull of the Sun just balances that of the Earth-Moon system — about 1.6 million kilometres away.

ISEE 3, the third in a series of International Sun Earth Explorer spacecraft, will measure the solar wind constantly emitted by the Sun and other solar phenomena such as sunspots and solar flares, unperturbed by the influence of Earth, while ISEE 1 and 2 — in looping trajectories around the Earth since 1977 — will measure the effect of these phenomena on the near-Earth environment.

The coordinated effort is expected to result in a better understanding of how the Sun controls the Earth's fluctuating near-space environment, and of a variety of solar-terrestrial phenomena, including weather and climate, energy production and ozone depletion in the atmosphere.

One interesting fact about ISEE 3 is that it does not simply "hang" at the liberation point. Instead, the spacecraft has been placed in a "halo" orbit around this point. The orbit has been designed to pass slightly above and below the ecliptic plane (the plane in which all the planets circle the Sun), so as to avoid excessive solar interference with spacecraft communications back to Earth.

## Transformer has no coil windings

A miniature transformer which operates without coil windings has been patented by a research institute at Kiev in the Soviet Union.

The new transformer uses a piezoelectric converter instead of a conventional electromagnet. At least two piezoelectric material limbs are secured together to form a "V" or "W", with electrodes chemically deposited on the limbs for the input and output supply. The current fed into one limb causes the limb to vibrate at the input frequency which, in turn, causes the next limb to vibrate in sympathy to produce an output voltage.

The size of the output relative to the input will depend on the relative length of the limbs.

It is claimed that a transformer of the type patented and measuring only 50mm in length can function on a 50Hz mains supply to produce 5000V while consuming only 0.1 watt. Such a transformer would be ideally suited for use in a portable TV set, and in other applications where high voltages are needed and space is at a premium.

Low-risk production of huge amounts of energy — that's the promise of controlled nuclear fusion. Unlike today's fission reactors, a fusion reactor would produce little in the way of radioactive by-products, could not become self-sustaining, and would "fail safe" in the event of a breakdown.

# Fusion reactors: in our future?

#### by MICHAEL BAUM

Baum is a writer and public information specialist in the NBS Public Information Division.

Standing in front of you in a crowded laboratory, the test apparatus takes up a good 100 square metres of floor space and looks like nothing in particular. It's long, flat, and massive, hooked to heavy cables and tubing, and the most noticeable feature is a clear horizontal glass cylinder just over two metres long and 8 centimetres in diameter, the centre third of it clamped with heavy bands of metal.

Two researchers charge the tube with gas and start the firing sequence. The tube suddenly blazes with a brilliant flash of light and a muffled thunderclap is heard.

The light doesn't last long — about four millionths of a second — but during that period you are looking into a model of the heart of a nuclear fusion

reactor.

The device is called a theta pinch, (see diagram) and William Rowan and James Roberts of the US National Bureau of Standards are using it to study some of the atomic processes that will take place in a fusion reactor. They do this in an ordinary physics laboratory, without ever coming close to starting a nuclear reaction. They do it by an elegant sort of "modelling" in which relatively low temperatures (1,000,000 degrees Celsius) represent unimaginably high temperatures (100,000,000 degrees Celsius) and small, light ions become scale models of large, heavy ions.

**Energy from Heavy Hydrogen** 

The reasons for all this are found in the basic concepts behind fusion research. There are a variety of theoretically possible nuclear fusion reactions in which the nuclei of two light atoms combine to form the nucleus of a heavier atom. The most "popular" reaction — popular because it requires considerably less energy to

start than the others — is shown in this equation:


 $D + T \rightarrow {}^{4}He + n + 17.6 MeV$ 

Inherent in this reaction are the advantages and disadvantages common to all fusion processes. This equation begins with deuterium and tritium, the heavy and superheavy isotopes of hydrogen. Fuel for such a reaction is abundant even though there is only about one deuterium atom for every 6500 common hydrogen atoms, because deuterium can be extracted from the Earth's greatest resource—water. The US Department of Energy estimates that the deuterium resources, if used to supply twice the world's current energy demand, would last for about 50 billion years.


Tritium, a radioactive isotope of hydrogen, is not found in nature and therefore has to be manufactured. But the same fusion reactors that burn the tritium can produce it by bombarding lithium with neutron radiation. DOE estimates that known lithium reserves would last for almost 50,000 years.

The other side of the equation is equally promising. The main reaction product is common helium, non-polluting and non-radioactive. The reaction produces a great deal of energy, close to 90,000 kilowatt hours per gram of fuel.

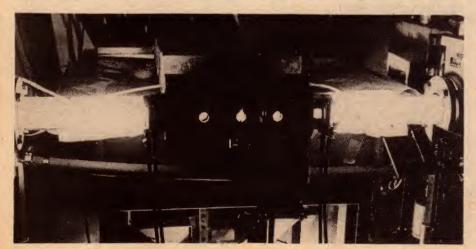The reaction also produces neutron radiation, which in turn produces radiation in the materials used to build the reactor. However, by selecting



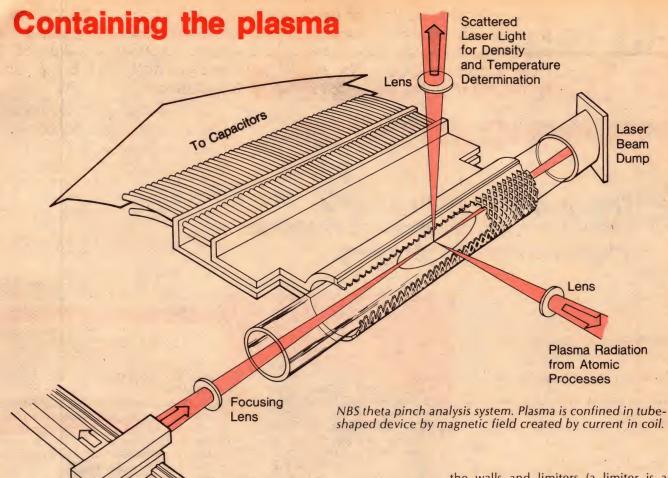Brilliant light fills a theta pinch reaction chamber at NBS as the rising magnetic field heats hydrogen plasma to 1 million degrees Celsius for 4 millionths of a second.



those materials carefully, the radiation hazard can be kept to a minimum.

For two reasons, fusion reactors would theoretically be many times safer than the fission reactors in operation today. First, the amounts of radioactive materials on hand in a fusion reactor are comparatively small. Second, the fusion process in a reactor cannot become self-sustaining. If the system inducing the process failed to operate properly, the reaction itself would "fail safe" simply by stopping.

Fusion looks like the rosy alternative on the basis of these comparisons, but there are other elements to consider before the picture is complete. For instance, power from fission reactors is today lighting up homes, businesses, and industries in various countries. A fusion reactor has never lit a single bulb anywhere in the world. And there's the rub.

#### How to Make It Work

The biggest problem with a fusion reactor is how to make it work. Some technical experts doubt that it's possible to do so. The NBS theta pinch project is designed to help find out.

The extreme conditions that must be achieved and maintained pose

formidable difficulties, according to Roberts, chief of the NBS theta pinch project.

100 MW Pulsed

for Diagnostics

Ruby Laser

In the ionized gas or plasma, which forms the fuel for the magnetic fusion reactor, the deuterium and tritium nuclei both carry electrical charges which tend to keep them apart. For the particles to fuse and ignite the fusion reaction, they must have a high kinetic energy (that is, be very hot) and be kept packed together for a sufficient length

The deuterium-tritium reaction has by far the lowest "ignition temperature" of the fusion reactions possible in a reactor, but even this reaction takes place at temperatures of approximately 100 million degrees Celsius or more. Think of that as comparable to the temperatures in the centre of the Sun:

. "But reaching the temperature is only part of the problem," says Roberts. "Serious considerations like radiated power losses from impurities, diffusion, and instabilities must be addressed."

Diffusion and instabilities refer to the inability of the confining magnetic field to hold the plasma together (see diagrams). Impurities are another matter.

Impurities are free atoms torn from

the walls and limiters (a limiter is a device designed to keep plasma away from the walls) of the reactor and surrounding space that mix with the plasma. They can be metals like tungsten, molybdenum, and iron or gases, including oxygen. Impurities in the plasma are a crucial problem in designing fusion reactors.

designing fusion reactors.

Why? "The impurities enter the plasma, soak up energy, and radiate it by the emission of light energy. This reduces the thermal kinetic (heat) energy of the particles, which is what we need to produce fusion," explains Roberts. "With high Z (Z being atomic number) impurities, such as the heavier metals from the walls and limiters of fusion devices, it takes more energy to ionize them — to strip them of electrons."

In addition, he says, "A large amount of energy goes to the remaining electrons in the heavy impurity atoms which can change temporarily to high energy states, return to their "ground" state, and give off the energy they've acquired by emission of light. That would be okay if the energy were given back to the plasma, but it's not. It's radiated as ordinary light."

#### Data to Build On

This is where the theta pinch comes in. "Basically what we're doing is providing atomic data to the fusion energy community — the people doing fusion research — so that they can better understand the dynamics of the plasmas," says Roberts. The project is

## At last: A budget-priced mosaic printer.

The new EUYIOE series is ideal for microprocessor-based systems or data logging.

How often have you needed a small printer which can produce many characters, alpha-numerals, symbols and graphs at 2 lines per second on 60 mm paper?

Matsushita's new quiet nonimpact Electrosensitive Printers use a 7 x 5 dot matrix and a choice of characters per line (15, 21, 32 or 40).

Added versatility is built into the EUY10E models because there is also a choice of scanning direction.

Even with all these features only a low 24 volts is needed to operate the units.


Due to low power consumption, it can operate on batteries with converters.

One motor drives both the printing head and recording paper through a dependable mangle gear. Special overall design reduces the number of parts needed and the natural result is less weight, smaller size and most important, greater reliability. Choice of drive units.

To drive the EUY10E printer you have the choice of two interface units. EUYPUD022A is a basic drive unit which provides signals to power the motor and printing head. It offers the user maximum versatility and flexibility. EUYPUD024C is designed to interface between the printer and microprocessor kits such as 2650KT9500, SC/MP or D2.

The EUYPUD024C contains a full 64 ASCII character generator.

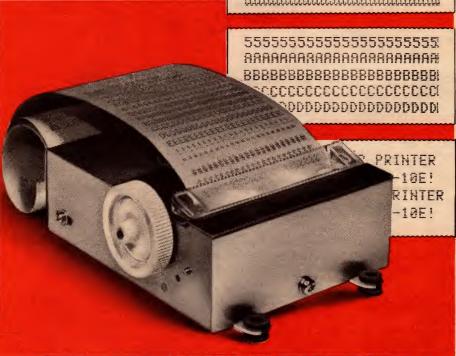NEW MATSUSHITA 0123456 EFGHIJKKKKKKKKKKKKKKK 89ABCDEFGHI0123456789A CDEFGHIJK0123456789ABC EEEEEEEEEEEEEEEEEE



#### **Specifications**

Printing method No. of characters per line

Types of characters Character composition

Printing speed Character height Input voltage

Current Life Dimensions

Weight (approx:)

Electrosensitive

15, 21, 32, 40

Alpha-numeral, symbol, graph

7 x 5 dot matrix Approx. 2 lines/sec.

2.4 ± 0.2 mm (0.094" ± 0.008")

-24V ± 5% 300mA

MCBF 1 x 10<sup>6</sup> lines

90.5(W) x 110(D) x 42.5(H) mm 3.56(W) x 4.33(D) x 1.67(H) inch

370 g (0.814 lb)

EUY10E Electrosensitive printers have all the features you need, at a price that makes them even more attractive.

You can purchase your EUY10E and interface from your local distributor of Philips components.

If you'd like more data and application information write to the:

Professional Component
Marketing Group

Philips Electronic and Materials P.O. Box 50, LANE COVE, N.S.W. 2066



Electronic Components and Materials

## **PHILIPS**

We want you to have the best

#### Fusion reactors: in our future?


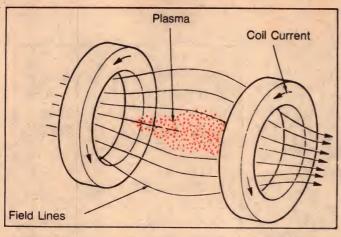


Diagram at top illustrates the principle of the magnetic mirror system, while at right is a diagram of a Tokamak. The bulk of fusion research is directed towards Tokamak devices.

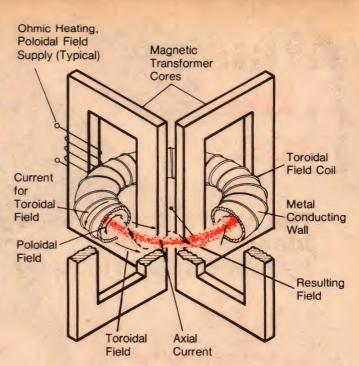

sponsored by the Department of Energy.

The data are used to make more accurate theoretical models of the atomic processes, which in turn are used to make critical decisions about the design of the reactors — decisions

such as what metals should be used to build the walls and limiters that will confine the plasma. To the people who are trying to develop fusion devices in places like the Princeton Plasma Physics Laboratory, Oak Ridge National Laboratory, and the Massachusetts Institute of Technology, the atomic scale models have a value many times their size.

Reprinted from "Dimensions", journal of the National Bureau of Standards, Washington, DC

## Plasma confinement techniques ...

Nuclear fusion reactors present a unique engineering problem: how to confine and heat a charged gas or plasma that reaches a temperature of 100 million degrees Celsius. Ordinary containers won't do — even if they could withstand the heat — because the plasma must be isolated in a vacuum, well away from walls or other structures that would cool it.

Current fusion research is investigating two separate ways of solving this problem. Inertial confinement, such as is being explored with the SHIVA laser at Lawrence Livermore Laboratory, uses fuel contained in small hollow spheres ("microballoons") which are burned and imploded one at a time by high energy laser beams. Each microballoon is heated so quickly that the expanding gas from the outside compresses and heats the remaining core to reaction conditions — the fuel becomes essentially its own container.

Magnetic confinement, more highly developed, uses invisible walls of magnetic force to hold the plasma while it is heated to reaction temperature. Magnetic confinement systems would hold the fuel at a much lower density than inertial confinement

systems, and for a much longer time (approximately one second for a test reactor, compared to 10<sup>-9</sup> seconds).

The theta pinch device at the National Bureau of Standards is an example of one of the simplest types of magnetic confinement.

Although they can be doughnutshaped, typical theta pinch instruments are simply long tube-shaped devices ringed by a single-turn current carrying coil. Since the gas which forms the fuel for a theta pinch is ionized — each particle carries an electric charge — it can be restrained by the tube-shaped magnetic field, which creates a kind of "bottle".

Once confined, the plasma has to be heated. Since the charged particles will carry an electric current, electrical induction (using the "theta pinch" coil to set up an electric current in the plasma) is a common heating technique. Theta pinch devices heat the plasma by a sudden, powerful increase in the magnetic field strength which squeezes the plasma in on itself, simultaneously increasing the density and raising the temperature. This "pinch" effect is the origin of the name.

Squeezing the plasma tends to force

it out the ends of the tube, lowering the density, and temperature. This problem, called diffusion, is partially solved by another confinement scheme: the magnetic mirror, which is also generally tube-shaped, but includes magnets of much greater power at the ends of the tube. These squeeze the ends of the plasma region together and tend to reflect the charged particles back along the tube.

Magnetic mirrors are more popular than theta pinches for actual reactor designs, but a still more popular design is the Tokamak, a name which comes from the Russian acronym for toroidal magnetic chamber. Tokamaks use toroidal or doughnut-shaped magnetic fields with no open ends. This design offers a number of advantages in controlling diffusion and accounts for the fact that the bulk of fusion research is directed towards Tokamak devices.

Both Tokamaks and magnetic mirrors commonly heat their fuel by induction; by bombarding the plasma with high energy, high frequency radio waves; by injecting into the plasma a stream of high energy neutral hydrogen atoms (neutral beam heating); or by some combinations of the three.



The soap powder commercial is terrible. Imagine being able to press the "zap" button on a small table-top unit to register your protest at a central monitoring station!

Television sets in American homes are turned on an average of six to seven hours a day. Yet no one knows how many are actually being watched at any one time, or how the viewers are reacting moment to moment to the programs they do watch.

The powerful Nielson ratings are established by the viewing habits of 1200 metered homes, supplemented by an additional panel who keep written records of the programs they watch.

Even the viewers in the metered homes have no way of immediately registering their opinions of what they see, other than by changing channels or turning their sets off.

Now R. D. Percy & Company in Seattle, Washington is moving to supply this missing audience feedback using a system designed by SRI (Stanford Research Institute) International researchers.

Moment-to-moment monitoring

For the past 18 months, the system has been monitoring the moment-tomoment reactions of a panel of 32 randomly selected TV viewers in the Seattle area. Currently the panel is being expanded to 200 Seattle families - approaching the size of the Nielson metered panel of 230 in the Chicago area.

The heart of the SRI-developed

system is a remote-controlled device connected to the viewer's television set. By pushing buttons on this device, the viewer can express a variety of reactions to the program.

These reactions are translated to digital code and transmitted instantaneously to the Percy offices, where they can be stored for future use or displayed on computer printout or video

There are six buttons on the monitoring device. One is marked "applause". Another is marked "more" — to indicate that the viewer wants more information about the product or subject being discussed.

There is a button to press if something is funny; another if the viewer agrees with what is being said; another if he doesn't believe it. Strong disapproval calls for the "zap" button, which turns off both sound and picture for as long as it is depressed!

According to Percy, the next generation of devices will contain four more buttons and a dial that will identify which family member is watching the

Watching viewers' reactions

Researchers in the Percy office can view panel members' reactions on a TV monitor in "real time" - as fast as the viewers push the various buttons. For example, if 10 per cent of the panel members who are tuned into a particular channel push the "applause" button at the same time, a light appears behind the letters "App" on the TV monitor and a bar graph measures 10 per cent (see photo).

Thus the lights and the bar graph reflect moment-to-moment changes in response as the program moves along.

Among the system's capabilities are the following:

- It is operational 24 hours a day, seven days a week.
- The device can be installed in a few minutes on any television set, whether cable or not.
- All channels being broadcast can be monitored simultaneously.
- Viewer responses can be attributed to each household and, in the newer devices, to each family member.

Even with the current devices, says R.D. Percy, president of the company, it is easy to tell from a viewer's response whether he or she is an adult or a child.

"Children have a different sense of humour from yours or mine," he points out. "For example, to a nine-year-old, underwear is hysterical."

At the present time, says Percy, the prime use of the feedback data collected by the system is for evaluating the effectiveness of advertising.

"We can find out whether an ad has stronger impact on one show or another or in the daytime or prime evening hours," he says, "and we can document our findings with computer printouts and videotapes comparing the actual viewer responses at different times."

Sometimes an ad that attracts favourable attention when it first appears ends either by being ignored or by grating on people's nerves so much that it actually kills sales. The feedback system can document this progressive wearout of a campaign.

The Percy people have their own system for tracking television advertising. Thus they can study competitive impact and exposure levels simultaneously for all products and ser-

vices advertised.

According to Percy, two companies that are experimenting with the audience feedback information for evaluating advertising are General Foods Corporation and Sears Roebuck and Co.

**Evaluating programs** 

The system is also being used to evaluate programming. For example, a preview of a Public Broadcasting System (PBS) program on the drought was monitored recently. A videtape of the audience response showed that the program was basically popular but that the audience found certain repetitive portions boring.

As a result, PBS aired an edited version nationally and requested Percy & Company to monitor all its programs

for 1978-79.

Audience reactions to current events and political speeches are also being monitored. Percy & Company has followed public response in the Seattle area to the energy issue for the past 15 months, documenting a 77 per cent decline in public interest in this subject.

Monitoring a recent Carter speech,

the company was able, overnight, to prepare a 15-page report on audience reactions, backed up by computer printout and videotape.

Even based on a tiny sample of 32 families, this report mirrored the results of the Roper organization on the same speech published three days later.

The "least objectionable" program
A fourth area of research made possible by the system is the study of general behaviour toward TV.

There is a theory, says Percy, that instead of actively choosing a particular program on TV, most people make the decision to "watch TV tonight". Then they switch about from one channel to another trying to find what researchers call the "least objectionable" program.
The viewing habits of the Percy &

Company panel members tend to confirm this theory, he says, adding that, insofar as possible, these families represent a cross-section of TV viewers.

The original 32 were selected by random sampling more than 500 families in the Seattle area. Special-interest groups are represented only in proportion to their numbers in the general popula-


Although the so-called "silent majority" of TV viewers tend to be passive in their viewing habits, Percy says he has found that his panel members welcome the opportunity to play a more active role in the process.

Although no one is paid to participate in the program, he says, there is

steady audience feedback.

After being panel members even for a short time, he notes, people get so used to being able to "talk back" that many report feeling frustrated when they watch a TV set without a response device.

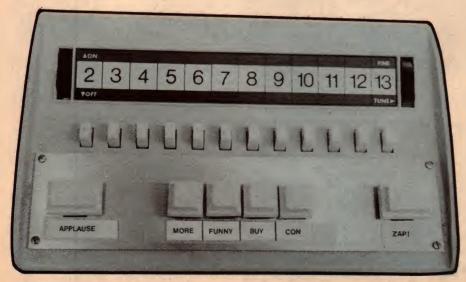Reprinted from "Investments in Tomorrow". by arrangement with SRI International, Menlo Park, California.



This monitoring device allows viewers to express their opinions on TV programs. These opinions are registered on a TV screen at the monitoring station.

## D.I. SERIES

P.A. AMPLIFIERS

THE FINEST SYSTEM AMPLIFIERS IN AUSTRALIA



Compare these technical features:-

- XLR microphone sockets.
- Balanced low impedance microphone inputs
- Separate bass and treble controls.
- Constant voltage and multi-tap low impedance outputs
- Master gain control.
- Self contained or rack mounting

#### LOW COST

35 watt . . . . . . . . . . . . \$177.00 60 watt . . . . . . . . . . . . \$220.00

100 watt . . . . . . . . . . . . \$266.00

from the BOGEN people

AUDIO TELEX COMMUNICATIONS PTY. LTD.

#### SYDNEY

54 Alfred St. Milsons Pt. 2061 Tel: 929 9848

#### MELBOURNE

828 Glenferrie Rd., Hawthorn, 3122 Tel: 819 2363

#### BRISBANE

294 Montague Rd., West End, 4101 Tel: 44 6328

#### ADELAIDE

Werner Industries, Unit 5, 28 Gray St., Kilkenny, 5009 Tel: 268 2801

#### PERTH

Electro Acoustic Co. Video & Sound 55 Frobisher St., Osborne Park, 6017 Tel: 444 8688

#### HOBART

Services 11-13 Andrew St., North Hobart, 7000 Tel: 34 1180

TRADE ENQUIRIES INVITED

# Telecom opens \$10m research complex

Rapidly changing electronics technology presents any country with a challenge to ensure that its communications links remain viable and up-do-date. Telecom Australia has responded to the challenge by building a new research laboratory complex at Clayton, Victoria.

The \$9.8 million first stage of Telecom's new Research Laboratories at Clayton (a suburb of Melbourne) were officially opened last June by the Minister for Post and Telecommunications, Mr A. A. Staley, MP. At the opening, Mr Staley congratulated all concerned with the project. The design, he said, would help provide the most modern communications to meet the social, commercial and industrial needs of Australians as economically as possible.

The new laboratories provide accommodation for 200 of the P&T Commission's 500 research staff, and represent the first step in a continuing program to centralise research activities.

Since the establishment of the Research Laboratories in 1923, the provision of building accommodation has followed an ad hoc pattern of leasing buildings in the Melbourne city area. At one stage, seven buildings at the eastern end of Melbourne plus one building in North Carlton were in use by the Laboratories.

These buildings were old, having been erected as factories or warehouses, and required considerable refurbishing and continual maintenance to keep them at a suitable standard for specialist laboratory work. A major problem was the provision of building services to meet the changing needs of a developing technology.

In the late 1960s the then Australian Post Office undertook a comprehensive review of its Research Laboratories' accommodation needs. It was agreed that the leased accommodation was unsatisfactory and it was recommended that the Laboratories should be consolidated in new, specially designed

buildings located well away from the Central Business District.

This culminated with the purchase, in 1972, of a seven hectare site in Blackburn Road, Clayton, near Monash University. Subsequently, a further 12 hectares adjoining the first site was purchased for long term development.

Parliamentary approval to proceed with construction of the first stage of development was received in November 1973. The project subsequently became known as the Monash Laboratories project.

The decision to develop a new Laboratories complex in the Clayton area was based on the economics of providing specialised laboratory buildings in a long term multi-staged expansion program. Feasibility studies conducted by the then Department of Works concluded that the most cost effective design would result from the establishment of a number of low rise buildings in a campus-style setting on a large block of land.

This arrangement made it possible to spread the development of the project over a number of years and required relatively small but regular funds commitments, compared to a large single investment for one high-rise building.

Land suited to this style of building was only available in the suburban area and this, combined with the popularity of the eastern suburbs as a residential area, and its proximity to the Monash University, led to the choice of the present site.

The Monash Laboratories project currently comprises one single story and two three storey laboratory buildings designed to accommodate some 200 staff; a single storey plant building; and a gatehouse. The buildings function as follows:

 Building 1 — houses the Physical Sciences Branch and the Microelectronics Section;

Building 2 — houses parts of the Advanced Techniques and the Standards & Laboratories Engineering Branches, the Laboratories Executive and Administrative staff, Cafeteria and Library;

and Library;
 Building 3 — houses the Environmental Physics activity; and

Building 4 — accommodates centralised mechanical and electrical



Mr Staley showed great interest in this advanced micro-welder which joins very thin metals. Showing him the technique is senior fitter and turner Neil McKenzie.



Above: Labs staffer Cheryl Crarey indicates the control panel of a bank of furnaces which fire thick film conductors at temperatures up to 850°C. View at right shows Tech. Assistant Eta Horvath setting up the Lab's new \$70,000 numerical-



ly controlled machine which automatically — and accurately — drills holes in printed circuit boards for telephone exchanges.



Above: TO2 Fred Gigliotti tests micro circuits in the new Thick Film Laboratory. At right, chemist Bob Western operates a mass spectrometer to test gold plated relays



which are replacing exposed mechanical switches in telephone exchanges. The reeds are bomarded with helium and any leakage detected means a defective reed.

plant for the building services systems.

Buildings 1 and 3 are connected by a single storey laboratory and office link to form an integrated structure.

The buildings conform to an overall master plan as a group of several low rise (up to three storey) buildings arranged in a campus-style configuration linked by garden courts. This approach allows the necessary flexibility for further stages to accommodate those sections which are still in the City and at Winterton Road, Clayton.

A feature of the modular design of the buildings is the ease with which laboratory needs may be altered in both size and function, and the practicality of converting offices into laboratory space.

The three-storey laboratory buildings are constructed of reinforced concrete

columns and floors with concrete block panel walls. Reinforced concrete has been used around stairs, lifts and service ducts to ensure lateral stability. Mechanical plant is located within the roof space.

The single storey buildings are steel framed with concrete block external walls. The roofs of all buildings are sheeted with corrugated aluminium, while facias and ducts are clad with prefinished steel sheeting. Windows are of anodised aluminium, fitted with reflective double glass to reduce solar heat build-up.

Air conditioning is provided to all laboratories, offices, cafeteria and amenities rooms to ensure maximum comfort.

The buildings incorporate amenities in accordance with the Commonwealth Amenities Code which applied at the

time of their design. These include a temporary cafeteria (Ground Floor, Building 2) to seat approximately 120 people, active and passive recreation rooms, showers and tea-making facilities.

The second stage of development will provide three buildings to accommodate sections currently in the city; Electrical Standards, Time & Frequency Standards, Laboratory Instrumentation and Customer Apparatus. Further facilities will be provided for an enlarged cafeteria, main library, etc. Documentation is now well advanced and completion is expected by 1982. A further stage will then be considered for those sections currently at Winterton Road, Clayton.

Reprinted from "Telecom", house journal of Telecom Australia.

Whatever the layout of your model railroad, it's about to become obsolete. Hornby Railways of England has developed a new multi-train control system which it says will bring a substantial advance in operational realism.

# Controller runs 16 trains on one track

The secretary swears that it's true . . . she entered the office of one of industry's leaders and, not realising that he was no longer alone, this top executive was gazing at the newly acquired model railway engine on his blotter and saying "choof choof" to it!

But whether small boys or top industrial executives, all model railroading enthusiasts are about to have one thing in common — their model train layouts are about to rerendered obsolete by a new electronic model railway control system recently unveiled by Hornby Railways in England.

Called "Zero One", Hornby's new train controller is built around a microcomputer. A highly advanced system, it will eventually permit control not only of locomotives but also of points and colour light signals, as well as offering inertia control and a range of realistic sound effects.

No longer will you have to say "choof, choof" to your model trains!!

Zero One was designed by Hornby engineer Lucien d'Sa, who says there's no other system like it. Up until now, the problem has been that in order to control more than one locomotive on a model train system, you had to divide the track into insulated sections. Each section was then connected to an independent control unit and the locomotives operated by controlling the power fed to the various sections.

Even a modest layout soon became a nightmare of wiring and switches, and the system placed severe limitations on the number of locomotives that could be controlled.

With the Zero One system, on the other hand, power control takes place in the locomotive and not via the rails. The system allows up to 16 locomotives

to be on the track, any of which can be "called up" and controlled by the master control unit. The addition of one or two slave control units alongside the master control unit permits two or three locomotives to be controlled entirely independently and simultaneously — or in computer jargon, "real-time control".

An essential component of Zero One is the miniature control module which can be fitted quite simply to the majority of Hornby locomotives. The modules have three colour-coded leads and connect between the motor and pickups. A switch on the module allows the modeller to assign any one of 16 codes to the locomotive.

Once the module is installed, the locomotive is registered as, for example, 01, 02 etc, and will respond only when its particular code is tapped out on the master control unit's keyboard. A locomotive's code may be altered at any time simply by changing the switch setting.

Hornby claim that Zero One will bring a substantial advance in operational realism. Even on small layouts, the traditional need to isolate sections of the track to perform such operations as shunting represents an undoubted handicap. It is worth noting too that, with Zero One, coach lights and the illuminated head codes of locomotives will remain at full brilliance at any speed, even when the trains are stationary.

Phase one of the Zero One system, scheduled for release in Britain towards the end of 1979, will offer locomotive control with selected levels of inertia. Phase two, available about a year later, will bring computer control of points and signals, while phase three will provide the sound effects and automatic program facility.

There is no information as to when the system will be available in Australia.



Artist's concept of Hornby's Zero One model train controller. View shows the master control unit together with one of the slave control units.

## SOLAR PANEL

Use free sunshine to keep your batteries charged. Ideal for boats, camper vans, holiday shacks or experiments and demonstrations.

The Solar Panel is manufactured by Sensor Technology Inc of the USA, for whom Amtex Electronics is the Australian distributor.


- \* Power output is 4.32 Watt at 14.4V under load
- \* Construction is on a rigid aluminium extrusion to assist with heat dissipation.
- \* Covered with tempered glass and sealed against dust and moisture
- \* Built-in Schottky diode prevents reverse current damaging the panel

\$147 including sales tax plu

\$5 Certified Post and handling

OR \$130 plus \$5 Certified Post and handling (if order is accompanied by an official sales tax exemption certificate).

HOW TO ORDER: Fill in BOTH sections of the coupon, in each section print your name and full postal address in block letters. Cut the entire coupon out around the dotted line. Send it with your money order or crossed cheque to this Magazine's Mail Order Dept (Solar Panel 74/78), Box 4000, GPO, Sydney, 2001. Cheques should be endorsed on the back with sender's name and address and made payable to this magazine. This offer is open to readers in Australia only. PLEASE ALLOW 4 WEEKS FOR DELIVERY.

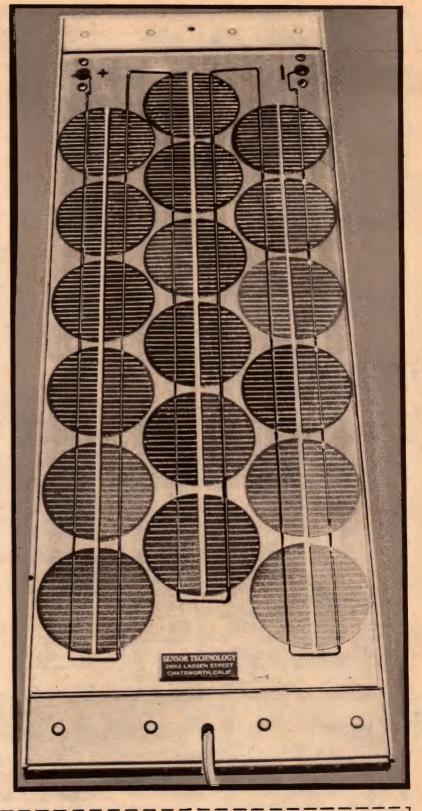

1		тн
1	Name	Name
i	Address	Address
1	State	Sta
-	Postcode Quantity	Please send cheque, posta

THIS MAGAZINE'S SOLAR PANEL OFFER 74/78
Name
Address
State Postcode
Please send me (state quantity) Solar Panel/s. I enclose my
cheque, postal/money order to the value of \$

#### **SAVE AT LEAST \$50**



It's got AM & FM radio plus stereo casserte dual power (mains or batteries) means you can use it wherever you like — even down on the beach! The opposition sell an equivalent model for over \$200. You reap the benefit of Dick's incredible bulk buying overseas plus DUTY FREE prices, Save!

THE OPPOSITION!

#### \$1.00 OFF 7 Segment display

Direct equivalents to famous DL-707 and NSN71L — but \$1.00 cheaper! 0.3" comm. cathode 7 seg. LED.

Mechanics charge a fortune

these days: save CA\$H by

doing your own tune-ups

it's so easy with these aids!

Right: Auto tune-up analyzer

checks most electrical funct-

ions including RPM & dwell

Cat A-8514

angle. Pays for itself in no

time at all!



(OR \$1.30 ea. 10+) Cat Z-4117

## Play chess with a computer!



game of chess — with a computer! Various levels of 'hardness' mean you CAN win if you're good enough. And now, save a whopping \$49.50 - was \$299!

Save \$\$

CASSETTE



C-3800

**BOX OF** •6 UNITS.

Protect your valuable cassettes! Store them in this handy library unit — either 30 or 48 depending on whether you use the cases. The units interlock, and can fasten on wall with screws supplied. Bargain storage!

Here's your chance to really save! Take advantage of Dick's incredible bulk-buying power. We're sure our Hitachi cassette prices are cheapest in town . if we are wrong, let us know!

C60 LN Cat C-3060 \$1.50 ea C90 LN Cat C-3065 \$1.95 ea C60 UD Cat C-3070 \$2.40 ea C90 UD Cat C-3075 \$2.85 ea

(Limit 5 per customer)



**SAVE 20%** 

Famous 'Weller' cordless soldering iron

is now reduced - we've rationalised the packaging and now supply only the bits you really need - so you save. In-built re-chargeable cells give hours of soldering away from a power source. A built-in light shows the way in dark Mains charger and one spare tip included.

> INCLUDES MAINS CHARGER AND **SPARE TIP \* 12 MONTH GUARANTEE**

RANGE OF SPARE TIPS IN STOCK !

## \$1525 on tantalum capacitors

You know how useful Tag Tantalum Pack of capacitors are — and usually how expensive they are — around 40 cents

So how much would a pack of 50 of the most used values cost? \$20.00? Here are 50 PRIME SPEC tantalum capacitors at less than 1/4 normal price! Buy now (in bulk) and save!

Left: Power timing light for

Cat A-8508 .. .. \$23.50

all-day ignition timing. Xenon flashtube for maximum light.

50

**SAVE \$610** on 1/4 watt

And here's a special computer-selected Pack of pack of prime spec. high quality carbon film resistors — ideal for use in projects, as service replacements,

Normally these resistors sell for 4c each — so a pack of 300 should sell for \$12.00. These are less than R-7010

#### RORDDIBLE Our famous multimeter/transistor checker **BUY DIRECT**

FROM THE IMPORTER! **NOW ALSO MEASURES CAPACITANCE!** 

We've sold thousands of the fantastic Q-1136 multimeter/transistor checkers. Until now, they have been by far the best value-for-money going: a 100,000 ohm per volt multimeter (including 10A AC & DC ranges) PLUS a transistor checker measuring her plus I CO. NOW IT'S EVEN BETTER!

Yes — this fantastic meter now measures capacitance too! In two ranges, 50pF to 3uF and 0.01uF to 50uF!

If you're in the market for a new multimeter (and let's face it — that old one is getting a little worn out, isn't it?) why stop at a multimeter.

For very little more than the price of a good 'normal' 100,000 ohm per volt instrument, you get all the advantages of a transistor checker and capacitance meter!



## SCOOP PURCHASE!



The current (1978) edition of the world famous 'Radio Amateur's Handbook' at a bargain basement price. Novices, students, amateurs, hobbyists - here's your chance to pick up this valuable textbook at a never-to-be-repeated price.

The new edition is just around the corner (stocks due late January - price \$14.95) so we want to clear our stock of the still current issue before then. You reap the benefit of our over stock!

X-1042

250 now \$ 850



#### SCOOP PURCHASE OF TINY DIGITAL ALARM CLOCKS

Amazing miniaturisation! This ultra-tiny digital alarm clock is ideal for appointment reminders, parking meters, etc etc etc.

Runs on two small batteries for thousands of hours - contains thousands of transistors. Slips easily into shirt pocket - complete with dust case and vinyl slip-in case.

Buy direct from the importer and save -NO DUTY on this incredible unit.

## TRY THESE OUT!



NOW IN PLASTIC CASE

Millions of applications and at this price you can afford to experiment! Motorbike kill switches, car bonnet & boot alarms. merchandise alarms, 'tilt' mechanisms on games to name but a few. Is 'off' only in horizontal position. Incredible!

125 York Street, SYDNEY. Ph. 290-3377

#### WATCH THIS SPACE

AND FIND OUT WHAT YOU MISSED Each month all of our stores feature an outstanding special which is actually **BELOW COST! N.B. Specials are** strictly while store stocks last. Don't miss out!

#### LAST MONTH:

PLESSEY SPEAKER (5x3", 15 ohm) FOR 38c - NORMALLY S1.50

SAVING \$1.12

WHAT'S THIS MONTH'S SPECIAL? CALL IN AND FIND OUT YOURSELF!

#### \*\*\*\*\*\*\*\*\*\*\*\*\* STOP PRESS!

Our new DUTY FREE STORE will be open in HONG KONG shortly. A new deal for Australian travellers: HONG KONG (duty free) prices with AUSTRALIAN guarantees!

NOTE: Prices and stock availability could change between publication deadline and on-sale date due to circumstances beyond our control. Please check with our stores for latest availability and prices.

## PARTS FOR **NEW KITS**

	SEPARATE PARTS:	00	. 11 0 4 5 5	\$29.50
	PC Board (only)	Ca	+ H-8356	\$3.50
	TA7214P IC	Car	7-2504	\$7.00
	Zippy Box ,	Ca	H-2752	\$3.75
	PLAYMASTER AM/FM TUNER (See Nov/Dec E	A)		
	Complete kit, including instructions	.Cat.	K-3494	\$159.50
	SEPARATE PARTS			
	Pre-wired and aligned tuner module	Cat.	F-4610	\$59.00
	Set of 4 PC Boards	.Cat.	H-8357	\$9.75
	Signal strength meter	Cat.	Q-2100·	\$4.95
	Tuning meter - centre zero	.Cat.	Q-2095	\$4.95
	Most other electronic parts for this project in stoc	k.		
	MODEL TRAIN CONTROLLER (See October EA			
	Not produced as a kit - all parts available from sto	ock:		
	PCB only	Cat.	H-8355	\$3.75
	Zippy box	Cat.	H-2752	\$3.75
	2N3055 transistor	.Cat.	Z-2145	\$0.95
	2N3053 transistor	.Cat.	Z-2130	\$0.80
	UNIVERSAL MOVIE MIXER (See September EA	()		
	Complete kit, including instructions	.Cat.	K-3492	\$49.50
	SEPARATE PARTS:			
	PC Board (only)	.Cat.	H-8354	\$2.95
	50k A curve 45mm slider pot	. Cat.	R-1980	\$0.85
	Knobs to suit slider pot	Cat.	H-3780	\$0.40
п	FET INPUT AC-DC VOLTMETER (See September	F EA	.)	
	Not produced as a special kit - all parts available es	x-sto	:k:	
п	PC Board (only)	.Cat.	H-8353	\$2.75
	1mA MRA-65B panel meter	Cat.	Q-2060	\$12.50
	rabricate your own meter scale using the Scotchca	al pro	CBSS:	
	8005 black Scotchcal photo-sensitive aluminium	Cat.	H-5694	\$6.00
	CA-3140 FET op-amp	.Cat.	Z-5417	\$2.50
п	VARI WIPER Mk 2 (See September ETI)			
-	Not produced as a kit - most parts available from s	tock		
	Relay	Cat.	S-7125	\$4.80
	C106YI SCR	.Cat.	Z-4315	\$1.00
	2N2646 (DS2646) unijunction	Cat.	Z-1786	\$1.20
	LIBCO ADED 40/200441- EDED COUNTED ID		44.	
١	UPGRADED 40/200MHz FREQ. COUNTER (See	Aug	ust EA)	
	Same style as previous kit, but new circuitry mean	S IT IS	easier to	
	build, set up and is more sensitive. Basic counter is by adding a single 95H90 IC the range is extended	401	- 2111	
-	Committee the standard of the range is extended	to 21	DUMHZ.	
п	Complete kit for 40MHz, inc. instructions	.Cat.	K-3437	\$99.50
	95H90 IC to extend range to 200MHz SEPARATE PARTS:	.cat.	2.5360	\$12.50
	PC Boards (set of two high quality boards)	Cor	H 9246	*0.50
ı	MC-10116L IC (triple differential amplifier)	Cat.	M-8346	\$8.50
	MM-5369M IC (cocillator - divider)	.Cat.	Z-5415	\$1.95
ı	74C926 IC (4 digit counter)	Cat.	Z-3/81	\$2.50
	3.579545MHz crystal (new low price)	Cat.	K 6021	62.00
ď	LT-303 7 segment display	Cat.	7.4102	\$3.00 61.50
	All other components are normal stock lines at all	. val.	2-4103	\$1.50
۱	ourer components are normal stock lines at all	UT OL	ir stores.	
۱				
	NEW 10 GAME TV GAME KIT (See July EA)			
	Complete kit, including instructions	Cat.	K-3491	\$49.50
	SEPARATE PARTS:			



147 Hume Hwy, CHULLORA. Ph. 642-8922 162 Pacific Hwy, GORE HILL, Ph. 439-5311 30 Grose Street, PARRAMATTA. Ph. 683-1133 ADELAIDE 203 Wright Street, ADELAIDE. Ph. 212 1962

MELBOURNE 399 Lonsdale Street, MELBOURNE. Ph. 67-9834 656 Bridge Road, RICHMOND. Ph. 42-1614 BRISBANE 166 Logan Road, BURANDA. Ph. 391-6233

MAIL ORDERS P.O. Box 747, Crows Nest, N.S.W. 2065. Post and packing extra. Dealers across Australia.

SHOPS OPEN 9AM to 5 30PM (Saturday 9AM 12 noun) 8RISBANE 1'2 Hour earber

Fully built audio modulator ......

PCB (only) ... Cat. H-8344 ... \$3.95
Fully built RF modulator ... Cat. K-6040 ... \$3.00
Fully built audio modulator ... Cat. K-6042 ... \$4.50
AY-3-8600 IC ... ... Cat. Z-6852 ... \$15.00

.Cat. H-8620

.Cat. Z-6856 .Cat. K-6040

Many lines available from the Bick Smith Electronics Contre

#### GRACE BROS

MAJOR DICK SMITH DEALERS: Listed below are the names and addresses of dealers who stock a large range of our products - however we cannot guarantee that the dealers listed will have all items in stock and at the prices advertised.

GM Electronics Crystal TV Rentals Ptv Ltd Lismore Kitronics

Sumner Electronic

78 Brisbane St Tamworth NSW Ph 66-1363 44 Brown Road, Newcastle NSW Ph 691-222 99 Fitzmaurice St, Wagga NSW Ph 21 3044 40 Princes Hwy Fairy Meadow NSW Ph 83 1219 66 Crystal St, Broken Hill NSW Ph 6897

Shop 15, Treasure Island, Coffs Harbour Jetty NSW Ph 521 570 95 Mrtchell Street, Bendigo VIC Ph 43 1977

Citcom Electronics **ADS Electronics** Aero Electronics Gawler CB Centre 11 Altronic

Hopkin's Arcade, West St, Mt Isa QLD. Ph 434 791 Hopkin's Areade, West St, Nil Sa GLD, Pri 434, 7312 Oxley Ave Marqate QLD Ph 204 1276 5a The Quadrant, Launceston TAS, Ph 31 7075 123a Bathurst St, Hobart TAS, Ph 34 8232 5 Elizabeth St, Mt Gambier SA, Ph 256 404 51 Hillier Road, Evanston SA, Ph 222 149 87 Hannan St. Kalgoo-lie WA Ph 211 906



## Peter O'Neill and the Metric System: We stand accused and plead guilty

Easily the longest letter in our mail for the month was one from a reader in South Australia, who protested bitterly about an article on "Electronics and the Metric System" in the July issue. Having dismissed such articles as "pontifications to be devoutly disseminated to the masses by the subservient media" he proceeded to set out in detail his own strongly held anti-metric views.

I read the letter, as did Editor Jim Rowe, and we discussed at some length whether we would publish it. Ultimately we decided against so doing, not because we are censors at heart, or disciples of metrication, but simply as an exercise in editorial discretion.

If this sounds sinister, I hasten to add that, implicit in every issue of the magazine there are many, maybe dozens of such decisions: what goes in, and what stays out. As a matter of course, we cull through all the material on hand and fill the available space with what we believe to be most pertinent at the particular time.

In the case of the letter in question, our reactions could be summed up as

follows:

 By and large, its contents had all been expressed before, by many people in many places. Readers other than dedicated antagonists or protagonists would most likely find its further repetition tedious.

 A great deal of anti/pro metric argument, involving currency, weights and measures, has nothing directly to do with electronics, however significant the personal and social implications.

 The publication of a couple of pages of anti-metric material would be the signal for a spate of non-electronic correspondence, thereby compoun-

ding the problem.

Most of the correspondence so generated would be at a superficial, even emotional level. While many may feel strongly about the subject, few (me included) really have the background or the resources adequately to equate short-term disadvantages with long-term benefits.

And that's really what it's all about. Those are basic editorial reasons, which would have applied just as forcibly had the correspondent been a champion of the cause. That, too, has all been said before!

Our reasons for publishing the original article by Peter O'Neill were

essentially pragmatic.

Like it or not, Australia, along with many other nations, has officially opted for the Metric system as the most effective way of rationalising the hotchpotch of weights and measures around the world. We simply feel that it is constructive to aid, rather than frustrate, moves towards international standardisation.



"It's our new Imperial model. It converts frequency in Kilohertz to wavelength in rods, poles or perches!" (With acknowledgement to "Electronics Weekly").

And, of course, Peter O'Neill's article dealt primarily with a branch of technology which is of sufficiently recent origin to have world-standard units and world-standard decimal derivatives. What a bind if we had to convert Australian conventions to those of other countries before we could compare potential, current, resistance, &c!

Is it any less a bind, having to convert

Is it any less a bind, having to convert other quantities involved in just about everything else we do? May not the effort be worthwhile, in the long run, to achieve international standards overall?

To be sure, even those of us accustomed to decimals have suffered some confusion with the changed units but the fact is that we do fairly soon acquire a familiarity with those we actually use. And the more complete the change, the more shortlived is the trauma.

A few years ago, the page sizes, picture sizes and column dimensions in this magazine were all expressed in inches and fractions of inches. At the suggested time for the printing industry, we changed over to metric measure. There's no way now that anyone on our staff would want to revert to inches and fractions which, by comparison, are clumsy to use, or express or to set in type. Quite automatically we think and work in millimetres or centrimetres as appropriate. (yes, centimetres!)

But, while saying this, I must agree with criticis of the Metric system (S.I.) that some of its conventions are based on curious logic and that this shows through in the pronouncements of the local Metrication Conversion Board. However, I do not see this as a reason to reject the whole concept out of hand. Rather would I hope that useage and commonsense will obviate some of the apparent inconsistencies — or make us less conscious of them!

#### PRINTING PROBLEMS

If I might get away from the original "some people hate metric" theme, Peter O'Neill's article did highlight a quite different problem which faces any journal carrying technical material, which is typeset on ordinary newspaper/magazine facilities. On the plus side is a good selection of type faces, speed and economy; on the minus side is the difficulty of inserting Greek letters, superior and inferior characters, and other than simple mathematical symbols.

They can be physically added to the typeset material as, indeed, some of them were for Peter O'Neill's article—as a matter of necessity. But there was, and is, a penalty: every non-standard symbol frustrates the flow of highly organised and automated procedures and becomes a significant component in overall setting and make-up costs. We avoid them wherever possible.

For example, the MCB prefers, and technical writers expect, that the Greek letter "mu" should be used as an abbreviation for "micro". Unfortunately, it is not available on normal photosetting discs or keyboards and so, in an effort to contain production costs, we substitute the English letter "u", as in uF, uH, uA, &c. It so happens that the MCB concedes that this liberty may have to be taken — along with a few others.

However, the Board is not so flexible when it suggests: "a thin space should be left between number and unit sym-

bol: 20 A NOT 20A".

There are two problems here. The first is that a normal computer controlled typesetter has no provision for a thing called "a thin space". The keyboard operator can only group letters close-up (as in a word) or spaced (as between words). If the latter, then the computer can expand those spaces as necessary in the process of "justifying" the line — i.e., making the line fill the full column width. What ideally should be a "thin space" may easily turn out to be a rather unsightly thick space!

(Note what the computer did with the word "justifying" in the above

paragraph).

The second problem follows on. It is the computer which decides how many words will fit into each line and it does this in accordance with inbuilt instructions involving vowels, consonants, punctuation marks, spaces, etc. If it encounters spaced characters such as 20 A, it will regard them as individual words, which may legitimately be separated, with the 20 on the end of one line and the A on the beginning of the next.

If one obeys the further rule "A.h. NOT Ah" the hazard is increased. Thus the expression 20 A.h has two chances of being broken up, with part of it on one line and the rest of it on the next. By setting it simply as 20Ah, the computer treats it as a word, to be accommodated as such, if at all possible.

The fact of the matter is that, if one insists on using conventions which are likely to produce an odd result, and also insists that each and every odd result be fixed when it occurs, then one must expect a higher typesetting charge. That this could be significant is confirmed by our printing contractors.

When it forms part of cleanly presented, plain language text, the time component in a single paragraph of an article like this is quite short, maybe a

couple of minutes.

But if the computer produces an unacceptable line turnover, it is rejected by the proof readers and returned to the keyboard operator. As a special job, he has to re-set a group of lines, or the whole paragraph, with manual intervention to prevent the computer from merely repeating its original "error". The tape is then fed into the photosetter, the bromide recovered




# "HOW TO TURN ELECTRONIC THEORY INTO PRACTICE AND MAKE IT PAY.".

"If you understand and enjoy radio and electronics and want to extend your knowledge and experience, then we at Stott's can help you.

Stott's have home-study courses for complete beginners in Radio theory and basic Electronics through to the standards

needed to maintain and service Colour Television.

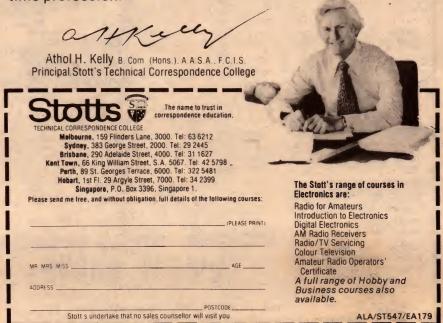Anyone who has these skills at their fingertips can make it pay by turning a fascinating hobby into a lucrative part or full time profession."



## PORTABLE OSCILLOSCOPES

Big Performance In A Small Package

MS-15 MINISCOPE



**AUTOMATIC** And Line Sync Modes \$358.00

MS215 MINISCOPE



**Dual-Trace-2 Channel** Separate, Chopped Or Alternate Modes

#### **FEATURES**

- 15 megahertz bandwidth
- External and internal trigger
- Weights only 3 pounds with batteries
- Size: 2.9"H x 6.4"W x 8.0"D.

For further information, contact Non-Linear Systems, 61 Lothian Street, North Melbourne, Vic. 3051. Phone 329 9951 or your closest distributor.

Radio Parts Group Pty Ltd Ph. (03) 329 7888

Radio Despatch Service, Ph. (02) 211 0191

QLD

L. E. Boughen & Co., Ph. (07) 36 1277

OLD

**Electronic Components (Qld)** Ph. (07) 371 5677

S.A.

**Protronics Pty Ltd** Ph. (08) 212 3111

\* Plus 15 per cent sales tax if applicable.

#### Dannebrog Elektromekano System 76000 for HF SSB/ISB Communication HF SSB/ISB TRANSMITTER S 76000

Frequency Range: 1.6 MHz to 30 MHz, the frequency increment being 100 Hz

MES064: Memory for 64 frequencies with corresponding modes

Frequency Stability: ±3 parts in 108

Types of Emission:

A2H and A3H, A3A, A3J with A1, A2H and A3 3 kHz BW USB

LSS230: LSB instead of USB ISS230: A3B with 2 × 3 kHz BW ISS260: A3B with 2 × 6 kHz BW FD6000: F1 (RTTY)

**Output Power:** Model S 76210:

SSB/ISB: 1000 W PEP, nominal 1000 W, nominal (continuous)

Model S 76150: SSB/ISB: 500 W PEP, nominal CW: 500 W, nominal

#### SSB/ISB RECEIVER M 76000

Frequency Indication: 7-digit eletronic display

Frequency Stability: Better than ±3 parts in 10°

**Modes of Reception:** A1, A2, A2H, A3, A3A, A3J and Options

LSM230: LSB instead of USB ISM230: A3B FD6000: F1 (RTTY)

**Spurious Rejection:** 

Cross Modulation: 100 dBµV unwanted signal produces 1% cross modulation

120 dB relative to 1µV causes a change of 3 dB in output level **Spurious Emissions:** Less than 10 9 W

Image Rejection:

IF Rejection: 100 dB

RF Controi: **Automatic:** 

An increase in input level of 120 dB above 2µV emf will produce a change in output of ess than 4 dB

Frequency Range: 10 kHz to 30 MHz

Frequency Setting:

tal keyboard. In addition, the frequency selected can be increased or decreased in steps of 100 Hz at variable speed for searching, using a single knob. A clarifier control provides fine tuning in steps of 5 Hz.

Option MEM064: Memory for 64 frequen-

cies with corresponding modes

Frequency is selected via a digi-

intermodulation:

20 dB SINAD for 1µV input from 1.6 MHz to 30 MHz. Reduced below 1.6 MHz

Sejectivity: A3A, A3J, A3B: Pass band, -3 dB: 250 Hz to

3000 Hz

90 dBµV per signal produces equivalent input signal of 30 dBuV

Pass band, -6 dB: 350 Hz to 2700 Hz

Pass band, -3 dB: 250 Hz to

A1, A2, A3, A2H, A3H, F1: "Very narrow": 0.2 kHz - 6 dB

'Narrow' 1 kHz - 6 dB 'Intermediate": 3 kHz - 6 dB "Wide": 8 kHz - 6 d Other filters on special order 8 kHz - 6 dB,

input Impedance: 50 ohms above 1.6 MHz

### VICOM

PROFESSIONAL

68 Eastern Road, Sth. Melbourne. Vic. 3205. Australia

DIVN

Dannebrog Elektronik AS

Telephone: National (03) 699.6700 International 61 3 6996700 TELEX: AA30566 GOODEAC CABLES: "IZYCOM" Melbourne


#### FORUM — continued

and re-read, and passed on to the compositor to be substituted for the reject paragraph. The disruption to routines may add several minutes to the time component of every paragraph so affected.

If one is in the publishing business, with the need to balance the budget, one does not lightly invite this kind of complication, by adding spaces and full points which are not strictly necessary

to preserve the sense.

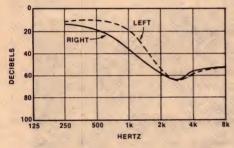So, if you notice that some of our conventions are not in line with Peter O'Neill and his MCB, or with your favourite set of standards, it is not simply because we are being stubborn or hard to get on with. It is more likely that, in a choice between efficiency and pedantry, we sometimes favour the former!



To change the subject to something at a more personal level, recent discussion about hearing problems has prompted a letter from a Victorian reader, who is anxious to offer what encouragement he can. He has this to say:

#### Dear Mr Williams,

As a reader of many years standing, I read with great interest your discussion on hearing problems and aids. Perhaps my personal experience might assist some other reader.

For many years, I complained that people spoke too softly or indistinctly to me. My wife, bless her, finally induced me to have a hearing test. I found that I had nerve deafness. I was then 56 years old; I am now 64.

An aid helped considerably and I still remember my first visit to the country after it was fitted. I could hear insects and birds again! I still had some difficulty with conversations in noisy situations, but not to the same degree.

The aid had the usual volume control, a preset tone control and a clipping device which could be also preset.' This I found of doubtful value as it in-

troduced distortion.

Over the years my hearing deteriorated and I found it increasingly difficut to cope with social and business situations. I am a counsellor in a youth group and am associated with elderly citizens homes and church groups.

I approached a consultant who kindly allowed me to try several aids. I settled on one which has overcome most of my problems. It has an electret microphone, AVC, the usual volume control, and also has an overall gain control which can be adjusted to the individual.

In noisy areas I am now reasonably comfortable, the AVC takes care of that and clarity is astonishing compared with my previous aid, perhaps due in part to the mic. I tried an aid with compression, but this, I found, reduced clarity. I transferred my old aid to my other ear and use it for extra boost at lectures, etc.

My aid is switched on when I arise in the morning until I go to bed (about 16 hours) and consumes one 675 battery in 10 days.

I am writing this letter to you in an effort to induce those who have a problem, admitted or unadmitted, to seek help. In my work, particularly among older people, I have seen miraculous personality transformations when a person hears once more. As you mention, it is sometimes difficult to come back to a noisy world from a comfortable silent shell.

Could I suggest that you publish a list of the many excellent organisations who have facilities, many free of charge to help those with hearing loss? Some come to local clinics and local halls, schools etc. if requested. They teach you how to listen, an accomplishment many of us lack, but also cover every aspect of hearing and referral for

assistance.

I have not seen any reference to tinnitus (head noises) in your articles. It amazed me how many people, particularly those with hearing loss, have it. In my case I have a singing noise, very loud at times, around 5kHz. The hearing aid helps me by raising the outside sounds above the level of the noise.

Best wishes to the publication, H.C. (Footscray, Vic.)

Appended to H.C.'s letter is an audiology test chart which he had taken recently. Without pretending to any expertise in this matter, it would seem to me that H.C. is a good candidate for a hearing aid. His loss of mid frequency is serious but not profound and, considering his age, he seems to have retained a surprising amount of response around 8kHz. What's more, his two ears are quite well balanced, which is the right situation for a stereo

While people with 80-100dB loss would face a much greater problem, the chances are that there are plenty of others who could share H.C.'s experience. Particularly should this be so with hearing aids using true AGC, as distinct from the rather distortionprone peak limiting systems.

H.C. refers to "the many excellent organisations who have facilities, many free of charge, to help those with hearing loss". We do not have a list of such organisations on hand but, if anyone does, we would be happy to consider it for publication.

## printed circuit

- nolic & fibreglass-gold tin plated
- EA R & H ET Philips Mullard available
- · Specials to your drawing
- POSTAGE small 80c large \$1.10

700000		78DB11	2.80	78UP9	4.80
78BBD9 650B	3.50 2.60	555 650A	4.00 4.00	650C 138	2.60 3.80
718	2.60	553	3.00	811	3.30
.590B 78E09	8.00 2.50	590A ET605	8.00 7.00 3.00	78MC10	4.00 2.50 ON/APP
ET391A	2.50	ET551	3.00	ET391B ET641 ET592	ON/APP
78UT9	2.20	78MX9	2.80		4.50
78UM8 ET638A	16.00	78CL8	3.30	78T9 ET638B	2.30 3.00
ET638A ET591	4.00 4.00	ET248	2.30	ET318	7.00
78TSC7	2.50	ET810 78PT7	2.80 2.50	78TM8 78VBG7	2.80 3.50
ET137B	2.80	ET137A	3.50	ET139	2.50
ET717 78F6B	3.50 3.50	ET587	7.00	78A06	16.50
246	4.00	489B	2.50	489A	2.80
78CD4	2.60	78P\$5	2.50	78C5	3.20
78UP5	4.20	ETI40D	4.00	ET140A ET487B	14.00 7.50
ETI140P ET487A	5.50 7.50	ET136 ET588 20	2.50 10.00	78NG4	3.00
78UT4	4.00	78EK3	3.30 2.60	78T3	3.60 2.60
78B2 E T450A	3.00 -2.80	781A2 ET716	1 00	ET4508 ET715	3 00
ET486	3 20	ET245	2 56	78C2	3 00
78AF2	3 00	78\$3	2 60	78CF1	2 80
77CB12 -ETi35	2 60 3.00	77PH12	2.60	77PM12 77MX11	3 50
775C11	3.80	ET586 77P\$11	2.50	77MX11 77UP6A	2.50 3.00
77MX11 ET504	2 50	77SC11 ET585T/R	3 00	77PS11 ET635	2 50 2 80 6 50
ET713	3 00	ASCII	2.80 3.00	77UP11	6 50
77759 ET134	3 00 2.60	ET603 77AL8	2.50	77T10	2 50 2.50
77DVM9	2.80	ET065	2.20	ETO71	2.20
ET067 ET072	2.20	ET063 ET085	2.50	ET083 ET084	2.20 2.50
ET485	2.80	ET484	3.00	ET581	2.50
ET481M ET547	2.50 2.50	ET582B ET317	2.60	ET582A ET712	3.00 2.50
7707	2.50	7787	.2.80	770LT7	6.00
77UP6 ET631/2	3.50 4.50	77TTY7 ET481PS	2.80 3.00	77QBF7 ET444M	3.20 2.00
ET444S	3.00	ET316	2.50	ET549A	2.50
ET548 77PTY7	3.20	77TTY6 77PTY6	2.50	HMS276	6.00 2.60
77E05	3.50	77PRE5	2.50	17UP5	8.50
ET081	2 20	ET062	2.50	ET546	2 50
77CC4	4 00 3 00	ET632 77UP2	7 00 3.00	77TTY4 ET132	2 50 2.50
ET632C	8.00	ET632B	6.50	ET632A	6.50
77UT2 ET633FR	3. <b>00</b> 6.00	77F1B 77UT2	2.50 3.00	77F1A ET633	3.20 6.00
ET632P	2.50	ET632M	7.50	ET4828	2.80
ET482A	6.50	76CL12	2.50	ET630	2.20
7684 ET631	7.00	ET480PS ET630	2.50	ET480 ET066	2.20
ET064	2.00	ET449	2.20	ET804	2.80
ET448A ET711B	2.20	ET448 ET068	2.80	ET711C ET061	2.00
ETO44	2.00	ETO43	2.00	76M19	3 50
ET711R ET544	2 50 2 50	E1711D 76PC9	6 00	E1447 76EX10	2.80 2.80
ET602	6 50	ET446	2 50	ET533A	C 350
ET711A	7.50	ET5438	2.50	ET543A	2.50
ET445 ET780A	2.50 3.00	ET241 ET541	2.80 2.50	ET780B ET444	2.50
7657	2.50	76M17	2.80	76LM5	3.00 2.50
76SS6 76M5	3 00 2.50	76SW4 76VG5	2.00 5.00	76R4 76E04	2.50 3.00
76VG5	5.00	76M5	2.50	76R4	2.50
ET708 ET514	2.50	ET740A ET707A	4.50 2.50	ET7408 ET7078	3.50. -2.50
ET706	2.50	ET130	2.50 2.50 2.50	76RT3	3.00
76T2	2.50 5.50	76A03 75SWILA	2.50 Bpr4.00	76G3 DRS-RC1	2.50 4.00
76E02 75PC12	2.50	EA78F1	2.80	ET534	2.50
ET514	2.50	ET129	2.50	ET28	2.50
ET439	3.00	ET4206	2.50	ET1238	2.50
ALL SI	LICO	N 30/	60w I	PA	

#### ALL SILICON 30/60w PORTABLE AMPLIFIER

"w x 812"D x 314"H 12 - 16V, two inputs 5 & 100mV. 125, 250, 500 ohm output only. No. 763A \$70 ea. 240V operation \$33 extra. Freight collect. COILS and IF's All \$2.50 ea plus post 60c

> MAIL cheque or money order (add postage) direct to -

## radio pty Itd

651 FOREST RD BEXLEY NSW 2207 587 3491




## What P.A. Amplifier sells itself? —The H.H. MA100

A compact and portable powerful mixer amplifier which has achieved outstanding success in Europe, it features: Five separate controllable channels. — Individual Bass, Treble Volume and push button Reverb on each channel. — 10 inputs (i.e. two per channel) available. — Master Volume, Master Presence and Master Reverb control the final mix to the integral 100 watt power amplifier. — Superb crystal clear sound for the vocalist.

Additional features include Auxiliary Input for connecting two MA. 100's together giving ten channels (i.e. twenty inputs), Echo send and return and Slave output connections.



## H. H. SOUNDS A LOT BETTER

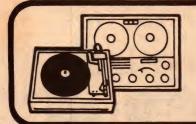

## Hi Fi News

#### 20.000 MASTERS: PORTRAIT OF A DISC RECORDING ENGINEER

Early in 1978, Frank Hulbert - Mastering Engineer at Astor Records, Clayton, Victoria, Australia — cut his 20,000th disc. This achievement is one which may startle many "experienced" experts in the cutting business, and boggle the mind of the novice.

#### by BILL HAWTIN\*

Frank's experience and expertise has earned him the respect of the recording industry in Australia, and has also surprised visitors from many of the foreign companies represented in Australia by Astor.

With such a background, what Frank has to say is well worth noting, as are his

three principal "gripes":

• The mastering engineer has to salvage studio disasters all too frequently - and without credit for his

\*Bill Hawtin is President of the Audio Engineering Society (Melbourne Chapter). Private address: 77 Canterbury Rd, Canterbury, Vic 3126.

effort in so doing.

• Too many Australian artists and promoters are ignorant of the expertise and equipment available in their own country. They prefer to "worship" anything done overseas, without even taking the trouble to see what can be done in Australia.

Despite the fact that the record industry depends heavily on the work of engineers, their work is given small recognition. They tend to be regarded as part of the equipment.

Predictably, perhaps, Frank's pet hate is the person who knocks the local product as "the thing to do" and finds



Frank Hulbert: from do-it-yourself battler to the engineer responsible for the quality of recordings cut at the Melbourne plant of Astor Records.

merit only in imports. Fair comment is one thing; "fashionable" bias is quite another!

Like many engineers in the audio business, Frank started the hard way by doing it himself, without tuition. He sees, as a sad commentary on a sophisticated industry that, even in Australia today, there are few, if any, training courses oriented to audio engineering.

Frank was born in London, UK. His working class parents could not afford to have him trained as an instrument maker, his career preference. He was obliged to leave school at the age of 14, so that he could contribute to family income.

As it transpired, his first job was as a "tea-boy" at an electrical manufacturing company. His aptitude for electro/mechanical devices soon led to promotion to the position of lathe operator, and he spent about a year turning bushes for tuning capacitors and similar hardware.

An asthmatic condition, which has continued to plague Frank throughout life, was aggravated by the factory conditions. He moved, at the age of 15, to work in a live theatre as a stage hand and assistant property master. His most important show in this period was "The Maid Of The Mountains", staged at the London Coliseum theatre, and it gave him a feeling for the world of showbiz.


In 1943, he joined the army, and



Frank Hulbert (centre) sets up the microscope to inspect the grooves of a directcut disc which has just been completed at the Astor plant in Melbourne. Anxious to see how it turned out are members of the Steve Murphy Quartet, who had just made the recording. (See our August 1978 issue, page 27).
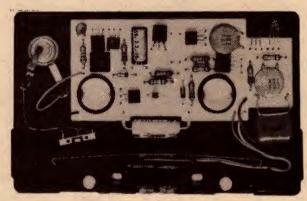
## TDK's Revolutionary New Product — The HD-01 Head Demagnetizer Built into a Cassette Shell.






## Simply load the HD-01 into any cassette recorder as you would a standard audio cassette and depress the 'play' button.

The HD-01 Head Demagnetizer was designed by TDK for easy, convenient head demagnetization of any cassette deck, insuring crystal-clear, perfect recordings every time.
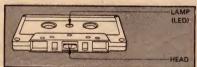
#### The TDK HD-01 Head Demagnetizer features:

- A unique cassette format, designed to insure complete compatibility with any cassette deck.
- Powerful de-gaussing circuit instantly demagnetizes recorder heads the moment the play button is depressed. The above diagram depicts the oscillating waveform applied to the recorder heads, removing every trace of residual magnetism in only one second!
- A red LED (Light Emitting Diode) built into the HD-01 cassette shell will light up the moment your recorder heads have been completely demagnetized.





The TDK HD-01 Head Demagnetizer ends forever the fuss and mystique surrounding the demagnetization process and is much easier to use than conventional wand-type tools. Anyone can use the HD-01 and get perfect results every time.

The TDK HD-01 Head Demagnetizer is completely self-contained, battery operated and portable. It can be taken anywhere and stored with your present audio cassettes. The TDK HD-01 is ideal for all types of cassette decks especially those with heads located in hard to get at places such as:

- recorders with heads positioned in the front of the unit but which point to the rear.
- those with 'pop up' loading mechanisms which can not be detached, thus making the heads almost inaccessible.
- cassette decks with heads positioned laterally with respect to cassette loading (car decks are good example of this type).
- automatic loading machines.


#### WHY IS DEMAGNETIZING SO IMPORTANT?


TDK, in conjunction with many cassette deck manufacturers, recommend that cassette decks be maintained on a regular basis. Cleaning the heads, capstan and pinch rollers is one important aspect of that maintenance program. — ?eriodic demagnetizing, about every thirty hours of use, is the other. Failure to do so will cause a build-up residual magnetism on the heads, which can seriously affect tape and machine performance in the following critical areas:

- The noise level in the low and midrange frequencies is increased by 5 to 7dB, thereby reducing the overall signal-to-noise ratio.
- Pre-recorded tapes can also be affected with midrange and high frequency distortion, as well as attenuation by as much as 2 to 6 dB, virtually eliminating any hopes for clear sound reproduction.

The interaction of these factors will not only prevent both the tape deck and tape from displaying their true performance capabilities, but will severely limit the Dynamic Range properties of both, rendering pure sound reproduction an impossibility.

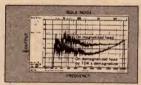The following comparison data clearly demonstrates the effect of residual magnetism on recorder heads in the areas of both Noise Level and Frequency Response.



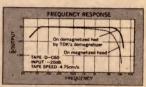

#### TECHNICAL DATA

Major Components: Transistors (8) Diodes (2) LED (Light Emitting Diode)


Power Supply - Control Section - Oscillation Section - Head Section

#### **Specifications:**

Maximum Magnetic Flux Density Oscillation Frequency Shape

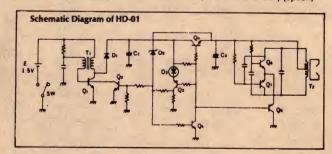**Battery for Power Supply** 

200 Gauss 630 Hz (External Dimensions) Conform to IEC Standards G-13 1.5 volt, Silver Oxide Battery (option)



For additional information, direct all inquiries to:

#### CONVOY INTERNATIONAL PTY. LTD.

4 Dowling Street, Woolloomooloo, N.S.W. 2011 Telephone: (02) 358-2088. Telex: AA23111



#### HI FI NEWS — Cont.

served as a Bofors gunner in the forts in the Thames Estuary. (Some of these forts were used later in the sixties as sites for the contentious "pirate" radio stations.) As a gunner, Frank learned to operate radar equipment and gunnery predictors, and his involvement renewed his interest in electronics.

In 1946 he left the army, and took a position as a comptometer operator. He hated it. "Figures aren't my bag, I was too interested in music, and got into importing discs from the United States." The discs were jazz, early Stan Kenton 78's and the like, and he sold these throughout the UK by mail order.

Through his dealings with these records, Frank became interested in disc cutting, and in 1948 purchased some portable gear. He recalls that the first side he cut was a 78 dub of Woody Merman's "Apple Honey". "At the time, I thought it was terrific — strictly illegal of course. In retrospect, it was probably bloody awful!"

He started taking the recorder to jazz clubs, and with the aid of a single microphone, produced live recordings of doubtful quality.

of doubtful quality.

The first group he recorded live was the Ronnie Scott Boptet, at the Club II. (In 1978 he cut his first Ronnie Scott disc as a professional engineer.)


The acetates produced from the live sessions were sold to musos and jazz fans for 15 shillings each. This enterprise led to an association with a photographer. They pooled their talents, and sold records on their own "Discfoto" label, together with photographs of the artists:

Soon after leaving school, Frank had also started playing drums, and the jazz club atmosphere in which he now worked enabled him to expand this activity. In the fifties he played percussion with an outfit called the Burne Regal Quartet, with an electric accordion as the featured instrument. The band played for food and drinks at weddings and balls. He later became a professional musician and played in many London clubs.

The tape era opened for Frank with the purchase of an early model Ferrograph. By modern standards, it produced "ghastly" tapes but he had them cut on LP discs, and sold them through the jazz magazine "Melody Maker". In 1950 he helped form the Glen Miller Society, and takes pleasure in noting that the Society is still very active. Later he produced Johnny Dankworth's first recording session, which sold well on the "Tempo" label.

The London smog was aggravating Frank's asthma and, at the recommendation of relatives, he moved to Australia in 1955. In 1956 he joined Mercury Records in Melbourne. The record company was housed in a
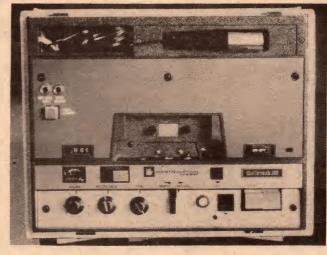
## "Wollensak" tape recorders, duplicators and teaching aids from 3M Aust.



Model 2551, a portable mono recorder with audio visual capability, including a public address facility.

3M Australia Pty Ltd has announced the release of a line of eight different "Wollensak" cassette recorders, cassette duplicators and language teaching aids.

Mr David Henderson, Product Manager for 3M Australia's MinCom Division, stresses that the units being introduced into Australia is the most recent generation of a range that the Company has been producing in the USA for over 20 years.

As a starting point, the model 2520ES is a heavy duty mono recorder with the emphasis on ruggedness and operational simplicity. It offers a response from 50 to 10,000Hz with a power output of 9W RMS into 8 ohms. Model 2551ES has similar basis specifications but includes facilities which enable it to be teamed with a slide projector for cued audio visual presentations.

Several models in the line are intended specifically for cassette duplication. The 2970AV is a portable high-speed duplicator which will produce a single copy at 13½ times original speed.

The 2770ES has facilities for producing two mono copies

The 2770ES has facilities for producing two mono copies simultaneously and has auto-stop and alarm facilities to alert the operator in case any one of the cassettes should malfuction. The 2772ES goes one step further in being able to provide, not only two simultaneous copies of mono tapes but, as well, copies of stereo tapes. Up to three further copies can be produced with the aid of the 2780ES add-on duplicator.

For those interested in language lab facilities, the Wollensak 2526ES provides the heart of such a system, being intended to operate in conjunction with the 10ES Lab console. It can serve up to 10 students, each wearing headsets and each with access to the learning track.

For further details inquire at 3M offices in capital cities around

For further details inquire at 3M offices in capital cities around Australia or direct to the Corporate Publicity Department, 3M of Australia Pty Ltd, PO Box 99 Pymble, NSW 2073. Tel (02) 498 0033 Ext 488.



The 2770 monophonic duplicator capable of producing two C-30 copies in just over one minute.

#### HIFI NEWS - Cont.

tin shed in the suburb of Richmond, and his first job was to listen to jazz records. "I'm getting paid for this?"

In those formative days the masters were dubbed on a Connoisseur lathe from imported pressings, often of poor quality. The overall quality of the subsequent copies was atrocious by today's standards. Later, the company purchased a Neumann lathe — one of the first in the country.

Frank became involved in inspection and "quality control", and when the company, now Astor Records, moved to the suburb of Huntingdale he helped design the matrix testing section. He then moved to tape editing and dubbing. In 1966 he was appointed to the position of mastering engineer, and the first side he cut in this role was a Tom Paxton single. He ruined this by inscribing the matrix number over the cut-out groove!

He has now been operating Neumann lathes for 12 years, and ironically, the 20,000th cut was a direct dub from an imported Greek pressing.

Anyone who has been in the audio business for very long always has a fund of anecdotes, and Frank is a goldmine of humour. His worst job was cutting 37½ minutes of re-issue Caruso tracks on one side of an LP.

The strangest task was to cut an album entitled "The Sounds of Silence" — two 12-inch sides of silent tracks of varying length — "to be played at any level without disturbing the neighbours.

But his pet story concerns another engineer who diligently cut a set of masters, marked them with matrix numbers and packed them for processing, without realising that he had failed to apply signal to the cutting head!

The shortest LP Frank has cut was Trini Lopez album which ran for the magnificent time of nine minutes per side!

Frank rates his involvement in the first direct-cut disc produced in Australia as his most exciting assignment. This was carried out for the Melbourne Jazznote label and, as the music was jazz, he was delighted.

His worst moment was the incidence of swarf problems during the direct-cut exercise.

Frank lives with his wife and family in the Melbourne suburb of Boronia, in the foothills of the Dandenong ranges. His hobbies are fixing things, and "my kind of music — jazz". Jazz has always been his first love, and in Australia he was involved for a period with an independent jazz label.

But, when he recently discovered himself tapping his feet to a steam train tape he was cutting, Frank decided that, maybe, he has been in the business too long!

#### REFURBISHING A BRAND IMAGE: PORTRAIT OF A HIFI EXECUTIVE

A recent visitor to Australia was Mr Herb Horowitz, Vice President of Teledyne Acoustic Research, of Boston Mass., USA. He was guest of honour at a function arranged by Acoustic Research Australia, who assembled, distribute and service AR loudpseakers in this country.

Primarily, Herb Horowitz' purpose was to emphasise the virtues of the current range of AR loudspeaker systems and, in particular, of their AR9, which was created with the design objective of being "the best loudspeaker in the World". While the AR9 is a story in its own right, Herb Horowitz also provided an interesting insight into the thinking and planning which brought to fruition the current very extensive AR range.

Many years ago, as a relatively young engineer, Herb Horowitz had founded the Empire Scientific Corporation, offering a range of prestige hifi products which were well known in Australia, with their characteristic burnished gold finish.

Subsequently, Herb Horowitz sold his interest in Empire to Harmon/Kardon, stayed with them for a while, and then decided to retire early in order to enjoy a life of leisure. But, after a few weeks of surf and sunshine, he became thoroughly bored and readily accepted an invitation to rejoin Harmon/Kardon with a specific task in view: to troubleshoot and revitalise the Tannoy operation, in which they owned a controlling interest.

With this assignment behind him, Herb Horowitz was approached by Dave Mulchler, President of Teledyne Acoustic Research, to do the same sort of thing for the AR loudspeaker line. He accepted the invitation and was named as Vice-President, in which role he visited Australia — apparently enjoying his "retirement" no end!

Years ago, AR had been number one for loudspeakers on the American market but, for reasons which were not immediately obvious, it had gradually slipped down the list. Firm action was needed to identify the problem areas and to reverse the trend.

Having accepted the assignment, Herb Horowitz' first step was to spend several weeks visiting hifi shops, examining their displays, listening to their sales spiels, seeking their reactions, and so on. One thing soon became obvious:

In most hifi stores, stereo loudspeaker systems were displayed with the grille removed from one of each pair to show the drivers. The AR



units looked okay with the grille in position but, without it, the finish looked rough. It shouldn't have mattered, but it did — for a reason which also became apparent.

In a typical store, there would be a dozen or more systems on display at any one time but a given customer might listen to three or four of them, at the most. Which three or four depended on a variety of factors but, numbered prominently among them, was eye appeal without the grille. For Herb Horowitz the first job was obvious: Improve the finish of the baffle assembly so that it had a professional, quality look to at least match that of its competitors.

That way, the AR systems would stand a better chance of being selected for audition.

Next came a statistical survey on the market which showed that success or failure depended on what happened in about 400 key hifi outlets spread across the USA. Sell well in those outlets and you had it made; miss out and the rest didn't really count for much.

Ignoring those loudspeakers that were brand-tied to complete systems, the key hifi shops might typically concentrate on four brands, say: JBL, Advent, Bose and AR. The problem was to somehow get AR back to the dominant position. How could the range best slot into the market?

Among the loudspeakers mentioned, the JBL range tended to be up-market, the Advent down-market and the Bose somewhere in the middle, with its particular philosophy of dispersed sound. The AR range was nowhere in particular!

Ultimately, it dawned on Herb Horowitz that the self-classification of its rivals posed a problem for the salesman, from which he might relish an escape. Either he or the customer had to start somewhere in their consideration of the systems on offer and. as often as not, discussion produced a shift up or down the price range. In the process, the salesman, having built a particular brand image, suddenly had to switch to another. Why not save him

the embarrassment?

So the idea of a complete AR family was born, which would range from the least pretentious system that the company could regard as hifi, to something that might reasonably aspire to be the very best. The salesman could steart at any price level that seemed appropriate and sell up or down as necessary, without ever needing to switch brands.

But, for a family image, there had to be a family likeness and this was lacking in the AR range, which had been built up spasmodically over the years. The task was not just to expand the range by plugging in extra models, but to harmonise the appearance of the whole and to devise a way in which they could be displayed to advantage.

And here, a leading US advertising agency made certain important contributions. They confirmed that the AR image was blurred. "Acoustic Research" could be a name or a motto; or was AR the name, or A&R or what?

Apart from that, the product had a stuffy, conservative image, heavily orientated towards traditional classical music — and therefore to a minority market in terms of potential buyers.

As Herb Horowitz explained: It wasn't that anyone was unhappy with the sound of AR speakers; they generally agreed that it was fine. It was just that the vast majority of hifi buyers - who are younger people with a variety of musical tastes - did not iden-

tify with the product.

From all this, the new AR family emerged: with careful attention to the baffle finish, with a harmony in exterior design and a new, modern AR logo. And it spanned the whole range from a compact bookshelf (rated at 100 watts) to the ambitious (and expensive) 400watt AR9. No less importantly, the various models had the same general balance in sound quality, so that there were no acoustic shocks in switching from one to the other - just the expected refinement that follows more and larger drivers and larger enclosures - all of the sealed variety, by the way.

And there was new look promotion, with an emphasis on modern rather than traditional classical music. Indeed, AR stress that their systems are as well suited as ever to the classical field; it's just that they want a much larger slice of the majority market involving younger buyers.

And, to judge from what Herb Horowitz has to say, they are getting it. The trend of a few years back has been reversed and AR is heading back towards the top in the vital markets.

Maybe AR should keep Herb where he is, until he really retires, just in case another manufacturer asks him to repeat the effort on their behalf!

PLESSEY COMMUNICATIONS SYSTEMS have added three new public address amplifiers to their product range. The UD-10 is an economy 10W model intended to meet a wide range of needs such as in office and industrial reception areas. It has a built-in electret microphone, a sloping panel with recessed controls and an ivory finish. Supplementary input facilities are provided for external microphone, tape recorder, record player, etc. Higher powered companion amplifiers are the UP-15 and UP-30, with multiple input facilities and power ratings of 15W and 20W respectively. Plessey Communications Systems are at 87 Racecourse Rd, North Melbourne 3051, and in other capital cities and Townsville.

#### New AM, FM tuners from Audiosound



Representing a welcome change from normal practice, two new radio tuners just announced by Audiosound provide the opportunity for better than normal quality from AM stations. The AM 101 is, in fact, an AM-only tuner offering variable selectivity, a 9 or 10kHz whistle filter, low distortion and coverage to 1750kHz. It uses manual rather than automatic gain control and has an easy-to-read tuning meter. The

T 751 tuner also provides good AM reception but combines it with a high performance FM-stereo facility, featuring a special muting circuit and LED indicator for easy and accurate tuning. For further information: Audiosound Electronic Services, 148 Pitt Rd, North Curl Curl 2099. Tel. (02) 938 2068.


#### Recording Engineering & **Production Courses**

If you are serious about Audio Engineering and are willing to attend lectures, hard study and and practical, contact
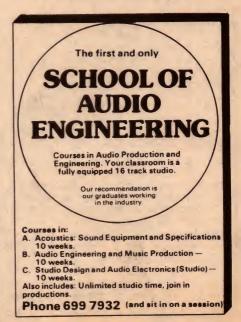
#### John Burnett & Steven Penning

A.S.R.E.

Tin Pan Alley Recording Studios, 54-56 Alfred Street, Milsons Point, 922 6301.



#### THE BEST OF BRITISH!

## **NEW!**

#### **G900 SUPER E MARK 2**

- Total weight only 4 grams.
- · Genuine tracking weight 1 gram.
- New construction process (patent applied for) achieves lower inductance, resulting in even lower mass and flatter frequency response.
- Improved clearance between record and cartridge body, enabling even the most severely warped records to be played.
- Micro nickel tie bar welded to magnets acts as earth path and as movement control for the system.
- Specially shaped Butyl polymer pad provides optimised damping.
- Micro miniture magnet and ultra thin walled hard aluminium alloy tube fitted with elliptical, naked diamond point result in low intermodulation distortion with excellent tracking at both higher and lower frequencies.
- Every G900 SE Mk 2 is tested to exacting tolerances.



FOR TECHNICAL EXCELLENCE IN HI-FI PICK-UP CARTRIDGES AND REPLACEMENT STYLI LOOK FOR

BRITISH MADE

Goldring

**ENGLAND** 

Australian Distributors for Goldring Products Ltd., U.K.

#### SOUNDRING DISTRIBUTORS

1/514 Miller St., Cammeray, 2062. Tel. (02) 92-1990

#### AGENTS:

VIC: Jasper Coote Pty. Ltd., 304 Coventry St., Sth. Melbourne, 3205. Tel. (03) 699-4455

ACT: Jason Enterprises, 47 Wollongong St., Fyhwick, 2609. Tel. (063) 80-6519 QLD: Sound Accessories, 22 Dunbil Ave., Ferney Hills, 4055. Tel. (07) 351-4737 — Green Brothers (Wholesale) Pty. Ltd., 83 West St., Rockhampton. Tel. 27-3047; 467 Flinders St., Townsville. Tel. 72-1544

## DISCOTHEQUE LIGHTING

ILLUMINATED DANCE FLOORS

WHITY ACRYLIC PLEXIGLASS 8'x4'x6' MODULAR

ALL SIZES MANUFACTURED TO REQUIREMENTS



● Low profile electronic dance floors ● Computerised wall lite units and display system ● Lighting + effects equipment + projectors, mirror balls, etc. ● Programmable lighting controls

chasers and musicolers ● Disco consoles — stereo + mono 200 and 400 watt power amps ● High power DC 300A Crown amplifiers ● Installation sale and hire of all equipment including party hire.

Available from

#### **CASH-MORE SOUND**

149-151 GEORGES RIVER ROAD, CROYDON PARK NSW 2133. TEL. 798 6782 298 5647

#### HIFI NEWS — Continued

A range of five new turntables under the brandname "Harksound" all feature low profile, European styling, with gun metal grey chassis, smoked acrylic lids and a black-finished straight tone-arm with offset head, rather than the more usual S-shaped, plated design. Harksound claim that the straight, unplated arms have acoustic advantages. The models HS 210 and HS 310 are belt drive semi-automatics; the HS 510 and HS 610 are direct drive designs with floating platter and tonearm assembly, while the top-of-the-line HS 910 has a quartz PLL speed control. The 210, 310 and 510 are fitted with Ortofon cartridges. For information: Harman Australian Pty Ltd, P.O. Box 6, Brookvale NSW 2100. Tel (02) 939 2922.

"SOUNDS VINTAGE" is the name of a new magazine which is to be produced on a bi-monthly basis, in England. Devoted primarily to the sounds of yesterday, it will cover vintage wireless equipment, gramophones and cylinder machines, vintage amplifiers and relevant pre-war literature. Articles will deal with the restoration and care of such equipment, stories of the pioneers, etc. Editor and Publisher will be Colin Riches, formerly Production and News Editor of "Practical Wireless". "Sounds Vintage" will comprise 32 A4 pages and will be available on subscription only, the rate being £6.80 for overseas subscribers. For further details: "Sounds Vintage", 28 Chestwood Close, Billericay, Essex, England.

BASF AUSTRALIA LTD, like the parent company, are still chafing at what they consider was an inspired "whispering" campaign to discredit chromium dioxide tapes on the grounds of head wear. Whatever might have been the merits or demerits of other companies' coatings, whether chrome or iron, BASF have been at pains to stress that their own chromium based coatings bear more than favourable comparison with their competitors' non-chromium counterparts.

Their latest batch of literature makes firm claims that their normal BASF Chromdioxid causes less headwear than popular chrome substitutes; that their Chromdioxide Super is better, in this respect, than either TDK SA or Maxell UDXL-II. This last statement, they would obviously have to be in a position to justify — or else! But, having made the point, they concede that the SA and UDXL tapes show excellent head wear characteristics anyway, leading to the conclusion that, in respect to the four tapes being compared, head wear is a non-issue.

ELMEASCO INSTRUMENTS PTY LTD, importers and manufacturers of electronic testing and measuring instruments for industry, research and communications, have been appointed Australian sales and service representatives for the Time Data, Acoustic and

Electronic Instrument Divisions of Genrad Incorporated of Massachusetts USA. Genrad Inc., were formerly known as General Radio Company.

(Elmeasco will not be representing the Test Systems

Divisions of Genrad.) Elmeasco Instruments, with sales offices in Sydney, Melbourne, Brisbane and Adelaide, are represented in Perth by Cairns Instruments Services.

The Genrad 1977/78 catalogue is

rad.) Elmeasco available by contacting any of the sales offices in Elmeasco sales offices or direct to:

available by contacting any of the Elmeasco sales offices or direct to: Elmeasco Instruments Pty Ltd, 15 Macdonald St, Mortlake, NSW. Postal address: P.O. Box 30, Concord NSW 2137. Tel (02) 736 2888.



## TASMAN ELECTRONICS

12 Victoria Street, Coburg 3058. Phone (03) 354 5062

FOR TOP QUALITY COMPONENTS
AT ROCK BOTTOM PRICES


Transistors & ICs, resistors, capacitors, transformers, switches, wire and cable, diodes, bridges, SCRs, triacs, audio and TV leads, plugs and sockets, power supplies & adaptors, stylii, DMMs, calculators, instrument cases and boxes, knobs, heat sinks, fuses, cassettes, batteries, TV antennas, musical instruments and accessories, etc, etc.

We are also dealers for "AIWA" quality hi-fi products.
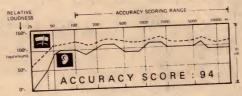
## STOP PRESS

**CONSUMER REPORT MAGAZINE RATE** MARANTZ HIGHEST ACCURACY SCORE IN HIGH PRICED LOUDSPEAKERS!







MARANTZ HD880 40% x 16 x 13% in. 62 lb. Bass half-loudness point: Very good (40 Hz). Freedom from bass distortion: Better than average. Power range required: 25-60 watts. Impedance: 4 ohms. Comments: Has very-high-frequency level control. Has removable bass-port plug to increase bass (see story). Had highest accuracy with tweeter control set at % of maximum, other controls set at maximum, and % of maximum, other controls set at maximum, and bass-port plug in.

Competitive	Accuracy Rating
FSS AMT 1B	
YAMAHA NS69011	92
AR 10 TT	90 -
EPICURE 400	90
ALTEC MODEL 15	89
DAHLQUIST DQ10	89
	89
JBL L166 PIONEER HPM 100	89
	88
JENSEN 550	87
EV INTERFACE C	86
ADS 810	
INFINITY QUANTUM	9
BOSE 901 SERIES 11"	
KLIPSCH HERESY HV	VO 83

The Report, which was prepared by the highly respected American organisation, Consumers Union, combined computer and laboratory measurements with expert listening tests to show that Marantz HD880 was the most accurate in a group of

listening tests to show that Marantz HD880 was the most accurate in a group of 14 highly regarded Hi Fi Loudspeakers.

"In CU's view, the most meaningful single standard for judging loudspeaker performance is accuracy - a speaker's ability to reproduce sound energy smoothly and uniformly over the entire musical spectrum. The higher a speaker's accuracy, and uniformly over the entire musical spectrum.

and uniformly over the entire musical spectrum. The higher a speaker's accuracy, or fidelity, the more fully it can respond to the entire spectrum of musical sound, from the tinkling of a triangle to the deepest tones of an organ."

But the sad truth is that most speaker manufacturers have given up on the accurate loudspeaker. Instead, they produce models with booming bass, sizzling highs and great vocal presence, and call it "personality". Trouble is, that "personality" doesn't come from the music at all, but from shortcomings in speaker design that actually distort sonic accuracy and create coloration. that actually distort sonic accuracy and create coloration.

Marantz chose instead, the more formidable task of working toward a loud-speaker which is as accurate as theoretically possible. When you combine accuracy with Marantz quality, YOU HAVE A WINNER.

## FULL COPIES OF REPORT AVAILABLE ON REQUEST

Superscope (A/Asia) Pty. Ltd. 32 Cross St. Brookvale. N.S.W. 2100 Tele: 939 1900



# **Technics SA-400 stereo receiver**

The Technics SA-400 is one of four new stereo receivers recently released on to the Australian market. The SA-400 is most powerful of the group, with a rated power output of 45 watts per channel for a bandwidth of 20Hz to 20kHz. The line is of particular interest because it represents a new engineering approach by Japanese manufacturers.

Compared with previous models, superficially there is not a great deal to indicate that a different approach has been taken with the new Technics SA-400. It has all the features normally found on a stereo receiver in the medium price range.

Overall dimensions of the Technics SA-400 are 430 x 142 x 300mm (W x H x D), including knobs and feet. Mass is 8.2kg. Those figures by themselves show the results of the new approach—the new receiver is appreciably smaller and lighter than some of its competitors.

Styling of the Technics receiver is low keyed, with brushed aluminium front panel and knobs to match. The control layout is well thought-out and easy to drive. There are two large knobs at the right-hand end of the panel; the upper knob is for tuning and is flywheel assisted. The knob below is the volume control and this is detented (40 detents in all).

We do not see the point of having 40 detents on the volume control, since it has neither logarithmic calibrations nor better than usual matching between sections. The Balance, Bass and Treble controls do not have detents.

Two push-buttons provide for selection of two pairs of loudspeaker systems. These buttons are neddlessly small, however and thus seem to require more than usual pressure. The buttons on the cheapest model in the line, the SA-100, are larger. Why?

High and low filters are included in the control line-up but, like filters on most amplifiers and receivers, they are inadequate in effect because of their modest slope of 6dB/octave.

A mono/stereo switch was one fature omitted which we find useful, albeit mainly when testing. It is handy to enable reproduction of a mono source through both channels.

Some receivers and tuners we have tested in the past have had too much dial illumination. The SA-400 is almost the opposite. In brightly lit rooms it is difficult to tell, by sight, whether or not it is on. At night or in dimly lit rooms, the dial illumination is just right. Perhaps the brilliance needs to be adjustable.

We also found the meters a little too deeply recessed for convenient use when tuning the receiver — unless the meters are almost at eye level.

On the rear panel, a noticeable change is the omission of the usual adjustable ferrite rod aerial for AM reception. Is this an admission by Technics that most users seldom have room behind their receivers to hinge out and correctly orientate the rod antenna, or is it just an economy measure? Whatever the answer, the rod is now relegated inside the receiver, to a fixed position above the tuning gang.

Another noticeable change concerns the loudspeaker connections. Previously, most amplifiers and receivers from Japan have had spring loaded terminals. On the SA-400, a different termination is used. The bared wires are pushed into a plastic fitting, which is then twisted to lock it.

which is then twisted to lock it.


This is a desirable feature since it shrouds the loudspeaker connections, prevents accidental contact by the user and also prevents short-circuits. Shrouded loudspeaker connections of one sort of another will eventually be a mandatory feature on all amplifiers and receivers capable of producing more than 32 volts RMS, according to an IEC recommendation.

Besides meeting the local standards concerning mains power connection, the Australian version of the SA-400 is the first receiver we have seen with isolating capacitors in series with the FM and AM antenna connections. Thus the antenna circuitry appears to conform to the intent of Australian Standard AS 3159 (Electronic Sound & Vision Equipment).

This involves the use of suitably rated antenna input coupling capacitors, so that a catastrophic fault within the receiver does not raise the possibility of electric shock via the antenna cable or the antenna itself.

Removing the timber cover reveals the major differences between this receiver and those produced up to now. For quite some time this reviewer has felt that typical receivers and amplifiers from Japan (and elsewhere, for that matter) have been far too complicated in their mechanical assemblies. There have been very complex chassis, expensively tooled front panels, multitudinous PCB assemblies and nightmarish wiring.

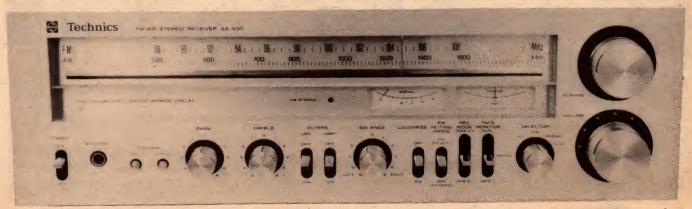This has meant, quite frankly, that the larger receivers have been nightmares to service. Fortunately, most of this equipment has been very reliable.



#### **TECHNICS SA-400 STEREO RECEIVER**

Now, however, the Japanese designers seem to be taking a simpler approach, as evidenced by the SA-400.

as evidenced by the SA-400.

Two large PC boards accommodate all of the circuitry. All the input and output connections and all the switches and controls are soldered directly to these boards. This means that apart from the mains wiring to the power transformer, there is very little "wiring" at all. Access to the underside of the two PCBs is gained by removing the hardboard base panel of the receiver.

So for the first time, we have a receiver of this power rating and circuit complexity with excellent accessibility to all parts of the circuit. This makes service easier, but the fact that there is such a great reduction in individually soldered or wire-wrapped joints must also increase the reliability of the design.

Most of the circuitry uses ICs. This is most apparent in the tuner section, where the limiter/detector, multiplex decoder and AM circuitry are all ICs with little in the way of ancillary discrete semiconductors. The phono preamplifiers are also integrated circuits using seven-lead in-line

The power amplifiers have a number of interesting features. First, there are no power transistors as such, with their individual sockets and connections thereto. Instead, there are two "Darlington power packs", one for each channel, bolted to the large heatsink assembly and each connected to the PCB by nine pins. Each of these

the differential input stage. It takes the form of a single transistor and diode arranged as a modified current source load for the output collector of the differential input pair.


Technics have not made a great deal of this feature and readers would be correct in concluding that it is another minor circuit variation. Yes, it evidently does work but other circuit variations might have been included which could have produced an equivalent result.

As in most receivers in this class, the

the bandwidth of 20Hz to 20kHz.

At a test frequency of 1kHz, we measured 50 watts per channel with both driven into 8-ohm loads, at the onset of clipping. With one channel driven, the figure rose to 57 watts. With 4-ohm loads the power was almost the same, at 56 watts per channel with both driven or 66 watts into one channel. With 16-ohm loads, the power output is 33 watts per channel with both driven and 36 watts with one channel.

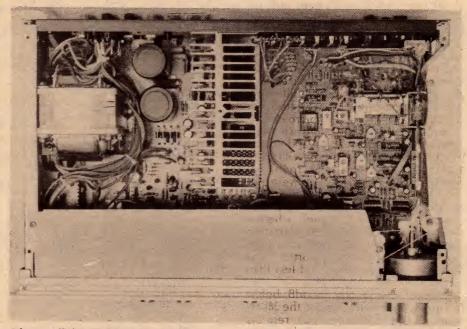At 20kHz, the harmonic distortion was above the rated figure of 0.04% but at powers of 20 watts and below it was 0.1% or less, which is still very good. Intermodulation figures were not quite as good as rated, but also quite



Almost all the wiring of the SA-400 is on two large PCBs, producing a neat interior.



packages contains not only the Darlington power stages of a conventional complementary output stage, but also the quiescent current stabilising circuit.

The early stages of the power amplifiers incorporate a "current mirror" circuit which is alluded to on the dial of the receiver. The "current mirror" is actually borrowed from integrated circuit technology and is used here to improve the symmetry of

SA-400 incorporates comprehensive protection circuitry which also eliminates switch-on and switch-off thumps.

Performance testing reveals that while the SA-400 might be lighter and more compact than its direct competitors, the results are directly comparable. Power output is rated at 45 watts per channel into 8-ohm loads, with both channels driven, for a rated distortion of 0.04 per cent or less over

creditable.

Frequency response at one watt into 8 ohms is 1dB down at 10Hz and 40kHz. RIAA equalisation is rated at ±0.2dB over the range 30Hz to 15kHz, but we measured the limits as ±1dB, which is more to be expected considering the tolerances of components in the equalisation networks. Still this is quite OK.

Phono sensitivity for 10 watts was 1.25mV at 1kHz. Signal to noise ratio

with respect to 10 watts and 10mV input was 66.5dB unweighted with a typical cartridge connected. These figures are about average. As with most receivers with conventional laminated core transofrmers, the noise figure can only be obtained if the turntable is 60cm, or more, away from the unit. Phono input overload is more than adequate at 250mV at 1kHz.

Using the auxiliary inputs the signalto-noise ratio is 76dB with respect to 10 watts, while separation between channels was 53dB at 10kHz and 54.5dB at 1kHz and 100Hz. Sensitivity for the 10W reference power was 73 millivolts RMS.

Stability testing with capacitances shunting the load revealed no

problems in this regard.

Reference to the tuner quieting performance graphs shows that they are marginally better than for other receivers in the class. The meter response characteristics are also perhaps a little more useful, although the meter is virtually saturated for signals of more than 500 microvolts.

Tuner frequency response was, almost identical in mono and stereo modes, within  $\pm 2dB$  from 30Hz to 15kHz which leaves little room for complaint. Separation figures were also very good, particularly in the midrange. Harmonic distortion was specified for 40kHz deviation, whereas we normally test at 75kHz deviation (100% modulation). Using the latter conditions, harmonic distortion was less than 0.2% in mono and less than 0.3% in stereo.

Residual 19kHz was —34dB below full modulation output while the 38kHz residual was -49dB. These residual signals have to be filtered out to produce the figures for signal-to-noise ratio, and separation between channels

and harmonic distortion.


Once again, the AM tuner in the SA-400 is just about as poor as any in typical Japanese stereo receivers — at least its narrow bandwidth will mean few problems with 9kHz heterodyne whistles.

Accessories provided with the SA-400 comprise a simple dipole antenna for FM reception and a packet of fuses for the loudspeaker protection block on the rear panel.


A comprehensive manual is included with the SA-400, and a full circuit diagram is supplied. Warranty is for 12 months from date of purchase.


Our overall impressions of the Technics SA-400 are favourable. It is well-designed both electrically and mechanically and should give many years of trouble-free performance. Recommended retail price of the SA-400 is \$489.00 including sales tax.

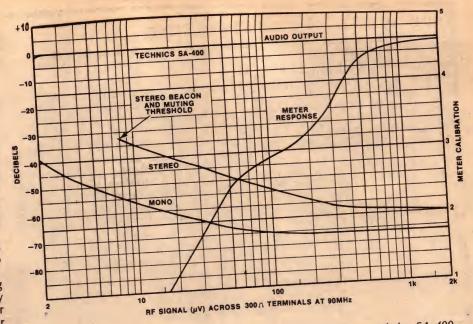Further information on Technics equipment can be obtained from high fidelity retailers or from the Australian distributors, National Panasonic (Australia) Pty Ltd, 57-59 Anzac Parade, Kensington, NSW 0233. (L.D.S.)



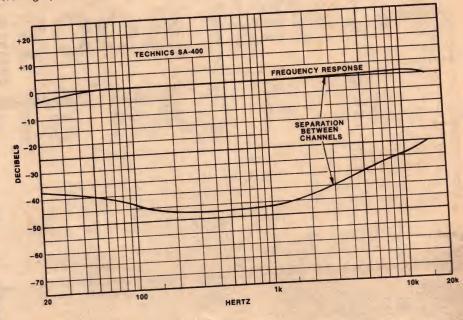These graphs summarise most of the performance parameters of the SA-400.



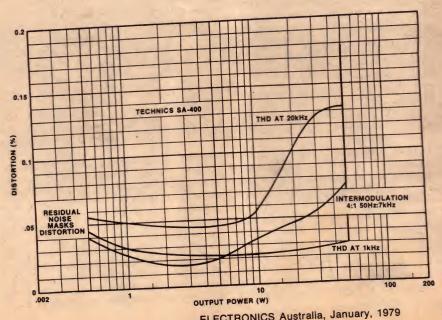

ELECTRONICS Australia, January, 1979



# POWER BOOSTER FOR CAR STEREOS

Does your car stereo system lack the punch and bite of your home hi-fi? If so, build and fit this new booster amplifier. The design is based on a rugged single IC amplifier module, and can supply 12W per channel from a nominal 13.8V DC source. It can be used with all negative earth electrical systems.

by DAVID EDWARDS

Car stereo systems based on either FM radio or cassette signal sources have become quite popular of late, but they tend to suffer in power capability compared with the more usual domestic hifi. A power booster is the obvious solution to this problem, and can be quite an economical addition to the system.

The unit described in this article is intended for connection in the speaker lines between an existing stereo amplifier (such as is normally included in a stereo cassette player or stereo FM radio) and a pair of 4 ohm speakers.

Operation of the unit is controlled by the OFF/BOOST switch, and a LED is provided as a reminder that the unit is turned on. Internal preset volume controls are provided, so that the gain of the booster can be adjusted. Under normal circumstances, the volume of the boosted sound is controlled by the volume control of the signal source.

Our design is based on a new audio

power IC, the TA7241P. This is a Toshiba device, and is mounted in a metal and plastic dual-in-line style package. Each IC contains two independent audio amplifiers, featuring self-centring DC output bias, overload protection, and with a high peak output current capability.

We have used two ICs, one per channel, with each one configured as a bridge amplifier. The load (in this case a loudspeaker), is connected between the two amplifier outputs, and the inputs are driven in antiphase. Since the two amplifiers are integrated onto the one chip, the DC offset between the two output is quite small, thus avoiding the need for an output coupling


The advantage of this scheme is that the effective peak-to-peak voltage across the loudspeaker is now nominally twice the DC input voltage, and hence the nominal output power is

four times that of a single class B amplifier. Of course, the actual output power is somewhat less than this, due to the inherent losses in the output stages.

In practice, with a 13.8V DC input voltage, we obtained an output power into a 4 ohm resistive load of 12W. At an output power of 10W, the distortion is typically less than 1%, while at a 1W output, distortion is typically less than 0.1%.

The distortion is primarily cross-over distortion, with a small element of 2nd harmonic distortion caused by a slight gain mismatch between the two halves of the bridge. The frequency response extends from 50Hz to 100kHz, measured at the —3dB points.

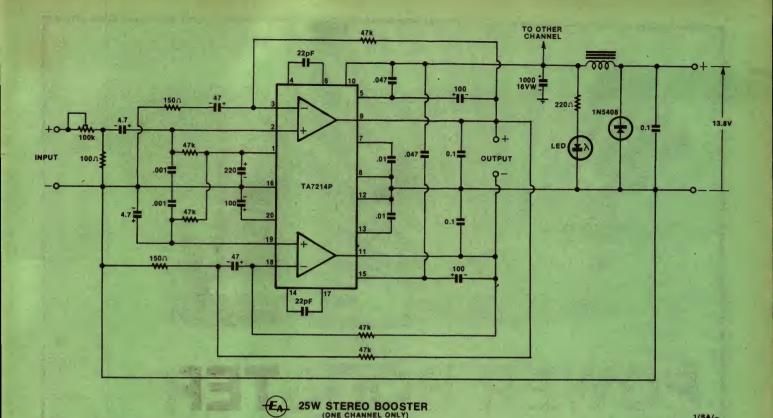Signal-to-noise ratio (with respect to 10W into 4 ohms), is —78dB, while separation between the two stereo channels is better than —51dB. Maximum sensitivity is 26mV, and the quies-



cent current drain is only 70mA. Current drain at full power is 3 amps.

The unit is only suitable for use with cars having the negative side of the battery connected to the chassis, and requires the speakers to be fully isolated from the chassis. The negative input leads of the booster are connected to the chassis.


As you can see from the photographs the unit is mounted in a plastic Zippy box, with the aluminium lid replaced by a more substantial aluminium heatsink which also doubles as a mounting bracket. The unit is intended to mount on the underside of the dashboard.

All of the circuitry is contained on a single printed circuit board, coded 78sb12 and measuring 122 x 80mm. The power ICs are mounted on the copper side of the board, so that they can be clamped directly to the heatsink. The machine screws used to do this also form the board mounts.

The interconnections to and from the unit are made with hookup wire, passing through grommetted holes in the rear of the case. An inline fuse is provided in the positive supply line. This provides protection against excessive currents, and also against supply

This latter facility depends on the reverse connected diode installed across the supply line at the PCB. If the supply polarity is reversed, the surge of current passing through this diode blows the fuse, preventing damage to both the diode and the remainder of the circuit.

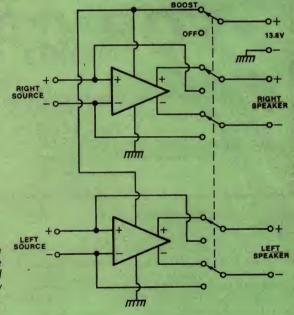The only control for the booster is a two position rotary switch. This serves as both a power switch and as a speaker The circuit diagram above is for one channel of the amplifier only, and shows only the circuitry contained on the printed board.



The schematic diagram on the right shows how the amplifiers are connected to the source stereo by the OFF/BOOST switch.

switch. In the off position, the booster is unenergised, and the outputs from the signal source are connected direct-


ly through to the speakers. In the on or "boost" position, the booster amplifier is energised, and the outputs from the signal source are connected to its inputs. The booster outputs are now connected to the speaker leads.

All of the parts for the booster should be readily available. The TA7214P ICs and the power choke are imported by Dick Smith Electronics, and should be available through the usual sources. The heatsink is fabricated from 1.2mm (185WG) aluminium. A dimensioned drawing is included elsewhere in this article.

The front panel of the prototype was made from self-adhesive photosen-sitive aluminium. A full sized reproduction of the artwork used is included with this article. In due course, commercial panels should become available from the usual sources.

Construction of the unit should be relatively easy, even for inexperienced constructors. Commence by fitting all the hardware to the case, including the LED indicator and the grommets. Check that the PCB mounting holes

1/SA/-

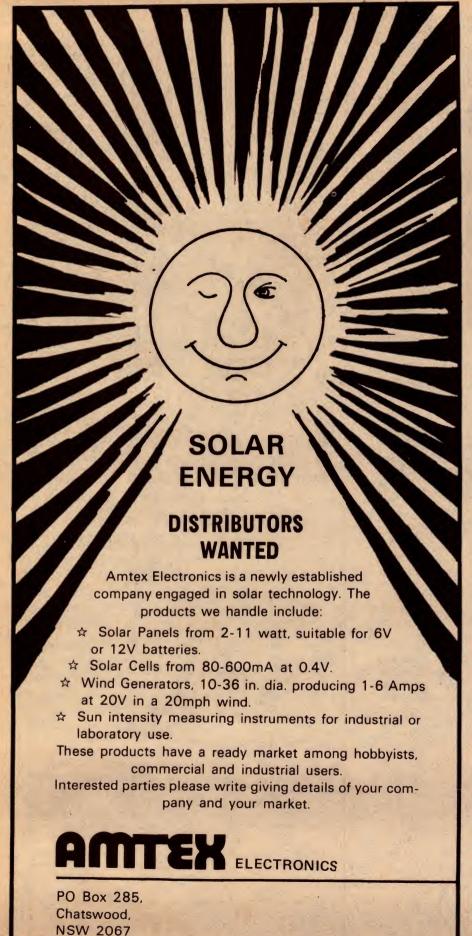

#### 25W stereo booster

align with those in the heatsink, and that the holes are free of burrs.

Now fit all the components to the PCB, apart from the ICs. Check carefully that all the electrolytic capacitors are orientated correctly, and that all joints are soldered correctly. Pay particular attention to the soldering of the mounting lugs of the choke, as these form part of the circuit. Set the volume presets to their mid points.

We recommend the use of PCB pins


for all external connections to the board, as these make the final wiring of the board much easier. The final stage of the PCB assembly is to fit the ICs. These mount on the copper side of the board, and must be orientated correct-

There is a small identifying mark at one end of the IC, signifying pin 1. This must be matched with the appropriate hole in the PCB. Refer to the overlay diagram, and also the PCB pattern itself, which has pin 1 marked
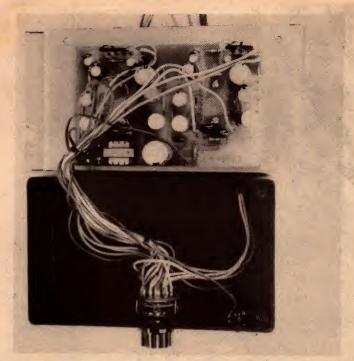
#### PARTS LIST

- 2 TA7214P audio power ICs
- 1 3A silicon diode, 1N5408 or similar
- power choke (see text)
- 1 red or green LEd and mounting clip
- aluminium heatsink (see text)
- 1 Zippy box, 150 x 90 x 50mm
- 2 position 6 pole rotary switch and knob to suit
- printed circuit board, 78sb 12, 122 x 80mm
- front panel (see text)
- 2 rubber grommets
- 4 machine screws and nuts
- 1 5A fuse and inline holder
- Solder, hookup wire, cable clamps, tinned copper wire RESISTORS (all 1/4W)
- 2 100 ohm, 4 150 ohm, 1 220 ohm, 10
- 2 100k 5mm lead spacing trimpots
- CAPACITORS 1 1000uF 16VW radial lead elec-
- trolytic 2 220uF 16VW radial lead elec-
- trolytics 6 100uF 16VW radial lead elec-
- trolytics
- 47uF 16VW radial lead electrolytics
- 4 4.7uF 16VW radial lead electrolytics
- 4 0.1uF polyester
- 4 0.047uF polyester
- 4 0.01uF polyester 4 0.001uF polyester

4 22pF ceramic NOTE: Resistor wattage ratings and capacitor voltage ratings are those used for our prototype. Com-ponents with higher ratings may generally be used provided they are physically compatible.



The photo above shows how the PCB and heatsink assembly is wired into the case. The PCB pattern is reproduced actual size at the right.


Use a minimum of solder for the joints to the PCB, and check carefully when you have soldered all 20 pins that there are no solder bridges. Any such bridges are best removed with the aid of some desoldering braid.

Now mount the PCB assembly to the heatsink, using a small amount of thermal grease to improve the heat transfer characteristics. All that remains now is to complete the internal wiring between the switch and the board.

Use the wiring diagram as a guide, and complete the wiring with multi-coloured hookup wire. We found it advantageous to code the individual wires using paper labels, as not enough colours were available to individually distinguish each wire.

Once the unit is completed, all that remains is to fit and wire it to the car. Start by determining the mounting location, which should be under the dashboard in some convenient place. Try to mount the unit away from either the driver's or the passenger's knees.

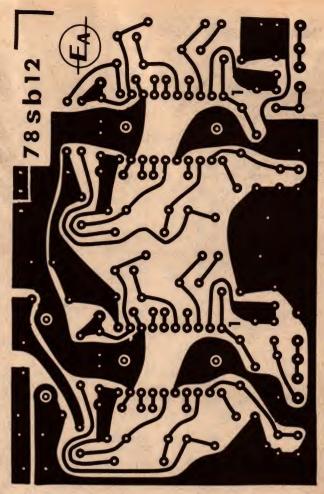There may be existing screws in the dashboard which can be utilized, or it may be necessary to use additional self-





tapping screws. In either case, mark and drill the heatsink first.

Now locate and identify the power wires to the signal source unit. One of these wires will be connected to the car chassis, and this wire must be connected to the negative supply line of the booster. The positive supply line of the booster must connect to the positive supply line of the source unit.

These connections can be made with either the new Scotchlok connectors, or by soldering. In the latter case, the joints must be well insulated. (Scotchlok connectors involve no stripping, soldering and insulating, and are available from auto electricians and also from DSE — cat. no. H-6720).

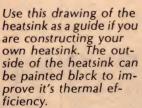Now locate the wiring to the left speaker. There should be two wires. Cut these, and join the speaker ends to



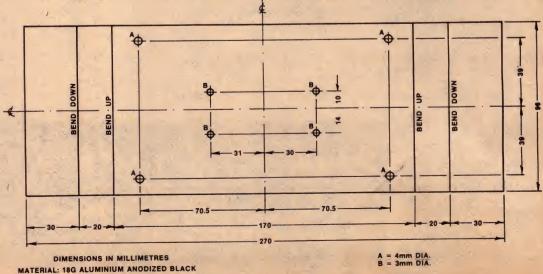

#### 25W stereo booster

the left booster output. Check before you do, however, that both wires are insulated from the vehicle chassis. If they are not, you will have to rewire the speaker so that they are.


Now locate the wire leading back to the source unit which is connected to the vehicle chassis. Connect this wire to the left negative input of the booster, and connect the remaining wire to the left positive input of the booster. Insulate all connections thoroughly.

The right speaker connections are treated in an identical manner to the left speaker connections. Once all the wiring has been completed, go over it and double check for mistakes. Then, leaving the booster switch in the off position, switch on the program source, and check that it operates correctly. At any sign of trouble, switch off and trace and rectify the fault.


With the program source volume control set at minimum, switch on the booster. There will probably be a thump from the speakers, and then silence. Now advance the volume control, and check that sound is coming

from both speakers.

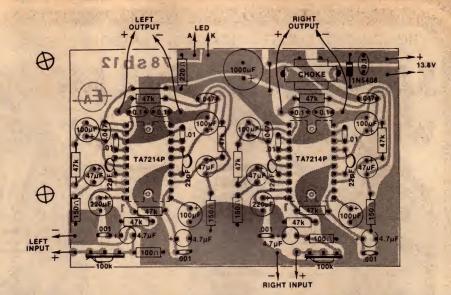
Switch the booster off, and note the change in sound intensity. With the booster on, the sound should be significantly louder. If it is not, adjust the two presets to suit. Do not adjust for too great an increase in intensity, as this will only make the operation of the source volume control rather fierce. It will not increase the available power level.



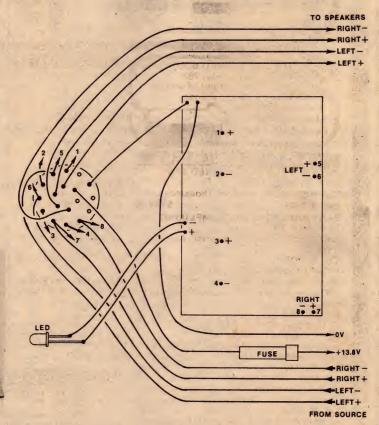Use the overlay diagram above as a guide when assembling the components onto the PCB. Note that the power ICs are mounted on the copper side of the board.



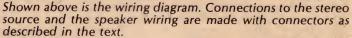The photograph above shows how the PCB assembly is mounted on the heatsink. Use thermal grease to improve the heat transfer rate.



The front panel artwork is reproduced at the right. It is actual size, and may be used directly if desired.



**BUILDING AN ELECTRONIC PROJECT THESE HOLIDAYS!** 

# SAVE TIME ~ SAVE MONEY With a Dick Smith kit and the fini


and the finished project will look so good your friends will never believe you built it!


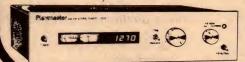
#### PLAYMASTER AM/FM TUNER KIT

(See page 46 November 1978 E.A. and page 42 December 1978 E.A.)

The perfect companion to the legendary Playmaster Twin 25 and 40/40 Amplifiers — matches them exactly. Full digital tuning on AM and FM modes. Inbuilt digital clock — digital readout displays the time at the flick of a switch. Time remains on display even if tuner is switched off. Superb performance with unbelievably good specially written step-by-step 32-page construction manual — exclusive to Dick Smith.



\$159<sup>50</sup>

newl. Boosts

#### CAR STEREO BOOSTER

(E.A. January '79)
Boosts power output of your car
cassette to 12W per channel.

Home-quality sound while you drive!

Cat K-3493 .. \$29.50

#### AUDIO AND AMPLIFIERS

PLAYMASTER 40/40 STEREO AMP. (E.A. December '76)

Our most popular kit ever. Thousands sold. Cat. K-3411 .. .. .. .. .. .. .. .. \$129.50

PLAYMASTER TWIN 25 AMPLIFIER (E.A. May '76)

Similar to above, but less power. Also a great kit.

Cat. K-3410 .. .. .. .. .. .. .. .. \$105.0

ETI480 100W POWER AMP MODULE (E.T.I. December '76)

100 watts for \$25.00? Unreal, man! (mono module)

Cat. K-3442 ..... ..... \$25.0 ETI480 50W POWER AMP MODULE (E.T.I. December '76)

As above, but 50W. Easily extendable to 100W version.

Cat. K-3440 ..... \$19. ETI480PS POWER SUPPLY MODULE

(E.T.I. December '76)
To run either 1 x 100W or 2 x 50W modules.

Cat. K-3438 .. .. .. .. .. .. .. .. \$19.50 MUSICOLOR MK 111 COLOR ORGAN

(E.A. September '76)
Turns your music into light! Just add the

lights.

Cat. K-3140 .. .. .. .. .. .. .. .. \$65.00

ETI601 MINI ORGAN (E.T.I. August '76)
YOU can play your favourite tune in style

Cat. K-3430 .. .. .. .. .. .. \$26.50 LOUDSPEAKER PROTECTOR

(E.A. June '76)

Eliminates turn-on and turn-off surges from most amps.

Cat. K-3425 .. .. .. .. .. \$13.50

#### COMPUTERS, ETC.

2650 MINI COMPUTER (E.A. May '78) ALL parts, case, front panel, power supply, etc. – not a 'part' kit. Ik of memory – a

LOW COST VIDEO DISPLAY UNIT

(E.A. February '78)
Mates with above. Communicate with a

computer!
Cat. K-3460 .. .. .. .. .. .. .. \$97.50
VIDEO MODULATOR for use with VDU

(E.A. April '78) Allows above VDU to be used with any TV

Set. Cat. K-3462 \$4.50

Cat. K-3462 .. .. .. .. .. .. .. .. \$4. ASCII KEYBOARD ENCODER

(E.A. April '78)
Uses our standard keyboard (Cat. X-1180)
Cat. K-3464 ... ... ... ... ... ... \$39.50

CASSETTE INTERFACE (E.A. April '77)
Use any cassette player to communicate with computer.

Cat. K-3465 .. .. .. .. .. .. \$24.50

#### TV GAMES

#### TANK BATTLE GAME KIT

(E.T.I. October '78)

Experience the excitement of commanding your own tank as you navigate through a minefield to destroy the enemy's tank.

Cat. K-3475 .. .. .. .. .. .. .. \$39.50 10-GAME VIDEO GAME

10-GAME VIDEO GAME (L.A. July '78)

Features 4-way bat control, many combinations of bat sizes, ball speeds, angles, etc.

(E.T.I. June '78)
Play 4 different games, motorcross, enduro, drag and stunt, easy to build!
Cat. K-3474 ... ... ... ... ... \$32.50

TEST EQUIPMENT

40MHz DIGITAL FREQUENCY COUNTER

(E.A, August/September '78) Versatile piece of test gear. Easily upgraded to 200MHz by adding 95H90 Pre-scaler IC

(Cat. Z-5360 . . . \$12.50) Cat. K-3437 . . . . . . . . . . . . . . . . \$99.50

NEW MODEL TRANSISTOR TESTER (E.A. July '78)

Checks most transistors and FETs quickly and easily.

Cat. K-3052 .. .. .. .. .. .. \$19.75

R-L-C BRIDGE (E.A. March '78)
Ideal project for the beginner. Handy to have around!

Cat. K-3468 .. .. .. .. .. .. \$34.50

#### AMATEUR CB, ETC.

VK POWERMATE (E.A. May '78) Short form kit — no metalwork, mains wiring etc.

Cat. K-3449 ...... \$32.00 CB POWER SUPPLY

13.8 volts at 2A continuous (4A peak) complete kit.

Cat. K-3448 ... .. .. .. .. .. .. \$29.50 45 WATT VHF AMPLIFIER

F'glass PCB, 13.8V operation. Req. 8 — 12W of drive.

30 WATT 80 METRE AMPLIFIÉR
Ideal for the povice 13 8V. Adaptable to

Ideal for the novice. 13.8V. Adaptable to 50W output.

Cat. K-3133 .. .. .. .. .. .. .. .. \$35.75

#### MISCELLANEOUS

CAPACITOR DISCHARGE IGNITION (E.A. July '75)

Save on petrol; end ignition troubles. Prewound coil.

Cat. K-3280 .. .. .. .. .. .. .. .. \$27.50 DRILL SPEED CONTROL Mk2

DRILL SPEED CONTROL Mk2 (E.A. July '76)

Suits 240V 'universal' motors (not electronically switched or controlled types). A must for the home handyman.

for the home handyman.

Cat. K-3080 .. .. .. .. .. .. .. .. .. \$13.50

HIGH POWER STROBE (E.T.I. August '71) A real blast — ideal for parties, discos, etc. Dazzler!

Cat. K-3150 .. .. .. .. .. .. .. .. \$29.50 TV MASTHEAD AMPLIFIER

(E.T.I. August '71)
Can turn an unwatchable mess into a brilliant picture.

Cat. K-3230 .. .. .. .. .. .. \$32.00

NOTE: Prices & stock availability could change between publication deadline & on-sale date due to circumstances beyond our control. Please check with our stores for latest availability & prices.

SEE OUR DOUBLE PAGE AD FOR FULL LIST OF STORES AND DEALERS





# "Universal" Tacho uses HT pickup

Here is a low cost portable electronic tachometer designed to work with almost any kind of ignition system — conventional, transistor-assisted, CDI, breakerless, magneto or what-have-you. It uses a standard tachometer IC, but feeds it from a special shielded capacitive HT pickup.

by J. de C. GRANDIN A.S.E. (Aust.)

155 The Boulevarde, Strathfield 2135.

This tachometer has been developed to check the speeds of modern petrol engines. Ignition systems today are many and various; some have no breaker points, while twin cylinder 4-stroke motor cycle engines can have firing on each cylinder as each piston reaches top dead centre. Some multicylinder engines divide the ignition lead between two systems. Capacitor discharge ignition systems are in use both in marine outboard engines and in motor cycles. Some have high tension distributors, others use a separate coil for each cylinder.

From all the complexity indicated above, almost the only common factor is high tension feeding a spark plug. Even here there are variations, for spark plugs can have resistors built into them

and can have either metal conductor or resistive suppressor-type high tension leads attached.

In view of these complications, it was decided that the tachometer would need to use a capacity-type pickup from the spark plug lead, in order to cope with the widest range of situations. However, when a simple capacity pickup was tried, it was found that false triggering could be produced due to coupling from nearby leads. The HT pulses have short risetimes, and can couple significant energy even via stray capacitance. In order to overcome this problem, a shielded capacity probe has been developed.

Reference to the circuit diagram will show that the coupling capacity pickup is required to charge firstly the self-capacity of the pickup itself and shielded connection cable. This cable is approximately 1½ metres long, giving a self-capacity of 100pF. The coupling capacity of the pickup to a 7mm high tension lead is in the order of 10pF, thus providing a capacitive divider of about 10:1 ratio for the ignition pulses. Should accidental contact be made to



At left is the author's prototype tacho, made using parts on hand. If you are building from scratch, a larger meter and case could be used to advantage. Above is a close-up of the shielded capacitive pickup probe, partly opened.

the ignition high tension, then provision is made, by means of a spark gap, to limit the voltage rise.

Radio frequency attenuation is provided by a 2mH RF choke. The particular choke used had low self-capacity, being made up of 3 "pies" on a ferrite core. It is suggested that this be the type used. The choke is followed by a 100k/TW resistor which is by-passed by a .0022uF capacitor having a 2kV rating. High voltage will be applied across this capacitor only when accidental contact is made to the ignition high tension. The primary of the coupling transformer is protected by an NE2 neon connected across it, together with a 50k pot. connected to give variable loading, and hence act as a sensitivity control.


The transformer used is one intended for interstage coupling in transistor audio amplifiers. It has a primary of nominal 3k impedance, and a centre-tapped secondary of the same impedance from end to end. The transformer I used came from Dick Smith Electronics, and is listed in their catalog as M-0222.

Half of the secondary is used, to give a 2:1 step down to a full wave bridge rectifier made up of four 1N914 diodes. The output is thus made up of positive pulses no matter what polarity the high tension pulses may be.

A .0022uF capacitor at the output of the bridge rectifier is designed to suppress any RF spikes that may get through. Further protection to the input of the SAK 140 tachometer IC is provided by a 10k resistor. The circuitry around the IC is arranged to make use of non-critical components and to provide ease of calibration. The 100k resistor between pins 10 and 6 and the 0.1uF capacitor between pins 6 and 4 determine the duty cycle. This duty cycle does not exceed 0.8 even at maximum RPM in the two-stroke position.

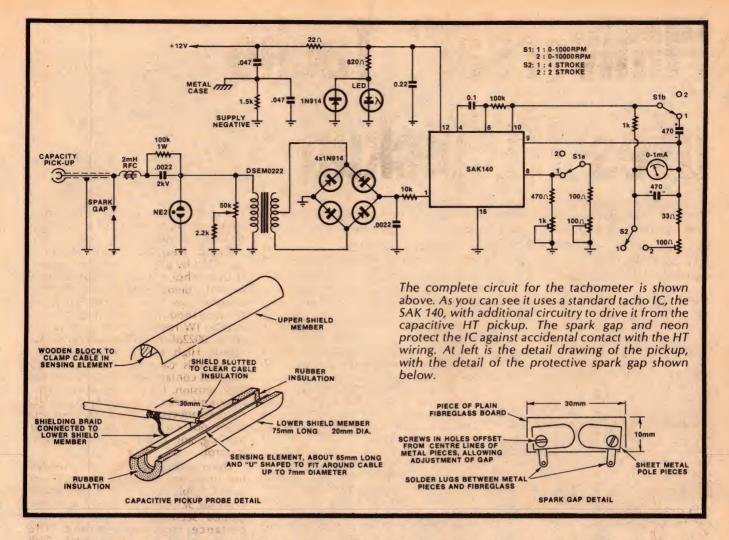In the 0-10,000 RPM position, only one 470uF capacitor is connected across the meter. This allows rapid response without excessive needle flicker. However, in the 0-1000 RPM range, flicker becomes very obvious with only 470uF in circuit. This is overcome by switching in an extra 470uF between pins 9 and 10 and arranging extra current drive for calibration in this range by switch \$1a. Shunting for





calibration in two-stroke mode (or one ignition per rev) is provided by \$2.

As the unit draws less than 20 milliamps it can be powered by eight penlight cells in a suitable carrier. The meter is thus portable and can be used even for engines with no battery system. Pickup can be taken from any plug's high tension lead. If the separate battery method is used, a jumper lead will be required between engine and battery negative.

Note that a metal case must be used for the instrument and is connected to the negative supply by means of a 1.5k resistor by-passed by a .047uF capacitor.

The prototype was built with what the author had to hand but constructors starting from scratch could use a large meter and case with advantage. However, the general layout of the prototype should be followed with the input leads and filter systems above the meter and the switches, sensitivity control, transformer and integrated circuit below the meter. This is to give maximum separation between input and meter circuits.

Some knowledge of metalworking is required for the construction of the capacity pickup. Use a metal that is readily solderable of approximately 24g. The inner sensing element is "U" shaped, with the diameter such that a

7mm high tension lead slides easily inside the "trough".

The two semicircular halves of the outer shield overlap when closed. The overall length is 75mm and the lower member has a 20mm inside diameter. Two pieces of rubber tubing, each 15mm long were cemented into the lower member and suitably cut to accept the sensing element. Contact cement was used to secure the rubber and to mount the sensing element centrally in the lower member. The rubber is flush with each end of the lower member but the sensing member will be 5mm in from each end.

The clamping mechanism is derived from a 50mm (2in) paper clip, with the jaws cut back and suitably bent. The shielded cable should be prepared as follows:

The prepared cable can be slid under the spring of the paper clip and the cable end soldered to the sensing element. Solder the lower jaw of the paper clip to the lower shield members.

The illustration of the capacity pickup will show that there is a piece of timber 75mm long cemented by epoxy to the upper member. A piece of waterproof plywood was used in the prototype and so shaped that with 7mm high tension cable in the sensing element, the upper shield member just

overlapped the lower member. The sides of the piece of plywood were filed away to allow a 4mm cable to be gripped. This is the smallest diameter cable likely to be encountered.

It may be necessary to slot the upper member to clear the cable soldered to the sensing element. With no high tension cable in the sensing element, the piece of plywood can be cemented to the upper member and the remaining jaw of the paper clip soldered to the upper member. It helps to tie the units in position with wire because of the spring loading of the paper clip. The wire ties can be removed after soldering.

Anchorage and earthing of the cable braid is as follows: a tongue of metal about 4mm by 25mm long is soldered to the lower finger grip of the paper clip and faces away from the sensing unit. To this is soldered also the earthing braid of the shielded cable. Then the whole is reinforced by an insulating sleeve and securely taped to the tongue of metal.

If the insulating plastic sleeve can be forced over the tongue of metal, so much the better. The plastic sleeve can be about 65mm long. Its sole purpose is to provide strain relief.

Construction of the indicating unit follows normal practice with the

#### TACHOMETER

proviso that inlet leads and functions be separated by the meter dimensions as indicated earlier.

The "spark gap is a simple device made up from two pieces of metal mounted on a plain piece of fibreglass board as shown.


Because the screws are offset, the rounded ends of the plates can be brought close together by slight rotation of each plate. The gap should be made 0.04mm (.0015in) using a feeler gauge. The plates are mounted away from the surface of the fibreglass board by the thickness of the solder lugs. The resulting air gap reduces surface leakage.

For calibration, a 12V 50Hz supply is required as well as a source of 12V DC such as the eight penlight cells previously mentioned. Apply 12V in the correct polarity and the LED should

Set the range switch to 10,000 RPM and the function switch to 4-stroke. Apply the 12V 50Hz across the .0022uF capacitor at the output of the diode bridge, via a 10k 1/2W series resistor.

Set the 1k trimpot to give a reading of 6000 (0.6 on the 1mA scale). Now set the function switch to 2-stroke and set the 100 ohm trimpot of the meter circuit to give a reading of 3000 (0.3 on the scale).

The 0-1000 RPM calibration requires that the unit be taken to a vehicle. If the vehicle is fitted with a six-cylinder engine then proceed as follows. Connect the battery leads of the tachometer to the battery terminals of the vehicle in the correct polarity. The LED should now be lit. Clip the capacity pickup to the lead coming from the high tension of the coil to the distributor. Set the range switch to 10,000 and the function switch to 4-stroke.

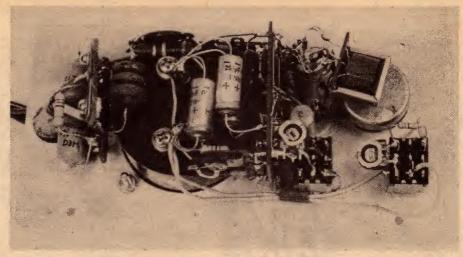

Here is a shot of the interior of the author's prototype, showing the general construction. The layout may be varied if desired, but it is advisable to keep the input circuitry and spark gap well away from the IC.

Start the vehicle engine and set the speed so that 6000 RPM are indicated. Because the ignition coil is delivering pulses to the six cylinders in firing order, the tachometer reads this as one cylinder having a speed of 6000 RPM when in fact the engine is set at a speed of 1000 RPM.

With the engine still running, transfer the capacity pickup to any one cylinder high tension lead and the reading should drop to 1000 RPM on the 0-10,000 RPM scale. Switch to 0-1000 and in all probability the meter will read close to full scale. At this stage set the function switch to 2-stroke and set the 100 ohm trimpot associated with S1a to read 500 RPM (0.5 on the scale).

You will note that the calibration method tries to keep readings as close to the initial setting on 12V 50Hz as possible. This reduces the possibility of errors and keeps readings in the mid scale area as accurate as possible. This is

the area where the majority of readings will be taken.

If a 4-cylinder engine is used for the low range calibration, then the engine would be set to read 4000 RPM with the capacity pickup on the ignition coil high tension lead. Similarly, 8000 RPM would be used in the case of an eightcylinder engine. In all cases the sensitivity control is adjusted to obtain readings that are steady.

### LANTHUR ECTRONICS

69 Buchanan Ave or PO Box 162 North Balwyn, Vic. 3104 Phone 859-4061

ELECTRIC MOTOR CONTROLLER KITS. Controls down to stop without loss of torque. Consists of triac mounted on heat sink, diodes, resistor, pot. and knob, 3 pin base and plug, and circuit. Use with hand tools, lathes, potters wheels, etc. Suitable for ac/dc brush type motors only. 10 amp 2400 watt capacity. Price including post. \$10.95.

LAMP DIMMER KITS. Controls from full to out incandescent lamps up to 2400 watt. Consists of triac mounted on heat sink, diac, pot. and knob, resistors, caps, ferrite rod and wire, circuit. Use for spots, stage, projector, etc. 10 amp 2400 watt capacity. Price including post, \$8.95 rotary or slider control avail. Please say which preferred.

Cabinets to suit above speed controller and lamp dimmer kits. Plastic with alum. lid \$1.95. All aluminium \$2.95.

#### TUNING CONDENSERS

Roblan RMS-Igang. 415pf. Suitable crystal sets, etc. Price including post \$3.75.

SLIDER SWITCHES. DPDT. 3 for \$1. 10 for \$3 post free.

DIODES - Silicon, 25 amp, 200 piv. Stud mount. Suitable alternators, battery chargers, etc. Price including post \$4.20 for 2, \$7.85

#### **PARTS LIST**

- 1 Metal case with metal front panel
- 4 Rubber feet
- Rubber grommet
- 1 0-1 milliamp meter
- Miniature switch, DPDT
- Miniature switch, SPDT
- 50k ohm potentiometer
- Knob
- Capacity pickup (see text)
- crocodile clips
- RF Choke 2mH (see text)
- Spark gap (see text)
  Transformer, DSE M-0222 or similar
- LED
- NE2 Neon
- 1N914 diodes
- 1 SAK 140 tachometer IC

#### RESISTORS

2 100 ohm trimpots

1 1k ohm trimpot 1 100k 1W

1/4W or 1/2W 5%:

1 x 22 ohm, 1 x 33 ohm, 1 x 100 ohm, 1 x 470 ohm, 1 x 820 ohm, 1 x 1.5k, 1 x

2.2k, 1 x 10k, 1 x 100k

CAPACITORS

1 .0022uF 2kV ceramic

2 470uF 10VW electro

1 .0022uF 100VW polyester

2 .047uF 100VW polyester 1 0.22uF 100VW polyester 1 0.1uF 100VW polyester

MISCELLANEOUS

Mounting hardware, tap strips, plain Veroboard, PC board pins, solder; 1½ metres of 4mm plastic covered shielded cable, 60pF per metre maximum; 11/2 metres each of red and black 2.5mm hookup wire.



tributor stocks. These include Philips Resistors and Capacitors.

If you need stock delivered in any capital city, call one of our major offices and the goods, if available ex stock, will be despatched within 24 hours. If you require delivery in another city, our on line computer can speed your order

Perth: Reserve Electronics is our agent in Perth with many products having off the shelf availability.

Canberra: Ortex, Canberra's specialist electronics firm are Cema's agents for the A.C.T. Ortex can deliver from their own stock or ex Sydney from Cema's stock.

Wollongong: Macelec have full access to all Cema products to service the industrial centre of Wollongong.

these semiconductor products.







Cema's retail division, Silicon Valley can give you over the counter delivery on more than 7,000 items. All Cema offices carry extensive distributor stock.

#### **ELECTRONICS PTY LTD** CEMA

21 Chandos Street, Crows Nest, N.S.W. 2065 Australia. Telephone 439 4655. Telex 22846. P.O. Box 578.

Melbourne Office:

208 Whitehorse Road, Blackburn, Victoria 3130, Australia. Telex 32295.

Telephone 877 5311.

BRISBANE: 22 Ross Street, Newstead, Qld. Telephone 51 6483

ADELAIDE: 170 Sturt Street, Adelaide, S.A. Telephone 51 6483

CANBERRA: Ortex (062) 81 0430

WOLLONGONG: Macelec (047) 29 1455

PERTH: Reserve Electronics (09) 328 3116

NEW ZEALAND: Cema Electronics (N.Z.) Ltd., 7-9 Kirk Street, Grey Lynn, Auckland.

PAPUA NEW GUINEA: Daltron Electronics, Goroka, Papua New Guinea, Telephone, 25, 6616



# TRIACS

# New high quality range for single and three-phase power control.

This comprehensive range offers a choice of commutation characteristics at most current and voltage levels. They are all recommended for new equipment designs, but for applications in the 40A region, attention is particularly drawn to the BTW41-G and BTW41-H series in the SOT-80 "Tripak" encapsulation.

Basic data is given in the

accompanying chart.



For further information contact Philips Electronic Components & Materials or their distributors.

Philips Electronic Components and Materials,

P.O. Box 50, Lane Cove. N.S.W. 2066 PH: 427 0888

38		(20)

Type No. Encapsulation		n RMS on-state current large l	peak off-state	current current	rise of	Rate of rise of off-state voltage dV <sub>D</sub> /dt max.		Gate trigger voltage	Gate tripper
			current		Normal	Commutating*	Veltage V <sub>ST</sub> min.	current le min.	
BT137-500 -600	TO 220 plastic	6A	500V 600V	55A	20A/μs	50V/µs	6V/μs (5A/ms)*	1.5V	35mA
BTW43-600G -800G -1000G -1200G	T0-64 metal (Metric thread)	12A	600V 800V 1000V 1200V	120A	50A/μs	50V/μs	10V/μs (5A/ms)*	2.5V	100mA
BTW43-600H -800H -1000H -1200H	1		43-600G to BTW for commutation	43-1200G series	shown immedia	itely :	10V/μs (12A/ms)*	-	
BT139-500 -600	TO 220 plastic	15A	500V 600V	115A	50A/µs	50V/µs	4V/μs (8A/ms)*	1.5V	35mA
8TX94-400H -600H -800H -1000H -1200H	TO-48 metal (UNF thread)	25A	400V 600V 800V 1000V 1200V	250A	50A/µs	100V/µs	30V/µs (25A/ms).*	3V	150mA
BTX94-400J -600J -800J -1000J -1200J			94-400H to BTX9 for commutation	4-1 200H series	shown immedia	tely	30V/μs (50A/ms)*		
BTW41-500G -600G -800G	SOT-80 plastic	40A	500V 600V 800V	260A	50A/μs	100V/µs	5V/μs (12A/ms)*	1.5V	75mA
BTW41-500H -600H -800H		Same as BTW above except	41-500G to BTW for commutation	/41-800G series	shown immedia	itely	5V/μs (23A/ms)*		
BTW34-600G -800G -1000G -1200G -1400G -1600G	T0-103 metal (Metric thread)	55A	600V 800V 1000V 1200V 1400V 1600V	400A	50A/µs	200V/μs	30V/µs (25A/ms)*	2.5V	200mA
BTW34-600H -800H -1000H -1200H -1400H -1600H	7		34-600G to BTW for commutation	34-1600G series	shown Immedia	itely	30V/μs (. 0A/ms)*		

(1) For derating curves see individual data sheets.

 $^{\circ}$  The figures in brackets following the dV<sub>D</sub>/dt rating show the -dl/dt of the preceding turn-off.

AVAILABLE THROUGHOUT AUSTRALIA FROM



and SOZNAR

**PHILIPS** 

We want you to have the best

HRME 153-0242



# Playmaster AM-FM Stereo Tuner-Clock

### third article has a useful trouble-shooting guide

In this third and final article on the new Playmaster AM/FM tuner clock, we give some tips on optimum reception, discuss some of the more likely faults and feature some photographs and PCB artwork held over from the last issue.

#### by LEO SIMPSON

The previous two articles have provided all the information that should normally be required to construct the tuner and make it fully operational. So now it is appropriate to discuss some features of the unit's operation in order that the best performance is realised by the constructor.

As far as FM reception is concerned, the most important point is the strength of signal fed to the antenna connections. Most people connect their FM tuners to their TV antenna, using a splitter for correct termination. This method should be adequate in most locations, but may prejudice both TV and FM reception in fringe areas, due to the signal losses involved in the splitter. In these cases, separate antennas will be necessary.

A good idea of the signal strength received can be gained by reading the tuner's signal meter and then referring to the meter response graph shown on page 39 of the December 1978 issue. A meter reading of "4", for example, indicates a signal strength of 100 microvolts (across the 300 ohm terminals).

A signal of this order will provide noise-free reception in the mono

mode. If the tuner is switched to stereo mode, background noise will be noticeable (as hiss). To eliminate noise from stereo reception, a signal strength of 300uV or more is required. This corresponds to a meter reading of "6" or more.

It is possible that signal strength may be adequate and the reception appropriately noise-free but marred by objectionable distortion. A likely cause of this problem is "multipath" reception, which is akin to "ghosting" in TV

If you suspect that "multipath" reception is a problem, the diagnosis can be confirmed by close observation of the signal strength meter. If the pointer can be seen to be fluctuating in time to the music or voice program, then there is definite indication of multipath. The solution may not be easy but involves the same process used to reduce TV ghosting — selection of a suitable directional antenna and orienting it for best reception. The signal strength meter can be used as an aid in orientation.

Similar remarks can be made about AM reception. While the quality of reception is nothing to become excited

about, the AM specifications of this tuner are actually better than those obtained from many commercial tuners. This may be hard to believe, but it's true.

For reasonably noise-free reception the signal strength meter should read "6" or more. If the listener is located in area of relatively weak signals, the tuner and its rod aerial will have to be oriented in order to maximise signal pickup. In areas where very strong signals produce overloading of the AM input stage, the signal pickup can be reduced by pulling the rod closer to the chassis.

It is possible that the aerial rod may need "peaking" to optimise signal pickup. This is done by tuning to a station in the middle of the range and tweaking the aerial rod slug for maximum deflection of the signal strength meter.

Multiplex hash will be audible between stations and will probably interfere with reception of weak stations. This tuner is not really suitable for DX reception of AM, so we do not regard this as a major drawback. Recepton of strong local stations should not be affected.

Should you wish to determine whether any interference in the tuner is multiplex hash, you can readily check by depressing both time-setting pushbuttons simultaneously. As noted previously, this action blanks the display and will reduce the hash radiation to a low level.


One point we did not mention when writing the earlier articles was the effect of the new AM station spacing of 9kHz which applies as from November 23,


1978. At the time of writing this article (early November) we have not observ-

ed the practical effect.

Fortunately, because the Wangine WT-7700 tuner module has a relatively narrow AM bandwidth, the audible effect of 9kHz heterodyne whistles will not be as bad as will be encountered with higher quality AM tuners.

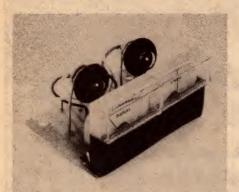As far as the frequency readout is concerned, the maximum error involved in tuning any one station will be



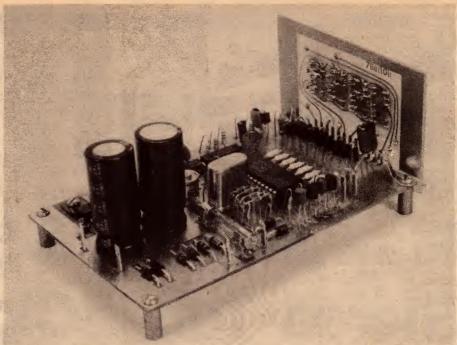

These photos show the two modules ready for installation in the chassis.

±5kHz. This is because the last digit of the AM frequency display is always zero, a constraint set by the AY-3-8112 IC which was designed to work with AM stations having 10kHz spacing.

Presumably, General Instrument Micro-electronics may eventually produce a frequency readout chip to suit the 9kHz spacing, which now applies to most of the world except for one major holdout, the USA.


The local distributors, General Electronic Services Pty Ltd, have notified General Instrument Corporation of the change.

For the present, the frequency readout error will show up in the following way. For example, Sydney station 2GB, now on 873kHz, will give an indication of 870kHz. And station 2F€, moved to 576kHz from 610kHz, will give an indication of 580kHz.

Constructors may also find that an error occurs with the FM frequency readout. This will be due to an offset error which can be corrected by omitting one or more of the programming diodes D1 to D4.

By using differing combinations of diodes D1 to D4, the FM offset for the 8112 IC can be varied to suit intermediate frequencies from 10.46mHz to 10.76MHz. The table is as follows:

	table is as lonows.
10.76MHz	D1, 2, 3, 4
10.74MHz	D1, 2, 3
10.72MHz	D1, 2
10.70MHz	D2, 3
10.68MHz	D2
10.66MHz	
10.64MHz	D3
10.62MHz	
10.60MHz	none
10.58MHz	D1, 4
	D1
10.54MHz	D1, 2

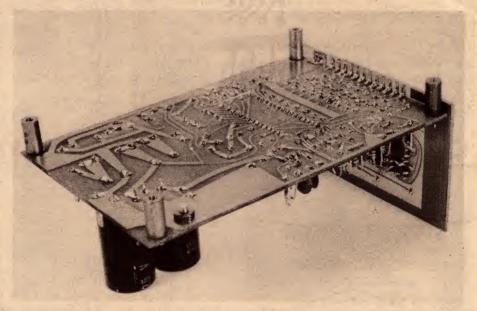

10.52MHz	D4	
10.50MHz	D3, 4	
10.48MHz	D2, 3, 4	
10.46MHz	D1, 3, 4	


By way of explanation, while most FM tuners have a nominal intermediate frequency of 10.7MHz, the actual IF may be up to several 100kHz above or below this figure. This applies whether or not the IF strip uses ceramic filters. The Murata SFE10.7MA filters used in the Wangine WT-7700 module are manufactured to five specified centrefrequencies, and are coded with a coloured dot:


10.80MHz +	35kHz	Yellow
10.75MHz ∓	35kHz	. White
10.70MHz ∓	35kHz	Red
10.65MHz +	35kHz	Black
10.60MHz <u>∓</u>	35kHz	. Green
Accordingly.	by looking at	the colour


code dots on the SFE10.7MA filters on your module (they're close to the oscillator shield), you can decide on which combination of diodes to use. Therefore, if the filters are coded with yellow or white dots, D1, 2, 3 and 4 can be left in place. If the code is red, omit D1 and D4. If green, omit D1 to D4.

The above selection is fairly rough and ready but is adequate since the 8112 gives a readout of the centre of the channel even if the tuner mistuned by ±100kHz. In any case, the frequency readout is used only as a guide to the tuned frequency. For accurate tuning, the tuning meter must be used.

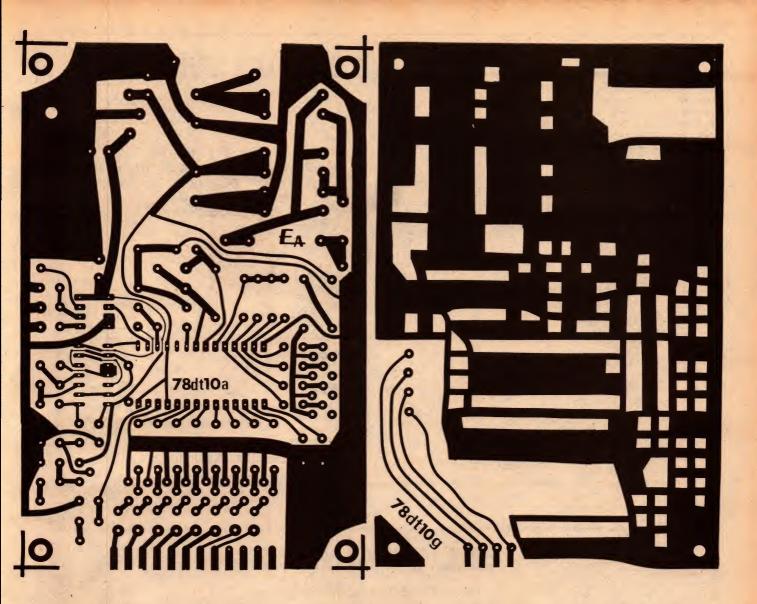
A more precise method of selecting the programming diodes is to use a digital frequency meter, in the following way. Accurately tune to an FM station of known frequency (using the



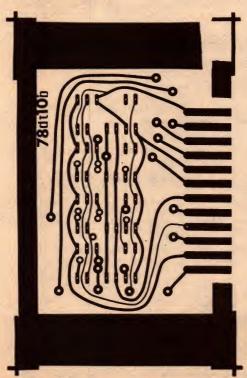


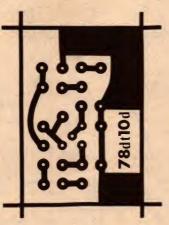

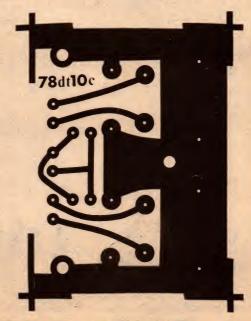These are the patterns for the four PCBs, including the ground plane.



### **AUDITEC A-SERIES AMPLIFIERS**

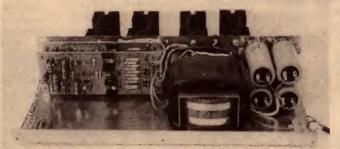

THE A-SERIES ARE NO-FRILLS BASIC POWER AMPLIFIERS **READY TO CONNECT TO YOUR** PREAMPLIFIERS OR MIXER AND LOUDSPEAKERS

AVAILABLE IN 1 x 100 WATT (1A009, 1A033) 2 x 100 WATT (2A009, 2A033)

1 x 200 WATT (1A027)

MELBOURNE: Zephyr Products. Phone 568 2922 BRISBANE: Delsound Pty Ltd. Phone 229 6155 ADELAIDE: Neil Muller Pty Ltd. Phone 272 8011 ADELAIDE: Protronics Pty Ltd. Phone 212 3111 CANBERRA: Musique Boutique. Phone 82 2553

PERTH: Willis Trading Co. Phone 321 7609

DARWIN: Darwin Communication Systems. Phone 85 3184 ALICE SPRINGS: Farmer & Davies Electronics. Phone 52 2967

BUNDABERG: Bundaberg Hi-Fi. Phone 71 3176 MARYBOROUGH (QLD): Keller Electronics. Phone 21 4559.

SURFERS PARADISE: Beno's Musical Supplies. Phone 38 1568. MERMAID BEACH: R.A.V.E. Phone 38 3331.

TAMWORTH: Hi-Fi Gallery. Phone 66 2525

ALBURY: Ray Walsh Sound Systems. Phone 21 1502 WENTWORTHVILLE: President Sound. Phone 631 6689

GLENFIELD: WMR Electronics. Phone 605 1203
BLAXLAND: Dawes Sound Systems. Phone 39 4421 BONDI: JAI Sound. Phone 389 8277

FOR DESCRIPTIVE LEAFLETS ON THESE AMPLIFIERS CALL, PHONE OR WRITE TO:

AUDITEC AUSTRALIA PTY LTD 10 WAITARA AVENUE, WAITARA, N.S.W. 2077 PHONE: 48 4116

(PACIFIC HIGHWAY SIDE OF WAITARA STATION)

### **ELLISTRONICS**

FOR JUST ABOUT ELECTRONIC

LARGE RANGE OF E.A. AND E.T.I. PROJECT CIRCUIT BOARDS ALWAYS IN STOCK. P.S. KITS WILL BE AVAILABLE SHORTLY.

#### NOW AVAILABLE EX STOCK:

The new SINCLAIR DM 235 Digital Multimeter.

Large 31/2 digit display reading to plus/minus 1999. Six functions in 26 ranges. DC volts, 1mV to 1000V, AC volts, 1mV to 750V. DC current, 1uA to 1A. AC current, 1uA to 1A Resistance, 1 ohm to 20M ohms. Diode test, 0.1uA to 1mA. Impedance, 10M ohms. 12 month guarantee. P&P \$2.

ONLY \$145 incl tax. (\$132 tax exempt)

Also available: The ideal pocket size digital multimeter, the SINCLAIR PDM 35, for only

\$61.50 incl. tax. (\$56 tax exempt) P&P \$2.

We also stock Soar, Sanwa and Arlec multimeters and Trio oscilloscopes, signal generators, etc.

Phillps AD12K 12 TK 3 way 12" 40 watt speaker kits, complete, \$279.50 pr inc tax.

- Philips AD 8K 40 3 way 8" 40 watt speaker kits, complete, \$195 pr inc tax.
- Philips AD 8K 30 2 way 8" 30 watt speaker kits, complete, \$137.50 pr inc. tax
- Philips AD0 160 T8 stereo tweeter kits incl. crossover caps, \$26.75 pr inc tax.
- Large range of Philips, Plessey-Foster and CTS speakers in stock.
- Philips EUY-10E 023LE Tape Printers, \$71.25 plus tax.
- South West Tech Keyboard kits, \$85 ea inc tax.
- Micro Honeywell Hall Effect Keyboards, \$120 ea inc tax.
- Daneva Keyboards (63 keys) \$45 ea inc tax.

WE NOW STOCK a huge range of semiconductors (incl micro chips) by all leading manufacturers at most competitive prices. Also a full range of capacitors, resistors, plugs, sockets, cables, connectors, instrument cases, transformers, Vero and Blob board, Continental breadboard, ETI and EA project boards, Chart Pak, potentiometers, in fact, just about everything electronic at Melbourne's leading electronic centre.

Send 30c stamp for catalogue. All components can be supplied tax exempt through our new wholesale division, Ellistronics Wholesale P/L.

# EUISTRONICS

289 LATROBE STREET, MELBOURNE 3000 PHONE (03) 602 3282

#### PLAYMASTER AM-FM TUNER-CLOCK



tuning meter). Measure the prescaled frequency at the output of the DS8629 IC (pin 2) and multiply by 100. Now subtract the station frequency to obtain the actual intermediate frequency for the tuner, and select the programming diodes accordingly.

Setting the crystal oscillator trimmer capacitor for accurate time-keeping is a matter of trial and error. Since the clock function has no "seconds" readout, the accuracy of the timekeeping can only be measured by comparing the changeover of the "minutes" digit with the time signals on the radio or telephone.

At the time of writing only a few of the Playmaster tuners have been built and these have been relatively faultfree. However, our experience with these prototypes is a guide to some of the common faults which constructors may come across.

Most of the likely faults will be visually indicated by the digital readout and most of these are likely to be missing

segments or missing digits.

First point to remember is that all segment lines are common. The table below shows the pin connections to LT-302 and DL-707 LED displays. The segment and digit connections to the AY-5-8112 are shown on the main circuit diagram published last month. This data enables the segment and digit lines to be checked for continuity, using a multimeter.

pin 1	segment A
pin 2	segment F
	anode E,F,G,DP
	decimal point
	segment E
	segment D
	anode C,D
pin 10	segment C
pin 11	segment G
pin 13	
pin 14	

Actually, the pin connections for the LT-302 and DL-707 are not exactly the same. With the LT-302, anode pins 3 and 14 are internally connected while pin 9 is used for the right-hand decimal point cathode. This means that a good few of the 15 links on the display PCB are superfluous if the LT-302s are used.

If the displays are very dim, then it is probable that you have inserted the transistors incorrectly. If you are supplied with 2N3904 and 2N3905 transistors their orientation should be reversed to that shown in the photographs. On the 2N3904/5 the leads are in a straight line and reversed in order to that for the BC328/338 series.

If one segment of one display is missing, the fault lies with that particular display — most probably it is a bad connection. On the other hand, if the "A" segment, for example, is missing from each digit, then the fault could lie with the display, transistor Q5 or the 8112. The latter case is the least likely of the three.


Q5 (and all the other bipolar transistors) can be checked with power applied. Just short Q5 between base and collector (carefully now). If the "A" segments all light up, then Q5 is okay. If not, then Q5 is faulty or there is an open-circuit between Q5 and the "A" segment line. If Q5 proves to okay, check if the "A" segments all light when the base of Q5 is shorted to the base of another segment driver transistor. If they do, there is an open-circuit in the base line to Q5 or the 8112 IC is now a useless piece of plastic.

Note: The display should be set to read "880" on AM or "88.9" on FM in order to be able to check segment operation on the last three digits. On the first digit, only two segments are displayed (ie, for "1").

A similar procedure can be used to

cure missing digits.

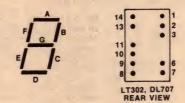Under dim lighting conditions, you may notice that when the leading digit should be blanked (for three-digit displays, for example), some segments are



glowing slightly. This can be improved by adding another diode in series with D5 and D6. Lift one end of D5 or D6 up and solder one end of the extra diode to the position vacated. Then twist the ends of the two diodes together and solder.

Does the frequency display work? If

not, it could be because the tuner module is not working or because Q13, Q14 or the interface ICs are malfunctioning.

If you are unlucky enough to short out the tuner supply (P12) accidentally, the most likely casualty apart from the fuse, is the regulator transistor on the tuner module, near P12. This can be replaced with a TIP31, which has the same lead configuration.

If the FM display becomes unreliable or intermittent as the tuned frequency goes higher, it is likely that Q14 is a little low in gain. The situation can be cured by reducing the 220 ohm resistor from Q14. The resistor should be reduced to the point where the display is reliable over the whole frequency range. Do not reduce it more than necessary, otherwise multiplex hash will become a significant component of the residual noise.

If the FM display shows "189.3" either Q14 or the 8629 IC is not working at all. Similarly, if the AM display shows "1550", either the 7400 IC or Q13 is not working. In both cases, check that the inputs from the respective local osicllators are actually connected. Apart from this, the easiest way to check these parts of the circuit is by substitution.

One other fault which occurred with one of our prototype modules was failure to operate in the stereo mode. This proved to be due to maladjustment of the multiplex decoder (HA1156) internal oscillator, probably as a result of an inadvertent nudge to the 10k preset potentiometer (associated with pin 14). This can be adjusted precisely with the aid of a frequency meter so that the output at pin 10 is exactly 19kHz.

Another method which will give reasonable results is as follows: Set the tuner to receive a station known to be transmitting in stereo. Now tweak the 10k pot (with 15k resistor adjacent) so that the stereo beacon lights. Continue turning the pot until the LED extinguishes. Now set the pot wiper in the middle of the range for optimum results.

## FUNDAMENTALS OF SOLID STATE

Fundamentals of Solid State is in its second reprinting, showing how popular it has been. It provides a wealth of information on semiconductor theory and operation, delving much deeper than very elementary works, but without the maths and abstract theory which make many of the more specialised texts very heavy going. 'Solid State' has also been widely acclaimed in colleges as recommended reading — but it's not just for the student. It's for anyone who wants to know just a little more about the operation of semiconductor devices.

Available from "Electronics Australia", 57 Regent St. Sydney. PRICE \$3.00. OR by mail order from "Electronics Australia", P.O. Box 163, Beaconsfield, 2014. PRICE \$3.60.

# The Playmaster trio:



Playmaster Stereo Amplifier Kits

And the perfect MATCH:

Twin 25: 25 watts RMS **\$** per channel into 8 ohms

105°°

Forty/Forty deluxe: 40 watts RMS per channel

12950



# Playmaster AM FM Tuner & Digital Clock Kit

AM, FM & FM Stereo tuner with digital display plus clock

See the articles in Electronics Aust. Nov & Dec '78, Jan '79.

\$159<sup>50</sup>

# Playmaster 3 Way Speaker System Kits

Designed by Neville Williams (MIREE) Editor-in-chief, Electronics Australia.


3/26L: 3 way, 26 litre 8 inch speaker system \$149<sup>50</sup>

3/53L: 3 way, 53 litre 10 inch speaker system \$224<sup>00</sup>

3/75L: 3 way, 75 litre \$ 12 inch deluxe system

\$28400 (all prices are per pair)



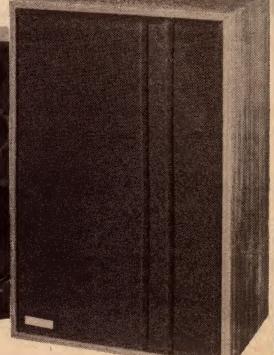

# leaders in audio value-for-money

NOW! Save hundreds of dollars on superb quality audio equipment, simply by putting it together yourself. Outstanding designs from 'Electronics Australia' magazine, brought to you in easy-to-build kit form by Dick Smith Electronics.

#### Famous Twin 25 & Forty/Forty Deluxe Amplifier kits.

Yes! Here's your chance to own a really top-class amplifier - without the price tags normally associated with top-class gear! These amplifiers are designed to give performance as good as (if not better than) many of the 'big name' amplifiers you'd pay double the price for. You save the money because you supply the labour. Professional appearance, too - gold finish front panel with matching imported knobs - and every kit comes with a comprehensive step-by-step construction manual.

Power output - 25 or 40 watts into 8 ohms, one channel driven (depending on model)

Freq. response - ±1dB 25Hz to 20kHz (controls flat)

Compensation - RIAA within ±1dB

- Phono 2mV into 56k for full power Sensitivity

Other inputs - 150mV into 36k minimum

Distortion - less than .05% at normal levels Stability: - Unconditional

Playmaster Twin 25 Stereo

Amplifier Kit - Cat K-3410

Playmaster Forty Forty Deluxe Stereo Amplifier Kit - Cat K-3411

#### **OPTIONS AVAILABLE:**

LOUDSPEAKER PROTECTOR: This easy-to-build printed circuit board suits most amplifiers protects speakers by eliminating turn-on 'thumps'. Cheap insurance for your valuable speakers.

950

Cat. K-3425

#### TIMBER DRESS SLEEVE:

Simulated walnut veneer sleeve suits both amplifiers and the new Playmaster Tuner, Gives them an 'expensive imported' look without the expense!

Cat H-3113

**D**50

#### Brand new: Superb AM/FM Digital Tuner plus Clock.

Now . . . a perfectly matching partner for the Playmaster amplifiers the all new Playmaster AM/FM Tuner with a digital frequency readout that doubles as a clock. It's got features you'd normally find in a tuner costing close to \$1000! Superb AM& FM reception from a pre-built module (all the hard work of construction has been done for you!) And the same high quality finish front panel and knobs as the amplifiers. Even at twice the price - a bargain!

#### (MEASURED PERFORMANCE OF PROTOTYPE)

FM: Tuning range - 87 to 108MHz

Sensitivity - 4uV for 50dB quieting (mono) Ultimate S/N ratio -64dB (unweighted) stereo

--70dB (unweighted) mono

Frequency resp. - - 4dBat 15kHz

- -36dB in both directions Separation

**Audio Output** - 500mV rms into 10k Harmonic Dist. - less that 1% stereo

less than 0.5% mono with full modulation

Playmaster AM/FM Digital Tuner/ Clock Kit - Cat K-3494

#### **OPTIONS AVAILABLE:**

#### TIMBER DRESS SLEEVE:

The dress sleeve above also suits the new Playmaster digital tuner, Makes a perfect match to the Playmaster amplifiers. Cat H-3113

**O** 50

#### TUNER MODULE (ONLY)

The AM/FM tuner module as used in this project is available as a separate item. Complete, pre-aligned and ready to go. Cat F-4610

#### Magnificent 3-way Infinite Baffle Speaker Systems.

Magnificent is hardly the word. But in trying to describe these speakers you run out of superlatives! From the compact 8 inch system, ideal for the flat or small room, right up to the big 12 inch models - complete with fader controls to give you sound just as YOU want it. Carefully manufactured so that all the component parts literally 'fall' into place, with a pre-built wiring harness to eliminate mistakes (and there's no soldering required!) All you need is a screwdriver and a tube of glue! Outstanding!

Two catalogue numbers are given: the first is for the enclosure kits, while the second is for the speakers themselves. These items are available separately if required.

Playmaster 2/26L 8 inch Speaker Kit - Cat C-2626 and C-2046

Playmaster 3/53L 10 inch Speaker Kit - Cat C-2624 and C-2044

Playmaster 3/75L 12 inch Speaker Kit - Cat C-2622 and C-2042

So you want a set of these superb speakers, but do not want to build them yourself?

No problem! Just for you we have the 10in and 12in systems available in ready built-up form. Just unpack them from their cartons, connect them to your amplifier and settle back for superb sound reproduction.

10in 3-way system: Cat A-2362. ready built-up . . . . . . . . . . . . \$325

12in 3-way system: Cat A-2364 ready built-up . . . . . . . . . . . \$395

SHOPS OPEN 9AM to 5 30PM (Saturday 9AM 12 noon) BRISBANE 1 2 Hour earlier



125 York Street, SYDNEY. Ph. 290-3377 147 Hume Hwy, CHULLORA. Ph. 642-8922 162 Pacific Hwy, GORE HILL. Ph. 439-5311 30 Grose Street, PARRAMATTA. Ph. 683-1133

MELBOURNE 399 Lonsdale Street, MELBOURNE. Ph. 67-9834 656 Bridge Road, RICHMOND, Ph. 42-1614 BRISBANE 166 Logan Road, BURANDA. Ph. 391-6233 ADELAIDE 203 Wright Street, ADELAIDE. Ph. 212-1962

MAIL ORDERS P.O. Box 747, Crows Nest, N.S.W. 2065. Post and packing extra.

NOTE: Prices and stock availability could change between publication deadline and on-sale date due to circumstances beyond our control. Please check with out stores for latest availability and prices.

# Direct reading capacitance meter

Following on from our direct reading capacitance meter of about two years ago, here is an updated version which should be equally as useful as its predecessor and just as popular.

by IAN POGSON

In October 1976, we described a Direct Reading Capacitance Meter which became a very popular piece of test equipment. Because of its success, we decided to have another look at it with the idea of updating the design and making any improvements desirable in the light of intervening experience.

The original unit was not built on a printed board; instead, we made use of a piece of general-purpose DIP board. Obviously, it would make it neater and easier to build if we used a custom PCB and this is one improvement which is very worthwhile. Similarly the case which we used to house the original was quite a good one, but it is now rather expensive and so we looked around for a case which was more modestly priced but would do the job just as well. The ever popular "zippy box" filled the bill and this is what we have used for the new meter.

Another idea which seemed worth considering was to use a 100uA meter instead of the 50uA unit. This would give decade readings which would possibly be more in keeping with present day usage. However, investigations along these lines revealed that the system would not fully drive a 100uA movement, so that idea had to be passed over.

After our first unit was described one of our readers, Mr B. M. Byrne, of Indooroopilly, suggested some modifications in the light of his experiences with it; his suggestions were given in Circuit & Design Ideas for July, 1977. Interested readers may wish to refer to Mr Byrne's comments.

Our own experience in making up the new unit is that we have found that it was better to leave the resistor values as for the earlier circuit. It would seem that there are a number of hidden factors, possibly layout, etc, which can affect the two lower ranges. We have found that a very satisfactory way out of the problem is to add a couple of extra calibrating trimpots.

Modifications aside, this little capacitance meter is a most useful device for anyone making use of capacitors. Most of us have a box of assorted capacitors, some good, some doubtful and more than likely quite a number without any capacitance marking. For sorting out such a box of capacitors this capacitance meter is invaluable

The unit effectively has six switched ranges. Capacitance measurements from as low as 1pF and up to 5uF are possible. Low values, below about 10pF, may be subject to a certain amount of inaccuracy. This is not unusual in simple types of capacitance measuring devices.


In addition to measuring ordinary capacitors, it is possible to measure electrolytics as there is a potential difference between the two terminals amounting to a volt or two. The polarity must be observed of course. Also, this potential difference makes it possible to measure the reverse biased capacitance of diodes, at the voltage appearing across the terminals. This is not all. Such other capacitance measurements as the junctions of transistors, coaxial cable, etc may also be made.

As may be seen from the circuit and pictures, the device is quite simple. It follows that the cost is quite modest by current standards. The operation of the circuit centres on the very popular 555 timer IC. I will give a very short description of the operation, but for readers who would like to go into this at greater depth, I suggest that you refer to the original article by Mr Willcox, in the May 1976 issue of "Television".

The two resistors selected by the



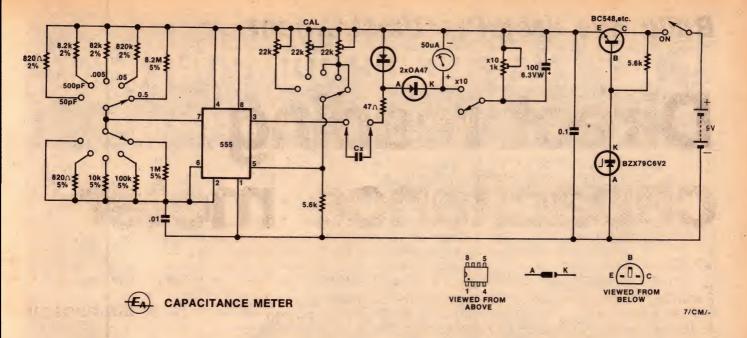A low-cost plastic "zippy" case was used to house the prototype.



range switch, together with the .01uF capacitor and part of the 555 timer, form an oscillator. After undergoing switching in other parts of the 555 timer the output emerges at pin 3 in the form of pulses. One part of the pulse is discharged through capacitor Cx, via the diode to the supply rail. The other part of the pulse discharges through the other diode and the meter. These pulses are integrated by the meter and give a reading in accordance with the capacitance Cx.

Calibration is achieved by adjusting the three 22k trimpots. One is common to the three highest ranges and need only be adjusted on one of those ranges. The other two trimpots are used for the two lower ranges, giving separate adjustments for each.

In the earlier version of the capacitance meter we specified close tolerance resistors for the oscillator ranges. The need still applies for the three highest ranges, as they are controlled by one calibrating trimpot. However, the other two ranges may not need such close tolerance resistors, as separate adjustment is provided for each. We have retained the close tolerance resistors on the circuit diagram and in the parts list, but readers may decide whether or not they adhere strictly to these.

In the bottom row of oscillator resistors it may be seen that three of them relate by a factor of 10, but the fourth resistor is reduced to 820 ohms and the fifth position is reduced to a link. These are due to the effective resistance presented by the IC at pin 7.

To increase the top range measurement of 0.5uF by a factor of 10, a shunt in the form of a 1k trimpot is switched across the meter. Due to the low frequency of the oscillator on the top range the pointer of the meter is inclined to "jitter", so a 100uF electrolytic capacitor is also switched across the

#### LIST OF COMPONENT PARTS

1 Zippy box, 196mm x 113mm x 60mm

1 Printed circuit board, 89mm x 76mm, code 78CII

50uA Meter, 86mm x 78mm (see text for alternative)

1 Rotary switch, 2 sections 2-pole 5position

2 Miniature toggle switches, SPDT

Knob

Terminals type D64, 1-red 1-black

2 Banana plugs

2 Crocodile clips

1 9V battery No 2362

1 555 IC 8-pin DIL 1 IC socket, 8-pin DIL (optional)

1 BC548 transistor or similar

1 Zener diode BZX79C6V2

2 OA47 germanium diodes

RESISTORS

(1/2 watt)

1 47 ohms

1 820 ohms 2%

1 820 ohms 5%

2 5.6k

1 8.2k 2%

1 10k 5%

1 82k 2%

1 100k 5% 1 820k 2%

1 1M 5%

1 8.2M 5%

1 1k Philips miniature trimpot, horizontal mounting

3 22k Philips miniature trimpots, horizontal mounting

CAPACITORS

1 .01uF greencap

1 0.1uF greencap

1 100uF 6.3VW electrolytic

MISCELLANEOUS

Hookup wire, solder, solder lugs, clips for battery.

NOTE: Resistor wattage ratings and capacitor voltage ratings are those used in the prototype. Components with higher ratings may generally be used provided they are physically compatible. Components with lower ratings may also be used in some cases, provided the ratings are not exceeded.

meter to eliminate this effect. Of course, when switching out the x10 facility, the jittering effect remains on the top range. It is not serious, but if you wish, the next lower range may be selected and the x10 switch added, again resulting in a 0.5uF range but with smooth meter operation.

To maintain accuracy of measurement, it is necessary to keep the supply voltage at a steady value. To this end, we have used a simple voltage regulator consisting of a 6.2V zener diode and a BC548 (or similar) transistor. It was found that this arrangement was slightly unstable under certain conditions and the 0.1uF bypass capacitor was added to cure this tendency.

The supply for our unit is derived from a small 9V battery, regulated as just described. If you wish to operate the unit from the mains, then the battery may be replaced by a suitable transformer, rectifier diodes and a large value electrolytic capacitor. However, we are of the opinion that this type of unit is better supplied by a battery, thus giving greater freedom and flexibility.

The matter of components can present problems in availability but there should be little or no trouble with this

# K ALL ELECTRONIC COMPONENTS

COME TO THE PEOPLE WHO SPECIALISE IN KIT SETS

MAJOR STOCKISTS OF ALL GENERAL
RADIO AND ELECTRONIC COMPONENT
PARTS — YOU NAME IT — WE WILL QUOTE

S

E.A. & E.T.I. KITSET SPECIALISTS.

P.C. BOARDS B & S ENAMELLED COPPER
WIRE FROM 10-38 GAUGE.

K

ONLY "RECOGNISED BRANDS" AND TOP QUALITY COMPONENTS STOCKED.

Resistors (incl. large industrial types), capacitors, semi-conductor devices, switches, meters, valves, metalwork, front panels, plugs, sockets, cable connectors, transformers, speakers, etc., etc.,

#### POPULAR KITS - TOP QUALITY - LOW PRICES - LEARN WHILE YOU BUILD

STEREO UNITS	TE29 — E.A. 1971 Transistor (F.E.T.)	A17 — E.A. Ignition Analyser Tachometer	DO EVI 700 Bating Batana
S1 - ETI 484, Compressor Expander	Tester	A18 — E.A. Strobe Adaptor for Ignition Analyses	R9 — ETI 708. Active Antenna R10 — ETI 710, R.F. Power Amplifier
S2 - ETI 482, 50 watt per channel Amplifier	TE30 - E.A. 1977 Digital Logic Trainer	A19 — E.A. 1975 C.D.I. Capacitor Discharge Ignition	R11 — ETI 780 Novice Transmitter
S3 — ETI 482A, Preamp Board S4 — ETI 482B, Tone Control Board	TE31 — E.A. 212 Digit Volt Öhm Meter TE32 — E.A. Simple Function Generator	A20 — E.A. Mains Supply for Car Cassettes A21 — E.A. Automatic Heavy Duty Battery Charger	R12 — ETI 703. Antenna Matching Unit R13 — E.A. 1967 All Wave 7
S5 — ETI 485. Graphic Equalizer	TE33 — E.A. Direct Reading Capacitance	A22 — ET1 318 Digital Car Tachometer	R13 — E.A. 1967 All Wave 7 R14 — E.A. 240 Communications Receiver
SS — ETI 485, Graphic Equalizer S6 — ETI 480, 50 wett Amplifier S7 — ETI 480, 100 wett Amplifier	Meter	A23 — ET1 319A Variwiper MK2	R15 — E.A. 110 Communications Receiver
S7 - ETI 480, 100 watt Amplifier	TE34 — ETI 487 Real Time Audio Analyser TE35 — ETI 483 Sound Level Meter	424 — ET1 319B Variwiper MK2	R16 — E.A. 160 Communications Receiver
S8 — ETI 480 Ps. Power Supply for Above S9 — ETI 443, Expander Compressor	TE36 — ETI 489 Real Time Audio Analyser	GUITAR UNITS	R17 — E.A. 130 Communications Receiver R18 — E.A. All Wave I C 2
\$10 - ETI 444. Five Watt Stereo	TE37 - ETI 717 Cross Hatch Generator	G1 - ETI 447. Audio Phaser	R19 — E.A. Deltahet Solid State Mk2
S11 - ETI 422B, Booster Amelitier	TE38 3 Megahertz Freq Counter TE40 — E.A. Direct Reading Ohm Meter	G2 - ETI 413, 2 x 200 watt Bridge Amplifier	Communications Receiver
S12 — ETI 438. Audio Level Meter S13 — ETI 440, 25 watt Stereo Amplifier	TE40 — E.A. Direct Reading Ohm Meter TE41 — E.A. Function Generator	G3 — ETI 424. Spring Reverb Mixer G4 — ETI 408. Reverberation Unit	R20 — E.A. Fremodyne 4 Complete Kit
S14 — ETI 420. Four channel Amelifier	TE42 — EA Transistor tester	G5 - FTI 413 100 watt Guitar Amalifier	R21 — E.A. Fremodyne 4 RF Section R22 — E.A. PM 138 Tuner-Receiver
\$14 — ETI 420, Four channel Amplifier \$15 — ETI 420E, SQ Decoder	TE43 - ET1 581 Up Down Pre-setable Counter	G6 - ETI 410, A.D.U. for your Guitar	R23 — E.A. Mos Fet 52Mhz Converter
S16 - ETI 423, Add-on Decoder Amplifier	TE44 — ET1 550 Digital Dial	G7 — E.A. PM 125 50 watt Guitar Amplifier G8 — E.A. PM 134 21 watt Guitar Amplifier	R24 — E.A. 2-6Mhz Converter
\$17 - ETI 422, 50 Watt per channel Amplifier \$18 - ETI 426, Rumble Filter	WARNING SYSTEMS	G8 — E.A. PM 134 21 watt Guitar Amplifier G9 — E.A. PM 138 20 watt Guitar Amplifier	R25 — E.A. 8-19Mhz Converter R26 — E.A. 100Khz Crystal Calibrator
\$19 - ETI 429, Simple Stereo Amplilier	WS1 - ETI 583, Gas Alarm	G10 - E.A. Was Was Unit	R27 — E.A. 1Mhz Crystal Calibrator
- ETI 416. 25 Watt Stereo Ampirier	WS2 — ETI 066, Temperature Alarm WS3 — ETI 528, Home Burglar Alarm	G11 — E.A. Fuzz Box	R28 - E.A. V.H.F. Power Malch
S21 — ETI 417, Over Led Distortion Monitor S22 — ETI 410, Super Stereo Sound Source	WS4 — ETI 702. Radar Intruder Alarm	G12 — E.A. Sustain Unit G13 — E.A. PM 135 12 watt Guitar Amalifier	R29 — E.A. Short Wave Converter for 27Mhz
Width Control	WS5 - ETI 220. Wailing Siren		R30 — E.A. Simple S.W.R. Meter
S23 — ETI 425, Integrated Stereo System	WS6 — ETI 219. Hee-Haw Siren WS7 — ETI 313. Car Alarm	PREAMPLIFIERS AND MIXERS	R30 — E.A. Simple S.W.R. Meter R31 — E.A. 27Mhz Pre-Amp R32 — E.A. 10-30Mhz Pre-Amp
S24 — ETI 427, Graphic Equalizer S25 — E.A. Playmaster 10 + 10	WS8 - ETI 518. Door Monitor	P1 — ETI 445. Stereo Preamplifier P2 — ETI 449. Balance Mic Pre-Amplifier	R32 — E.A. 10-30Mhz Pre-Amp
S26 — E.A. Playmaster 128 40 watt	WS9 - ETI 503. Electronic Third Tran	P4 — ETI 449. Gashic Equalizer	COMPUTER & DIGITAL UNITS
S27 - E.A. Playmaster 132 40 watt	WS10 - ETI 506, Infra Red Intruder Alarm	P5 - ETI 414, Master Mixer 8 Channel	C1 - ETI 633, Video Synch Board
S28 - E.A. Playmaster 136 13 watt	WS11 — ETI 305. Automatic Car Alarm System WS12 — ETI 582, House Alarm	P6 - ETI 419, Mixer Preamplifier	C2 — ETI 632M, Part 1 Memory Board V.D.U.
S29 — E.A. Playmaster 137 3 watt S30 — E.A. Playmaster 143 12.5 watt	WS13 - FA Flectronic Sizen	P7 - ETI 401, F.E.T. 4 Input Mixer P8 - ETI 485 Graphic Founding	C3 — ETI 632P, Part 1 Power Supply V.D.I. C4 — ETI 632A, Part 2 Control Logic V.D.U.
S31 — E.A. Playmaster Twin 25 watt	WS14 — E.A. 1976 Car Alarm	P8 — ETI 485, Graphic Equalizer P9 — E.A. PM 127 Control Unit	C5 — ETI 632B. Part 2 Control Lovic V.D.U.
S32 - E.A. Musicolour II 1000 w ch		P10 - E.A. Simple Mixer for Pick	C6 — ETI 632C, Part 2 Character Generator
S33 — E.A. Musicolour III 1000 w ch S34 — E.A. Stereo Dynamic Noise Filter	PHOTOGRAPHIC	Up & Microphone	C7 — ETI 632. Mother Board inc. P S
	PH1 — ETI 586. Shutter Speed Timer PH2 — ETI 548. Photographic Strobe	P11 — E.A. PM 145 Mixer P12 — ET1 446. Audio Limiter	C8 — ETI 63ZU, (U.A.R.T.) Board
AUDIO TEST UNITS	PH3 — ETI 514B. Sound Light Flash Trigger	TUNERS	C9 - ETI 631-2, Keyboard Encoder
AT1 — ETI 441. Audio Noise Generator AT2 — ETI 128. Audio Millivolt Meter	DUA ETI 522 Dheta Times	T1 - ETI 062, A.M. Tuner	C10 - ETI 631, A. Sch. Keyboard Encoder
AT3 — ETI 112. Audio Attenuator	PH5 — ET1 509, 50 Day Timer PH6 — ET1 505, 19th Powered Strobe PH7 — ET1 513, Tape Side Synchronizer PH8 — ET1 512, Photographic Process Timer	T2 - ETI 740. FM Tuner	(less keyboard) C11 — ETI 670. Hex Display
AT4 — ETI 102. Audio Signal Generator	PH7 — ETI 513 Tane Slide Synchronizer	T2 — ETI 740. FM Tuner T3 — E.A. PM 138 Tuner	C12 — E.A. Educ-8 Computer
ATS — E.A. A.F. Tone Burst Generator AT6 — E.A. Laboratory Solid State A.F.	PH8 - ETI 512, Photographic Process Timer	T4 — E.A. PM 146 AM-FM Tuner	C 13 — E.A. Cassette-Tape Interface
Ganaratas	Fris - CII 313. Siave Flash	VOLTAGE CURRENT CONTROLS	C14 - ET1 638. Eprom Programmer
AT7 — ETI 137 Audio Oscillator	PH10 — ETI 540. Universal Timer PH11 — E.A. 1970 Stroboscope Unit	V1 — ETI 481, 12 volt to +40 VDC 100 watt inverter	C15 — ET1 637. Cuts Cassette Interface
TEST EQUIPMENT	PH12 - E.A. Sync-A-Slide	V2 — ETI 525. Drill Speed Controller V3 — E.A. S.C.R. Speed Controller	MISCELLANEOUS KITS
TE1 - ETI 134 True RMS Voltmeter		V4 - E.A. Stage (etc.) Auto Dimmer 2 K.W.	M1 — ETI 604, Accentuated Beat Metronome
TE2 — ETI 133. Phase Meter TE3 — ETI 533c, Digital Display 1976 Display	PH14 — E.A. Digital Photo Timer	V5 — E.A. Stage (etc) Auto Dimmer	M2 — ETI 546, G.S.R. Meter M3 — ETI 549, Induction Balance
TE4 - ETI 129, R.F. Signal Generator -	PH15 — EA Movie Mimer	4 K.W. & 6 K.W. V6 — E.A. 1976 Speed Control	Metal Locator
TE5 — ETI 130, Temperature Meter	MODEL TRAIN UNITS	V7 — ET1 592. Light Show Controller	M4 — ETI 547. Telephone Bell Extender M5 — ETI 602, Mini Organ
TE6 — ETI 706. Marker Generator TE7 — ETI 709. R.F. Attenuator	MT1 - ETI 541, Model Train Control	POWER SUPPLIES	M6 - ETI 544. Heart Rate Monitor
TE8 — ETI 122, Logic Tester	MT2 - E.A. 1974 Model Train Control	PS1 - ETI 132. Experimenters Power Supply	M7 — ETI 044, Two Tone Doorbell
TE9 — ETI 124. Tone Burst Generator	MT3 - 1.A. 1971 S.C.R. P.U.T. Control Unit	PS1 — ETI 132, Experimenters Power Supply PS2 — ETI 581, Dual Power Supply (High	M8 — ETI 043. Heads or Tails
TE10 — ETI 123. C Mos Tester TE11 — ETI 116. Impedance Meter	MT4 E.A.\ Electronic Steam Whistle MT5 — E.A. Electronic Chuffer	Powered Versien) PS3 — ETI 712. CB Power Supply	M9 — ETI 068. L.E.D. Dice Circuit M10 — ETI 539, Touch Switch
TE12 — ETI 533. Digital Display 1975 Display	MT6 - EA 1978 Train Control	PS4 — ETI 131, Power Supply	M11 - ETI 529, Electronic Poker Machine
TE13 - ETI 117, Digital Voltmeter 1975 Display	AUTOMOTIVE UNITS	PS5 - ETI 119. 5 Volt Switching Regulator Supply	M12 - ETI 236, Code Practice Oscillator -
TE14 - ETI 117. Digital Voltmeter 1976 Display	A1 — ETI 317, Rev. Monitor	1 - PSb - FII III I shorslory Power Supply	M13 — ETI 218. Monophonic Organ M14 — ETI 701. Masthead Amplifier
TE15 — ETI 704, Cross Hatch Dot Generator TE16 — ETI 120, Logic Probe	A2 — ETI 081, Tachometer A3 — ETI 316, Transistor Assisted Ignition	PS7 — ETI 111. I C Power Supply PS8 — E.A. D.C. Voltage Reference	M15 — E.A. I C Volume Compressor
TE17 - ETI 121, Logic Pulser	A4 - ETI 240. High Power Emergency Flasher	PS9 — E.A. 1976 Power Supply	M 16 — E.A. Geiger Counter M 17 — E.A. Electronic Anemometer
TE18 - ETI 118, Digital Frequency Meter	A5 - ETI 239, Break Down Beacon	PS10 - E.A. Dual 30-2 0-30V to 24 or	M17 — E.A. Electronic Anemometer M18 — E.A. 240 Volt Lamp Flasher
1975 Display TE19 — ETI 118, Digital Frequency Meter	A6 — ETI 312, Electronic Ignition System A7 — ETI 301, Vari-Winer	0-60V (a 2A	M19 - E.A. A C Line Filter
1976 Display	A7 — ETI 301, Vari-Wiper	PS11 — E.A. CB Power Supply	M20 — E.A. Bongo Drums
TE20 — ETI 222, Transistor Tester	A8 — ETI 502, Emergency Flasher A9 — ETI 302, Tacho and Dwell Meter	PS11 — E.A. CB Power Supply PS12 — E.A. Dual Regulated Supply	M21 — E.A. Keyless Organ M22 — E.A. Auto Drums
TE21 — ETI 113. 7 Input Thermocouple Meter	AIU - EII 303, Brake Light Indicator	RECEIVERS TRANSMITTERS	M23 - E.A. Electronic Roulette Wheel
TE22 — ETI 107. Wide Range Voltmeter TE23 — ETI 108. Decade Resistance Box	A11 — ETI 309, Battery Charger A12 — E.A. 1970 C.D.I. Canacitor	R1 - ETI 711 Remote Control Transmitter Switch	M24 - E.A. Video Ball Game
TE24 - ETI 109. Digital Frequency Meter	A12 — E.A. 1970 C.D.I. Capacitor Discharge Ignition	R2 — ETI 711R. Remote Control Receiver R3 — ETI 711D. Remote Control Decoder	M25 — E.A. Digital Metronome
TE25 — E.A. SWR Reflectometer	A13 — E.A. High Efficiency Flasher	R3 — ETI 711D, Remote Control Decoder R4 — ETI 711B, Single Control	M26 — E.A. Voice Operated Relay M2 — E.A. Gas Detector
TE26 — E.A. R.F. Impedance Meter TE27 — E.A. Antenna Mouse Rudge	A14 — E.A. Dwell Meter	1 - K5 - ETI/11C, Double Control	M28 L.E.D. Chaser
TE27 — E.A. Antenna Noise Bridge TE28 — E.A. 1968 Transistor Test Set	A15 — E.A. Variwiper A16 — E.A. Tacho for Tune-ups	R6 — ETI 711P. Power Supply	M29 Sound Effects
गामावस्य १६स ३६।	ATO - C.A. Tacho for Tune-ups	R7 — ETI 707A, 144MhZ Converter	M30 — ET1 551. Light Chaser

#### ALL ELECTRONIC COMPONENTS

TELEPHONE 662-3506

The Family Business
118 LONSDALE STREET, MELBOURNE 3000


TELEPHONE 662-3506

#### Direct reading capacitance meter

project. The zippy box is available from Dick Smith Electronics stores and many other suppliers. As usual, copies of the artworks for the printed board and the front panel label will be distributed to various suppliers and these items should be readily available.

If you wish to make your own printed board and front panel label, we can supply the usual dyeline transparencies through the Information Centre.

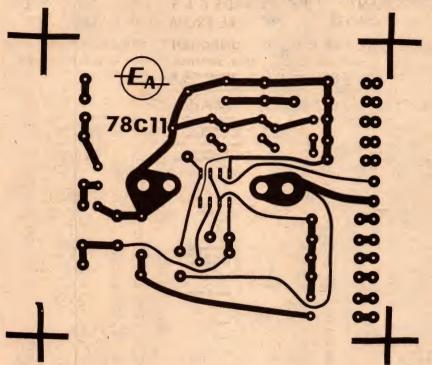The meter which we have used on the prototype is one imported by University Graham and it should be



Here are actual size reproductions of the PC pattern and front panel artwork.

available through most components sellers. On the other hand Dick Smith Electronics offer a much smaller meter which would also do the job. Naturally, if you elect to use this smaller meter but still use the same box, then the different mounting requirements will have to be taken into account. The terminal centres on the back of the small meter are closer than for the larger meter, but we have provided for this on the printed board.

The close tolerance resistors for the prototype were obtained from Radio Despatch Service, but these should also be available from most components sellers. OA47 or similar gold bonded germanium diodes are required, but supplies of these seem to be readily

available.


Construction is quite straightforward and should present no difficulties. Most of the components are accommodated on the PCB and this in turn is mounted on the back of the meter by means of the two terminals. The range selector switch, the two toggle switches and two terminals are mounted on the front panel. The battery is accommodated on the bottom of the box at one end.

The usual precautions should be observed. Care should be taken to make good soldered joints and not to overheat the components in the process. Also, it is important to observe the polarity of such components as diodes, transistors, electrolytic capacitors and the IC. With regard to the IC, we used a socket for it but if you wish, it may be dispensed with providing care is taken when soldering it in place.

Having completed the assembly of



### CAPACITANCE METER

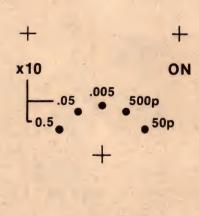

#### Capacitance meter

the printed board, it should be carefully checked to make sure that there are no errors or omissions. Leads of hookup wire should now be soldered to all points on the board, with sufficient length in each case so that they will reach the external destination point. When wiring the range switch for the resistors, I used different colours of wire for each range with the same colour for the two sides of the switch. This makes wiring and subsequent tracing easier.

The meter may now be fixed to the front panel and the printed board assembly may be screwed to it. The switches and terminals may also be fixed to the panel prior to doing all the in-

terwiring.

On the range switch, I used the wafer nearest to the panel for the two sets of resistors. The other wafer also has two sections but only one is used. The three calibrating trimpots are wired to this section, one trimpot being used for the three highest ranges and a trimpot each


for the other two ranges.

The leads to the two test terminals should be taken as directly as possible, but they should also be kept away from other near objects and from each other. This will keep stray capacitance to a minimum, which could become significant on the lowest range. Having done the external wiring it is a good idea to check over it before


proceeding.

With all the rest of the unit now completed, you will find that the battery will just fit nicely into the bottom of the box at the end nearest the switches. Also, as an extra facility, I made up a pair of crocodile clips with plugs attached. I obtained a pair of clips and dispensed with one handle insulator in each case. I then soldered a short piece of 16 gauge tinned copper wire to each one. The clips were then screwed to banana plugs with the insulating pieces removed. The finished items can then be plugged into the tops of the terminals as required. Of course the terminals may be used without the clips when this is more convenient.

To calibrate the meter, you will need some capacitors of suitable values and close tolerance. You will need at least one capacitor which will give a close to full scale reading on one of the three highest ranges, preferably not the highest range because of the wider tolerance in the 8.2M resistor. A capacitor of say, .047uF or .0047uF would be satisfactory. With the capacitor in place, the three 22k trimpots set to mid travel and the range switch on and adjust the trimpot so that the correct reading is given on the meter. The other two ranges controlled by this trimpot should also be correct.

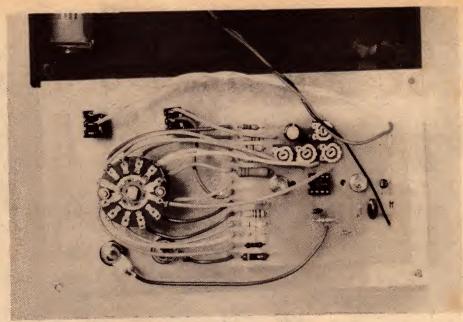

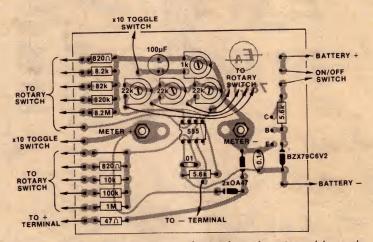Inside view of the prototype showing how the PC board is mounted across the meter terminals. Note routing of leads to the two test terminals.



The component overlay diagram shows the PC board as viewed from the component side. Take care to ensure correct orientation of polarised components.

The other two ranges should also be calibrated in the same way. A 470pF and a 47pF capacitor could be used to calibrate the respective ranges as before, by adjusting the appropriate 22k trimpot.

In addition to the above calibrations, we still have to calibrate the x10 multiplier. To do this, the range switch is set to the 0 to 0.5uF range. You will need a capacitor of known value close to the maximum scale reading of 5uF. The 1k trimpot is set so that the reading on the

meter scale corresponds with the value of the calibrating capacitor. The capacitance meter is now ready for use.

In using the meter, one precaution should always be taken. Before adding a capacitor to the Cx terminals, the range switch should be rotated to the extreme left or 0 to 0.5uF position. If this is not done and a large capacitor is connected to the terminals, the meter will be "slammed", which is a practice

which should be avoided as much as possible. Another point which should be noted is that the x10 multiplier should only be used with the 0 to 0.5uF and the 0 to .05uF ranges. Errors could be experienced with the lower ranges.

It should also be noted that there is a small zero error on the lowest range. Without the clips plugged in, the prototype gives a zero error reading of 1.5pF and with the clips plugged in the error increases to about 1.8pF. Very low capacitance measurements are subject to some error, particularly below about 10pF. However, experience will soon establish what these errors are and they may be allowed for.

It can be an interesting procedure to take a handful of capacitors, including some electrolytics, diodes, transistors, coaxial cable, etc, and make some measurements. This will soon show just how useful our little capacitance meter can be.

# Sensor Tech's solar arrays now in Australia

Silicon solar power cell arrays made by the experienced US firm Sensor Technology are now available in Australia via distributors Amtex Electronics. To promote the product range, Amtex and our reader offer department are offering readers a special introductory price on a useful 14.4V/4.3W battery charging array.

Although silicon solar cells are not as yet cheap enough to make solar electricity directly competitive with mains power, they're getting cheaper all the time. And as this happens, more and more practical applications are opening

At first, solar arrays were only used by public utilities to power remote telephone exchanges, microwave repeaters and railway signalling circuits. But as prices fall they're being used for an ever-increasing range of more mundane jobs — both big and small.

In Nebraska, for example, a massive irrigation project near Mead is using an array of 120,000 cells from Sensor Technology. The array produces 25kW peak in summer, and is used to power a 10hp pump which irrigates 32 hectares of corn and soybeans. During winter the same array is used to power crop driers and dehumidifiers.

A much smaller Sensor Technology array with only 60W peak output is being used to power a mobile receiving

set used for tracking satellites in the Arctic Circle. Similarly a 300W peak array from the same firm is being used to power the instrumentation package on an off-shore data collection plat-

Sensor Technology has of course also supplied many arrays for powering remote communications terminals. Three systems with 1000W peak output have been installed in the Bahamas, replacing diesel-driven generators powering part of the islands' telephone system. Similarly the US Air Force is us-ing 220W peak Sensor Tech arrays to provide dependable power for isolated defence communications repeaters.

A great deal of practical experience is thus behind Sensor Technology's range of solar arrays, to help ensure that they are capable of efficient and maintenance-free operation. And Australian users will now be able to take advantage of the experience generated to date, now that the firm's products are being distributed here by


Sydney firm Amtex Electronics.

The range of solar array modules available covers five basic models. Two give a nominal 7.2V output, for use with 6V accumulator systems, while the other three give a nominal 14.4V output for use with 12V accumulators. The two 7.2V modules give 3.6W and 4.32W peak output respectively, while the 14.4V modules give 2.16W, 4.32W and 8.4W peak output respectively. Each model is available with either tempered glass or Lexan covering, and either with or without a built-in Schottky diode to prevent the batteries from discharging back through the array in darkness.

As a special introductory promotion, Amtex Electronics is offering EA readers the 14.4V/4.32W array type 2036EDG at a reduced price of \$147.00 plus \$5 for certified post and packing. This price includes 15% sales tax.


The array is fitted with a tempered glass cover plate, and has a built-in series Schottky diode. It measures 483 x 165 x 29.3mm, and is built in a sturdy cast aluminium frame which also serves as a heat dissipator.

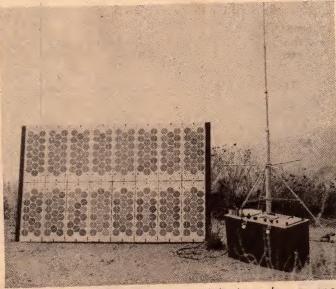Information on Sensor Technology products is available from Amtex Electronics, PO Box 285, Chatswood 2067. Details of the offer are given elsewhere in this issue.



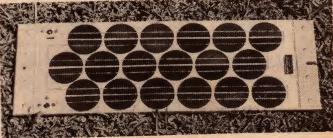This array of Sensor Technology modules is used to power a mobile satellite tracking receiver.





TOP: The 25kW array used by the Nebraska irrigation project. ABOVE: The 14.4V/4.32W module being offered.

# **Tandy Books for Electronics Expertise**



#### **DATA BOOKS**

Voltage Regulator Handbook. How to select a three-terminal regulator. Also heat sink selection and design, power transformer and filter specs. 62-1371. . . . . . . . . . . . 2.95

Linear Integrated Circuits. Covers voltage regulators, operational amplifiers, voltage comparators/buffers, transistor/diode arrays, more. With glossary, dimensions.

Linear Applications. Fully indexed and crossreferenced. Considers both monolithic and hybrid circuits. Subject index with 1200 references to text.

62-1373. 2.95
Linear Applications. Vol2. The latest data sheets, application briefs and articles. Index and cross-reference guide for rapid location of information. 62-1374. 2.95

Memory Data Book. Complete information on MOS and bipolar memory components, systems, application notes and support circuits. An indispensable reference tool.

#### **COMPUTER BOOKS**

Understanding Calculator Math. Contains the basic information, formulas, facts and mathematical tools needed to discover the full capabilities of hand-held calculators.

BASIC Computer Language. 232 pages of programmed instruction and user programs. Teaches you the BASIC computer language and starts you toward becoming a competent programmer.

Understanding Digital Computers. An easy-reading programmed course on digital computer basics. Instruction for the layman with basic rules, chapter reviews, problem and anwer checkpoints.

3.95

#### CB-SWL-HAM

CBer's Handy Atlas/Dictionary. Almost 1000 listings of radio jargon, slang, technical terms, 10-codes. Q-signals. Up-to-date atlas of CB channels. 62-2026. . . . . . . 1.25

CB-SWL-HAM Log Book. Keep an accurate record of stations heard. Tables for recording frequency, call letters, date, time. 64 pages.

CB-SWL-HAM Mini-Log. Compact, spiral-bound book keeps a permanent record of stations received. With same tables as log book, above. Easy to use. 50 pages.

From 5 Watts to 1000. A programmed course to take you from CB to Ham radio in easy-to-understand sections. Theory, test questions, tips to learn code, more.

#### **ELECTRONICS STUDY**

Practical Electronics. Vol.2. Introduction to bread boards, perf box construction, PC

boards. Includes projects for making practical applications. 62-2028......1.95

Understanding Solid-State Electronics. 12 lessons self-teaching course in semiconductor theory by Texas instruments Learning Centre. 242 pages.

Practical Electronics. Vol. 1. Simple to understand approach to DC circuits and theory. Gives questions (and answers) to make learning easier. Illustrated.

62-2037. 1.95


Electronics Data Book. Handy reference for electronics information—formulas, laws, math and more. 112 pages.

Math for the Electronics Student. How to solve problems in circuits, induction, capacitance, RMS peak power, power factor, resonance. 112 pages. 62-2057......1.50
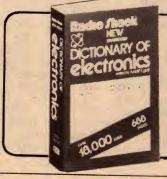
#### GENERAL

Guide to Stereo High Fidelity. Covers component hi-fi, loudspeakers, amplifiers, record-playing and tape equipment. 4-channel sound, assembling a hi-fi system. 175 pages. 62-2029. . . . . . 1.75

Building Speaker Enclosures. Get extra value by building your own speaker system—bassreflex, infinite baffle, plus many more designs. 96 pages. 62-2055. . . . . 1.25



#### Dictionary of Electronics

95 •Over


Over 20,000 •832 Pages
Terms •Illustrated


# Circuit & Design Ideas


Conducted by Ian Pogson


Interesting circuit ideas and design notes selected from technical literature, reader contributions and staff jottings. As they have not necessarily been tested in our laboratory, responsibility cannot be accepted. Your contributions are welcome, and will be paid for if used.
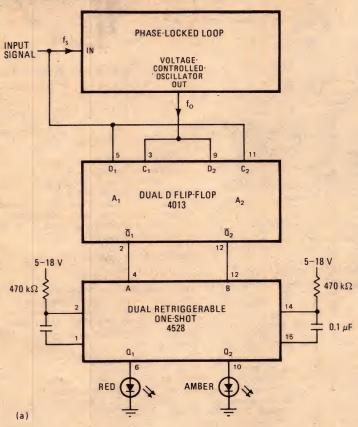
#### D flipflops sense locked state of PLL



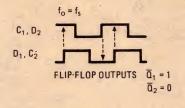

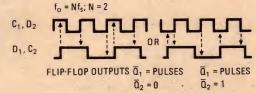

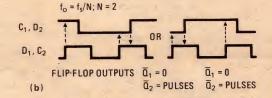

OCKED STATE	RED LED	AMBER LED
UT OF LOCK	ON	ON
OCKED ON fs	OFF	OFF
OCKED ON Nfs	ON	OFF
OCKED ON f <sub>s</sub> /N	OFF	ON
	OCKED STATE  UT OF LOCK  OCKED ON fs  OCKED ON fs  OCKED ON fs/N	OCKED ON Nfs ON

This circuit uses a dual D flip-flop to sense the locked state of many popular phase-locked loops, such as the Signetics 562 and 565. By adding a dual one-shot and LED combination to the flip-flops, the circuit visually indicates locking for the conditions where the output frequency fo is locked to the input signal fs, to its harmonics Nfs, or to its subharmonics fs/N.

The circuit shown in (a) determines whether a fixed (that is locked) relationship between fs and fo exists by employing both flip-flops in a simple phase detector. The fs signal drives the D input of flip-flop A1 and the C input of A2, and the fo signal emanating from the voltage-controlled oscillator output of the PLL drives C1 and D2. The design of the phase detector accommodates a PLL having a phase comparator that can generate an upper and lower fs-to-fo phase displacement of 180° and 0° respectively, for the locked condition. The comparator does this by deriving an fo that is displaced 90° with respect

of fs when the loop is in the centre of its

(c)

The circuit response for a constant fo and fs may be understood with the aid of (b). Because the D flip-flops read the data signals (Di) on the positive edge of each clock (Ci), whenever the data frequency fdi equals the clock frequency fci, Q1-bar and Q2-bar of the 4013 remain fixed at either logic 1 or logic 0, depending upon whether the signals at Ci and Di are in phase or out of phase. In either case, the output from the corresponding edge-triggered one-shot in the 4528 will be zero.

When fc is an integral multiple of fd, or fd is an integral multiple of fc, there will be a pulsed output signal from one of the output ports of the 4013 and a corresponding signal at the 4528 to light the LED. Note that because the one-shot is retriggerable, its output will be constantly at logic 1 for a pulsed input signal. The output (logic 1 or logic 0) from the other port of the flip-flop will be constant. When fo and fs are out of

lock, each flip-flop reads random 1s and 0s, causing pulsed output signals to appear at both ports of the 4013. The table (c) summarises circuit operation.

In cases where it is necessary to detect only the condition fo = fs, a simpler monitor can be constructed using only a single D flip-flop and one LED that is connected to its Q-bar output. The LED will light whenever fo = fs.

(By L. W. Shacklette and H. A. Ashworth, in "Electronics".)

# Novel variable power supply has many uses

This variable voltage power supply is being used by my son to power his slot car set and other small electric toys. The reference voltage (2V) is supplied by the voltage drop across the green LED

# PHILIPS SPEAKERS & SPEAKER KITS

3-WAY SYSTEM AD 12 K 12 SPEAKER KIT \$289.00 pair



An excellent range of Philips world famous speakers and speaker kits are now stocked by Electronic Agencies, 115 - 117 Parramatta Road, Concord, 2137, Phone: 747 6472

3-WAY SYSTEM AD 8 K30 SPEAKER KIT \$205.00 pair

Consisting of:

AD12K12SK Speaker Kit \$200.00 Pair AD12K12TK Timber Kit \$ 89.00 Pair

Buy Speaker and Timber Kit separately or together for \$289.00 Pair (AD12K12)

#### AD12K12SK SPEAKER KIT contains:

2 x AD0140/T8 1" Tweeters 2 x A D5060/SQ8 5" Mid Range 2 x AD12100/W8 Woofers

2 x ADF500/4500/8 Crossover Networks

2 x Level Control Modules Wood Glue, Woodscrews, Damping Material, Caulking Compound.

#### AD12K12TK TIMBER KIT contains:

2 x Enclosure kits with walnut grain material "Wrap-Around" walls, black stained baffles and backs and grille cloth assemblies, with black grille cloth.

TOOLS REQUIRED FOR COMPLETION 1 x Screwdriver, 1 pair of Scissors
Optional: Hammer and nail or small drill

#### SPECIFICATIONS

Power Handling Capacity: 40 watts RMS per channel Impedance: 8 OHMS Crossover Frequency: 500 and 4500 Hertz Enclose Volume: 62 litres (2.2 cu. ft.) **Enclosure Dimensions:** Height Width

720 mm 460 mm

Depth 261 mm



No electronic knowledge required to construct these enclosures.

Woodwork completely precut and veneered.

Consisting of:

AD8K30SK Speaker Kit \$141.45 Pair AD8K30TK Timber Kit \$ 63.55 Pair

Buy Speaker and Timber Kit separately or together for \$205.00 Pair (AD8K30)

### AD8K30SK SPEAKER KIT

2 x AD0140/T8 1" Tweeters 2 x AD5060/SQ8 5" Mid Range 2 x AD8066/W8 8" Woofers 2 x ADF600/4000/8 Crossover Networks 2 x Level Control Modules, Wood Glue, Woodscrews, Damping Material, Caulking Compound.

#### AD8K30TK TIMBER KIT contains:

2 x Enclosure Kits with walnut grain material "Wrap-Around" walls, walnut grain baffles, black backs and grille cloth assemblies with black grille cloth TOOLS REQUIRED FOR COMPLETION: 1 x Screwdriver, 1 x Pair of Scissors.

Optional Hammer and nail or small drill.

#### **SPECIFICATIONS**

Power Handling Capacity: 40 watts RMS per channel Impedance: 8 OHMS Crossover Frequency: 600 and 4000 Hertz Enclose Volume: 27 litres **Enclosure Dimensions:** Height Width Depth 550 mm 340 mm 245 mm

## SEPARATE SPEAKERS and CROSSOVERS



AD 0160/T8 1" High Fidelity **Dome Tweeter** \$13.00

Power Handling Capacity: 20 W rms with 1600 Hz crossover filter ADF 1600/8. 40W rms with 4500 cross-over filter ADF 500/4500/8 Impedance: 8 OHMS Resonance Frequency: 1 kHz Frequency Range: 1.5-22 kHz



AD 5060/SQ8 5" High Fidelity Mid Range \$18.00 ea

Power Handling Capacity: 40 W rms with cross-over filter ADF 500/4500/8 Impedance: 8 OHMS Resonance Frequency: 210 Hz Frequency Range: 180 Hz-



AD 8066/W8 High Fidelity Woofer \$22.00 ea

Power Handling Capacity: Impedance: 8 OHMS Resonance Frequency: 28 Hz Frequency Range: 35 Hz -



AD12100/W8 12" High Fidelity Woofer \$59.00 ea

Power Handling Capacity: 40 W rms Impedance: 8 OHMS Resonance Frequency: 19 Hz Frequency Range: 40 Hz -1.2 kHz

ADF500/4500/8 CROSSOVER NETWORK: \$50.00 Pair

ADF600/4000/8 CROSSOVER NETWORK: \$69.00 Pair (Includes leads, fastons and attenuators)

SPECIALISTS IN ELECTRONIC COMPONENTS

## **ELECTRONIC AGEN**


115 — 117 Parramatta Road, Concord, 2137. Telephone 747 6472

9 a.m. - 5.30 p.m. MON - FRI 9 a.m. - NOON SAT BUSINESS

MAIL ORDER: P.O. Box 1005, Burwood North, 2134.

All large Philips speakers sent "Freight On" through Comet Transport.

Small items add 5% for postage.

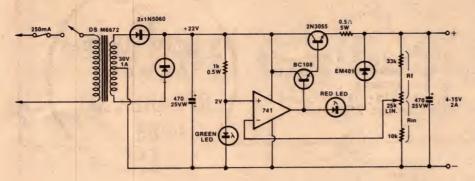

which also serves as a "power on" indicator light. With the resistance values shown the output voltage can be varied from 4V to 15V. Vo = Vref (1 + Rf/Rin).

The 0.5 ohm resistor, the EM401 diode and the red LED form a current limiting circuit which limits the maximum current to 2A, with low resistance loads or short circuits. The red LED lights when current limiting occurs, allowing it to be used as a fault indicating light. With the 2N3055 mounted on a 5cm length of Philips type 35 heat sink it can withstand a short circuit on the output indefinitely.

(By Mr M. J. Lauritsen, 7 Nicolle Avenue, Hawthorndene, 5th Aust.

5051.)

#### Handy patch panel in a box

Here is a handy little unit I have evolved to solve interconnection problems. As an entertainer, I work with a variety of audio and lighting equipment of my own, which frequently has to be interconnected with inhouse audio and lighting systems at various venues. Needless to say, Murphy's Law always seems to operate, so that the plugs and sockets don't mate.

To solve the problem I made up the patching box shown. It simply provides a variety of audio and other connectors, interconnected in groups. Inside the lid I carry a number of patching


cords, which may be used to interconnect between the groups to provide even more permutations and combinations. Between the cords and the interconnected sockets, this provides a solution to just about every patching problem I have met.

Just which sockets you provide is up to you, of course, and you can also make the box in any convenient form. But I pass on the basic idea, as it should be of value to anyone who must set up audio and similar equipment in a variety of situations.

(By Mr. M. Ronell, 14 Griffen Street, Surry Hills NSW 2010)

......
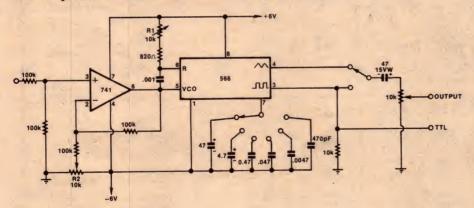
### FM square & triangular wave generator




A useful signal generator that can provide both square and triangular waveforms is shown in the circuit. It can be made to oscillate over a wide range of frequencies. The device will operate from 0.5Hz to 500kHz with the values of components illustrated.

The maximum output voltage of the square waveform is approximately 6Vpp into a load greater than 2K and approximately 2.2Vp-p for a triangular waveform. R1 provides a 10 to 1 frequency variation while the selector switch S1 selects the frequency range by switching different values of capacitance into the circuit.

The 741 operational amplifier not only acts as a buffer stage to the input but also provides the correct DC level to the input of the VCO. This DC level is adjusted with the potentiometer R2. It should be set at approximately 4V to obtain minimum FM distortion.

The maximum VCO input voltage is  $\pm 0.5$  V and the corresponding frequency deviation is  $\pm 3.3$ kHz. The frequency of the modulating signal may extend from DC to about 100kHz which is adequate for most applications.

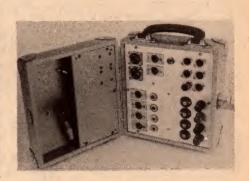(By Mr T. G. Tang, PO Box 26, St Lucia, Qld 4067.)



### MERUN

## WIRE WOUND RESISTORS POWER RHEOSTATS

"SINGLE UNIT" orders accepted Prompt deliveries
RESISTOR RANGE: 3 to 750W rating Values from 0.01
Tolerances to 0.1%. Fixed & Adjustable RHEOSTATS: 20-400W in 5 body sizes Values 0.1 — 100k
Linear & tapered windings

Specialised repetition windings & low ohmage, high wattage "Load Bank" units designed to customer requirements.

Manufactured in Australia by

#### HURTLE WEBSTER PTY LTD

11 Spray Avenue, MORDIALLOC, Vic. 3195 Tel: (03) 90 4144, 90 4344

Queensland — Colourview Wholesale, 56 Raynham Street, SALISBURY NORTH. (07) 275 3188

Tasmania — W. & G. Genders Pty Ltd.
All Branches

South Instant Component Service,
Australia — Suite 8 — 147 Ward Street,
NORTH ADELAIDE.
(08) 267 2393

Western
Australia — W. J. Moncrieff Pty Ltd,
176 Wittnoon Street.
EAST PERTH.
(09) 325 5722

# Audio impedance meter

Part 2

Last month, we detailed the performance characteristics of this new audio impedance meter, and described the circuit. In this second article we present the constructional details, and describe how the completed instrument is used.

by RONALD SALTER

12 Ayr St, Macleod, 3085.

The only part of the circuit left to describe is the power supply, which consists of two type 216 9V batteries, and double-pole switch S4. The writer originally intended the power supply to be 9 volts total, so that a package supply could be used, but there was insufficient AC drive to the coupling transformer at this voltage. The drain from each battery is close to 8mA so, unless the unit is left switched on for long periods, the batteries will last a good while. Rechargeable cells in this size are now available if you are prepared to pay the price.

The instrument is built in a 196 x 112 x 60mm plastic box with aluminium panel, and both are easy to drill, ream, or file. A Scotchcal panel can be made from the panel drawing (Fig. 5a). The components, aside from panel controls, meter, batteries terminals and three resistors, are mounted on a 55mm x 155mm PCB. Fibreglass is the preferred material for this board since insulation resistance, particularly around the inputs to ICs 3 and 4, should be as high as possible.

The PCB is attached on the front panel with two angle brackets and the board mounting has been arranged to keep the leads from S2 to the multiplier resistors to a minimum length. The angle brackets are in turn attached to the front panel by machine screws, one of which must be countersunk to clear the potentiometer knob. Put a solder lug under one of these brackets, and run a wire to the PCB earth strip, to earth the front panel. The measuring terminals are mounted in the left-hand end of the box, in line with the front panel marks, on 3/4in centres to accommodate a 2-pin banana plug.

The oscillator frequency switch, and input jack for the signal generator, are mounted in the right-hand end of the box. This allows the oscillator to be deleted without altering the panel layout. The prototype employed Dymo labels for the frequency selection, but a Scotchcal label could be made from Fig. 5h

If the gain potentiometer option is preferred, simply drill a hole for the pot. shaft, using the centre of the gain switch cutout as the drilling point. The panel lettering is arranged to allow the lettering "HI" and "LO" to be obscured by the pot. knob. Because of the gain control options, resistors R15, R16 and R17 are not on the PCB; they are mounted on a small lug strip, which is secured to the front panel by slipping the strip mounting lug under the switch mounting flange, and putting the switch screw through both.

For the gain pot., the only resistor to be accommodated is R17, and this can be soldered between the pot. lug and the pot. case, care being taken to ensure that the case is earthed to the front panel. If in doubt, run an earth wire from the case to the PCB. The batteries can be held in the bottom of the plastic case by a small bracket made of aluminium strip.

In an effort to be a little different, the ratio dial pointer is made from a pin, fastened to the underside of the knob skirt with contact cement. Make sure the shaft of the pin is accurately aligned with the white pointer line on the knob. If desired the pointer could be made from a scrap of perspex with a line scribed on it.

Take care with the assembly of ratio pot. P4, because the accuracy of the instrument depends on it. The dial pointer must align accurately with the end stop marks on the dials, and the pot. shaft must be absolutely concentric with the dial scale. Check this by noting whether the tip of the pointer remains concentric with the scale as the knob is rotated. Take care also with the wiring from the PCB to the various switches.

The leads from S2 to the multiplier resistors R7 to R12, the trimpot P6, and the trimmer C12, must be kept as short as possible. It is also desirable that the leads to the switch S1 be kept short, although trouble will be experienced in fitting S1 into the case if these leads are



Typical test set-up using the new instrument. Here the impedance of a loudspeaker is being measured at various frequencies provided by an audio oscillator.

cut to the bare minimum. An average length of 50 to 70mm seems a reasonable compromise.

The lead from the PCB to the hot side of the test terminals should also be kept as short as possible. The writer first wired this in shielded cable, but found that the cable capacitance affected the calibration severely at high frequencies. Use small-diameter hookup wire for this lead.

Coming now to the calibration and use of the meter, the first step is to set the oscillator gain pot. This is best done using an oscilloscope. With \$1 set to F1, put the probe on the output of IC1, and adjust P1 until oscillation just occurs, with little or no visible distortion. Switch to F2, and again check the waveform. If an oscilloscope is not available, simply turn on the meter with the Z terminals open circuit, and set P1 on minimum gain. (Pot. moving contact at earth end.) Slowly increase P1 until the meter deflects suddenly to one side. Check that the meter deflects on both F1 and F2. If not, increase the setting of P1 a little.

Next, set the buffer amplifier gain. Put a resistor across the Z terminals, and roughly balance the meter. With the oscilloscope probe on the hot Z terminal, adjust P2 for maximum output without visible clipping of the waveform. Without an oscilloscope, put a resistor across the Z terminals, and adjust the controls until the meter is nearly, but not quite, balanced. Now adjust P2 for minimum meter deflection, then slowly increase it again while watching the meter. A point will be reached at which the meter deflection will remain constant despite increases in P2. Set P2 just below this point.

If the oscillator has been omitted, a slightly different procedure is required. Adjust P2 for minimum gain (minimum meter deflection or oscilloscope signal), then slowly advance the signal generator output control, until waveform clipping occurs or meter deflection ceases. Back the output off a little and note the output control setting. This will be the maximum permissible level, and will give the most linear calibration, although voltages less than this can be used.

Now for the ratio dial calibration. You will need three close-tolerance resistors with values of 100 ohms, 10 kilohms, and 1 megohm. Put the 100 ohm resistor across the Z terminals and set Rm to the 1 kilohm position. Set the ratio dial to 0.1 on the P scale and adjust P5 to null the meter. (If the null occurs at the other end of the scale, reverse the end connections to P4, then repeat the adjustment.) Now put the 10 kilohm resistor across the terminals, turn the dial to 10.0, and adjust P3 to null the meter. This may upset the 100 ohm adjustment a little, so repeat these steps several times.

All that remains is calibration of the 1 megohm range, which is best done us-

ing a signal generator. Before beginning the calibration, the signal generator output voltage must be set as described above. With the 1 megohm resistor across the Z terminals, adjust the signal generator to 100Hz, switch to the 1 megohm range and set the ratio dial to 1. Adjust P6 until the meter nulls. Set the signal generator to 10kHz and adjust C12 to null the meter again. If the meter will not null, reduce the frequency to 5kHz and re-adjust C12. If a signal generator is unavailable, set P6 in the F1 position and C12 in the F2 position. Your Meter is now calibrated.

RESISTANCE MEASUREMENT: Simply place the unknown resistor across the Z terminals, and adjust the multiplier switch and ratio pot. dial until the meter nulls. Read the value from the resistance scale on the multiplier, and the P scale on the pot.

Example:

The multiplier switch is set to 1 kilohm. The ratio dial reads 0.3 on the P scale. The resistance value is 1 kilohm x 0.3 = 300 ohms.

Either F1 or F2 may be used, or any signal generator frequency from 10Hz to 10kHz. For extreme high and low resistance, consult calibration charts.


**IMPEDANCE MEASUREMENT:** Place the unknown impedance across Z, and adjust the dial for balance, using the ohms scale and P scale as above. Use a signal generator if the impedance at a particular frequency is desired.

**INDUCTANCE MEASUREMENT:** The 2-frequency measurement of inductance is, with a little practice, easier to do than to describe. Follow these steps:

- Turn the oscillator switch to F2, or adjust the signal generator to 1590Hz.
- b. Adjust the dials for a null setting, and read the value on the P<sup>2</sup> scale.
- Turn the oscillator switch to F1, or adjust the signal generator to 159Hz.
- d. Again null the meter, and read the value of P<sup>2</sup>. If it is necessary to change the multiplier switch to obtain the second null, repeat steps (a) to (d), using the next higher or lower position of Rm, as required.
- e. Subtract the reading obtained in (d) from the reading obtained in (b). Turn the knob to this value on the P<sup>2</sup> scale.
- f. Read the value under the pointer on the P scale.
- g. Multiply this number by the inductance reading on the multiplier scale.

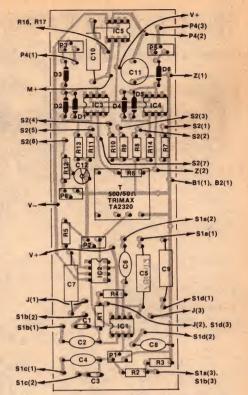Example:
Reading at F2 — The multiplier switch is set to 10 henries. The ratio dial reads 6 on the P<sup>2</sup> scale.

Reading at F1 — The multiplier switch is set to 10 henries. The ratio dial reads 2 on the  $P^2$  scale. Subtract 2 from 6: 6 - 2 = 4. Turn the dial to  $P^2$  = 4.



Layout of components on the PC board. Note that resistor R6 is soldered directly across the transformer terminals.

Read the corresponding point on the P scale. P = 2. Therefore the value of the inductance is 10 henries x = 20 henries.

CAPACITANCE MEASUREMENTS: For capacitors with negligible leakage, which is the usual case, follow these steps:

- a. Turn the oscillator to F1, or adjust the signal generator to 159Hz.
- b. Adjust the dials for a null setting, and read the value on the 1/P scale.
- c. Then the value of the capacitor can be read from the capacitance scale on the multiplier, and the 1/P scale on the pot.

  Example:

The multiplier switch is set to 10

The ratio dial reads 0.2 on the 1/P scale.

The capacitance or value is  $10uF \times 0.2 = 2uF$ .

If leakage is suspected, repeat (a) and (b) above, reading the value on the P<sup>2</sup> scale. Then proceed as follows:—

- d. Turn to F2, or set the signal generator to 1590Hz.
- e. Null the meter, and again read the value of P<sup>2</sup>.
- f. Subtract the second reading from the first, and set the dial to the resultant, on the P<sup>2</sup> scale.
- g. Read the value under the pointer on the 1/P scale, and multiply it by the capacitance reading on Rm.

# More SUPER MAIL ORDER BARGAINS!

If you can buy the same quality cheaper, let us know and we will refund the difference.

36 HELEN ST., AND 14 DUNCAN ST., VALLEY, BRISBANE, QUEENSLAND 4006, PH. (07) 52 4833, 3 LINES, EST. 1946. MAIL ORDER SPECIALISTS

\$21.50



1978 MODEL

20 WATT OTL HI-FI STEREO AMPLIFIER

SPECIFICATIONS CIRCUIT

OUTPUT POWER OUTPUT IMP. FREQUENCY RESPONSE

INPUT IMP POWER SOURCE for P.A. Systems

8-transistor OTL circuit 10 Watt maximum, per channel 8 ohms

20-25:000Hz

100K ohms DC 24V. 800mA

# \$11.50

All silicon 4-transistor OTI. circuit

IDEAL P.A. SYSTEMS

#### WATT OTL HI-FI AUDIO AMPLIFIER FREQUENCY RESPONSE : 40 - 40,000Hz

INPUT IMPEDANCE OUTPUT IMPEDANCE

POWER SOURCE CURRENT CONSUMPTION: 50mA at no signal, 500mA

120mV input for non-dist-

orted max. output About 50KQ

Pzt transcription cartridge

The latest from "ACOS".
type 104 transcription P.Z.T. ceramic stereo cartridge.
Buy from us and

Designed exclusively for micro-groove records. Complete with fix-ing adaptors.

Has diamond stylus. 2 Dz.

ACOS REPLACEMENT LONG LIFE CARTRIDGES

Famous English "ACOS" complete PICK-UP cartridges with STYLUS. Current issue to fit "Garrand" and most other types of players and decks from all common sapphire c.tridge which will play steres records. A special purchase. \$1.95. C.P. 91-2 steres apphire \$2.500. C.P. 93-1 sapphire \$3.500. C.P. 94-1 ceramic sapphire \$3.500. C.P. 94-1 ceramic sapphire \$7.500. C.P. 94-1 ceramic sapphire \$7.500. C.P. 94-1 ceramic sapphire \$7.500. S.P. 94-1 ceramic sapphire \$7.500. S.P. 95-00. All sapphire \$7.500. All sap

Replacement STYLI available G.P. 91 sap. \$1.20; G.P. 91 dia. \$1.85; G.P. 93 & G.P. 94 sap. \$1.25; G.P. 93 & G.P. 94 dia. \$1.85; G.P.

24 HOUR TIME **CLOCKS \$14.50** 

240 volt A.C. 15 amps rating. Made in the U.K. Days of the Week and 24 hour setting— also push on/off test button. Ideal swimming pools, all

20z.

104 dia. \$1.85

save. \$7.50.

: 4 ~ 16 \\ : D. C. 24 \( \nu \) 30 \( \nu \) for max. output

135 4-81

#### STEREO AMPLIFIERS

9v DC supply

watt with tone and vol. controls sillus.) \$13.95. full diagrams and

steins. \$16.95 1 lb. 6 watt



AUDIO AMPLIFIERS FROM \$11.50

24V DC Supply for P.A. System 15 Watt (as Illus) \$11.5 20 Watt \$21.5

019

UNI DIRECTIONAL DYNAMIC MICROPHONE CARDIOID TYPE



Features dual impedance — 600 ohm and 50K ohm netted ball head, on/off switch, stand holder, 201t. cable. Extremely wide range frequency response This microphone has the unique facility of shutting out onwanted noise originating from the opposite direction placed due to its unique control of the companies of th

Fantastic Purchase! CONDENSER MICROPHONES



One of the finest made Used by the B.B.C. in their outside broad casts. Our huge direct import just arrived makes this price possible Freq. response 30—16.000 HZ. imperance 500 ohms, output level —68. BB at 1.000 HZ. Polar pattern underectional (cardiorid): Max sound level 125 DB. 201t of shielded cahle and on-off switch Complete with battery Us. \$45.

PANEL METERS \$6.75

PANEL METERS. Dimension

#### MULLARD AM/FM TUNERS

INPUT 35 V D.C.

INPUT 35 V D.C.

Made in U.K. Slight manu-lacturing faults and deficiencies with ferrite antenna for AM reception. Covers full IFM. Band to 108 MICs. Beautiful air spaced turning gang covers full AM/FM Band width. Provision for tuning meter and FM light. Sold AS IS and NOT accept-ed for return. Good Value air

\$9.95 New in "As Is" condition

#### **7 WATT ENGLISH MULLARD STEREO AMPLIFIERS**

Top quality British manu-facture. Slight imperfections. Can be used with above tuner. Not accepted for return. Again good value in "As Is" condition at

\$6.95 New 1 lb.



\$1.95 for 3 assorted boards. COMPUTER BOARDS 2 16.

Set of 3 comprising 2 boards 7" x 5" with 1 board 5" x 4" comprising minimum of 25 transistors plus hosts of diodes, resistors, capacitators, inductors, etc.

#### **VEEDER ROOT** COUNTER

0 -- 9999999 240 V A.C Brand New in Carton \$5.95

#### DIGITAL CLOCK BOARDS \$5.95

REALLY EXCELLENT CON-DITION and the finest Boards we have ever imported to Australia Contain a real wealth in Power Transistors, Diodes, Ordinary Transistors, Relays, Resistors, Capacita-tors, etc. Exceptional value, Board size is 3½ x 5°. less cut out of 3½ x x 5°. less cut out of 3½ x x 2½°.

New 1 lb.



#### INTRUDER **ALARMS**

ALAHNIS

Strident alarm horn gives instant warning of intrusion and unnerving deterrent to the prowler. The self contained battery operated system guards up to 4 entry positions. Consists of 4 switch mats, connecting wire and connectors. Master control unit incorporates alarm tool unit incorporates alarm

\$45.00 without batteries 6 lb. FORMERS \$13.50

British made. 240 volt input A.C. Output 18 volts at 3 amps. Complete with inbuilt thermal relay. New. 2½ lbs.

### \$46.95

12 volt DC 24 VOLT D.C.

#### **POWER** SUPPLIES

Ex Computer. Fully smooth-ed, stabilized and adjustable. Rated 12 volts at 4 amps D.C. Input 220-240 volts A.C. and made by Olivettl. Size 10" x 7" x 6". 14 lb.



240 volt AC Dimmers/Temp. Controllers \$21.50

LonkToller's X-1.5U
Orig temp. controllers for Rank
Xerox. Are solid state and mig
by Gresham Electronics Ltd..
U.K. Will dim up to 3000 axis
with no flicker or fluctuation in
voltage. Use also lor DC motors
up to 3.0 Are see simple of the conwith use of thyristors. New.
complete with instructions. Size
6 y x 4 x 3 x 3 31b.



#### **TIMING CLOCK**

Absolutely brand spanking new. Manufactured by Midgley Harmer of England for famous stove manufacturer. A magnificent time piece and can switch on and off many devices within a 12 hour time cycle. One set of contacts rated at 240 VAC, 18 amps. Another set at 240 VAC, 30 amps. Very easy setting arrangement. Separate setting facility.

A ONE TIME ONLY OFFER 21.2 by 2. Inserting new Manufacturers of the contacts and setting facility.

\$12.50 2 lbs.

- C

LIFE MULTITESTER EXCLUSIVE

\$10.95

Life compact versatile meter is ideal for

home, school or lab.
Accuracy combined with
wide view colour-coded
scale. Make it ideal for field
us. Precision meter move-

us. Precision meter move-ment and complete with test leads and batt. Specifications: AC volts 0-10-50-250.1000, DC volts 0-10-250-1000, DC current 0-1-100 DC Mr OHMS 0-150 K (3000 OHMS CENTRE. 8 oz.



240v AC. \$5.95 Exceptionally robust, brush-type, series wound motor

Six speeds: 500, 850, 1100 8,000, 12,000 and 15,000 r.p.m (ideal polishing speeds) main disve-shalt. Very powerful and useful motor. Size approx. 2,1/2 dia-meter. 5' long. 2,1b.

10,000 R.P.M. 240V MOTORS, \$11.50 AC

1/3 h.p. cont. duty ball bearing construction Beautifully made Brand new Edeal polishers. etc.

'Magic Eye' Light Sensitive Switch Marine or Automobile



This new device will AUTO-MATICALLY switch on your Riding or Parking lights at DIISK and switch them off again at DAWN. Completinstructions with all units. Panel or Dashboard size 4" x 12". Brand new, Price. \$5.95 Post 60c

12 voit D.C.



#### PRESSURE SWITCH

A high quality, sensitive and reliable air operated 3 level unit designed for close limit control of liquid levels or low pressure air. Originally made for use in washing machines, dishwashers, etc of the automatic type where variations of programme call for different levels of liquid, but is ideally suited to applications involving pump control, water level switches,

#### LINEAR **ACTUATOR Plessey Type**

\$25



A compact aircraft actuator, in a rectangular case, with split series field motor having an operating voltage range 18-29 Volts DC, and a normal current consumption of 3 amps. Working load 100 lb. normal, 150 lb. maximum. Stroke 3 in. Operating time 6-7 secs. Rating of motor under normal load 1.5 mins.; output 0.03 hp. at 12,000 r.p.m. The actuator includes snep-action limit switches, and a clutch to prevent damage in the event of over-

load. The plunger is fitted with a spring-loaded connector drilled two holes 376 in. diam. x 376 in. deep, and the rear end fitting is drilled 3716 in. diam. x 578 in. wide. Distance between retracted centres 1, ½ in. A breeze plug is provided for cal connections. Overall dimensions; 7, 38 in. x 3 in. x 2 in. Weight 2 ib. 3 oz. As new, in excellent working order. Cost Gov. \$280. Also available in 6" stroke.



LENSES \$4.50

FRESNEL

12 In. sq. x 1 mm. thick. f.l. 13, 1/2 in.

f.1. 13, 1/2 in.
Precision werker in thin optical plastic and providing large area magnification equivalent to expensive glass leness. Fine optical quality permits use as solar furnace elements, condensers, image magnifiers, light intensifiers, overhead and back projection optics, camera image brighteners (disco scenes). Use our low RPM geared motors to drive these.

Uouble Fresnel Lenses (condenser same size as above \$7.50 11b.



#### 1/2 HP "DELCO" MOTOR 240V AC \$45

500 to 10,000 RPM fully ball bea controlled by speed control

Special 3" pulley EXTRA \$5.75 Speed control EXTRA \$45.00 These are one of the latter #160 Life Meedingment in 740 AC motions have tremendous applications in workshops, cold winding machines, purings, finds, lather, lest machinesy expenses, finds, lather, lest machinesy expenses, finds, lather, lest machinesy expenses, finds, lather, life speed control or the latter sile to the latter sile machinesy expenses to the latter sile machinesy and latter with 1 a adjustment of 1 PPM. Motor can be, applied with instructions from making you own speed control. \$45

LOW SPEED MOTOR

\$5.95

"Meccano" Power Units \$9.50

Type 8156. Reautifully made in England by this famous manufacturer. 240 volt A.C. mains input gives 26 volts at .63 amp. and 26 volts at .63 a



12 VOLT POWER

12 YOLF POWER
UNITS, \$7.50


Made in England by "Smoothflow",
a division of "Meccano", 240 volt
6 amp. Fully protected from damage by automatic cutout which
resets itself automatically. Branch may in, cartons with instructions,
ideal models, battery charger for
small batteries (especially our Nife
Batteries). Terrific bargain!

#### **VEEDER ROOT** COUNTER 0-999

Brand new 240 V. A.C. 50 C.P.S. 10 v/a Veeder Root Counters. Has reset wheel to zero unit. A 1001 applications in repetitive function monitoring.\$10.50 12 oz

P.O. Box 165 VALLEY. BRISBANE
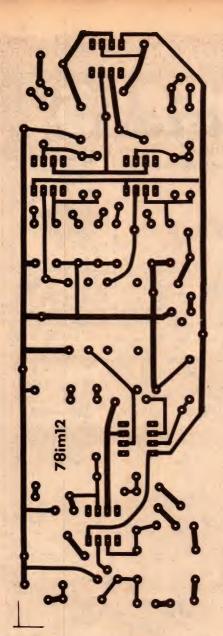
#### Ideal swimming pools, all motors to 15 amps, lights, etc. Brand New. 1 lb. AUSTRALIA'S BARGAIN CENTRE — DIRECT DISPOSALS TRADING CO



Actual size reproductions of the PC pattern and the front and side panels.

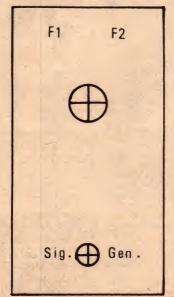


FIG. 5b

58 FIG. 0 0

Example:-

Reading at F1 — The multiplier is set to 0.1uF. The ratio dial reads 1.0 on the P<sup>2</sup> scale.

Reading at F2 — The multiplier is set to 0.1uF. The ratio dial reads 0.2 on the P<sup>2</sup> scale.

Subtract 0.2 from 1.0: 1-0.2 = 0.8. Turn the diai to  $P^2 = 0.8$ .

The corresponding point on the 1/P scale is 1.1.


Then the value of the capacitor is  $0.1 \text{uF} \times 1.1 = 0.11 \text{uF}$ .

RESONANT FREQUENCY MEAS-UREMENT: Using the signal generator, adjust its frequency to give the highest impedance reading for a parallel L-C tuned circuit, or the lowest impedance for a series L-C tuned circuit.
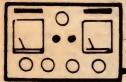
#### References

- "Measurement of Iron-cored Inductances", Radiotron Designers Handbook, 4th Edition, P. 250.
- 2 "Easy-to-Build R-L-C Bridge", Electronics Australia, P. 40, Vol. 39 No. 12 March 1978
- 3 Unpublished contribution for "Circuit and Design Ideas", titled "Improved R-C Oscillator", from the writer, to Electronics Australia.





# The Serviceman

### The customer's story — valuable or misleading?

While it is generally agreed that the customer's story should always be taken into account on any job — to avoid misunderstandings or overlooking intermittents — there are times when such information is not only of little value, but also when it can be positively misleading.

This story really started when a customer brought in a cassette tape deck and small commercial amplifier which, by now, was a bit long in the tooth. According to the owner, the whole system had been playing up in several respects and he wanted to known whether it was worth repairing or whether he should scrap it, and buy a new one; probably something better than the simple "radiogram" concept which this represented.

I duly gave the system the once-over and, while the cassette tape deck was performing quite well, the amplifier system was in a bad way. While I don't normally like advising customers that equipment is not worth repairing, I felt that this was a case where I honestly could not recommend any money be-

ing spent on it.

For a number of reasons I considered that repairs would cost nearly as much as the original amplifier (it wasn't a particularly expensive one) and that, if he was content with this standard of performance, he would be better advised to buy a new unit of the same general kind. One the other hand, if he wanted something better — as I suspected — he would be better off putting that amount of money towards a more expensive unit.

He accepted my advice, said he would think about it, and that was the last I saw of him for several weeks. When he next appeared he had what looked like a brand new amplifier tucked under his arm and an expression which suggested that he had lost \$10

and picked up five cents!

I was right (well almost) on both counts. It was a brand new amplifier and, while he hadn't actually lost any money, he was feeling pretty despondent. It seemed that he had decided to invest in a better quality amplifier and, after seeing one demonstrated at a friend's home had been most impressed by the Playmaster

This story really started when a Twin 40 amplifier. (December 1976, ustomer brought in a cassette tape January 1977.)

Although described as a do-ityourself project he had found a firm which not only marketed kits, but also completely wired units. This latter approach appealed to him, as the price was quite reasonable compared with other commercial units of similar quality. So this was the unit he now pushed across the counter.


And the reason for the long face? He freely admitted that, in an attempt to connect his speakers, he had shorted both outputs. As a result he had blown

all four fuses; one each from the positive and negative rails of each channel. This much was obvious, but what he really wanted to know was how much more damage he had done.

At that stage I wasn't committing myself, but I told him he would be lucky if he hadn't wrecked the output transistors and, possibly, the driver transistors as well. All he could do was leave it with me to check out.

One of the first things I did was dig out the appropriate copies of the magazine and study the circuit, the relevant portion of which is shown here. It is a fairly conventional system in line with the present state of the art.

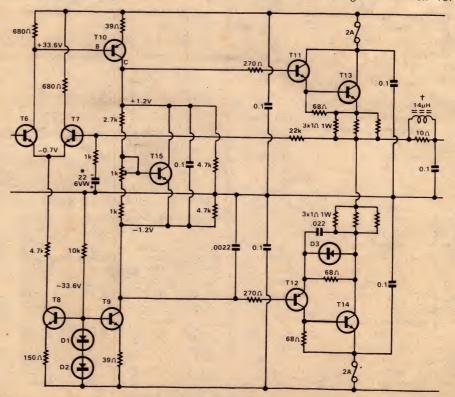In the unit itself, one of the first things I noticed was what appeared to be a burn mark on the case of one of the 2N3055 output transistors; which didn't seem to augur too well for



The section of the circuit involved in this story. A quite ridiculous voltage across the speaker terminals was finally traced to an equally silly reading on the collector of T8. From here, a process of elimination revealed the fault.

finding the system intact.

My first step was to go over the output and driver transistors with an ohmmeter and, allowing for the fact that they were in circuit, try to determine if there were any obvious baseemitter or base collector breakdowns. Rather surprisingly, I could find none.

Thus encouraged I fitted new fuses and prepared to apply power, taking the precaution of not connecting any speakers at this stage. When I finally pressed the switch, half expecting to produce smoke, fire, and confusion, it was a complete let down. All the fuses remained intact and there were no fireworks of any kind.

I went over the circuit with a voltmeter, with particular attention to the base-emitter voltages of the output transistors, then the driver transistors, and then the earlier stages. As far as I could determine everything was normal.

The next logical step was to connect a speaker and feed a tone into the system and see what happened. Having only one speaker which was convenient to use I connected it first to the left hand channel, connected the audio generator and, lo and behold, out came a nice clean signal from the speaker. As far as I could determine, short of an actual power output test, this half was behaving normally.

I moved the speaker over to the right hand channel and tried again. This time it was a different story; the fuse from the -35V rail promptly disintegrated. I disconnected the speaker, replaced the fuse, and switched on again, knowing that this set-up was quite stable. Then I checked the voltage across the open speaker terminals.

Normally one would expect to find only a few millivolts between these points but in fact it turned out to be around 18V! Well, at least I had finally found something to work on.

Not knowing quite what might be wrong I decided to play safe. I disconnected the speaker, then removed both fuses and substituted a 100 ohm resistor in both cases. That way I could work without fear that something else was on the point of breaking down.

To be honest, the whole thing had me puzzled. It appeared that the shorted speaker connections had damaged something which was causing a gross unbalance in the output circuit. By far the most likely culprit would be one of the transistors, yet, from my preliminary testing, they all seemed to be intact.

I could only conclude that the fault was rather more subtle than could be detected by a multimeter, remembering that direct coupled circuits can produce some quite drastic effects from, seemingly, small defects in early stages.

The logical conclusion was that each transistor should be tested, which meant removing each one from the

#### MAIL ORDER Service

We guarantee all orders will be despatched within 24 hours of receipt of order.

#### 7400 SERIES TTL

7400	\$0.28	7425	\$0.40	7474	\$0.50	74122	\$0.60
7401	0.28	7426	0.40	7475	0.65	74123	0.90
7402	0.28	7427	0.40	7476	0.55	74125	0.70
7403	0.28	7430	0.28	7480	0.90	74126	0.70
7404	0.28	7432	0.40	7482	1.00	74132	1.10
7405	0.28	7437	0.40	7483	1.00	74141	1.25
7406	0.40	7438	0.40	7485	1.30	74145	1.10
7407	0.40	7440	0.28	7486	0.50	74151	1.10
7408	0.28	7442	0.65	7489	2.40	74153	1.10
7409	0.28	7446	1.10	7490	0.65	74154	1.50
7410	0.28	7447	1.10	7491	0.90	74157	1.00
7411	0.28	7448	1.10	7492	0.65	74160	1.20
7412	0.28	7450	0.28	7493	0.65	74164	1.50
7413	0.40	7451	0.28	7494	0.90	74165	1.50
7414	1.00	7453	0.28	7495	0.90	74174	1.50
7416	0.50	7454	0.28	7496	1.00	74176	1.20
7417	0.50	7460	0.28	74100	1.50	74177	1.20
7420	0.28	7470	0.45	74107	0.50	74184	2.20
7421	0.30	7472	0.45	74109	0.55	74185	2.20
7423	0.40	7473	0.45	74121	0.55	74192	1.20

#### ☆ SPECIALS ☆

309K	\$1.30	741	\$0.30
555	. 0.35	7805	0.95
723	. 0.50	DL704	1.40
2200uf/40V Axial Electro			0.80
F'glass laminate 1oz	Cu		
230mm x 115mm x	1.5mm		0.50



2N3055 with washers

75c

0	I.C. SOCKET PINS Pack of 50
molex	Pack of 50 0.85 500 8.00

4P AMP JACK PHONO TERMINAL c/w RCA PHONO PLUGS 75c



#### FREE! 78/79 CATALOGUE



WRITE FOR YOUR COPY

NOTE: All components are factory first well known brands of the highest quality. We guarantee our products against any defects --- we well replace or refund if goods are returned within 30 days of receipt of order

Pack & Post 50c minimum - please allow more for heavier items.

LINEAR ELECTRONICS PUNCHBOWL 2196

P.O. BOX 254.

#### RADIO DESPATCH SERVICE THE SPECIALIST STORE


869 GEORGE STREET, SYDNEY, NSW 2000. (NEAR HARRIS STREET) PHONES: 211 0816, 211 0191

#### A 31/2 LCD MULTIMETER SOAR MODEL ME-522

General Specifications -Display: Liquid Crystal Display. Maximum indications: 1999 or -1999. Measuring mode: DC V, AC V DC mA, AC mA, OHMS. Measuring range: 5range change-over in each mode. Polarity: Automatic, negative polarity indication. Zero adjustment: Automatic. Overrange indication: The top of digit of (1) or (-1) is

displayed.



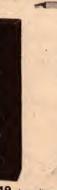



PRICE \$106.49 inc. s/tax

Complete Unit PRICE: \$54.00

OPEN: MON-FRI 8.00 am-5.30 pm Thursday late night shopping until 8.30 pm, Saturday 8.00 am-11.45 am.

#### BRASS SHIPS CLOCKS SMITHS 8 DAY 7 INCH

DIAMETER \$110. Post A \$1.75; B \$3.00; C \$3.60.

GENUINE EX ARMY WRIST WATCHES Complete with nylon band \$19.50 Post \$1.10

#### P.M.G. TYPE TELEPHONES

Standard desk type with magneto bell calling device. Range 30 miles. Uses standard batteries at each phone. Any number can be connected together on single line. \$39.50

(2 TELEPHONE SETS)

\$2 Cartage to Rail. Freight payable at nearest attended Railway Station.

#### RECEIVER No. 210

2-16 M/cs \$65. Transmitter No. 11 suits 210 \$35. 24 volt Power supply to suit above \$15. Or complete station with Headphones. Mic. Morse Key, Antenna \$110.

#### EX ABC MAGNETIC RECORDING TAPES 14"

PROFESSIONAL QUALITY	
5" x 600"	\$1.50
7" x 1200'	\$2.75
P + P \$1.30	
10½" x 2400' \$7.95	
P + P A.\$1.65 B.\$2.75 C.\$3.10	

#### COLLINS INDEPENDENT SIDEBAND TRANSCEIVER TRC/75

Fully synthesised transceiver with am, upper, lower and independent sideband operation. 1KHz steps from 2MHz to 29.999MHz 1 microvolt sensitivity, 2.5KHz bandwidth ssb, 6KHz bandwidth AM 1 RW, PEP max output. Fully automatic tuning of both transmitter and receiver from remote control unit. Complete with automatic aerial coupling unit, mic, headset, etc. 400Hz supply. Ideal for amateur use.
PRICE \$750

#### COLLINS SYNTHESISED 1 SB RECEIVER

TRC/75 receiver section of transceiver specification as above.
PRICE \$400

#### TELEPHONE WIRE

1 mile twin (2 miles) genuine ex-Army Don, 8 perfection condition \$35 per \$2.00 cartage to rail freight payable at destination.

#### **RCA 44BX MICROPHONES**

PROFESSIONAL QUALITY \$75 P&P A. \$1.80, B. \$3.50, C. \$4.55, D. \$4.55.

#### 20X to 60X ZOOM TELESCOPE

With Tripod, \$115.50. Post A\$2.25, B\$4.10, C\$6.10

#### SIEMENS Typing Perforator

240 Volt Type with Keyboard \$57.50

#### SELSYN MOTORS MAGSLIP

RECEIVERS 2" MK2 \$5.50 TRANSMITTER 3" MK2 \$15.00

Post Packing A. \$1.75, B. \$2.75, C. \$2.75, D. \$3.65. P+P: A. \$1.75, B. \$3.00, C. \$3.10

#### SOLENOIDS

200 MA 24 volt, ½in push movement. \$2.50 P+P 80c

#### NIFE CELLS

1.2 volt, fully charged, 4in x 3in x 1in 4 AH.

\$1.50 each. P&P 80c.

CENTRE DRILLS 15"/64 x 5/64 Carbon Steel, \$3 dozen Post 60c

#### ARTILLERY DIAL SIGHTS MK2

Can also be adapted as a Dumpy Level or as base for a telescope has full 360? 5½" diam. gunmetal rotating circle. Adjustable elevation and depression. Has top grade 34" diam. object lens. F.L. 10" with cross hairs, eyepiece, ½" right angle prism — height 10" — weight 3½kgs. With leather carrying case. Original cost \$300.

Our Special only \$27.50 P&P A.\$2.25 B.\$4.00 C.\$6.00

#### POSTAGE KEY:

A: NSW B: Vic, Qld, SA C: NT, Tas. D: WA


#### VALVES

RAND	NEW
NIZ	61

6SN7	\$1.95	6BN8	\$1.95
5U4	\$1.95	6GV8	\$1.95
EF50			
5Y3			
2x2			
	P+P		
6x4			\$1.95

#### ROLA 66 MK 2 TAPE RECORDERS

Good condition \$275.00

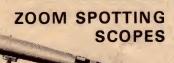

30 x 30 LENGTH 12½", HEIGHT WEIGHT 1¾ lb

\$32.50

45 x 40 Length: 16in Height: 10in Weight: 2lb \$49.50

High grade coated lenses. Ideal for pistol and rifle ranges or general viewing. Zooms in from very low to high powers. Complete with tripods.
POST: A. \$1.75, B. \$3.00,
C. \$3.60

TELESCOPES

25 x 30 \$13.50 P&P A. \$1.30

#### SPY TELESCOPES

8 x 17 mag size of a rifle cartridge extends to 8". Only \$7.95 each, post 60c.

#### BINOCULARS

PRISMATIC Coated Lenses. Brand new

Coi	mp	lete	with case.		
8	x	30	\$36.50	20 x	60 \$102.00
7	X	50	\$48.95	P&P	
10	X	50	51.00	A	\$1.75
12	x	50	53.00	В	\$3.00

20 x 50 \$56.00 C \$3.10 SMALL CLIP-ON

POCKET TELESCOPE 15X \$6.50, P+P 80c

#### 3" ASTRONOMICAL REFLECTOR TELESCOPE

117X magnification FL 700mm with 5x24mm finder scope and two section hardwood tripod. \$169.25.
Post A\$2.25, B\$4.10, C\$6.10.

#### 3000 TYPE RELAYS

P.M.G. 200 ohms — 1.500 ohm Coils \$2.50 each P+P 80c

#### AIRCRAFT INSTRUMENTS

Directional Gyros. AN5735-1 Air Operated. \$35 Sperry Artificial Horizon. AN5736-1 Air Operated. \$45. Slip and Turn Indicators \$17.50 PRP

A. \$1.65, B. \$2.75, C. \$3.10

#### TV WAVEFORM MONITOR

Tektronix type 525 \$175.00.

P.M.G. TYPE KEY SWITCHES. 75c P+P 80c

#### CONDENSER LENS

F.L. \$1.50 each or \$2.50 per pair. P&P 80c

#### IMPELLER PUMPS

New gunmetal body, Stainless Steel Shaft, Neoprene Impeller. Up to 15ft. Lift, suitable for almost any type of liquid. Self priming. Ideal boat bilge pump, sullage drains, etc. Approx. size 8" x 5" %" \$30.35, ½" \$43.30, ¾" \$47.60 P+P- A \$1.95 B. \$3.50 C. \$4.60

Liquid filled compass



With magnified lens sight and degree reader

Only \$7.95 each. Post \$1.30

#### POLARITY & CURRENT CHECKER

3 volt to 400 volt. Simple leads and prods quickly determines positive or negative with illuminated indicators, also checks AC current and intensity, fully insulated only \$4.95, pp \$1.30.

#### MAGNESIUM DRY CELL BATTERIES

Suits PRC 25 and dozens of other uses. 15 volts long life only \$1.50 ea P+P: A. \$135. B. \$275. C. \$360.

#### WRIST WATCHES **SWISS JAEGER**

Le Coultre ex RAAF rated one of the world's best in smart chrome case with black dial. Original cost \$250.

> **SPECIAL \$49.50** Post \$1.30

#### THEODOLITES

Made by Wilds Microptic, with tripod Model T1, reads down to one minute of ARC \$750.

(Usual Price \$1750).

Model T2 reads down to one second of ARC \$1000 (Usual Price \$3200). Freight payable at nearest attended R'way Stn.

#### 200Z FOCUSING MICROSCOPES

200m focusing microscopes, 750X battery and mirror illuminated \$31.75. 200m 1200X similar to above \$47.95 P&P A \$1.65, B \$2.75, C \$3.10.

#### TRANSCEIVERS Ex Army

No. C45 set. 23 to 38MHz with headphones, mic. 24V power supply, etc.

\$2.00 cartage to rail, freight payable at nearest railway station.



#### **EX-ARMY** TWO-WAY FM RADIOS

1.2 WATTS OUTPUT SUPERHET PRC9 AND 9A 27 to 39M/HZ PRC10 AND 10A 38 to 55M/HZ WITH HANDSET ANTENNA \$25 EA. UNTESTED

Battery \$3.95 extra. Harnes \$4.50 extra \$2 Cartage to Rail. Freight payable nearest attended Railway Station.

#### 16MM SOUND PROJECTORS IN GOOD WORKING ORDER

240 volts operated complete with Speaker and Amplifier.

RCA \$275 BELL & HOWELL \$195. \$1 Cartage to Rail. Freight payable at nearest attended Railway Station.

#### CB RADIOS

PMG Approved Famous Pony Brand on 27 Meg 7 transistor model \$55 per set of two

(hand held). 11 transistor model 1 watt (hand held)

\$72 ea.

5 watt 6 channel \$99 ea. Post A. \$1.75, B. \$3.00, C. \$3.60

#### COMMUNICATIONS RECEIVER

COLLINS R — 391/URR Continuous tuning of range 500 Kills 32MHz in 32 bands. Receive frequency indicated directly on digital counter type readout to within 300Hz. Selectivity adjustable in six steps. From 100Hz to 16KHz bandwidth. Sensitivity 1 microvolt or better 240 VAC operation

 10 inch rack mount — autotone on eight preset channels available complete with instructions and service manual and tested.

PRICE \$500.

### Deitch Bros.

70 OXFORD STREET, SYDNEY 2010


SORRY NO COD

#### THE SERVICEMAN

board. Fortunately, the layout was reasonably open and this would not present any real problem. Having made that decision, I decided that the best way to test each transistor was simply to replace it with a new one. A quick check confirmed that I had all the types on hand, and such a check is by far the best one.

(This is not to say that I have anything against transistor testers. It is just that, in sticky situations like this one, a

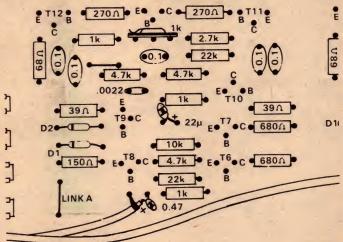The area of the board where the trouble occurred. On the right is a 39 ohm resistor with two 680 ohm resistors below it. On the left is a 39 ohm resistor with a 150 ohm resistor below it. 'Nuff said!



replacement test inspires more confidence. Nor is it any greater effort; they have to come out anyway.)

So, stage by stage, I replaced each transistor, making appropriate voltage checks after each change. Alas, no joy. After I replaced all the transistors the symptoms were exactly the same as before. All that I had established was that it was not a faulty transistor.

But if not a transistor, then what was it? What kind of a fault could have been caused by the speaker short, other than

a damaged transistor?

At this point I decided to put the thing to one side. For one thing, I felt that a break from it might allow more rational thinking when I came back to it. For another, there were more urgent jobs which I just had to finish. Nevertheless, every time I looked over to the corner of the bench where the monster sat, I attempted to rationalise the problem.

By the time I came back to the job I decided that I would do what, I suppose, I should have done earlier; make a very careful voltage check of every stage and at least try to rationalise each reading. Some voltages were shown on the circuit, while the very comprehensive setting up and trouble shooting instructions in the January issue provided additional voltage references.

The first few readings provided little in the way of clues, but I became suspicious when I checked T8, and particularly the collector voltage. This was

correctly, but I realised that I had found something when I checked the 150 ohm. It was reading over 600 ohms and a closer look showed why — it was, in fact, a 680 ohm resistor.

about 4V but, having skimmed through the trouble shooting instructions, I

recalled a reference to T8 and a quite different voltage. Sure enough, when I

found the reference, it suggested

-22V; a much more reasonable figure

associated with this transistor; the 4.7k

collector resistor, the 10k resistor from base to the 0V rail, the 150 ohm resistor

in the emitter circuit, and the two diodes D1 and D2 from base to the

-35V rail. I had already checked the

diodes, so that really left the three

The 4.7k and the 10k measured out

There were only a few components

when one studies the circuit.

resistors as the main suspects.

I put down the test prods and, I'm afraid, said some very naughty words; words which reflected on the immediate ancestory of whoever had

assembled the amplifier.

When I felt a little calmer I realised how easy it would be to make such a mistake. There are two 680 ohm resistors in the nearby circuitry and, in fact, their position on the printed board is quite close to that of the 150 ohm resistor. Fair enough, but what about the bloke who tested the amplifier? Or was it ever tested?

We shall probably never know, but I mentally transferred my wrath to whoever it was who should have tested

it, but didn't!

Mind you, I'd been well and truly caught. The customer's red herring about the shorted speaker connections had sent me off on a wild goose chase. (Sorry about that mixture!) But, seriously, the story is a classic example of how the customer's story can be a hindrance rather than a help.

Fortunately, such situations are rare and it would be unwise to offer them as a reason for disregarding the customer's story, or failing to encourage it if it is not offered. It is something we just have to accept on the rare occasions that it happens.

### KNOW Where you are going?

Choose a carrer in the field of Electronics — the Nation's most progressive and fastest expanding industry

#### BROADCASTING COMMUNICATIONS — marine

Full time classes commence on 5/2/79.

Home Study Courses may be commenced at any time

SEND FOR PROSPECTUS or PHONE 560 8644 There is no obligation

ADDRESS .....

MARCONI SCHOOL OF WIRELESS Box 218, P.O. Leichhardt 2040 A service of

Amalgamated Wireless (Australasia) Ltd

## MEGASPARK

"The easiest"

#### ELECTRONIC IGNITION

- Improves fuel economy and performance by maintaining optimum ignition timing.
- Eliminates ignition misfire due to contact bounce.
- Protects the points and eliminates expensive adjustment costs.
- Easier starting and smoother running.
- Inductive principle ensures optimum spark duration.
- Easily installed by the competent handyman. No Stroboscope or special tools required.
- Rev counter will not be effected.
- 12 mths replacement guarantee.

\$32.50

each plus postage.

Early dispatch from

#### **ENSON EQUIPMENT**

PO Box 355, Narrabeen 2101 or phone 913 8386

# Add a low cost printer to your 2650

Here are the details of how to interface the Matsushita model EUY-10E023LE printer and its companion driver board, model EUY-PUD024C to your microprocessor. Details of a suitable power supply are also provided, as well as driver routines to suit the 2650 microprocessor.

by DAVID EDWARDS

Obtaining hard copy has always been one of the major bugbears of the home computerist. Secondhand ASCII teleprinters are available, but can cost several times the price of the rest of the system put together. (If you can afford a new teleprinter, you needn't read any further!)

Baudot teleprinters are available at quite reasonable cost, but require a code conversion from ASCII to Baudot, which as well as being messy, tends to raise the overall package price quite markedly. So when Philips (the local

agents for Matsushita printers) supplied us with details of the new printer, we at once decided that this would be a boon for the home hobbyist.

Approximate price of the printer unit and the interface board is \$200.00 plus tax if applicable. Power supply requirements are quite modest, and could possibly be met from existing supplies, or from junk box (or redundant, if you want to be nice!) components.


The units are supplied with comprehensive instruction manuals, giving


full details on both mechanical and electrical interfaces, as well as flowcharts and programs suitable for use with the Motorola 6800 "D2" evaluation kit.


Overall size of the printing unit is 110 x 90.5 x 39.5mm. Printing is on electrosensitive paper 60mm wide, utilising a travelling head containing seven electrodes. The head scans from left to right, and can print 32 characters on each line. Approximately two lines can be printed each second.

Characters are formed from a 7 x 5

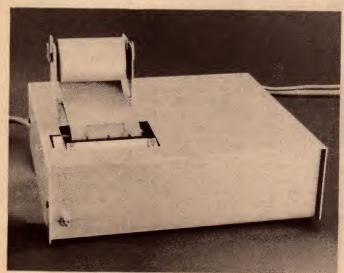These two photographs show the printer module and interface board assembled in a small aluminium case, along with the power supply components. Note the paper roll holder mounted on the lid of the case.



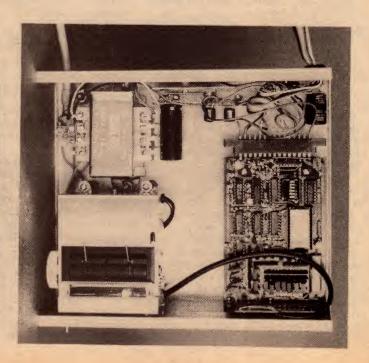

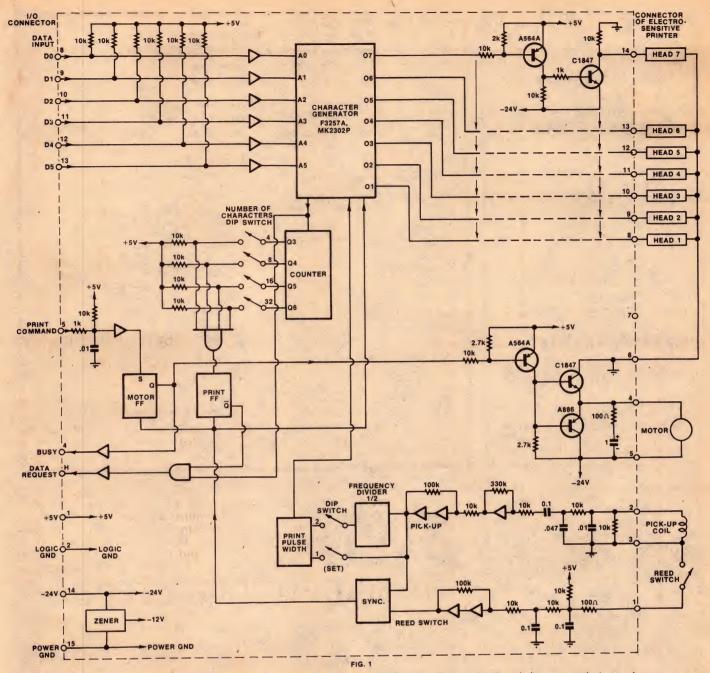

Here is the schematic diagram of the interface board, which is used to generate the head drive signals from the computer outputs.

dot matrix, and are approximately 2.4mm high. Lines are spaced 2mm apart. The dots are formed by passing current pulses from the appropriate electrodes to the aluminised paper. This burns off the top layer of the paper, leaving a black dot.

Head movement is achieved with the aid of a 24V DC motor. A cam and switch synchronised to the head provide pulses to strobe the characters in time, thus ensuring even character spacing, even if the motor speed varies.

The motor unit does not contain any electronics, and is provided with two cables to connect to the interface board. This board (Fig. 1) contains an I/O circuit, an input data processing circuit, a timing circuit and a character

generator ROM. Data is input in the form of a six bit parallel ASCII code, and converted to the appropriate dot format by the character generator.

A DIP switch is provided to select either 16 or 32 characters per line; normally this would be set at the 32 character position. Three control signal lines are provided, but only two are necessary for a simple interface.

The PRINT signal is used to initiate printing. When this signal is received from the CPU on the interface board, the printing motor is started, and the head starts to scan across the paper. Once the first character has been printed, the DATA REQ signal is pulsed, to signify to the CPU that a second character is required. This sequence is

repeated until the complete line has been printed.

The third control signal is BUSY, which is used to tell the CPU that the printer is occupied in printing a line. Provided the CPU waits for an adequate time after the last character has been sent to the printer, it is not necessary to use this signal.

Two power supplies are required for the interface board: +5V at 50mA and -24V at 200mA. The printer derives its supply voltages from the interface board. Fig. 2 shows a simple supply which is suitable, using two three-terminal regulators and a readily available transformer.

The printer is connected to the CPU via an 8-bit I/O port. For 2650-based

#### Can you afford not to know about microprocessors?



This book will help you find out what the revolution is all about....

#### **GETTING INTO MICROPROCESSORS**

Available from "Electronics Australia", 57 Regent St, Sydney. PRICE \$4.50 OR by mail order from "Electronics Australia", PO Box 163, Beaconsfield 2014. PRICE \$5.10.

#### **ELECTROCRAFT** PTY. LTD.

**68 WHITING STREET, ARTARMON 2064** TELEPHONE 438 4308, 438 3266

We have the largest range of TV antenna accessories in Sydney. (Check our prices)

#### TRADE AND WHOLESALE SUPPLIED

Television, complete range of Aerials — Fly Leads Splitters — Baluns — Plugs etc.

Masting, 8' to 15'. Telescopic masts (not self supporting 20' \$23.55, 30' \$37.60, 40' \$51.30, 50' \$66.00.

Field Strength Meter for TV TES Mc661 40-480Mhz continuous in 6 ranges, battery operated in Leather case, \$257.60.

Caravans Antennas . . . . . . . . . . . . . . . . . . 14.73

#### CB EQUIPMENT

GB TM/13 UHF CB Beam 15dB forward gain (Ref Dipole) 465 to 477Mhz \$35.95. GB ¼ wave spiral tuned base station aerial, good skip work. SWR 1.1.1. Rotators CDE ARXL Fully approved \$124.14.
CB27 Belling Lee Helical whip 5' complete with base and 3.6M of cable, \$18.

#### **SWR & POWER METER**

Model ME-11X. Specifications: maximum handling power 100W - SWR indication 1:1 to 3:1 - frequency range 3.5 to 150MHz. \$16.20.

FM ANTENNAS Channelmaster 7.el H. Gain .................................. 19.68 Hills FM1 Local Hills FM1 Local
Hills 353 3.el Met:
Matchmaster FMG/2 Semi fringe 14.72 Matchmaster FMG/6 Outer fringe . . . . . . TV ANTENNAS Hills outer fringe CA.16 phase array ..... Hills 215 (Australia's best selling high gain Hills 215 (Australia's best selling mgir year. 8 el antenna at a new low price) . . . . 25.29 Hills EFC.3 (The best of the colour 75 ohm antennas very high gain. good anti-62.41 Channelmaster 3111A 300-75 ohm (Best metropolitan Anti-ghosting antenna) Channelmaster 3110 300-75 ohm local antighosting 27.96
Belling Lee plugs 0.80 R.F. Amplifiers, Masthead & Distribution for FM & TV from 16dB Ecraft ..... 25dB Ecraft ..... 61.00

Please enclose postage with all orders

WE ARE THE EXPERTS - 30 YEARS IN THE ANTENNA BUSINESS

OPEN SATURDAY MORNINGS 8.30-12

#### ASP?

ASP is the superb ASP SYSTEM ONE Computer for business, scientific or educational use. Problem solving at a very reasonable price.

ASP is a professional quality conversion of the IBM SELECTRIC typewriter to a word processing quality printer with either \$100 or R\$232 interfaces.

ASP is the magnificent MALIBU DESIGN GROUP printer. 160 cps bi-directional and graphics capability with the looks of a high quality piece of furniture.

ASP is the new ASP Computer Portrait System - a profitable small business that can be transported in your vehicle.

DEAR ALI please rush me brochures on: MALIBU

EVERYTHING! ASP SYSTEM ONE SELECTRICS COMPUTER PORTRAITS DEALERSHIPS!

SELECTRIC is a Trademark of IBM

NOTE OUR NEW ADDRESS:

799 DANDENONG ROAD EAST MALVERN 3145

& OUR NEW TELEPHONE NUMBERS:

211 8855 211 8344



#### Adding a printer to your 2650 system

systems, this would normally be the D port. The connections we used, based on the I/O port diagram published in the November 1978 article on expanding the 2650 Minicomputer, are shown in Fig. 3.

Connections to other processor systems will be broadly similar in concept. The BUSY signal, if required, is available at pin 4 of the edge connec-

tor.

Needless to say, one needs suitable driver routines in the computer so that it can communicate properly with the printer via the interface. For the benefit of those with 2650 systems I have written some utility routines to do this. One is a basic printer driver subroutine, while the other two are a hex memory dump routine and a message printing routine. Both of these call the basic subroutine for the actual printing.

Fig. 4 shows a flow chart of the main subroutine, PRINT. This treats a portion of memory as a 32 byte buffer, and transfers the ASCII characters stored in it to the printer with the appropriate timing. It will detect a null character in the buffer, and then fill the remainder of the line with spaces. This gives the effect of a carriage return.

To print a number of lines, it is necessary to call the routine the appropriate number of times, changing the buffer contents between calls. To achieve the effect of a blank line, place a null character (X'00) in the first buffer

location.

Fig. 5 is a disassembler listing of the PRINT subroutine in 2650 machine code. It occupies locations X'1400 to X'143E inclusive, and requires a 32 byte area of RAM to be set aside as the buffer. At present this occupies

	1409	77	02			
	4CB	3F	00	A4	BSTA, UN	
	14CE	07	00		LODI, R3	
	14D0	OC	84	0.0	LODA, RO	
	14D3	CF	34	3 L	STRA, R3	
-	14D6	18	14		BCIR, EQ	14EC
1	14D8	09	F 7		LODR, R1	14D1
	14DA	OE	04	O.E.	LODA, R2	
	14DD	DA	02		BIRR, R2	14E1
1	4DF	D9	00		BIHR, R1	14E1
1	14E1	38	E9		BS1R, UN	14CC
	14E3	£7	20		CUMI.H3	
	4E5	98	69		BCFR, EG	14D0
1	4E.7	3F	14	00	BSTA, UN	
1	4EA	18	62		BC1R, UN	14CE
1	4EC	3B	FA		BS1R.UN	14E8
	4EE	17				-
						FIG. 7

Shown above is a dissassembler listing of the message printing routine, while below is a flow chart of the print routine, which is used to control the printer.

145F	51			A 100	
1460	51				
1461	51				
1462	51				
1463	45	OF		ANDI, H1	
1465	OD	62	59	LODA, KI	
1468	CF	34	3Ł	STRA.R3	
	17	34	SE	SINATIO	
		00			
146C	77	02	2.75		
146E	3F	05	DB	BSTA, UN	
1471	3F	00	P4	bSTA, UN	
1474	38	19		BSTR, UN	146F
1476	CD	04	OF	STHANHI	
1479	CE	04	10	STRA, R2	
147C	07	00		LODI,R3	
147E	09	94		LUDR, R1	1514
1480	3B	5D		BSTR, UN	145F
1482	09	90		LUDH, R1	1514
1484	3B	SD		HSTH, UN	1463
1486	OD	04	OŁ	LODA, HI	
			02	BSTR, UN	145F
1489	38	54			1487
148B	09	FA		LOUR, R1	
148D	3B	54		BSTR, UN	1463
148F	04	50		LODI, RO	1
1491	3B	55		BSTR. UN	1468
1493	OD	84	00	LODA, R1	
1496	3B	47		BSTR, UN	145F
1498	OD	84	OD	LUDA, R1	
1498	38	46		BS1R, UN	1463
149D	08	1.8		LODE, RO	1487
149F	E8	D9		CUME, RO	147A
14A1	98	OE	Ā	BCFR, EQ	1481
14A3	08	F4		LUER, RO	1499
14A5	ES	DO		COMR. RO	1477
14A7	98	08		BCFR, EG	1481
		Un		LORZ, HO	9
14A9	50	06		BSTR, UN	1542
14AA	38	96	00	BSTA, UN	
14AC	3F	14	00		14D3
14AF	9B	55		BCFR, UN	
1481	09	E6		LODR, R1	1499
14B3	40	DS		LODR, R2	1487
1485	DA	05		BIRK, R2	1469
1487	109	00		BIRH, R1	1489
14B9	3F	00	P4	HS1A, UN	17
14BC	46	07		ANDI.K2	
14BE	98	41		BCFR, LQ	148F
1400	20			LUKZ, RO	
14C1	3F	14	68	BSTA, UN	
1404	3B	£7	30	BSTR. UN	14AD
1404	1F	14	7C	BCIA, UN	
1400	1.	1-4	10	23	

1400	77	18	87	99	F3	94	28	F8	
1408	7E	97	48	F3	87	00	96	88	
1410	82	98	18	<b>⊕</b> F	34	3E	18	19	
1418	64	49	FØ	94	07	Ce	F8	70	
1420	E7	28	18	11	70	F4	88	98	
1428	7B	18	65	08	88	84	20	18	
1430	67	96	FF	18	78	29	95	28	
1438	F8	7E	F9	70	75	10	17	31	
1448	34	34	30	20	33	34	20	33	
1448	34	20	33	33	20	33	33	20	
1450	32	30	20	33	33	20	33	33	
1458	20	33	33	99	47	4F	4F	51	
1460	51	51	51	45	ØF	<b>6</b> D	62	59	
1468	CF	34	3E	17	77	02	3F	92	
1470	DB	3F	88	<b>A4</b>	38	F9	CD	94	
1478	0F	CE	94	16	97	98	89	94	
1489	38	50	89	90	38	50	90	94	
1488	ØE,	38	54	09	FA	3B	54	64	
1490	20	38	55	<b>9D</b>	84	00	38	47	
1498	90	84	90	3B	46	88	E8	E8	
1488	09	98	ØE	98	F4	E8	DØ	98	
1488	96	20	38	96	3F	14	99	9B	
1480	22	99	E6	8A	02	DA	92	09	
14B8	99	3F	99	A4	46	97	-98	4F	
1408	20	3F	14	68	3B	E7	1F	14	
1408	70	77	92	3F	99	94	97	99	
1400	00	84	<b>0</b> D	CF	34	3E	18	14	
1408	89	F7	ØE	94	8E	DA	92	09	
14E0	00	38	E9	E7	20	98	69	3F	
14E8	14	99	18	62	38	FA	17		

FIG. 8

To the left is a listing of the hex listing routine. This was used to produce the listing above of all the programs presented in this article, on the new printer. It is reproduced actual size.

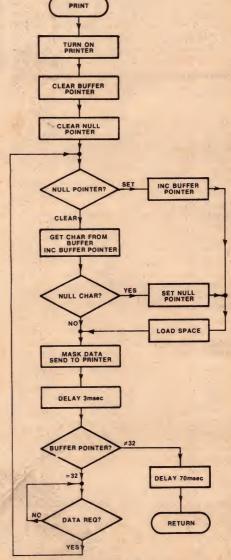


FIG. 4 FLOW CHART FOR PRINT ROUTINE

#### Adding a printer to your 2650 system

locations X'143F to X'145E inclusive.

The PRINT subroutine is relocatable. To change the starting address of the buffer, which must be in the same page as the subroutine, put the address of the byte before the desired starting address into locations X'1414 and X'1415. Note that bits 6 and 7 of location X'1414 must remain as zeroes, while bit 5 must remain a 1.

Fig. 6 is a disassembler listing of the listing program, which will print out a listing of a specified area of memory. As the print format is only 32 characters wide, it prints only the line starting address and eight bytes per line. To call the program, type G 146C XXXX YYYY cr, where XXXX and YYYY are the start and end respectively of the required memory block.

The program occupies locations X'145F to X'14C8 inclusive. It uses Pipbug routines GNUM, STRT, ANSI and PIPBUG. It contains absolute addresses, but can be moved fairly easily.


but can be moved fairly easily.

Locations X'1469 and X'146A must point to the byte before the start of the PRINT subroutine's buffer memory.

Bytes X'14AD and X'14AE must point to the starting address of the PRINT subroutine. Bytes X'14C2 and X'14C3 must point to the new location of


1400	77	10			
1402	07			LODI,R3	
1404	1				
1405				LODI, RO	
1407	F8	7E		BDRR.RO	1407
1409	07	40		LODI.R3	
140B	F3				
140C	07	00		LODI, R3	
140E	-	00		LODI, R2	
1410	-			LODZ, R2	
1411		18		BCFk, LQ	142B
1413	OF	34	3E	LODA, R3	,
	18	19	-	BCIR, EG	1431
1418	64	40		IORI, RO	
141A	FO			10	
141B	04	C7		LODI, RO	
141D	CO	•		STRZ.RO	
141E	FB	7D		BDRR, RO	141D
1420	E7			COMI.R3	
1		11		BCTR. EQ	1435
1424	70				
1425		80			
1427	98	7B		BCFR, EG	1424
1429	18	65		BCTR, UN	1410
142B	DB	00		BIRR, R3	1420
142D	04	20		LODI, RO	
142F	18	67		HCIR, UN	1418
1431	06	FF		LODI, k2	
1433	18	78		BCTR, UN	142D
1435	20			EORZ, RO	
1436	05	20		LODI,R1	
1438	F8	7E		BDRH. HO	1438
143A	F9	7C		BURR, H1	1438
143C	75	10			
143E	17				FIG. 5

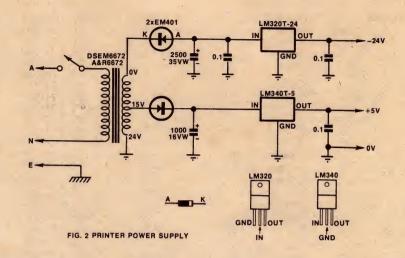The hex listing reproduced above is for the routine used to control the printer. It is written as a subroutine.



The connection diagram for the 2650 Mini Computer is shown below. We used the "D" output port.

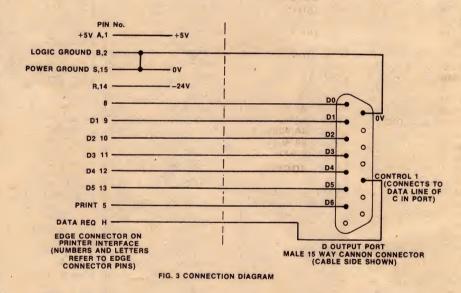Shown above is the circuit diagram of the suggested power supply. It uses a readily available transformer.



current location X'1468, and bytes X'14C7 and X'14C8 must point to the new location of current location X'147C.

Fig. 7 is a disassembler listing of a message printing subroutine. This expects R1 and R2 to contain the starting address of an ASCII message. This message is printed when the subroutine is called. The end of the message is signified by a null character. Messages can be stored anywhere in available memory, provided they are in the same page as the message program.

The message subroutine is relocatable, and uses the Pipbug routine STRT. Locations X'14D4 and X'14D5 must point to the byte before the first byte of the PRINT buffer, and locations X'14E8 and X'14E9 must point to the PRINT routine itself.

Fig. 8 is a hex listing of all three routines, produced by the hex listing

program on the new printer itself. It is reproduced actual size, so you can see directly the size and quality of the printing.

Further details on the model EUY-10E023LE printer and companion interface board (model EUY-PUD024C) can be obtained from the local agents, ELCOMA, of 67 Mars Road, Lane Cove, NSW 2066!

#### THE "ELECTRONICS AUSTRALIA"

#### LOG BOOK

FOR: RADIO AMATEURS.
DX LISTENERS,
CB OPERATORS. \$2.99

From "ELECTRONICS Australia", 57-59 Regent St, Sydney OR by mail order from PO Box 163, Beaconsfield 2014. Price includes postage.

## ROD IRVING

LINEARS				
	1N4002 7	7430 30	74LS28 40	4002 25
301 40	1N4003 8	7432 40	74LS30 30	4006 1.40
307 65	1N4004 9	7437 50	74LS32 30	4007 25
308 1.25	100 for 7.00 °	7438 50	74LS37 45	4008 1.25
309K 1.90	1N5625 50	7440 30	74LS38 45	4010 1.25
311 80 /		7441	74LS40 30	4011 25
317K 2.90	RESISTORS	7442 70	74LS42 1.10	4012 25
	1/2 Watt I.R.H. Metal			
3183.25		7447 95	74LS471.40	4013 55
324 1.25	Glaze 1 ohm to 1M (E24	7448	74LS48 1.50	4014 1.30
325 4.60	Values), 1-99 3	7450 35	74LS49 1.80	4015 1.20
339 85	100-999 2.5	7451 35	74LS51 45	4016 50
	(Mixed)			
348	(11111100)	7453 35	74LS54 45	40171.30
3492.25	TRANSISTORS	7454 30	74LS55 45	40181.40
356		7460 35	74LS73 90	4019
377 2.75	BC547/8/9 15	7470 65	74LS74 50	4020
	BC557/8/9 20	7472 45	74LS75 70	4021
379S 6.95	BD139 55			
380 14 Pin 1.30	BD140 55	7473 60	74LS76 95	4022 1.60
381 1.95	2N3055 85	7474 65	74LS78 50	4023 25
382 1.95		7475 65	74LS83 1.50	4024 90
3871.90	MJ2955 95	7476 45	74LS85 1.50	4025 40
	BC337 25	7480 1.25		
386 1.90	BC338 25		74LS86 50	40262.10
555	BF115 85	7483 1.25	74LS901.10	4027 80
556 85	BF180 75	7485 1.45	74LS921.20	4028 1.25
565		7486 65	74LS931.10	4029 1.85
566 2.40	PN3643 25	7489 1.90	74LS95 1.50	4030 40
	PN3645 25	7490 50		
567	Open Street Control		74LS1071.20	40401.30
709 70	BRIDGES	74911.00	74LS109 50	40411.25
723 (VR) 50	MDA3501 35A	7492 65	74LS112 1.20	4042 1.25
741	100V 4.10	7493 65	74LS113 55	4043 1.59
747 90	MDA3502 35A	7494 1.10	74LS114 55	4044 1.50
		7495 95	74LS122 2.00	4046 1.80
3900 85	200V 4.20		74LS123 1.90	
3909	MDA3504 35A	74100 24.5		4049 60
CA3028 2.90	400V4.50	74107 65	74LS125 1.90	4050 60
CA3046 2.10	W04 1.5A 400V 80	74121 50	74LS126 1.50	40511.20
CA3130 1.95		74123 90	74LS132 1.60	4052 1.20
CA3140 1.95	SCR	74132 1.25	74LS126 79	40531.20
RL4136 2.90	C103YY .8A 60V 80	74150 1.60	74LS138 1.20	4060 2.60
	C106A1 4A-100V 95	741511.10	74LS139 1.90	4066 1.00
REGULATORS				
7805 1.00	C106D1 4A 400V .1.30	741531.10	74LS151 1.20	4068 40
7806 1.20	C122D1 8A 400V .2.50	74154 1.70	74LS153 1.90	4069 35
7808 1.20	C122E 8A 500V 2.60	74157 1.10	74LS1541.60	4070 40
		74400 455		
7010 100	LO COOKETC	74160 1.55	74LS15/ 1.00	4071 40
7812 1.00	I.C. SOCKETS	74160 1.55	74LS157 1.00 74LS158 1.90	
7812 1.00 7815 1.20	8 PIN 25	741611.75	74LS158 1.90	4072 40
7812	8 PIN 25	74161	74LS158 1.90 74LS160 2.20	4072 40 4073 40
7812 1.00 7815 1.20	8 PIN	74161 1.75 74164 1.55 74165 1.55	74LS158	4072
7812	8 PIN	74161	74LS158       1.90         74LS160       2.20         74LS161       2.20         74LS162       2.30	4072
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50	74161	74LS158       1.90         74LS160       2.20         74LS161       2.20         74LS162       2.30         74LS163       1.20	4072       40         4073       40         4074       40         4076       1.85         4077       40
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50 7906 1.50	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60	74161	74LS158       1.90         74LS160       2.20         74LS161       2.20         74LS162       2.30	4072
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50 7906 1.50 7908 1.50	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75	74161 1.75 74164 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35	74LS158     1.90       74LS160     2.20       74LS161     2.20       74LS162     2.30       74LS163     1.20       74LS164     1.30	4072     40       4073     40       4074     40       4076     1.85       4077     40       4078     40
7812     1.00       7815     1.20       7818     1.20       7824     1.20       7905     1.50       7906     1.50       7908     1.50       7924     1.50	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60	74161 1.75 74164 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40	74LS158     1.90       74LS160     2.20       74LS161     2.20       74LS162     2.30       74LS163     1.20       74LS164     1.30       74LS168     3.30	4072     40       4073     40       4074     40       4076     1.85       4077     40       4078     40       4081     40
7812     1.00       7815     1.20       7818     1.20       7824     1.20       7905     1.50       7906     1.50       7908     1.50       7924     1.50       7912     1.50	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80	74161 1.75 74164 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40	74LS158     1.90       74LS160     2.20       74LS161     2.20       74LS162     2.30       74LS163     1.20       74LS164     1.30       74LS168     3.30       74LS169     3.50	4072     40       4073     40       4074     40       4076     1.85       4077     40       4078     40       4081     40       4082     40
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50 7906 1.50 7908 1.50 7924 1.50 7915 1.50	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90	74161 1.75 74164 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50	74LS158     1.90       74LS160     2.20       74LS161     2.20       74LS162     2.30       74LS163     1.20       74LS164     1.30       74LS168     3.30       74LS169     3.50       74LS170     3.50	4072     40       4073     40       4074     40       4076     1.85       4077     40       4078     40       4081     40       4082     40       4510     1.40
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50 7906 1.50 7908 1.50 7924 1.50 7915 1.50	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90 40 PIN 1.00	74161 1.75 74164 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50 74221 1.50	74LS158 1.90 74LS160 2.20 74LS161 2.20 74LS162 2.30 74LS163 1.20 74LS164 1.30 74LS168 3.30 74LS169 3.50 74LS170 3.50 74LS173 2.10	4072     40       4073     40       4074     40       4076     1.85       4077     40       4078     40       4081     40       4082     40       4510     1.40       4511     1.40
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50 7906 1.50 7908 1.50 7924 1.50 7911 1.50 7915 1.50 78105 40	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90 40 PIN 1.00	74161 1.75 74164 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50	74LS158     1.90       74LS160     2.20       74LS161     2.20       74LS162     2.30       74LS163     1.20       74LS164     1.30       74LS168     3.30       74LS169     3.50       74LS170     3.50	4072     40       4073     40       4074     40       4076     1.85       4077     40       4078     40       4081     40       4082     40       4510     1.40       4511     1.40       4518     1.50
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50 7906 1.50 7908 1.50 7912 1.50 7915 1.50 7915 1.50 78105 40 78L12 40	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90 40 PIN 1.00	74161 1.75 74164 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50 74221 1.50	74LS158 1.90 74LS160 2.20 74LS161 2.20 74LS162 2.30 74LS163 1.20 74LS164 1.30 74LS168 3.30 74LS169 3.50 74LS170 3.50 74LS173 2.10	4072     40       4073     40       4074     40       4076     1.85       4077     40       4078     40       4081     40       4082     40       4510     1.40       4511     1.40
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50 7906 1.50 7908 1.50 7912 1.50 7912 1.50 7915 1.50 7915 1.50 7915 4.0 78105 40 78105 40 78112 40 78HGKC 8.50	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90 40 PIN 1.00  TTL 7400 25	74161 1.75 74164 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50 74221 1.50 74251 1.50 74367 1.20	74LS158         1.90           74LS160         2.20           74LS161         2.20           74LS162         2.30           74LS163         1.20           74LS164         1.30           74LS168         3.30           74LS169         3.50           74LS170         3.50           74LS173         2.10           74LS174         1.00           74LS175         1.00	4072     40       4073     40       4074     40       4076     1.85       4077     40       4081     40       4082     40       4510     1.40       4511     1.40       4518     1.50       4519     95
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50 7906 1.50 7908 1.50 7912 1.50 7912 1.50 7915 1.50 78105 40 781405 40 78HGKC 8.50 78H05 7.90	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90 40 PIN 1.00	74161 1.75 74164 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50 74221 1.50 74251 1.50 74367 1.20 74368 1.20	74LS158         1.90           74LS160         2.20           74LS161         2.20           74LS162         2.30           74LS163         1.20           74LS164         1.30           74LS168         3.30           74LS169         3.50           74LS170         3.50           74LS173         2.10           74LS174         1.00           74LS175         1.00           74LS190         2.80	4072     40       4073     40       4074     40       4076     1.85       4077     40       4078     40       4081     40       4082     40       4510     1.40       4511     1.40       4518     1.50       4519     95       4520     1.45
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50 7906 1.50 7908 1.50 7912 1.50 7915 1.50 7915 4.50 78105 40 78105 5 78105 78105 790 78105 7.90 78105 7.90	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90 40 PIN 1.00  TTL 7400 25	74161 1.75 74164 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50 74221 1.50 74251 1.50 74367 1.20	74LS158         1.90           74LS160         2.20           74LS161         2.20           74LS162         2.30           74LS163         1.20           74LS164         1.30           74LS168         3.30           74LS169         3.50           74LS170         3.50           74LS173         2.10           74LS174         1.00           74LS175         1.00           74LS190         2.80           74LS191         1.20	4072     40       4073     40       4074     40       4076     1.85       4077     40       4078     40       4081     40       4082     40       4510     1.40       4511     1.50       4519     95       4520     1.45       4528     1.20
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50 7906 1.50 7908 1.50 7912 1.50 7915 1.50 7915 4.50 78105 40 78105 5 78105 78105 790 78105 7.90 78105 7.90	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90 40 PIN 1.00  TTL  7400 25 7401 25 7402 25	74161 1.75 74164 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50 74221 1.50 74251 1.50 74367 1.20 74368 1.20	74LS158     1.90       74LS160     2.20       74LS161     2.20       74LS162     2.30       74LS163     1.20       74LS164     1.30       74LS169     3.50       74LS170     3.50       74LS173     2.10       74LS174     1.00       74LS175     1.00       74LS190     2.80       74LS191     1.20       74LS192     1.20	4072     40       4073     40       4074     40       4076     1.85       4077     40       4081     40       4082     40       4510     1.40       4511     1.40       4518     1.50       4519     95       4520     1.45       4528     1.20       14533     7.30
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50 7906 1.50 7908 1.50 7912 1.50 7915 1.50 78105 40 78112 40 78HGKC 8.50 78H05 7.90 78H12 7.90 723 50	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90 40 PIN 1.00  TTL  7400 25 7401 25 7402 25 7403 25	74161 1.75 74164 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50 74221 1.50 74221 1.50 74367 1.20 74368 1.20 74LS	74LS158 1.90 74LS160 2.20 74LS161 2.20 74LS162 2.30 74LS163 1.20 74LS164 1.30 74LS168 3.30 74LS169 3.50 74LS170 3.50 74LS173 2.10 74LS174 1.00 74LS175 1.00 74LS190 2.80 74LS191 1.20 74LS192 1.20 74LS193 1.20	4072     40       4073     40       4074     40       4076     1.85       4077     40       4081     40       4082     40       4510     1.40       4511     1.40       4518     1.50       4519     95       4520     1.45       4528     1.20       14584     1.25
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50 7906 1.50 7908 1.50 7912 1.50 7912 1.50 7915 1.50 78105 40 78L12 40 78L12 40 78HGKC 8.50 78H05 7.90 78H12 7.90 78H12 7.90 783 50 309K 1.90	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90 40 PIN 1.00  TTL  7400 25 7401 25 7402 25 7403 25 7404 35	74161 1.75 74164 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50 74221 1.50 74251 1.50 74367 1.20 74368 1.20 74LS 74LS00 25 74LS01 30	74LS158     1.90       74LS160     2.20       74LS161     2.20       74LS162     2.30       74LS163     1.20       74LS164     1.30       74LS169     3.50       74LS170     3.50       74LS173     2.10       74LS174     1.00       74LS175     1.00       74LS190     2.80       74LS191     1.20       74LS192     1.20	4072     40       4073     40       4074     40       4076     1.85       4077     40       4081     40       4082     40       4510     1.40       4511     1.40       4518     1.50       4519     95       4520     1.45       4528     1.20       14584     1.25       74000     40
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50 7906 1.50 7908 1.50 7912 1.50 7912 1.50 7915 1.50 78105 40 78L12 40 78L12 40 78HGKC 8.50 78H05 7.90 78H12 7.90 78H12 7.90 723 50 309K 1.90 317K 2.90	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90 40 PIN 1.00  TTL  7400 25 7401 25 7402 25 7403 25 7404 35 7405 35	74161 1.75 74164 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50 74221 1.50 74221 1.50 74367 1.20 74368 1.20 74LS 74LS00 25 74LS01 30 74LS02 25	74LS158         1.90           74LS160         2.20           74LS161         2.20           74LS162         2.30           74LS163         1.20           74LS164         1.30           74LS168         3.30           74LS169         3.50           74LS170         3.50           74LS173         2.10           74LS174         1.00           74LS190         2.80           74LS191         1.20           74LS192         1.20           74LS193         1.20           74LS194         1.20           74LS194         1.20	4072     40       4073     40       4074     40       4076     1.85       4077     40       4081     40       4082     40       4510     1.40       4511     1.40       4518     1.50       4519     95       4520     1.45       4528     1.20       14584     1.25       74000     40
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50 7906 1.50 7908 1.50 7912 1.50 7912 1.50 7915 1.50 78105 40 78L12 40 78L12 40 78HGKC 8.50 78H05 7.90 78H12 7.90 78H12 7.90 783 50 309K 1.90	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90 40 PIN 1.00  TTL  7400 25 7401 25 7402 25 7403 25 7404 35 7405 35 7406 50	74161 1.75 74164 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50 74221 1.50 74251 1.50 74367 1.20 74368 1.20 741S0 25 74LS00 25 74LS01 30 74LS01 30 74LS02 25 74LS03 30	74LS158         1.90           74LS160         2.20           74LS161         2.20           74LS162         2.30           74LS163         1.20           74LS164         1.30           74LS168         3.30           74LS169         3.50           74LS170         3.50           74LS173         2.10           74LS174         1.00           74LS175         1.00           74LS190         2.80           74LS191         1.20           74LS192         1.20           74LS193         1.20           74LS194         1.20           74LS195         1.20	4072     40       4073     40       4074     40       4076     1.85       4077     40       4081     40       4082     40       4510     1.40       4511     1.40       4518     1.50       4519     95       4520     1.45       4528     1.20       14533     7.30       14584     1.25       74C00     40       74C02     40
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50 7906 1.50 7908 1.50 7912 1.50 7912 1.50 7915 1.50 78105 40 78L12 40 78HGKC 8.50 78H05 7.90 78H05 7.90 78H12 7.90 78H12 7.90 70 309K 1.90 317K 2.90	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90 40 PIN 1.00  TTL  7400 25 7401 25 7402 25 7403 25 7404 35 7405 35	74161 1.75 74164 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50 74221 1.50 74221 1.50 74367 1.20 74368 1.20 74LS 74LS00 25 74LS01 30 74LS02 25	74LS158         1.90           74LS160         2.20           74LS161         2.20           74LS162         2.30           74LS163         1.20           74LS164         1.30           74LS168         3.30           74LS170         3.50           74LS171         2.10           74LS173         2.10           74LS174         1.00           74LS175         1.00           74LS190         2.80           74LS191         1.20           74LS192         1.20           74LS193         1.20           74LS194         1.20           74LS195         1.20           74LS196         1.20	4072     40       4073     40       4074     40       4076     1.85       4077     40       4081     40       4082     40       4510     1.40       4511     1.40       4518     1.50       4519     95       4520     1.45       4528     1.20       14584     1.25       7400     40       7402     40       7404     40
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50 7906 1.50 7908 1.50 7912 1.50 7912 1.50 7915 1.50 7915 4.05 78105 40 78L12 40 78L12 40 78HGKC 8.50 78H05 7.90 78H12 7.90 723 50 309K 1.90 317K 2.90  OPTO FND357 C.C 1.30	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90 40 PIN 1.00  TTL  7400 25 7401 25 7402 25 7403 25 7404 35 7405 35 7406 50	74161 1.75 74164 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50 74221 1.50 74251 1.50 74367 1.20 74368 1.20 741S0 25 74LS00 25 74LS01 30 74LS01 30 74LS02 25 74LS03 30	74LS158         1.90           74LS160         2.20           74LS161         2.20           74LS162         2.30           74LS163         1.20           74LS164         1.30           74LS169         3.50           74LS170         3.50           74LS173         2.10           74LS174         1.00           74LS175         1.00           74LS190         2.80           74LS191         1.20           74LS193         1.20           74LS194         1.20           74LS195         1.20           74LS196         1.20           74LS197         1.90	4072     40       4073     40       4074     40       4076     1.85       4077     40       4078     40       4081     40       4082     40       4510     1.40       4511     1.50       4519     95       4520     1.45       4528     1.20       14553     7.30       14584     1.25       74000     40       74C02     40       74C04     40       74C08     40
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50 7906 1.50 7908 1.50 7912 1.50 7912 1.50 78105 40 78112 40 78HGKC 8.50 78H05 7.90 78H12 7.90 78H12 7.90 723 50 309K 1.90 317K 2.90  OPTO  FND357 C.C. 1.30 FND500 C.C. 1.25	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90 40 PIN 1.00  TTL  7400 25 7401 25 7402 25 7403 25 7404 35 7405 35 7406 50 7407 50	74161 1.75 74164 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50 74221 1.50 74251 1.50 74367 1.20 74368 1.20 74LS0 74LS01 30 74LS02 25 74LS01 30 74LS02 35	74LS158 1.90 74LS160 2.20 74LS161 2.20 74LS162 2.30 74LS163 1.20 74LS164 1.30 74LS168 3.30 74LS169 3.50 74LS170 3.50 74LS173 2.10 74LS174 1.00 74LS175 1.00 74LS190 2.80 74LS191 1.20 74LS192 1.20 74LS193 1.20 74LS194 1.20 74LS195 1.20 74LS196 1.20 74LS196 1.20 74LS197 1.90 74LS197 1.90 74LS197 1.90	4072     40       4073     40       4074     40       4076     1.85       4077     40       4081     40       4082     40       4510     1.40       4518     1.50       4519     95       4520     1.45       4528     1.20       14584     1.25       74000     40       74024     40       7408     40       7401     40       7401     40       7401     40
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50 7906 1.50 7908 1.50 7912 1.50 7912 1.50 7912 1.50 78105 40 78112 40 78HGKC 8.50 78H05 7.90 78H12 7.90 78H12 7.90 73 50 309K 1.90 317K 2.90  OPTO  FND357 C.C. 1.30 FND500 C.C. 1.25 FND507 C.A. 1.40	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90 40 PIN 1.00  TTL  7400 25 7401 25 7401 25 7402 25 7404 35 7405 35 7406 50 7407 50 7408 32 7409 32	74161 1.75 74164 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50 74221 1.50 74221 1.50 74367 1.20 74368 1.20 74LS0 74LS00 25 74LS01 30 74LS02 25 74LS03 30 74LS04 35 74LS04 35 74LS04 35 74LS05 35 74LS05 35	74LS158         1.90           74LS160         2.20           74LS161         2.20           74LS162         2.30           74LS163         1.20           74LS164         1.30           74LS168         3.30           74LS169         3.50           74LS170         3.50           74LS173         2.10           74LS174         1.00           74LS195         1.00           74LS190         2.80           74LS191         1.20           74LS192         1.20           74LS193         1.20           74LS194         1.20           74LS195         1.20           74LS196         1.20           74LS197         1.90           74LS221         1.90           74LS253         1.85	4072     40       4073     40       4074     40       4076     1.85       4077     40       4081     40       4082     40       4510     1.40       4511     1.40       4518     1.50       4519     95       4520     1.45       4528     1.20       14553     7.30       14584     1.25       74000     40       74C02     40       74C08     40       74C10     40       74C14     1.75
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50 7906 1.50 7908 1.50 7912 1.50 7915 1.50 7915 1.50 78105 40 78112 40 78HGKC 8.50 78H05 7.90 78H12 7.90 723 50 309K 1.90 317K 2.90 FND357 C.C. 1.30 FND500 C.C. 1.25 FND507 C.A. 1.40 FND800 C.C. 3.50	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90 40 PIN 1.00  TTL  7400 25 7401 25 7402 25 7403 25 7404 35 7405 35 7406 50 7407 50 7408 32 7409 32 7410 25	74161 1.75 74164 1.55 74164 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50 74221 1.50 74221 1.50 74367 1.20 74368 1.20 74180 25 74LS0 25 74LS0 3 74LS0 35 74LS0 35 74LS0 35 74LS0 35 74LS0 35 74LS0 35 74LS0 30 74LS0 30 74LS0 30 74LS0 30 74LS0 30	74LS158         1.90           74LS160         2.20           74LS161         2.20           74LS162         2.30           74LS163         1.20           74LS164         1.30           74LS168         3.30           74LS169         3.50           74LS170         3.50           74LS173         2.10           74LS174         1.00           74LS195         1.00           74LS191         1.20           74LS192         1.20           74LS193         1.20           74LS194         1.20           74LS195         1.20           74LS196         1.20           74LS197         1.90           74LS21         1.90           74LS221         1.90           74LS253         1.85           74LS279         65	4072     40       4073     40       4074     40       4076     1.85       4077     40       4081     40       4082     40       4510     1.40       4511     1.40       4518     1.50       4519     95       4528     1.20       14553     7.30       14584     1.25       74000     40       7402     40       7408     40       7401     40       7404     1.75       74048     2.40
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50 7906 1.50 7908 1.50 7912 1.50 7912 1.50 7912 1.50 78105 40 78112 40 78HGKC 8.50 78H05 7.90 78H12 7.90 78H12 7.90 73 50 309K 1.90 317K 2.90  OPTO  FND357 C.C. 1.30 FND500 C.C. 1.25 FND507 C.A. 1.40	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90 40 PIN 1.00  TTL  7400 25 7401 25 7402 25 7403 25 7404 35 7405 35 7406 50 7407 50 7408 32 7409 32 7410 25 7411 35	74161 1.75 74164 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50 74221 1.50 74251 1.50 74367 1.20 74368 1.20 741S0 25 74LS01 30 74LS02 25 74LS01 30 74LS04 35 74LS05 35 74LS05 35 74LS08 30 74LS08 30 74LS09 30 74LS09 30 74LS09 30	74LS158         1.90           74LS160         2.20           74LS161         2.20           74LS162         2.30           74LS163         1.20           74LS164         1.30           74LS168         3.30           74LS169         3.50           74LS170         3.50           74LS173         2.10           74LS174         1.00           74LS195         1.00           74LS190         2.80           74LS191         1.20           74LS192         1.20           74LS193         1.20           74LS194         1.20           74LS195         1.20           74LS196         1.20           74LS197         1.90           74LS221         1.90           74LS253         1.85	4072     40       4073     40       4074     40       4076     1.85       4077     40       4081     40       4082     40       4510     1.40       4511     1.40       4518     1.50       4519     95       4520     1.45       4528     1.20       14553     7.30       14584     1.25       74000     40       74C02     40       74C08     40       74C10     40       74C14     1.75
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50 7906 1.50 7908 1.50 7912 1.50 7915 1.50 78105 40 78112 40 78HGKC 8.50 78H05 7.90 78H05 7.90 78H12 7.90 723 50 309K 1.90 317K 2.90 OPTO FND357 C.C. 1.30 FND500 C.C. 1.25 FND507 C.A. 1.40 FND800 C.C. 3.50 TIL209 Leds 20	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90 40 PIN 1.00  TTL  7400 25 7401 25 7402 25 7403 25 7404 35 7405 35 7406 50 7407 50 7408 32 7409 32 7410 25 7411 35 7411 35	74161 1.75 74164 1.55 74165 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50 74221 1.50 74251 1.50 74367 1.20 74368 1.20 74LS 74LS00 25 74LS01 30 74LS02 25 74LS03 30 74LS04 35 74LS05 35 74LS05 35 74LS08 30 74LS09 30 74LS09 30 74LS10 25 74LS10 30 74LS09 30 74LS09 30 74LS10 25 74LS11 30	74LS158         1.90           74LS160         2.20           74LS161         2.20           74LS162         2.30           74LS163         1.20           74LS164         1.30           74LS168         3.30           74LS169         3.50           74LS170         3.50           74LS173         2.10           74LS174         1.00           74LS195         1.00           74LS190         2.80           74LS191         1.20           74LS192         1.20           74LS193         1.20           74LS194         1.20           74LS195         1.20           74LS196         1.20           74LS197         1.90           74LS221         1.90           74LS253         1.85           74LS279         65           74LS365         75	4072     40       4073     40       4074     40       4076     1.85       4077     40       4078     40       4081     40       4082     40       4510     1.40       4511     1.40       4518     1.50       4519     95       4520     1.45       4528     1.20       14584     1.25       74C00     40       74C04     40       74C10     40       74C14     1.75       74C48     2.40       74C73     1.20
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50 7906 1.50 7908 1.50 7912 1.50 7912 1.50 7915 1.50 7915 40 78105 40 78112 40 78HGKC 8.50 78H05 7.90 78H05 7.90 78H12 7.90 723 50 309K 1.90 317K 2.90  OPTO  FND357 C.C 1.30 FND500 C.C 1.25 FND507 C.A 1.40 FND800 C.C 3.50 TIL209 Leds 20 RED LEDS 18	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90 40 PIN 1.00  TTL  7400 25 7401 25 7402 25 7403 25 7404 35 7405 35 7406 50 7407 50 7408 32 7409 32 7410 25 7411 35 7411 35 7413 55 7414 90	74161 1.75 74164 1.55 74165 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50 74221 1.50 74251 1.50 74367 1.20 74368 1.20 74LS0 74LS01 30 74LS02 25 74LS01 30 74LS04 35 74LS05 35 74LS05 35 74LS08 30 74LS09 30 74LS10 25 74LS10 30 74LS10 25 74LS01 35 74LS02 35 74LS03 30 74LS04 35 74LS05 35 74LS05 35 74LS08 30 74LS09 30 74LS10 25 74LS11 30 74LS11 30 74LS11 30	74LS158         1.90           74LS160         2.20           74LS161         2.20           74LS162         2.30           74LS163         1.20           74LS168         3.30           74LS169         3.50           74LS170         3.50           74LS173         2.10           74LS174         1.00           74LS175         1.00           74LS190         2.80           74LS191         1.20           74LS192         1.20           74LS193         1.20           74LS194         1.20           74LS195         1.20           74LS196         1.20           74LS197         1.90           74LS221         1.90           74LS253         1.85           74LS279         65           74LS365         75           74LS366         90	4072     40       4073     40       4074     40       4076     1.85       4077     40       4078     40       4081     40       4082     40       4510     1.40       4511     1.40       4518     1.50       4519     95       4520     1.45       4528     1.20       14584     1.25       74000     40       74C02     40       74C04     40       74C10     40       74C14     1.75       74C48     2.40       74C75     1.20
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50 7906 1.50 7908 1.50 7912 1.50 7912 1.50 7912 1.50 7915 1.50 78105 40 78112 40 78112 40 7816C 8.50 78H05 7.90 78H12 7.90 723 50 309K 1.90 317K 2.90  OPTO  FND357 C.C. 1.30 FND500 C.C. 1.25 FND507 C.A. 1.40 FND800 C.C. 3.50 TIL209 Leds 20 RED LEDS 18 100 for 13.00	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90 40 PIN 1.00  TTL  7400 25 7401 25 7402 25 7403 25 7404 35 7405 35 7406 50 7407 50 7408 32 7409 32 7410 25 7411 35 7411 35	74161 1.75 74164 1.55 74165 1.55 74173 2.75 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50 74221 1.50 74221 1.50 74367 1.20 74368 1.20 74LS0 74LS0 25 74LS01 30 74LS02 25 74LS03 30 74LS04 35 74LS04 35 74LS05 35 74LS08 30 74LS09 30 74LS09 30 74LS11 30 74LS11 30 74LS12 30 74LS11 30 74LS12 30	74LS158         1.90           74LS160         2.20           74LS161         2.20           74LS162         2.30           74LS163         1.20           74LS164         1.30           74LS169         3.50           74LS170         3.50           74LS173         2.10           74LS174         1.00           74LS195         1.00           74LS190         2.80           74LS191         1.20           74LS192         1.20           74LS193         1.20           74LS194         1.20           74LS195         1.20           74LS196         1.20           74LS197         1.90           74LS221         1.90           74LS253         1.85           74LS265         75           74LS366         90           74LS367         75	4072       40         4073       40         4074       40         4076       1.85         4077       40         4078       40         4081       40         4510       1.40         4511       1.40         4518       1.50         4519       95         4520       1.45         4528       1.20         14553       7.30         14584       1.25         74000       40         74024       40         74008       40         74C10       40         74C14       1.75         74C48       2.40         74C75       1.20         74C76       1.35
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50 7906 1.50 7908 1.50 7912 1.50 7912 1.50 7912 1.50 7915 1.50 78105 40 78112 40 78112 40 7816C 8.50 78112 7.90 78112 7.90 78112 7.90 78112 7.90 723 50 309K 1.90 317K 2.90  OPTO  FND357 C.C. 1.30 FND500 C.C. 1.25 FND507 C.A. 1.40 FND800 C.C. 3.50 TIL209 Leds 20 RED LEDS 18 100 for 13.00 YELLOW 30	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90 40 PIN 1.00  TTL  7400 25 7401 25 7402 25 7403 25 7404 35 7405 35 7406 50 7407 50 7408 32 7409 32 7410 25 7411 35 7411 35 7413 55 7414 90	74161 1.75 74164 1.55 74165 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50 74221 1.50 74251 1.50 74367 1.20 74368 1.20 74LS0 74LS01 30 74LS02 25 74LS01 30 74LS04 35 74LS05 35 74LS05 35 74LS08 30 74LS09 30 74LS10 25 74LS10 30 74LS10 25 74LS01 35 74LS02 35 74LS03 30 74LS04 35 74LS05 35 74LS05 35 74LS08 30 74LS09 30 74LS10 25 74LS11 30 74LS11 30 74LS11 30	74LS158         1.90           74LS160         2.20           74LS161         2.20           74LS162         2.30           74LS163         1.20           74LS164         1.30           74LS168         3.50           74LS170         3.50           74LS173         2.10           74LS174         1.00           74LS175         1.00           74LS190         2.80           74LS191         1.20           74LS192         1.20           74LS193         1.20           74LS194         1.20           74LS195         1.20           74LS197         1.90           74LS197         1.90           74LS221         1.90           74LS253         1.85           74LS265         75           74LS366         90           74LS367         75           74LS368         75	4072       40         4073       40         4074       40         4076       1.85         4077       40         4081       40         4082       40         4510       1.40         4511       1.40         4518       1.50         4519       95         4520       1.45         4528       1.20         14553       7.30         14584       1.25         74000       40         74C02       40         74C04       40         74C10       40         74C14       1.75         74C48       2.40         74C75       1.20         74C76       1.35         74C90       2.20
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7896 1.50 7906 1.50 7908 1.50 7912 1.50 7915 1.50 7915 1.50 78105 40 78112 40 7816C 8.50 78105 7.90 78112 7.90 723 50 309K 1.90 317K 2.90  PND357 C.C. 1.30 FND507 C.A. 1.40 FND800 C.C. 1.25 FND507 C.A. 1.40 FND800 C.C. 3.50 TIL209 Leds 20 RED LEDS 18 100 for 13.00 YELLOW 30 GREEN 30	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90 40 PIN 1.00  TTL  7400 25 7401 25 7401 25 7402 25 7404 35 7405 35 7406 50 7407 50 7408 32 7410 25 7411 35 7413 55 7414 90 7416 60 7417 60	74161 1.75 74164 1.55 74165 1.55 74173 2.75 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50 74221 1.50 74221 1.50 74367 1.20 74368 1.20 74LS0 74LS0 25 74LS01 30 74LS02 25 74LS03 30 74LS04 35 74LS04 35 74LS05 35 74LS08 30 74LS09 30 74LS09 30 74LS11 30 74LS11 30 74LS12 30 74LS11 30 74LS12 30	74LS158         1.90           74LS160         2.20           74LS161         2.20           74LS162         2.30           74LS163         1.20           74LS164         1.30           74LS169         3.50           74LS170         3.50           74LS173         2.10           74LS174         1.00           74LS195         1.00           74LS190         2.80           74LS191         1.20           74LS192         1.20           74LS193         1.20           74LS194         1.20           74LS195         1.20           74LS196         1.20           74LS197         1.90           74LS221         1.90           74LS253         1.85           74LS265         75           74LS366         90           74LS367         75	4072       40         4073       40         4074       40         4076       1.85         4077       40         4081       40         4082       40         4510       1.40         4511       1.40         4518       1.50         4519       95         4520       1.45         4528       1.20         14553       7.30         14584       1.25         74000       40         74C02       40         74C04       40         74C10       40         74C10       40         74C14       1.75         74C48       2.40         74C75       1.20         74C76       1.35         74C90       2.20         74C93       2.20
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50 7906 1.50 7908 1.50 7912 1.50 7912 1.50 7912 1.50 7915 1.50 78105 40 78112 40 78112 40 7816C 8.50 78112 7.90 78112 7.90 78112 7.90 78112 7.90 723 50 309K 1.90 317K 2.90  OPTO  FND357 C.C. 1.30 FND500 C.C. 1.25 FND507 C.A. 1.40 FND800 C.C. 3.50 TIL209 Leds 20 RED LEDS 18 100 for 13.00 YELLOW 30	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90 40 PIN 1.00  TTL  7400 25 7401 25 7402 25 7403 25 7404 35 7405 35 7406 50 7407 50 7408 32 7409 32 7410 25 7411 35 7413 55 7414 90 7416 60 7420 25	74161 1.75 74164 1.55 74165 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50 74221 1.50 74251 1.50 74367 1.20 74368 1.20 74LS 74LS00 25 74LS01 30 74LS02 25 74LS01 30 74LS04 35 74LS05 35 74LS08 30 74LS09 30 74LS09 30 74LS10 25 74LS11 30 74LS11 30 74LS12 30 74LS14 1.00 74LS14 1.00 74LS14 1.00 74LS15 35 74LS08 30	74LS158         1.90           74LS160         2.20           74LS161         2.20           74LS162         2.30           74LS163         1.20           74LS164         1.30           74LS168         3.50           74LS170         3.50           74LS173         2.10           74LS174         1.00           74LS175         1.00           74LS190         2.80           74LS191         1.20           74LS192         1.20           74LS193         1.20           74LS194         1.20           74LS195         1.20           74LS197         1.90           74LS197         1.90           74LS221         1.90           74LS253         1.85           74LS265         75           74LS366         90           74LS367         75           74LS368         75	4072       40         4073       40         4074       40         4076       1.85         4077       40         4081       40         4082       40         4510       1.40         4511       1.40         4518       1.50         4519       95         4520       1.45         4528       1.20         14553       7.30         14584       1.25         74000       40         74C02       40         74C04       40         74C10       40         74C14       1.75         74C48       2.40         74C75       1.20         74C76       1.35         74C90       2.20
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50 7906 1.50 7908 1.50 7912 1.50 7915 1.50 7915 1.50 78105 40 78112 40 78112 40 78112 7.90 78112 7.90 723 50 309K 1.90 317K 2.90  PND357 C.C. 1.30 FND500 C.C. 1.25 FND507 C.A. 1.40 FND800 C.C. 1.25 FND507 C.A. 1.40 FND800 C.C. 3.50 TIL209 Leds 20 RED LEDS 18 100 for 13.00 YELLOW 30 GREEN 30 Mounting Clips 3	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90 40 PIN 1.00  TTL  7400 25 7401 25 7402 25 7403 25 7404 35 7405 35 7406 50 7407 50 7408 32 7409 32 7410 25 7411 35 7413 55 7414 90 7416 60 7417 60 7420 25 7421 50	74161 1.75 74164 1.55 74165 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50 74221 1.50 74251 1.50 74367 1.20 74368 1.20 74180 25 74LS01 30 74LS01 30 74LS02 25 74LS03 30 74LS04 35 74LS05 35 74LS05 35 74LS09 30 74LS09 30 74LS10 25 74LS11 30 74LS12 30 74LS12 30 74LS12 30 74LS14 1.00 74LS15 35 74LS00 30 74LS14 1.00 74LS15 35 74LS00 30 74LS14 30 74LS15 35 74LS00 30 74LS14 30	74LS158         1.90           74LS160         2.20           74LS161         2.20           74LS162         2.30           74LS163         1.20           74LS164         1.30           74LS168         3.50           74LS170         3.50           74LS173         2.10           74LS174         1.00           74LS175         1.00           74LS190         2.80           74LS191         1.20           74LS192         1.20           74LS193         1.20           74LS194         1.20           74LS195         1.20           74LS196         1.20           74LS197         1.90           74LS21         1.90           74LS221         1.90           74LS253         1.85           74LS365         75           74LS366         90           74LS367         75           74LS368         75           74LS366         95	4072       40         4073       40         4074       40         4076       1.85         4077       40         4081       40         4082       40         4510       1.40         4511       1.40         4518       1.50         4519       95         4520       1.45         4528       1.20         14553       7.30         14584       1.25         74000       40         74C02       40         74C04       40         74C10       40         74C10       40         74C14       1.75         74C48       2.40         74C75       1.20         74C76       1.35         74C90       2.20         74C93       2.20
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7896 1.50 7906 1.50 7908 1.50 7912 1.50 7915 1.50 7915 1.50 78105 40 78112 40 78112 40 78112 7.90 78112 7.90 723 50 309K 1.90 317K 2.90  PND FND357 C.C. 1.30 FND500 C.C. 1.25 FND507 C.A. 1.40 FND800 C.C. 1.25 FND507 C.A. 1.40 FND800 C.C. 3.50 TIL209 Leds 20 RED LEDS 18 100 for 13.00 YELLOW 30 GREEN 30 Mounting Clips 3	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90 40 PIN 1.00  TTL  7400 25 7401 25 7402 25 7403 25 7404 35 7406 50 7407 50 7408 32 7409 32 7410 25 7411 35 7411 35 7414 90 7416 60 7417 60 7420 25 7421 50 7422 30	74161 1.75 74164 1.55 74165 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50 74221 1.50 74251 1.50 74367 1.20 74368 1.20 74LS 74LS00 25 74LS01 30 74LS02 25 74LS01 30 74LS04 35 74LS05 35 74LS05 35 74LS08 30 74LS09 30 74LS10 25 74LS10 25 74LS10 25 74LS10 30 74LS10 25 74LS10 30 74LS10 35 74LS09 30 74LS10 25 74LS11 30 74LS10 25 74LS11 30 74LS10 35 74LS10 35 74LS10 35 74LS10 35 74LS10 36 74LS10 37 74LS10 36 74LS10 37 74LS10 37 74LS11 30 74LS12 30 74LS14 1.00 74LS15 35 74LS20 30 74LS20 30 74LS21 30 74LS21 30 74LS21 30 74LS21 30	74LS158 1.90 74LS160 2.20 74LS161 2.20 74LS162 2.30 74LS163 1.20 74LS168 3.30 74LS168 3.50 74LS170 3.50 74LS173 2.10 74LS174 1.00 74LS175 1.00 74LS190 2.80 74LS191 1.20 74LS192 1.20 74LS194 1.20 74LS195 1.20 74LS196 1.20 74LS196 1.20 74LS197 1.90 74LS21 1.90 74LS21 1.90 74LS21 1.90 74LS21 1.90 74LS279 65 74LS365 75 74LS366 90 74LS367 75 74LS368 75 74LS368 75 74LS368 75 74LS368 75	4072       40         4073       40         4074       40         4076       1.85         4077       40         4081       40         4082       40         4510       1.40         4511       1.40         4518       1.50         4519       95         4520       1.45         4528       1.20         14553       7.30         14584       1.25         74000       40         74022       40         7404       40         74010       40         74014       1.75         74048       2.40         74075       1.20         74076       1.35         74090       2.20         74093       2.20         740192       2.20
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7905 1.50 7906 1.50 7908 1.50 7912 1.50 7915 1.50 78105 40 78112 40 7816KC 8.50 78105 7.90 78H05 7.90 78H05 7.90 78H05 7.90 78H05 1.50 78H12 1.50 790 723 50 309K 1.90 721 1.50 722 1.30 723 50 309K 1.90 317K 2.90 721 1.30 722 1.30 723 1.30 724 1.40 725 1.30 726 1.30 727 1.30 728 1.30 728 1.30 728 1.30 728 1.30 730 74 1.30 75 1.3	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90 40 PIN 1.00  TTL  7400 25 7401 25 7401 25 7402 25 7404 35 7405 35 7406 50 7407 50 7408 32 7409 32 7410 25 7411 35 7413 55 7414 90 7416 60 7417 60 7420 25 7421 50 7422 30 7426 45	74161 1.75 74164 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50 74251 1.50 74251 1.50 74367 1.20 74368 1.20 74LS0 74LS01 30 74LS02 25 74LS03 30 74LS04 35 74LS05 35 74LS08 30 74LS04 35 74LS09 30 74LS09 30 74LS11 30 74LS11 30 74LS12 30 74LS11 30 74LS12 30 74LS11 30 74LS12 30 74LS14 1.00 74LS15 35 74LS20 30 74LS15 35 74LS11 30 74LS12 30 74LS14 1.00 74LS15 35 74LS20 30 74LS21 30	74LS158 1.90 74LS160 2.20 74LS161 2.20 74LS162 2.30 74LS163 1.20 74LS168 3.30 74LS168 3.50 74LS170 3.50 74LS170 3.50 74LS173 2.10 74LS174 1.00 74LS175 1.00 74LS191 1.20 74LS191 1.20 74LS192 1.20 74LS193 1.20 74LS194 1.20 74LS195 1.20 74LS195 1.20 74LS195 1.20 74LS196 1.20 74LS197 1.90 74LS21 1.90 74LS21 1.90 74LS21 1.90 74LS253 1.85 74LS365 75 74LS366 90 74LS367 75 74LS368 75 74LS368 75 74LS386 95	4072       40         4073       40         4074       40         4076       1.85         4077       40         4081       40         4082       40         4510       1.40         4511       1.40         4518       1.50         4519       95         4520       1.45         4528       1.20         14553       7.30         14584       1.25         74C00       40         74C02       40         74C04       40         74C10       40         74C14       1.75         74C48       2.40         74C75       1.20         74C76       1.35         74C90       2.20         74C175       1.85         74C192       2.20         74C193       2.20         74C193       2.20
7812 1.00 7815 1.20 7818 1.20 7824 1.20 7896 1.50 7906 1.50 7908 1.50 7912 1.50 7915 1.50 7915 1.50 78105 40 78112 40 78112 40 78112 7.90 78112 7.90 723 50 309K 1.90 317K 2.90  PND FND357 C.C. 1.30 FND500 C.C. 1.25 FND507 C.A. 1.40 FND800 C.C. 1.25 FND507 C.A. 1.40 FND800 C.C. 3.50 TIL209 Leds 20 RED LEDS 18 100 for 13.00 YELLOW 30 GREEN 30 Mounting Clips 3	8 PIN 25 14 PIN 33 16 PIN 35 18 PIN 50 20 PIN 60 22 PIN 75 24 PIN 80 28 PIN 90 40 PIN 1.00  TTL  7400 25 7401 25 7402 25 7403 25 7404 35 7406 50 7407 50 7408 32 7409 32 7410 25 7411 35 7411 35 7414 90 7416 60 7417 60 7420 25 7421 50 7422 30	74161 1.75 74164 1.55 74165 1.55 74165 1.55 74173 2.75 74175 1.65 74180 1.35 74192 1.40 74193 1.40 74197 1.50 74221 1.50 74251 1.50 74367 1.20 74368 1.20 74LS 74LS00 25 74LS01 30 74LS02 25 74LS01 30 74LS04 35 74LS05 35 74LS05 35 74LS08 30 74LS09 30 74LS10 25 74LS10 25 74LS10 25 74LS10 30 74LS10 25 74LS10 30 74LS10 35 74LS09 30 74LS10 25 74LS11 30 74LS10 25 74LS11 30 74LS10 35 74LS10 35 74LS10 35 74LS10 35 74LS10 36 74LS10 37 74LS10 36 74LS10 37 74LS10 37 74LS11 30 74LS12 30 74LS14 1.00 74LS15 35 74LS20 30 74LS20 30 74LS21 30 74LS21 30 74LS21 30 74LS21 30	74LS158 1.90 74LS160 2.20 74LS161 2.20 74LS162 2.30 74LS163 1.20 74LS168 3.30 74LS168 3.50 74LS170 3.50 74LS173 2.10 74LS174 1.00 74LS175 1.00 74LS190 2.80 74LS191 1.20 74LS192 1.20 74LS194 1.20 74LS195 1.20 74LS196 1.20 74LS196 1.20 74LS197 1.90 74LS21 1.90 74LS21 1.90 74LS21 1.90 74LS21 1.90 74LS279 65 74LS365 75 74LS366 90 74LS367 75 74LS368 75 74LS368 75 74LS368 75 74LS368 75	4072       40         4073       40         4074       40         4076       1.85         4077       40         4081       40         4082       40         4510       1.40         4511       1.40         4518       1.50         4519       95         4520       1.45         4528       1.20         14553       7.30         14584       1.25         74000       40         74022       40         7404       40         74010       40         74014       1.75         74048       2.40         74075       1.20         74076       1.35         74090       2.20         74093       2.20         740192       2.20

Minimum pack and post \$1.00 please sipulate if any items are out of stock that a credit be issued or the items to be backordered or an immediate refund be issued. Send 40c stamp for copy of free condensed catalogue. op open from:8 mon-THURS 8.00am—5.30pm; FRI 8.00am—7.00pm; SAT 8.30am—12.30pm.

ALL GOODS ARE PRIME SPEC. FROM LEADING MANUFACTURERS

MAIL ORDERS TO: P.O. BOX 135 NORTHCOTE VIC. 3070 PERSONAL SHOPPING AT THE SHOP AT 499 HIGH ST NORTHCOTE,
VIC. 3070.

# Calculator chart for hex displacements

Probably the biggest chore when you are programming a microcomputer in hexadecimal code is calculating relative address displacements. Here is an improved displacement lookup table which the author claims is easier and more rapidly used than any method yet published.

#### by COLIN KEAY

Associate Professor of Physics, The University of Newcastle NSW 2308

Unless you happen to be proficient at subtraction in hexadecimal arithmetic, the determination of relative address displacements is the most irksome task faced by microcomputer programmers who attempt to assemble programs manually. Even when using a microcomputer with a built-in displacement calculator routine the required button-pushing takes time, especially if you forget or mistake the addresses in memory where the origin and destination bytes must be lodged for processing. Furthermore each microcomputer with this facility has a different procedure to follow.

Alternatively, one may work from sequential hexadecimal number tables which require tedious counting, buy a Texas Instruments "Programmer" calculator or use a Relative Jump Ruler


as described by John S. MacDougall (Interface Age, March 1978). This requires that the program be coded on a line-per-byte basis, which is a considerable nuisance for the majority of microcomputers.

There had to be a better way, and it was found by analogy with the unique way the old IBM 1620 computer performed its decimal arithmetic with binary coded numbers. This is the reverse problem: getting decimal-oriented humans to work in hexadecimal. The solution is a simple but universal look-up table for finding hexadecimal differences one digit at a time, with provision for borrowing when necessary between digits. The resulting Microcomputer Program Displacement Table shown in Fig. 1 has been used to assist the manual


assembly of programs for a variety of different microprocessors and has proved very successful as a programming teaching aid.

Using the Displacement Table is almost self-explanatory. A few examples will make the procedure clear. First, a program branch back from A7 to 54 as demonstrated in Fig. 2. Take the low order digit first, descending column 7 to the row containing the destination digit 4 which also contains the digit D in the column under X1. Similarly, descend from A to 5 and in the same row as 5 the digit A is found in the column under X2. The required displacement byte is therefore AD.

Had the first destination digit been located within the dotted triangle the second digit of the displacement byte would have been obtained from the column under X1. This takes into account the absence of a "borrow" from the subtraction of the first digit. So for our second example consider a branch from A7 to 8D as shown in Fig. 3. Descending from 7 we find D is within the dotted triangle. In the row containing D we find the digit 6 under X1, but for the next digit we must this time find it again under X1 and not X2.

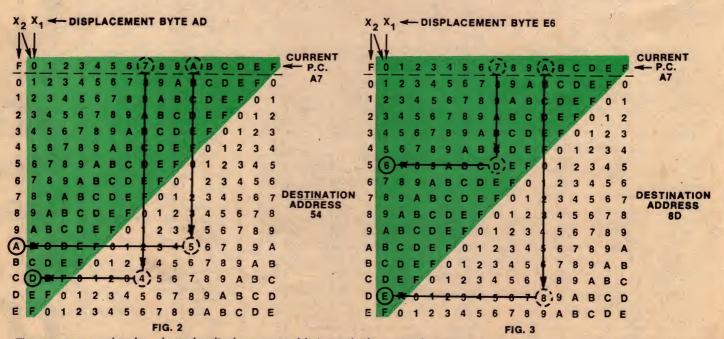

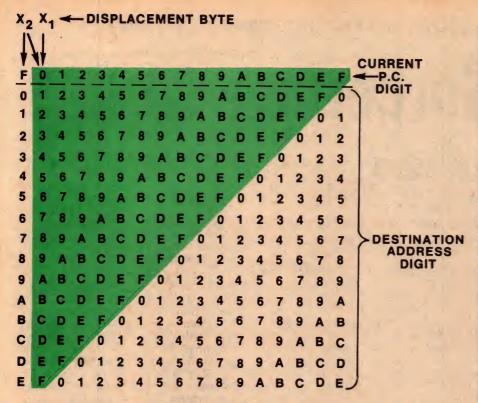These two examples show how the displacement table is used. The example in Fig. 2 shows a jump from A7 to 54, while that in Fig. 3 shows a jump from A7 to 8D.



#### RULE: IF FIRST DESTINATION IS WITHIN SHADED TRIANGLE X2 WILL BE ALSO

#### FIG. 1 MICROCOMPUTER PROGRAM DISPLACEMENT TABLE

Here is Professor Keay's table, inspired by the computational method used by an early computer. Using it you can find relative address and branch displacements very rapidly and conveniently.

Descending from A to 8 we find in the row containing 8 the digit E under X1. The required displacement byte is therefore E6.

We have assumed that the highorder byte is identical for the current address and the destination. Whenever the high order bytes differ, a single byte may be insufficient for the displacement. In such a case the Displacement Table can be employed to obtain X3 and X4 in exactly the same way as for X2. One must simply obey the rule that whenever a destination digit falls within the dotted triangle the subsequent displacement digit must also be within the dotted triangle. For this reason the dotted region of the table has been nicknamed "The Bermuda Triangle" when landing in it one stays in it, but only for the next turn!

Besides calculating program displacements the table is useful for determining the length of program segments, subroutines, etc. For example, can a program extending from 27B9 to 3C63 be relocated in a gap between 0FA2 and 1455? Using the table we find that the program is 4AA bytes in length and the gap is found to be of 4B3 bytes, so it will fit with 4B3-4AA = 19 (hex) bytes to spare.

This technique uses hexadecimal numbers exclusively and thereby avoids the confusion inherent in the Address Calculator Tables (such as Ray Boaz's table in Byte Magazine, April 1978) and Multi-base Conversion Charts (wall-size or otherwise) where the actual arithmetic is performed in decimal notation.

Finally, when time permits, it is a good idea to check the results obtained using the Displacement Table by attempting to perform an actual hexadecimal subtraction and if necessary, counting digits, in hexadecimal to verify the result. After a few weeks (or months?) of practice the terrors of hexadecimal arithmetic will vanish and the Displacement Table can then be thrown away — even when calculating fearsome reverse jump displacements!

NOTE: The foregoing article is reproduced by arrangement with the author and copyright holder, C.S.L. Keay. Reproduction by educational bodies for tuitional purposes is permitted, providing due acknowledgement is given. Reproduction for any other purpose by negotiation only.

#### On sale now

#### "ELECTRONICS AUSTRALIA" PROJECTS & CIRCUITS NO. 2

\$3.00 plus 60c p & p
Electronics Australia,
Box 163, Beaconsfield, NSW 2014

# SEMICONDUCTORS AT DISPOSAL PRICES

limited	qu	ant	itie	S	0	nly
Transistors		-	-	-		10
BC 107						\$0.18
BC 108						\$0.18
BC 109 BC 177						\$0.18 \$0.20
BC 177						\$0.20
BC 178						\$0.20
BC 179						\$0.20
BC 547						\$0.14
BC 548						\$0.14
BC 549						\$0.14
BC 557						\$0.15
BC 558						\$0.15
BC 559		••.			••	\$0.15
BD 139						\$0.40
BD 140				. '		\$0.40
BFY 50						\$0.26
BU 126						\$2.65
BU 208A						\$2.65
MJ 2955						\$1.20
PN 3568						\$0.10
TIP 31.1						\$0.25
TIP 32A						\$0.26
TIP 32A TIP 2955	١			'	••	\$0.72
TIP 3055				. /		\$0.68
2N 3055						\$0.45
2N 3642						\$0.14
2N 3772						\$2.35
2N 3773						\$3.40
2N 3819				••		\$0.25
2N 4250						\$0.12
Diodes/Bridges						
BYX 2IL20	0				"	\$0.74
BYX 2IL20	OR					\$0.74
OA 91				.,		\$0.07
IN 914					••	\$0.05
IN 400A						\$0.08
IN 5060		••		••		\$0.10
VK 1048					••-	\$2.20
SCR <sup>s</sup> /Triacs						
C 106D						\$0.68
SC 141D						\$0.77
V 413 DIA	C					\$0.13
Linear I.C.S.						3
LM 555 CN						\$0.35
LM 723 CH						\$0.56
LM 741 CN						\$0.22
UA 706						\$1.00
UA 7906 C	U/L	M 3	20T-	6		\$1.55
Opto Devices						
TIL 306 Di	splay	y wi	th Ic	gic		\$8.00
REDLED						\$0.14
YELLOW L				••		\$0.28
GREEN LE		5 n				\$0.18
Mos I.C.S.	1	-				1000
MM 1702 A	Q.,					\$4.50
MM 2102 -	450	ns				\$1.35
MM 5017 -	Dua	1 51	2 SF	3		\$1.00
I.C. Sockets						
8 PIN						\$0.21
14 PIN		1				\$0.23
16 PIN		-				\$0.25

QUALITY DISCOUNTS AVAILABLE All Prices Plus Tax If Applicable

ELECTRONIC and SEMICONDUCTOR DISPOSALS Post Office Box 72, Parkville, Vic 3052

#### It offers 8K BASIC in ROM, user-programmed graphics:

## Exidy's Sorcerer

One of the most recent entries in the blossoming personal computer market is the Exidy Sorcerer, which offers features like programmable graphics and 8K Standard BASIC in a plug-in ROM pack. Sorcerers are now available in Australia, and our Editor Jim Rowe has been able to try one out for a few weeks. Here is what he found:

I first came across the Exidy Sorcerer in April last year, when I visited the Percomp '78 hobby computer exhibition in Long Beach. It had just been announced, and the firm had an early prototype on their stand displaying graphics. It looked good, as reported later in the magazine, although at that stage hardly anyone had even heard of Exidy — at least in the small computer field.

It turned out that Exidy Inc was a firm based in Sunnyvale, California, who had been making very successful coinoperated video arcade games for about five years. They had decided to use their microprocessor experience and branch into the personal computer area, and Sorcerer was the first of their

new products.

In the months that have followed, the Sorcerer seems to have met with quite a warm reception in the USA. It has also started to appear "in disguise", under other brand names. So it was with some interest that I learned recently that Dick Smith Electronics had arranged with Exidy to market the Sorcerer in Australia, and that there would be an opportunity to try out one of the systems for myself.

A few weeks ago the sample Sorcerer arrived, and since then I have had quite

a good chance to use it.

The Sorcerer itself is a single-board Z80 based microcomputer which is housed, along with its power supply, in a compact keyboard case. It is complete with inbuilt video interface, providing a video output suitable for either a standard video monitor or for connection via an RF modulator to a standard TV set.

The keyboard on the front of the unit has a total of 79 keys: 63 in a standard alphanumerical array and the remaining 16 in a numeric/graphics control pad. The main array offers both upper and lower case characters, together with provision for encoding up to 128 graphics codes.

Sorcerer has an inbuilt audio cassette

Sorcerer has an inbuilt audio cassette interface, capable of working at either 300 or 1200 baud and with optional software control of up to two cassette deck motors. There is also an RS232

serial interface, 8-bit parallel input and output ports, and a 50-pin expansion port which mates with a forthcoming S-100 bus expansion unit.

The basic Sorcerer comes with either 8K or 16K bytes of user RAM memory, together with 4K bytes of ROM containing a powerful monitor program. With it also comes a plug-in "ROM-PAC" containing an 8K byte BASIC interpreter, written by Microsoft Inc. The ROM PAC is housed in what appears to be a converted 8-track tape cartridge moulding, and plugs into a slot in Sorcerer's right-hand end.

The idea of having the interpreter in a plug-in module is that you have greater flexibility; other software can be plugged in instead. In fact you can apparently already get cartridges with 8K of blank PROMs, to load with custom software. And Exidy itself is apparently about to release a second "Development System" ROM PAC, containing things like an assembler, a text editor, a debugging program and similar development aids.

The 4K monitor program which is

permanently resident in Sorcerer has some powerful commands. When you dump programs onto a tape cassette, you give them a file name which can then be used by the load routine to seek and load a specified program from the cassette at a later stage. A file listing program can also be used to list all of the programs stored on a cassette.


The BASIC interpreter which comes with Sorcerer is a full 8K standard BASIC. It allows named-program loading and dumping, a wide range of functions, 6-digit floating point arithmetic, and all normal BASIC commands. Other desirable features include PEEK and POKE statements, a USR command to link with machine language routines, string handling, and both numerical and string arrays.

And of course there are the graphics facilities. Sorcerer allows you to have up to 128 different graphics characters, any of which may be placed on the display screen in a 64 x 30 matrix. As the characters are themselves based on an 8 x 8 dot matrix, this gives an overall graphics resolution of 512 x 240 points.

All of the graphics character generation information is stored in RAM, and is potentially programmable by the user. However the monitor program normally creates the information for 64 "standard" graphics characters on power-up, and stores these away in half of the allocated 1K of memory space. The user can use these,



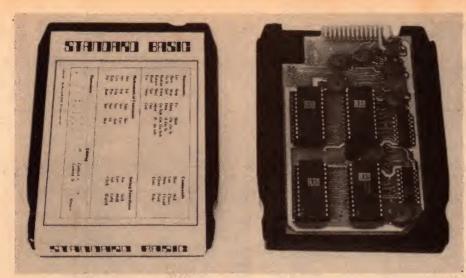Here is the Sorcerer in a typical user situation, with the BASIC interpreter cartridge plugged in the side. The TV monitor, cassette recorder and books don't come with it for the price quoted — they're extra!



Outside and inside views of the plug-in ROM PAC, containing 8K BAŞIC.

together with another 64 customprogrammed characters, or can replace them if desired with a further 64 programmed characters.

Programming the graphics characters themselves is simply a matter of storing appropriate bit patterns in the right memory locations. Each character occupies eight consecutive memory locations, with the bits of each location corresponding to the eight graphics elements in each of the eight horizontal rows making up the character.

Two books come with the basic

Sorcerer. One is a user manual, titled "A Guided Tour of Personal Computing"; the other is an introduction to BASIC programming called "A Short Tour of BASIC". Both are in ring binder form for ease of use, but I found them both rather disappointing in terms of content and organisation.

A significant proportion of the material in the user manual is little more than a repetition of material in the BASIC BOOK. At the same time, there is very little information on machine language programming, and

none on such things as the significance of monitor error messages, and the use of monitor subroutines by user programs. To my mind this is almost essential information for any intelligent system user.

Similarly although both books describe the way the user can program graphics characters, neither devotes any space at all to explaining how the graphics are actually used in programming!

I understand that Dick Smith Electronics is going to remedy these shortcomings by providing some supplementary information.

The Sorcerer itself seems a well made unit. I did have a little trouble initially with faulty program reloading from cassettes, but this was apparently due to overload of the recorder's ALC circuitry during record. It was solved by fitting a small fixed attenuator in the recording lead. The recorder does not come with the Exidy; this probably explains the incompatibility.

I found the Sorcerer quite easy to use. The BASIC interpreter is a good one, and provides all the commands one would normally require. The monitor is also powerful, although I would have liked to see at least one breakpoint facility.

Still, at \$995 for the 8K version and \$1250 for the 16K version, it seems very good value for money. You can see the Sorcerer at most DSE stores; it's well worth a closer look.





EME-20 (as shown) connects directly to CPU serial lines at RS232C, current loop or TTL levels at rates up to 9600 baud, and operates with a standard TV monitor. The keyboard has hall effect keys for reliability.

The EME-20 is based on the EME-2 module (See EA. Aug. 78)

EME-20 in kit form (excluding monitor \$450.00 EME-20 assembled and

(excluding monitor) \$540.00 Add 15% sales tax if applic.

> Contact us for your special requirements. Engineering assistance is always available.

> > **AUSTRALIAN** DESIGNED & MANUFACTURED

For further information contact:

#### **E&M ELECTRONICS PTY LTD**

136 Marrickville Road, Marrickville, NSW 2204. Telephone (02) 51 5880

#### Note:

The monitors available may vary from the style shown.

#### Also available:

EME-1(See EA Jan. 77) Kit \$169.00 plus tax Assem. \$249.00

EME-2 (See EA. Aug. 78) Kit \$232.00 plus tax Assem. \$295.00

See demonstrations at our premises.

Also keyboards, cases, cassette interfaces, etc.

### Microcomputer News & Products



## Locally designed VDT, micro system


A new "glass teletype" video data terminal and a Z80-based microcomputer system — both locally designed and manufactured — have been released by General Electronic Developments Pty Ltd, of Gladesville, NSW. GED is a relatively new name in the digital field, having until recently been active mainly in the area of analog instrumentation, but their latest products demonstrate that they lack no expertise in the data processing area.

The model 135 teletype-replacement VDT features a 30cm black and white CRT with a 24 x 80 display format. The character set uses a 7 x 9 matrix, with descending lower case characters. The display is normally white letters on a black background, but black on white is available. Four cursor options are available: underline, blinking underline, reverse block and blinking reverse block. N-key rollover is standard, with three keyboard options.

The modem interface is RS232 or 20mA loop, while baud rates from 75—19,200 are standard. An unusual feature is a high speed option which will run at up to 153,600 baud.

The model 136 computer system is

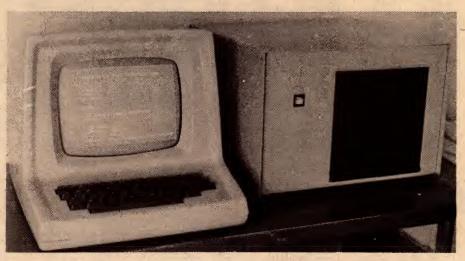The model 136 computer system is built into the same basic case as the terminal, and has a 16 x 64 terminal



inbuilt. It is a Z80-based system, with provision for up to 48K of on-board RAM. Provision is also made for 8K or 16K of ROM for resident user software, with a ROM debug, disk bootstrap and CP/M disc operating system (2K) supplied as standard.

The system provides four full duplex serial ports which interface with either RS232 or 20mA terminals (i.e., model 135s). There are also four 8-bit parallel I/O ports, fully buffered and with handshake control lines, for printers, card readers, etc. The disk interface will accept up to eight IBM-compatible standard single density soft sectored 8-

in floppy disks (it will also accept dualsided drives). The standard system comes with two Shugart SA800 drives, as shown in the picture.

A built-in interface allows two cassette recorders to be connected for simultaneous read and write operation.

On the software side, languages available with the 136 system include Pascal, Fortran (ANSI), Cobol (ANSI), five different types of BASIC, a stack oriented language similar to FORTH, PILOT, and a string processing language similar to TRAC.

Utility software available includes the resident ROM debugger, symbolic debug utility, text editors, text editing language, text output processor, assemblers, macro pre-processor, macro assemblers, disk file utilities, disk format utility, disk analysis, dump and patch utilities.

Both the 135 VDT and the 136 computer employ GED's model 117 high performance video monitor module, which is also available to OEMs as a separate item. Using a 30cm tube, the monitor accepts composite video from a 75 ohm source, and is capable of a sharp 24 x 80 character display with very little geometric distortion.

Further information on all three products is available from General Electronic Developments Pty Ltd, 396 Victoria Road, Gladesville, NSW. Telephone (02) 816 2211.

#### Courses in Brisbane

The Brisbane Microcomputer Interest Group is planning to continue its series of 10-week educational courses this year, in conjunction with the Department of Technical and



Further Education. There will be five different courses in operation, titled 1. A Course in Digital Electronics; 2. Beginners Course in Microcomputers; 3. Advanced Course in Microcomputers; 4. Introduction to Programming Microcomputers; 5. Advanced Programming, Microcomputers.

Those interested in taking the courses should ring the T.A.F.E. office on either (04) 224-7847 or 224-7839 to reserve a place. Further information is available from Norman Wilson, Brisbane MIG, P.O. Box 81, Albion Qld 4010

#### **DC-DC** converters

A series of very compact PCB-mounting DC-DC power converter modules is available from Instant Component Service. Made by ITT Components, the "Powermod" modules are suitable for microprocessor systems and any similar applications requiring high reliability, excellent regulation and thorough filtering.

The converters are available in two sizes, designated E and R respectively. The R series modules are available to suit input voltages of 5, 12, 24 and 48V, while the E series are available in two input voltage types: 5V and 12V. All modules have internal short-circuit protection.

Further information is available from ICS offices in all main states.

#### KILOBAUD

LEADING U.S. SMALL
COMPUTER MAGAZINE
UNDERSTANDABLE FOR
BEGINNERS, INTERESTING
FOR EXPERTS

Due to increases in internal postage costs, rates have increased as follows:

Air freight subscriptions \$45.00 p.a. Sea freight subscriptions \$33.00 p.a.

Or see your major technical book store for individual copies.

Special discounts offered to clubs and educational institutions for quantity purchase.

Send \$3.00 for special introductory offer.

Distributed in Australia by:


### SONTRON


P.O. Box 156, Carnegie, Vic. 3163. Tel: (03) 569 7867 or 568 0642
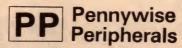
#### 16K PROM CARD + PROGRAMMER

FOR LATEST 2K x 8 SINGLE +5V 2516 EPROMS

- For INTEL 2716 & TEXAS 2516 EPROMs.
- Runs entirely from +5V.
- Execute programs from any PROM.
- Program any PROM location in 50mS with a single store instruction.
- Write protect switch.
- Motorola Exorcisor bus as on D2 Kit.
- Compatible with 6800, 8080/5, 6502, 2650, SC/MP etc.
- Two 8K switch addressable blocks.
- PCB plated through with solder resist.



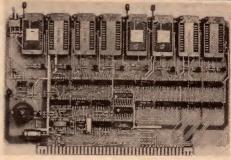

Assembled & tested only.
\$197.30 with Low Insertion Force Sockets
\$236.20 with Zero Insertion Force Sockets
(P&P \$3.00, add 15% if Sales Tax is Applicable)
2716's available \$43.50 each
DEALER ENQUIRIES WELCOME

Peripherals

Designed & Manufacutred in Australia.

19 Suemar St., Mulgrave Vic. 3170.

(03) 546 0308

#### 2650 SYSTEM USERS!

This 175mm 33-1/3rpm record provides 11 useful programs for small computer systems based on the Signetics 2650 microprocessor. You feed them into your system via a normal cassette interface ("Kansas City" standard).

The programs include hex input and listing routines, block move and search, tape measure and verifier, a disassembler, 300-baud binary dump and loader, and two amusing games for relaxation. All load in via Signetics' PIPBUG.

The EA-Philips 2650 System Software Record is available from the Electronics Australia office for \$2.50, or \$3.00 posted anywhere in Australia from EA, P.O. Box 163, Beaconsfield, NSW 2014.



## THE BUTE SHOP

COLBEE COURT PHILLIP

2708(8708)

1µS EPROMS

\$12.50 +(1-50 s.t) each

ADD \$1 p&p Per Order

PO BOX 118, MAWSON, ACT 2607

#### DON'T LET YOUR VALUABLE ISSUES GO ASTRAY


## **ELECTRONICS AUSTRALIA** BINDERS

These attractive binders finished in brown plastic with gold lettering will keep your back issues of Electronics Australia neat and tidy.

#### Available from
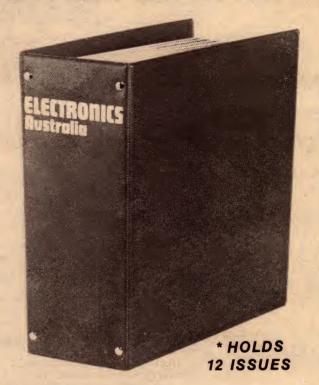
#### **Electronics Australia**,

57 Regent St, Sydney. PRICE: \$4.50 or by mail order from Electronics Australia, P.O. Box 163, Beaconsfield 2014. PRICE \$5.50 NSW: \$6.50 other states.



\*Magazines prior to April 1971 will need to be trimmed to fit binder.

## the audiosound ASC-1/LD40

#### Professional Pre/Power Amplifier System

#### Cloud nine performance at a down-to-earth price.

This new system with its extremely functional simplicity offers low T.I.M. performance from the pickup to the loudspeaker and includes a built-in high performance head amp. for moving-coil cartridges.

The LD40 PM highly developed class A/B power amplifier is widely used by the Australian Broadcasting Commission who have hundreds in service throughout Australia.

The separate Pre/Power amplifier system with its 40

watt output is easily converted to 120 watts/channel output by simply adding another LD40 power amplifier.

With enough gain to suit any cartridge within the forseeable future, new high slew-rate tone controls and ultra low distortion RIAA stage we feel at around \$700 it is a state-of-art bargain. You'll now be able to afford the loudspeakers as well!



Jdiosol

938 2068

Suppliers of monitoring amplifiers and loudspeakers to the Australian Broadcasting Commission.

## Classical scord

Reviewed by Julian Russell

#### Janacek — Katya Kabanova: unique

JANACEK — Katya Kabanova. Complete Opera. Elisabeth Soderstrom, Petr Dvorsky, Nadezda Kniplova with the Vienna Philharmonic Orchestra conducted by Charles Mackerras. Decca Stereo. Two boxed discs with brochurelibretto. D51D 2.

Despite the general excellence of the whole production, two artists dominate this recording — Elisabeth Soderstrom as Katya and conductor Charles Mackerras. Mackerras' years of study in Czechslovakia under that fine conductor Vaclav Talisch gave him an insight into not only the Czech character but especially into the music of Janacek. His admiration of the latter has persisted throughout his career, as has his continuing study of his works.

None of his performances that I have heard either live or recorded, fine as they were, approaches his superb account of Katya on these two discs. True he has all the advantages of the great Vienna Philharmonic as his orchestra, and also a Katya of rare sensibility and the keenest imaginable perception of the many sides of this complex character. It is a combination that is unlikely to be matched in the foreseeable future.

For those unacquainted with Janacek's music I had better explain that his style is unique. He has no forerunner of any consequence, and founded no school to successfully follow him. His peculiarly laconic and sometimes ejaculatory style — was based for the most part on the rhythms and intonations of his native Moravian speech. It is way outside the general trend of central European music of his period, or any other period for that matter. Added to this he had a fine sense of melody that can ravish you with the intensity of its lyricism, all the more so when it frequently interrupts the more fragmentary structure of the rest of his music.

He can establish a character instantly and, by subtle changes, reveal his or her innermost thoughts without the cumbersome process of the use of leit motifs in the Wagnerian style. By this statement I do not intend to disparage in any way the great Wagnerian achievements in the development of music drama.

Janacek's music is so different from that of any other composer I know that you may need a couple of repetitions to appreciate its beauty and originality. Once this is done your appreciation and enjoyment of it should be as endless as that of Mackerras himself.

You don't have to wait long to realise the superb quality of sound he produces from his great orchestra. The very first bars of the opera open ppp. swell gradually to pp. and then to piano, the whole quiet, even pastoral sounding introduction filled with underlying sadness. The music swells with a moving sense of drama and then changes into a beguiling dance-like theme, all scored in a manner that I can only describe as inimitable. It is a masterpiece of preparation of what is to

Mackerras never fails to display an incomparable sense of rhythm and lightning changes of mood. He maintains a perfect balance between voices and orchestra throughout the whole work, encouraging the singers when necessary and giving them their heads when the situation demands it.

To go into the subtleties of Soderstrom's performance of this most difficult role would take far more space than is available to me here. To put it as briefly as I can, she never misses a point, either vocal or dramatic. The whole company pays the two principals what is perhaps the greatest possible compliment any combination can pay any director or star - they obviously enjoy every bar. The voices often have that slightly hard sound which the music demands — except, of course, Soderstrom's — and, thank heaven, none of the female singers have that wide wobble that characterises so many Slavic singers.

Most of the cast - again not Soderstrom - are Czech and, even with the aid of the English translation that accompanies the set, most listeners will often find the English libretto a bit hard to follow. I recommend that before playing the opera you spend a little time studying the very useful explanation of Czech pronunciation found at the beginning of the accompanying brochure.

All — orchestra and cast — maintain Janacek's deep sense of humanity, a humanity unimpaired by the destructive activities of the 12-tone school, those musical wreckers who tried to reduce music to a mathematical formula. They have, barring one or two outstanding exceptions, failed ignominiously to do so over a period of over 70 years, though at times they have bullied their way into espousal by trendy, untalented sycophants, of which Australia has more than its fair share.

The moods in this great opera vary from sadness to savagery, from didacticism to glowing love themes. There are no Madam Butterfly facile emotions, fine though that score can be made to sound in the right hands and throats. Here are characters in the Moussorgsky manner, real people, angry, loving, uncertain sometimes in their reaction to thoughts and deeds that will inevitably destroy them - a veritable Hamlet among operas.

The whole production — and this includes the really first class engineering offers you a collaboration at all times eloquent, without a dull bar and many quite overpowering ones. And in the libretto there is also a very readable article by Mackerras himself, in which he gives a graphic account of his growing interest in, and affection for, Janacek's works.

Since most of the singers will be strangers — again except Soderstrom to the average musician I have mentioned by name only the three chief characters among the large cast at the head of this column. (P.S. Mackerras will return to Australia in 1979 to conduct Janacek's Jenufa, which is not unknown to Australian audiences).

Very highly recommended.

#### Strauss — excerpts from Salome

STRAUSS, RICHARD - Vocal and orchestral excerpts from the opera Salome. Closing Scene. Dance of the Seven Veils. Five songs for voice and orchestra. Montserrat Caballe and the National Orchestra of France conducted by Leonard Bernstein. DGG Stereo Disc 2530 963.

The Salome excerpt starts with the orchestral passage describing Salome's

obscene excitement while awaiting the execution of John the Baptist. Then she starts to sing in a disappointingly coarse grained performance of the role, vocally and dramatically. She sounds revengeful rather than lustful, though the ideal reading of the part should be a combination of both. Moreover she is sometimes surprisingly off pitch.
Salome is an immensely difficult role

to bring off successfully and I have heard some great performances in my time, and also some which were far from good. The trouble is that by the time a dramatic soprano acquires the vocal demands of the character, she has reached a size that makes her appearance as a teenage girl look ridiculous. The best looking Salome I ever saw was Lisa della Casa, performing in Munich some years ago. But against that, the memory of our own Joan Hammond galumphing about the stage of the Elizabethan Theatre, Newtown, in the Dance of the Seven Veils still fills me with awe. In terms of Miss Hammond's other accomplishment, golf, she was way over par for the course in Salome. And I wonder how many people remember that Maria Prerauer stepped into the role at a moment's notice without a word, so far as I can recall, having been written about her feat.

Bernstein's reading of the orchestral part is also far from refined, with far too much runaway excitement and overblown passion. Strauss' sinister richness of orchestration is swamped by something very close to hysteria. And, for the moment, again reverting to the past, there was Marjorie Lawrence's 78 recordings of great merit, especially when the engineering of the 78 period was considered. She gave a less impressive performance live in the Town Hall with, in the absence of an orchestra, an organ accompaniment (for heaven's sake!).

I cannot imagine Caballe ever growing into a great Salome, but she might with further expert coaching in the role, become a very passable one. At present she is loud and soft in the right places, but I found her quite unmoving. The whole production sounded too like a rehearsal awaiting the conductor's final polish. The orchestra makes a grand row but, except in the soft bars, lacks detailed definition. And emotion is splashed all over the place instead of being concentrated on Salome's deadly purpose.

Oscar Wilde wrote his original play in French and Strauss used an almost word for word German translation of the text. But the French orchestra used by Bernstein sounds a bit alien when confronted by this perfervid, boiling score. Anyone who compares the sound produced by the Vienna Philharmonic in the now oldish, complete Solti version of the opera will immediately recognise the difference.

The songs, too, are uneven in quality, again both vocally and orchestrally. The first, Cecilia, she sings beautifully and never pushes her voice up into an ugly register, though I have heard better accompaniments. The restrained and lovely Lullaby is more tranquil and offers some beguiling soft singing. Moreover, here Bernstein's accompaniment is much more acceptable. And the same might be said of the

evergreen Morgen. In these, the scoring is much more suited to the French temperament of the orchestra. I Love You is a mess, untidy in voice and orchestra, and Caballe again forces her voice unmercifully.

There is a good deal of playing space left on the first side and Bernstein starts the second with the Dance of the Seven Veils, its sound beautifully recorded, but the playing unimpressive. The delicate playing of the flute and other woodwind at the beginning of the first theme is quite delicious, but the music soon starts to lose its ballet-like quality, though plenty of detail is comfortably

audible. And later, a peculiar Massenet-like flavour intrudes.

Bernstein drags the tempo of the big waltz theme for a while in order to mount what he hoped might be an astounding climax, so that the early effect tends to be very ponderous indeed. My impression was that it was taking Salome a long time to get undressed.

Of the songs, I enjoyed best Caballe's superb account of Dedication, with the revised 1940 orchestration under Bernstein really fine. But summing up the whole disc it was not a really good day for anyone — and that includes Strauss.

#### Schubert, Mahler & Ruckert

SCHUBERT — Schwestergruss. Der Zwerg. Ellen's Songs.

MAHLER — Three songs from Des Knaben Wunderhorn.

RUCKERT — Two Lieder. Jessye Norman (soprano) with Irwin Gage (piano). Philips Stereo Disc 6500412.

I shall never forget the effect on me of the first notes sung by Jessye Norman at a recital in the Sydney Concert Hall last year. They were — and I am not exaggerating — electrifying. Uniform from top to bottom of her unusually large range, produced as effortlessly as if she were speaking, and of a quality of such exquisite timbre and purity, that I was absolutely flabbergasted. As her program progressed she presented every aspect of her art and every example of many varied styles, each as perfect as the last.

I thought here must be the voice of the century; and I was mindful of the greatest of them. I might mention that Miss Norman is very large, monumentally so, and very black with a good looking face that establishes at once her intelligence and amiability.

I must however confess, albeit with a good deal of reluctance, that this disc does not give me all the thrill of that first performance. But please don't mistake me, it is still full of some glorious singing. Side 1 is devoted to Schubert songs, the reverse to Mahler items from his Des Knaben Wunderhorn.

The Schubert numbers, except for the Ave Maria, are blessedly unhackneyed. She starts the first, Schustergruss, a tiny bit unsteadily but soon settles down into some ravishing pianissimos that rise to full throated fortissimos which seem to float effortlessly, each bar perfectly phrased. The second, sinister Der Zwerg, is contrasted with a magnificent dramatic sense against the first. Then comes Raste Krieger, a setting of words by Sir Walter Scott, in the form of a berceuse, presented so smoothly that it would soon have the most recalcitrant child asleep.

In the middle come battle scenes of quite extraordinary descriptive power and the song then returns to the tranquil mood of the beginning. Even in this difficult feat she seems never to need to breathe, so naturally do the lovely sounds emerge.

The fourth is a hunting song, complete with horn accompaniment in jaunty rhythm of a true chase. The Ave Maria she sings with an innocence reminiscent of a convent, without any effort at drama or sentimentality. There is something childlike about it that I find irresistably alluring.

On the Mahler side she gets just the right grisly atmosphere into Das Irdischel Leben, the moving story of a starving child. Her eloquent account of Wo Die Schonen Trompeten Blasen captures all Mahler's bitter irony, interspersed with joy.

Urlicht, taken from Mahler's 2nd Symphony, is begun in a quietly mystical mood that swells into a long, shapely lustrous phase before returning to the original mood. All her other items are on the same level of greatness of interpretation and vocal grandeur.

I mentioned at the beginning of this review that I was ever so slightly disappointed with this disc but on reflection I think it was only Miss Norman's presence that I missed. I am sure that in a concert hall I would have enjoyed the recital as much as the one in the Sydney Concert Hall.

I cannot finish this review without a special word of praise for her accompanist, Irwin Gage.

THE "ELECTRONICS AUSTRALIA"

#### LOG BOOK

FOR: RADIO AMATEURS DX LISTENERS CB OPERATORS

\$2.95

From "Electronics Australia", 57-59 Regent St, Sydney OR by mail order from PO Box 163, Beaconsfield 2014. Price includes postage.



#### **Devotional Records**

FINALLY HOME. Sixteen Singing Men, arranged and conducted by Dick Bolks. Stereo, Singcord ZLP-3022S. (From S. John Bacon, 13 Windsor Ave, Waverley, Vic. 3149.)
The jacket credits the program here to "Sixteen Singing Men" but, in all

fairness I must also acknowledge the presence of a significant number of "singing women", some assistance from reverberation, and a sparing but sensitive instrumental backing.

But, ingredients aside, it adds up to some very pleasant choral sound, featuring recent Gospel songs and updated arrangements but performed in a sufficiently traditional style to delight those who are growing weary of the "mod" Gospel sound.

Don't worry if the titles are unfamiliar; they're all highly melodic and diction is excellent: Give Them All To lesus — He Was There All The Time — It Was For You — It Took A Miracle — It Is Finished - Greater Is He That Is In Me - Now Let This Be The Day -All The Time In The World — Learning To Learn - Finally Home.

The recording is clean and well balanced and the sound very smooth. For those who enjoy old-fashioned harmony from a not so old-fashioned group: recommended. (W.N.W.)



THINGS ARE GONNA CHANGE SOME DAY. The Celebration, arranged and directed by Ben Markley. Singcord, Stereo ZLP-3021S. (From S. John Bacon Pty Ltd, 13 Windsor Ave Mount Waverley, Vic. 3149.)
First reaction to the sound on this

recording is a mental picture of a large



reverberant auditorium, with a full orchestra ranged behind the Celebration singing group — all responding to the baton of a dedicated conductor. But, from the jacket, one learns with surprise that the orchestral backing was recorded in Wembley, England under Bob Krogstad; the vocals were added later at Alhambra, California. However, I would defy anyone to pick the fact, so smooth is the blend in terms of both timing and mood. A superb piece of production.

The program, a mix of newer and

older Gospel songs, employs ambitious modern arrangements that should find wide appeal: God Gave The Song Suite — How Rich Am I — Things Are Gonna Change Some Day — O Love That Will Not Let Me Go — When He Shall Come Tis So Sweet The Trust In Jesus — Swing Low, Sweet Chariot — A Country Road — Be Still My Soul And Listen — It Took A Miracle.

The diction is excellent, the vocal work of the highest standard and the orchestral backing highly appropriate. Add a fine recording, as clean as they come, and it adds up to another album that I can thoroughly recommend. (W.N.W.)

FOREVER HIS, BETSY OHMAN Milk & Honey MHI006. Distributed by S. John Bacon Pty Ltd, P.O. Box 345 Mt

Waverley 3149. The record jacket tells us that Betsy Ohman is a new voice on the Gospel music scene and, if this disc is any guide, further appearances will be most

Her voice is strong and true, with clear enunciation, so you don't miss a word of the ten tracks: There's Something In The Air — I'll Never Be The Same Again — Sweet Song Of Salvation — Take The World But Give Me Jesus — Oh How I Love Jesus — All Your Anxiety — This Little Light Of Mine - The Blood Will Never Lose Its Power — Thank You Saviour — Shepherd Of Love.

The tempo varies from Rock to soft ballad, with a patch of Boogie piano thrown in. The backing group, all listed on the jacket, give an excellent account of themselves. Recommended for youth group listening. (N.J.M.)

#### Instrumental, Vocal and Humour

KEEP MUSIC ALIVE. Tchaikovsky & Wagner with the Sydney Symphony Orchestra. HMV stereo SMP 0040.

This odd record is the outcome of a promotional concert staged by the Sydney Symphony Orchestra with the theme "Keep Music Alive". According to the sleeve notes the concert was the S.S.O.'s "answer to various suggestions that symphony orchestras may lack relevance to the present age and belong to an elite group". That is probably correct.

The two works recorded are the prelude to the "Mastersingers of Nuremburg" by Wagner conducted by Sir Bernard Heinze and Symphony No. 5 in E Minor by Tchaikovsky, conducted by John Hopkins. These are both enjoyable works although quite different in nature. But they do not seem to be the most appropriate works for

promoting the performance of classical music - more like preaching to the converted.

To me, if the Sydney Symphony Orchestra, the ABC and EMI (Australia) Ltd are really interested in keeping music alive, then they will have to use more imagination than this record gives evidence of. I hope many buy this record but in the clamour of the marketplace I think it may be missed. (L.D.S.)

☆ MANTOVANI TODAY. World Record WRC R 05080.

Originally released on Decca, this disc from Mantovani gives the usual polished performance one expects from this man and his orchestra. In other words a very enjoyable disc, either as background or to listen to for its own sake.

Judging by the fourteen titles, the original release would have been a few

#### THE LIGHTER SIDE — continued

years ago: Leaving On A Jet Plane — Midnight Cowboy — Up Up And Away — The Windmills Of Your Mind Lemon Tree - Wand'rin Star -Theme From 'The Virginian' — Where Is Love - I'll Never Fall In Love Again Aquarius — Deserted Shore — Good Morning Starshine — Mozart Piano Theme from 'Elvira Madigan' — My

The quality and stereo image are excellent. (N.J.M.)

#### GRACEFUL YEARS, Palm Court Orchestra. ASH BGLP 1002. Astor release.

The name "Palm Court Orchestra" brings visions of cups of tea and cucumber sandwiches, reminiscent of a more leisurely style of living for those that could afford it.

The fourteen old-style dance tunes relate to the second decade of this century and no one alive in those days could escape a pang of nostalgia to hear them again, particularly played in such a pleasing manner as on this disc.

A few of the titles: The Pink Lady -Mighty Lak'a Rose — Lady Of The Lake Vision Of Salome - Desir Du Moment - The Whirl Of The Waltz - Ragtime Cowboy Joe. Give the record a listen, it will grow on you. (N.J.M.)

#### YOU LIGHT UP MY LIFE. The Magic Organ. Stereo, Interfusion L-25314.

Festival release. Having started off eight or more albums back, with the simulated sounds of a fairground organ, the Magic Organ seems gradually to have moved to a straight-out strict tempo formula appropriate for dancing or party games. Be that as it may, the "magic organist" Jerry Smith seems to have acquired a fan club whose address in Nashville, Tennessee, is given on the jacket.

The titles on this album include: Chatanooga Choo Choo — You Light Up My Life — Southern Nights — Don't It Make My Brown Eyes Blue American Patrol — King Tut Polka — Blue Eyes Crying In The Rain — Heartaches — Wonderland World — Lucille — Joplin Junction.

The recording quality is clean which isn't surprising, considering that the dynamics are as rigidly controlled as the

tempo. (W.N.W.)

#### THE MILLS BROTHERS. A Collection of Golden Performances. Stereo, ABC Records, ABCA 30022. RCA release.

I must confess to being initially puzzled by this ABC release. The colour and styling of the jacket, the pen drawing of four relatively young men, and

the notes which recall their prominence in the early thirties, all suggest a re-release of their early recordings. Compounding this is the omission of any reference to stereo or

stereo re-processing.

But it is immediately obvious that the recordings are indeed in stereo, which either had to mean a much more recent origin or, less likely, some very smart over-dubbing with a new stereo backing. I'll settle for the former, because of the clean quality and freedom from background noise.

But, that aside, you get a generous program of eighteen songs, mainly in close harmony, with bright instrumental backing. Here's a sampling of the titles: Glow Worm - Chanson D'Amour — Standing On The Corner Moon River — The Jones Boy — Lazy River - Canadian Sunset - My Shy Violet — I'll Be Around — Paper Doll.



#### OKLAHOMA. Motion Picture Soundtrack. Stereo, World Record Club, WRC R-04666.

When the film was shown recently on television, someone remarked to me that they found the songs somewhat less satisfying than when presented by present-day top line artists. Perhaps one could argue along these lines but that doesn't mean that there's much to complain about, really, in the performances of Gordon MacRae, Shirley Jones, Charlotte Greenwood and others of the original cast. And, heard in full stereo, the orchestra is fine.

The 12 tracks are as follows: Overture - Oh, What A Beautiful Morning — The Surrey With The Fringe On Top — Kansas City — I Cain't Say No — Many A New Day — People Will Say We're In Love — Poor Jud Is Dead — Out Of My Dreams — The Farmer And The Cowman — All Er Nothin' — Oklahoma.

If you saw the film in the theatre or on TV, this album will be enjoyed as a reprise. Even if you didn't see the film, the music of this well known Rogers and Hammerstein musical is very easy to take, with its blend of melody, rhythm and humour. A good one. (W.N.W.)

If you're old enough to remember the Mills Brothers in their heyday, - or if you've since grown to like their style you'll have no difficulty in enjoying this piece of nostalgia. (W.N.W.)

#### LARRY GATLIN, OH BROTHER Monument L 36655 Festival release.

Larry Gatlin comes from a family background of Gospel and country music and this reflects in this album of his own songs, recorded in places as widespread as London, Los Angeles and Nashville.

The ten tracks are: Do It Again Tonight — I've Done Enough Dying Today — L.A. You're A Killer — I've Got You — Standin' By Me — Night Time Magic - You Happened To Me -Nothin' You Do — Cold Day In Hell — Everything I Know About Cheatin'.

His diction leaves nothing to be desired, so there is no problem following the lyrics. I think this is a talent we will see more of in the future. (N.J.M.)

#### QUINCY JONES, SOUNDS. A&M L36551. Festival release.

Quite a mixture from Quincy lones and his crew on this, ranging from disco

to protest and songs of empty love.
There are seven lengthy tracks: Stuff Like That — I'm Gonna Miss You In The Morning — Love, I Never Had It So Good — Tell Me A Bedtime Story — Love Me By My Name — Superwoman Takin' It To The Streets.

The credits on the inner sleeve look like a "Who's Who" of today's musical talent in terms of session musicians and the technical excellence of the whole deal make an exciting record to listen to. (N.J.M.)

#### **MOVIE FEVER, ENOCH LIGHT. Project** 3 L 36634 Festival release.

If you like your movie themes with olenty of disco flavour, give this disc a hearing, with ten themes from recent and current movies: Rocky - Close Encounters Of The Third Kind - The Goodbye Girl — Star Wars — Saturday Night Fever — A Star Is Born — The One And Only — You Light Up My Life.

The disc bears the usual Enoch Light stamp of very high technical quality, with skillful use of the stereo stage. (N.J.M.)

#### BRUCE COCKBURN, Circles In The Stream. Interfusion L70091/2. Festival release.

I had never heard of Bruce Cockburn before this record, more the pity as he produces some excellent music in the folk idiom. If this double album, recorded in Toronto is a true sample I feel sure he will soon have a following out here. There are seventeen titles, with the lyrics in French and English on the sleeves: The Pipes, The Pipes — Star

Wheel — Never So Free — Deer Dancing Round A Broken Mirror — Homme Brulant — Free To Be — Mama Just Wants To Barrelhouse All Night Long — Caderidris — Arrows Of Light — One Day I Walk — Love Song — Red Brother Red Sister — Lord Of The Star Fields — All The Diamonds In The World — Dialogue With The Devil — Joy Will Find A Way — God Bless The Children.

The instrumental treatment is unusual, with Oriental overtones. In all, an album that grows on one. (N.J.M.)

4 4

#### THREE'S A CROWD. The trio. Batjazz BAT2068. RCA release.

George Golla is no stranger to the local music scene and on this outstanding record gets together with Tony Ansell (keyboards and percussion), Stuart Livingston (Vibes, drums and percussion), Doug Gallacher (percussion) and Janice Slater (vocals).

Three of the ten tracks: Time After Time — Solitude — Play Off — are recorded direct to a two track master without any pre-mixing, and the effect is quite startling; you are really there in the middle, the sound is so "live".

The other tracks are not far behind in quality. They are: Feelin' Feline — Good Times Passing — Too Marvellous For Words — How Insensitive — But Beautiful — Minha Saudade — Night Moyes

Janice Slater's vocals on "How Insensitive" and "Night Moves" are a pleasure to listen to but I'm still puzzled by the last track "Play Off"; it lasts only 25 seconds.

To sum up, superb local jazz. (N.J.M.)

4 4 4

## THE GLORY THAT WAS GERSHWIN. Frank Chacksfield & His Orchestra. Stereo, World Record Club WRCP. 03218

Featuring the big, dynamic orchestra of Frank Chacksfield and the compelling music of Gershwin, this is very much an album to be listened to, rather than treated as background music.

There are nine tracks altogether:
"Porgy & Bess" Introduction; I Got
Rhythm — The Man I Love — Embraceable You — Rhapsody In Blue —
Fascinatin' Rhythm — But Not For Me
— Strike Up The Band — Liza — Suite
From "Porgy & Bess".

Released originally by Decca, the recording is clean and well balanced, with the strongest potential appeal to those who prefer something more distinctive than the soft lights and sweet music kind of sound. (W.N.W.)

4 4 4

#### THE BEST OF ENOCH LIGHT. Project 3 L458II/12 Festival release.

Enoch Light Fans have a feast in this double album of the best tracks he has put down with his Orchestra over re-

History according to Borge!

VICTOR BORGE in Excerpts from "My Favourite Intervals". Stereo, 2-record set, Astor NSPD-502. \$8.95. (Also available on cassette.)

Introducing this double album, Kenneth Robinson, broadcaster and writer for "Punch", describes Victor Borge as "the funniest man I've ever come across". And, indeed, Borge can be transparently funny at the keyboard, in ways which Kenneth Robinson enlarges upon in his notes.

But the humour is of a quite different character in this recording, which is composed essentially of readings from Borge's book "My Favourite Intervals".

One at a time, he nominates various famous composers, explains when and where they lived and uses a brief — and usually brilliant — orchestral snippet as an example of their work. Then follows the Borge version of their life story, a mixture of fact, fancy, whimsy and more miniscule musical segments.

Composers who receive the treat-



ment are Bach, Beethoven, Handel, Mozart, Offenbach and Rossini. If you're well up on your classical literature, you'll know when to nod, when to raise your eyebrows, when to titter and when to guffaw out loud. Come to think of it, I might send this one on to Julian Russell, so that he can speak for the classical music buffs to whom it is directed. (W.N.W.)

cent years, twenty two in all.

Here are some of them: April In Portugal — Light My Fire — Marrakesh Express — With A Little Help From My Friends — What A Difference A Day Makes — Alfie — The Windmills Of Your Mind — Hey Jude — People Got To Be Free — My Foolish Heart — Help

Yourself.

Some of the solo artists featured include Tony Mottola, Stan Freeman and Doc Severinsen. Enoch Light's well known technical expertise in the recording field is well to the fore in the quality department, making a record well worth keeping. (N.J.M.)

## A POSITION ON OUR TECHNICAL STAFF ...

#### It could be yours:

- If you have a sound all-round knowledge of electronics, with special emphasis on digital techniques, microprocessors, etc.
- If you have the practical approach, and the ability to conceive, design, build and test projects of the kind featured regularly in this magazine.
- If your involvement with electronics extends to a personal, hobby level, paralleling that of a typical reader of "Electronics Australia".
- If you have a proven ability to write well organised, easyto-read prose, substantially free from spelling and grammatical errors.

For a suitable applicant, this would be a permanent position, carrying full leave, sickness and superannuation benefits. He/she must be free to take up duties in our Sydney office during March at the latest. Salary, by negotiation, in the range \$11,000 to \$13,600 and subject to cost of living adjustments.

Application must be by letter only and should include a statement of qualifications and experience, references, and any available examples of articles or essays. Address your application to: The Editor-in-Chief, "Electronics Australia", PO Box 163, Beaconsfield 2014.

## Australian and NZ Broadcasting Services

#### **Australian Medium Wave Stations**

1.11-	0-11	1 41	-	144				-	104					
kHz	Call		туре	Watts	kHz	Call	Location	Type	Watts	kHz	Call	Location	Туре	Watts
531	2KM	Kempsey	С	2k		5RM	Renmark	C	2k	1044	2UH	Muswellbrook	n	1k
	3UL	Warragul	С	2k	810	2BA	Bega	n	10k		5PI	Crystal Brook	С	2k
	4KZ	Innisfail-Tully	С	5k		6WN	Perth	n	10k		4WP	Weipa	n	500
	6DL	Dalwallinu	n	10k	819	2GL	Glen Innes	n	10k	1053	2CA	Canberra	С	5k
540	4QL	Longreach	n	10k	828	3GI	Sale	n	10k	1071	3CV	Maryborough	С	5k
	7SD	Scottsdale	С	5k		6GN	Geraldton	n	2k		4SB	Kingaroy	С	2k
549	2CR	Orange	n	50k		4NA	Nambour	С	5k		6WB	Katanning	С	2k
558	4GY	Gympie	С	2k	837	4RK	Rockhampton	n	10k	1080	2MO	Gunnedah <sup>1</sup>	C	2k
	4AM	Atherton	C	5k		6ED	Esperance	n	1k	.000	4MI	Mount Isa	n	200
	6WA	Wagin	n	50k		7QT	Queenstown	c	500			Perth	C	2k
	7BU	Burnie	C	2k		3CR	Melbourne	C	250		7HT	Hobart		
567	2BH	Broken Hill	C	500	846	2CY	Canberra		10k	1089			С	2k
007	4JK	Julia Creek	n	10k	040	4CA	Cairns	n	2k	1009	2GZ	Orange	С	2k
	6MN	Mount Newmai		100		6CA		C		1000		Horsham	С	2k
576	2FC			50k	055		Carnarvon	n	200	1098	4LG	Longreach	С	2k
		Sydney	n		855	4QB	Maryborough	n	10k		6MD	Merredin	С	2k
594	3WV	Horsham	n	50k	004	400	Eidsvold	n	10k		7LA	Launceston	С	2k
603	6PH	Port Hedland	n	2k	864	4GR	Toowoomba	С	2k	1107	2UW	Sydney	С	5k
040	7ZL	Hobart	n	10k		6AM	Northam	С	2k	1116	3EA	Melbourne	е	500
612	6NM	Northam	n	200		7H0	Hobart	С	2k		4BC	Brisbane	С	5k
	4QR	Brisbane	n	50k	873	2GB	Sydney	С	5k	1134	2AD	Armidale	С	2k
621	3AR	Melbourne	n	50k		6DB	Derby	n	2k		3CS	Colac	С	2k
630	4QN	Townsville	n	50k	882	3YB	Warrnambool	С	2k		6CI	Collie	С	2k
	7QN	Queenstown	n	400		6PR	Perth	С	2k	1143	2HD	Newcastle	С	2k
	6AL	Albany	n	400		4BH	Brisbane	С	5k	1152	2WG	Wagga	С	2k
639	5CK	Port Pirie	n	10k	891	5AN	Adelaide	n	50k	1161	4MB	Maryborough	С	2k
	4MS	Mossman	n	1k	900	2LM	Lismore	С	2k	1	5PA	Naracoorte	n	10k
648	2NU	Tamworth	n	10k		6BY	Bridgetown	С	2k		7FG	Fingal	n	1k
	6GF	Kalgoorlie	n	2k		7AD	Devonport <sup>1</sup>	С	2k	1170	2CH	Sydney	С	5k
657	2BY	Byrock	n	10k		8HA	Alice Springs	С	2k		4GC	Charters Towers	С	2k
	8DR	Darwin	n	2k	918	2XL	Cooma <sup>1</sup>	С	2k	1179	3KZ	Melbourne	С	5k
675	2CO	Albury	n	10k		4VL	Charleville <sup>1</sup>	С	2k	1188	2NZ	Inverell	С	2k
	6BE	Broome	n	50		6NA	Narrogin	С	2k		6XM	Exmouth	n	2k
	8KN	Katherine	n	50	927	3UZ	Melbourne	C	5k	1197	4GG	Gold Coast	С	2k
684	2KP	Kempsey	n	10k		4CD	Biloela	C	0		5KA	Adelaide	C	2k
	6BS	Busselton	n	4k			(Translator)			1206	2GF	Grafton	С	2k
	8TC	Tennant Creek	n	1k		4CD	Gladstone	С	2k	.200	6KY	Perth	C	2k
693	4KQ	Brisbane	С	5k		6NR	Perth	ŭ			2CC	Canberra	c	5k
	5SY	Streaky Bay	n	2k	936	4AY	Ayr	С	5k	1224	2WS	Sydney	C	5k
702	2BL	Sydney	n	50k	000	7ZR	Hobart	n	10k	1233	2NC	Newcastle	n	10k
711		St George	n	10k	945	3BO	Bendigo	C	21	1242	3TR	Sale	C	2k
	7NT	Launceston	n	10k	954	2UE	Sydney	C	51	1242	8DN	Darwin	C	2k
720	2ML	Murwillumbah	n	400	963	6TZ	Bunbury	C	2k	1242	5AU	Port Augusta		2k
		Atherton	n	4k	303		Warwick		5k	1272	4AK		С	
	6WF	Perth	n	50k		2RG	Griffith <sup>1</sup>	C	2k	1251	2DU	Oakey Dubbo	С	2k
	3MT	Omeo	n	2k	972		Murwillumbah		2k	1260			С	2k
		Armidale	n	50	3/2	5DN		С		1260	3SR	Shepparton	С	2k
729		Adelaide		50k	981		Adelaide	С	2k	1260	6KA	Karratha		-
738		Grafton	n	50k	301	3HA	Hamilton	С	2k	1269		Sydney	С	5k
747		Toowoomba	n	10k	001	4RO	Rockhampton	С	2k	1278		Melbourne	С	5k
756		Mackay			981	6KG	Kalgoorlie	С	2k	1287		Tamworth	С	2k
750		Kununurra	n	2k 100	990	8G0	Gove	n	500	1296	4BK	Brisbane	С	5k
		Taree	n		000	6PM	Perth	С	2k	1011	5SE	Mount Gambier	С	2k
765			n	2k	999	2NB	Broken, Hill	n	2k	1314	ЗВА	Ballarat	С	5k
705	2BE 2BE	Bega <sup>1</sup> Moruya	C	2k	4000	2ST	Nowra	С	5k	1000		Wollongong	С	2k
	200		С	500	1008	2XX	Canberra		300	1323		Adelaide	С	2k
774	21.0	(Translator)		501		4IP	Ipswich	С	5k			Gosford	С	2k
774		Melbourne	n	50k		6GE	Geraldton	С	2k	1332	3SH	Swan Hill	C	2k
783		Townsville	С	780		7EX	Launceston	С	2k	1 1000		Bundaberg	С	2k
		Katoomba	С	2k	1017	2KY	Sydney	С	5k	1341	2NX	Bolwarra	С	2k
700		Albany	С	2k			Wyndham	С	100			(Newcastle)		
792		Brisbane	n	10k	1026	3DB	Melbourne	С	5k	1350		Geelong	С	2k
801		Sydney	е	500			Mackay	С	5k	1359		Young	С	2k
	4QY		n	2k		6NW	Port Hedland			1368	4LM	Mount Isa	С	2k
92	ELE	CTRONICS Aus	tralia	, Janua	ry, 1979									

Call	Location	Туре	Watts	kHz	Call	Location	Туре	Watts	kHz	Call	Location	Туре	Watts
2GN	Goulburn	C	2k	1476	4ZR	Roma <sup>1</sup>	С	2k	1557	2RE	Taree	C	2k
3MP	Melbourne	С	5k		2KA	Penrith	С	2k	1566	4GM	Gympie	n	200
8AL	Alice Springs	n	200			(Translator)				3NE	Wangaratta	C	2k
5AA	Adelaide	С	5k	1485	2LG	Lithgow	n	200	1575	200	Wollongong	С	
2LT	Lithgow	С	500		4HU	Hughenden	- n	50	1584	5MG	Mount Gambier	r n	200
- 2PK	Parkes	С	2k		5LN	Port Lincoln	· n	200		5WM	Woomera	n	50
2KO	Newcastle	С	2k	1494	2AY	Albury	С	2k		7SH	St Helens	n	100
3XY	Melbourne	С	5k	1503	2BS	Bathurst <sup>1</sup>	С	5k		2WA	Wilcannia	n	100
2WN	Wollongong	n	2k		3AK	Melbourne	С	5k	1593	450	Southport	n	200
2CN	Canberra	n	2k	1512	2NA	Newcastle	n	10k		5MV	Renmark	n	2k
2MG	Mudgee	С	2k	1521	2QN	Deniliquin	С	2k	1602	2CP	Cooma	n	50
2NM	Muswellbrook <sup>1</sup>	С	2k	1530	2VM	Moree	C	2k		3WL	Warrnambool	n	200
5MU	Murray Bridge	1 C	2k	1539	2JJ	Sydney	n	10k		5LC	Leigh Creek	n	50
3MA	Mildura	С	2k	1548	4QD	Emerald	n	50k		2CT	Campbelltown	С	100
	2GN 3MP 8AL 5AA 2LT 2PK 2KO 3XY 2WN 2CN 2MG 2NM 5MU	2GN Goulburn 3MP Melbourne 8AL Alice Springs 5AA Adelaide 2LT Lithgow 2PK Parkes 2KO Newcastle 3XY Melbourne 2WN Wollongong 2CN Canberra 2MG Mudgee 2NM Muswellbrook 5MU Murray Bridge	2GN Goulburn c 3MP Melbourne c 8AL Alice Springs n 5AA Adelaide c 2LT Lithgow c 2PK Parkes c 2KO Newcastle c 3XY Melbourne c 2WN Wollongong n 2CN Canberra n 2MG Mudgee c 2NM Muswellbrook¹ c 5MU Murray Bridge¹ c	2GN Goulburn c 2k 3MP Melbourne c 5k 8AL Alice Springs n 200 5AA Adelaide c 5k 2LT Lithgow c 500 2PK Parkes c 2k 2KO Newcastle c 2k 3XY Melbourne c 5k 2WN Wollongong n 2k 2CN Canberra n 2k 2MG Mudgee c 2k 3MU Muswellbrook¹ c 2k 5MU Murray Bridge¹ c 2k	2GN         Goulburn         c         2k         1476           3MP         Melbourne         c         5k         8AL           8AL         Alice Springs         n         200         5AA         Adelaide         c         5k         1485           2LT         Lithgow         c         500         2FK         Parkes         c         2k           2KO         Newcastle         c         2k         1494           3XY         Melbourne         c         5k         1503           2WN         Wollongong         n         2k         1512           2MG         Mudgee         c         2k         1521           2NM         Muswellbrook¹         c         2k         1530           5MU         Murray         Bridge¹         c         2k         1539	2GN         Goulburn         c         2k         1476         4ZR           3MP         Melbourne         c         5k         2KA           8AL         Alice Springs         n         200           5AA         Adelaide         c         5k         1485         2LG           2LT         Lithgow         c         500         4HU           2PK         Parkes         c         2k         5LN           2KO         Newcastle         c         2k         1494         2AY           3XY         Melbourne         c         5k         1503         2BS           2WN         Wollongong         n         2k         3AK           2CN         Canberra         n         2k         1512         2NA           2MG         Mudgee         c         2k         1530         2VM           5MU         Murray         Bridge¹         c         2k         1539         2JJ           3MA         Mildura         c         2k         1548         4QD	2GN Goulburn c 2k 1476 4ZR Roma¹ 3MP Melbourne c 5k 2KA Penrith 8AL Alice Springs n 200 (Translator) 5AA Adelaide c 5k 1485 2LG Lithgow 2LT Lithgow c 500 4HU Hughenden 2PK Parkes c 2k 5LN Port Lincoln 2KO Newcastle c 2k 1494 2AY Albury 3XY Melbourne c 5k 1503 2BS Bathurst¹ 2WN Wollongong n 2k 3AK Melbourne 2CN Canberra n 2k 1512 2NA Newcastle 2MG Mudgee c 2k 1521 2QN Deniliquin 2NM Muswellbrook¹ c 2k 1530 2VM Moree 5MU Murray Bridge¹ c 2k 1539 2JJ Sydney 3MA Mildura c 2k 1548 4QD Emerald	2GN         Goulburn         c         2k         1476         4ZR         Roma¹         c           3MP         Melbourne         c         5k         2KA         Penrith         c           8AL         Alice Springs         n         200         (Translator)         (Translator)           5AA         Adelaide         c         5k         1485         2LG         Lithgow         n           2LT         Lithgow         c         500         4HU         Hughenden         n           2PK         Parkes         c         2k         5LN         Port Lincoln         n           2KO         Newcastle         c         2k         1494         2AY         Albury         c           3XY         Melbourne         c         5k         1503         2BS         Bathurst¹         c           2WN         Wollongong         n         2k         1512         2NA         Newcastle         n           2MG         Mudgee         c         2k         1521         2QN         Deniliquin         c           2MW         Muswellbrook¹         c         2k         1539         2JJ         Sydney         n	2GN         Goulburn         c         2k         1476         4ZR         Roma¹         c         2k           3MP         Melbourne         c         5k         2KA         Penrith         c         2k           8AL         Alice Springs         n         200         (Translator)         (Translator)         c         2k           5AA         Adelaide         c         5k         1485         2LG         Lithgow         n         200           2LT         Lithgow         c         500         4HU         Hughenden         n         50           2PK         Parkes         c         2k         5LN         Port Lincoln         n         200           2KO         Newcastle         c         2k         1494         2AY         Albury         c         2k           3XY         Melbourne         c         5k         1503         2BS         Bathurst¹         c         5k           2WN         Wollongong         n         2k         3AK         Melbourne         c         5k           2CN         Canberra         n         2k         1512         2NA         Newcastle         n         10k <td>2GN Goulburn         c         2k         1476         4ZR         Roma¹         c         2k         1557           3MP Melbourne         c         5k         2KA         Penrith         c         2k         1566           8AL Alice Springs         n         200         (Translator)         (Translator)         1566           5AA Adelaide         c         5k         1485         2LG         Lithgow         n         200         1575           2LT Lithgow         c         500         4HU         Hughenden         n         50         1584           2PK Parkes         c         2k         5LN         Port Lincoln         n         200           2KO Newcastle         c         2k         1494         2AY         Albury         c         2k           3XY Melbourne         c         5k         1503         2BS         Bathurst¹         c         5k           2WN Wollongong         n         2k         3AK         Melbourne         c         5k         1593           2CN Canberra         n         2k         1521         2N         Newcastle         n         10k           2MG Mudgee         c         2k</td> <td>2GN Goulburn         c         2k         1476         4ZR         Roma¹         c         2k         1557         2RE           3MP Melbourne         c         5k         2KA         Penrith         c         2k         1566         4GM           8AL Alice Springs         n         200         (Translator)         3NE           5AA Adelaide         c         5k         1485         2LG Lithgow         n         200         1575         200           2LT Lithgow         c         500         4HU Hughenden         n         50         1584         5MG           2PK Parkes         c         2k         5LN Port Lincoln         n         200         5WM           2KO Newcastle         c         2k         1494         2AY Albury         c         2k         7SH           3XY Melbourne         c         5k         1503         2BS Bathurst¹         c         5k         2WA           2WN Wollongong         n         2k         3AK Melbourne         c         5k         1593         4SO           2CN Canberra         n         2k         1521         2NA Newcastle         n         10k         5MV           2MG Mudgee</td> <td>2GN         Goulburn         c         2k         1476         4ZR         Roma¹         c         2k         1557         2RE         Taree           3MP         Melbourne         c         5k         2KA         Penrith         c         2k         1566         4GM         Gympie           8AL         Alice Springs         n         200         (Translator)         3NE         Wangaratta           5AA         Adelaide         c         5k         1485         2LG         Lithgow         n         200         1575         200         Wollongong           2LT         Lithgow         c         500         4HU         Hughenden         n         50         1584         5MG         Mount Gambiel           2PK         Parkes         c         2k         5LN         Port Lincoln         n         200         5WM         Woomera           2KO         Newcastle         c         2k         1494         2AY         Albury         c         2k         7SH         St Helens           3XY         Melbourne         c         5k         1503         2BS         Bathurst¹         c         5k         2WA         Wilcannia      <tr< td=""><td>2GN Goulburn         c         2k         1476         4ZR         Roma¹         c         2k         1557         2RE         Taree         c           3MP Melbourne         c         5k         2KA         Penrith         c         2k         1566         4GM         Gympie         n           8AL Alice Springs         n         200         (Translator)         3NE         Wangaratta         c           5AA Adelaide         c         5k         1485         2LG         Lithgow         n         200         1575         200         Wollongong         c           2LT Lithgow         c         500         4HU Hughenden         n         50         1584         5MG         Mount Gambier         n           2PK Parkes         c         2k         1494         2AY         Albury         c         2k         7SH         5MM         Woomera         n           2KO Newcastle         c         2k         1494         2AY         Albury         c         2k         7SH         St Helens         n           3XY Melbourne         c         5k         1503         2BS         Bathurst¹         c         5k         2WA         Wilcannia</td></tr<></td>	2GN Goulburn         c         2k         1476         4ZR         Roma¹         c         2k         1557           3MP Melbourne         c         5k         2KA         Penrith         c         2k         1566           8AL Alice Springs         n         200         (Translator)         (Translator)         1566           5AA Adelaide         c         5k         1485         2LG         Lithgow         n         200         1575           2LT Lithgow         c         500         4HU         Hughenden         n         50         1584           2PK Parkes         c         2k         5LN         Port Lincoln         n         200           2KO Newcastle         c         2k         1494         2AY         Albury         c         2k           3XY Melbourne         c         5k         1503         2BS         Bathurst¹         c         5k           2WN Wollongong         n         2k         3AK         Melbourne         c         5k         1593           2CN Canberra         n         2k         1521         2N         Newcastle         n         10k           2MG Mudgee         c         2k	2GN Goulburn         c         2k         1476         4ZR         Roma¹         c         2k         1557         2RE           3MP Melbourne         c         5k         2KA         Penrith         c         2k         1566         4GM           8AL Alice Springs         n         200         (Translator)         3NE           5AA Adelaide         c         5k         1485         2LG Lithgow         n         200         1575         200           2LT Lithgow         c         500         4HU Hughenden         n         50         1584         5MG           2PK Parkes         c         2k         5LN Port Lincoln         n         200         5WM           2KO Newcastle         c         2k         1494         2AY Albury         c         2k         7SH           3XY Melbourne         c         5k         1503         2BS Bathurst¹         c         5k         2WA           2WN Wollongong         n         2k         3AK Melbourne         c         5k         1593         4SO           2CN Canberra         n         2k         1521         2NA Newcastle         n         10k         5MV           2MG Mudgee	2GN         Goulburn         c         2k         1476         4ZR         Roma¹         c         2k         1557         2RE         Taree           3MP         Melbourne         c         5k         2KA         Penrith         c         2k         1566         4GM         Gympie           8AL         Alice Springs         n         200         (Translator)         3NE         Wangaratta           5AA         Adelaide         c         5k         1485         2LG         Lithgow         n         200         1575         200         Wollongong           2LT         Lithgow         c         500         4HU         Hughenden         n         50         1584         5MG         Mount Gambiel           2PK         Parkes         c         2k         5LN         Port Lincoln         n         200         5WM         Woomera           2KO         Newcastle         c         2k         1494         2AY         Albury         c         2k         7SH         St Helens           3XY         Melbourne         c         5k         1503         2BS         Bathurst¹         c         5k         2WA         Wilcannia <tr< td=""><td>2GN Goulburn         c         2k         1476         4ZR         Roma¹         c         2k         1557         2RE         Taree         c           3MP Melbourne         c         5k         2KA         Penrith         c         2k         1566         4GM         Gympie         n           8AL Alice Springs         n         200         (Translator)         3NE         Wangaratta         c           5AA Adelaide         c         5k         1485         2LG         Lithgow         n         200         1575         200         Wollongong         c           2LT Lithgow         c         500         4HU Hughenden         n         50         1584         5MG         Mount Gambier         n           2PK Parkes         c         2k         1494         2AY         Albury         c         2k         7SH         5MM         Woomera         n           2KO Newcastle         c         2k         1494         2AY         Albury         c         2k         7SH         St Helens         n           3XY Melbourne         c         5k         1503         2BS         Bathurst¹         c         5k         2WA         Wilcannia</td></tr<>	2GN Goulburn         c         2k         1476         4ZR         Roma¹         c         2k         1557         2RE         Taree         c           3MP Melbourne         c         5k         2KA         Penrith         c         2k         1566         4GM         Gympie         n           8AL Alice Springs         n         200         (Translator)         3NE         Wangaratta         c           5AA Adelaide         c         5k         1485         2LG         Lithgow         n         200         1575         200         Wollongong         c           2LT Lithgow         c         500         4HU Hughenden         n         50         1584         5MG         Mount Gambier         n           2PK Parkes         c         2k         1494         2AY         Albury         c         2k         7SH         5MM         Woomera         n           2KO Newcastle         c         2k         1494         2AY         Albury         c         2k         7SH         St Helens         n           3XY Melbourne         c         5k         1503         2BS         Bathurst¹         c         5k         2WA         Wilcannia

c commercial broadcasting station; n national broadcasting station; e ethnic; 2 New South Wales and the Australian Capital Territory; 3 Victoria; 4 Queensland; 5 South Australia; 6 Western Australia; 7 Tasmania; 8 Northern Territory.

#### **Australian Frequency Modulation Stations**

MHz	Call	Location	Watts	Polarity	Operator
92.1	7CAE-FM	Hobart	1k	Н	Tasmanian College of Advanced Education
	6UWA-FM	Perth	5k	H or M	University of Western Australia
	ABC-FM	Adelaide	50k	Н	Australian Broadcasting Commission
92.3	2ARM-FM	Armidale	0.1k	M	University of New England
	2MCE-FM	Bathurst	1.6k	V	Mitchell College of Advanced Education
92.5	2NCR-FM	Lismore	1.5k	H or M	Northern Rivers College of Advanced Education
92,9	ABC-FM	Sydney	50k	Н	Australian Broadcasting Commission
93.7	3MBS-FM	Melbourne	10k	H	Music Broadcasting Society of Victoria
101.9	ABC-FM	Canberra	50k	V	Australian Broadcasting Commission
102.1	4ZZZ-FM	Brisbane	5k-10k	H or M	Creative Broadcasters Limited
102.5	2MBS-FM	Sydney	10k	Н	Music Broadcasting Society of New South Wales
102.7	3RRR-FM	Melbourne	3k	Н	Royal Melbourne Institute of Technology
103.5	2CBA-FM	Sydney	_	<u>·</u>	Christian Broadcasting Association
	3GCR-FM	Churchill	1k	M	Gippsland Institute of Advanced Education
103:9	2NUR-FM	Newcastle	3k	C	University of Newcastle
105.7	ABC-FM	Melbourne	50k	Н	Australian Broadcasting Commission
107.5		Sydney		-	Macquarie University & NNSW Institute of Technolog
_		Melbourne	- 01		Progressive Broadcasting Service
	3GCR-FM	La Trobe Valley	-	_	Gippsland Community Radio Society
	_	Brisbane		_	Creative Broadcasters Limited
_	4MBS-FM	Brisbane	_		Music Broadcasting Society of Queensland
_	4DDB-FM	Toowoomba		Per	Darling Downs Broadcasting Society
_	_	Adelaide	_ ~	_	Progressive Music Broadcasting Association
_	_	Adelaide	_	_	Ethnic Broadcasters
_	6UVS-FM	Perth	- 2	_	University of Western Australia
_		Newman			Newman Community Radio
	7HFC-FM	Hobart		_	Hope Foundation Limited

The polarity of the transmission is indicated with C-circular; H-horizontal; V-vertical; M-mixed

#### **New Zealand Medium Wave Stations**

khz	Call	Location	Watts	kHz	Call	Location	Watts	kHz	Call	Location	Watts
567	2YA	Wellington	100k	954	1XW	Hamilton	2k	1260	3XA	Christchurch	2k
630	2YZ	Орара	20k	963	3YC	Christchurch	10k	1278	2ZC	Napier	2k
639	4YW	Alexandra	2k	981	1YE	Kaikohe	2k	1296	1ZH	Hamilton	2k
657	2YC	Wellington	60k	1008	1ZD	Paengaroa	10k	1314	2YW	Gisborne	2k
675	3YA	Christchurch	20k	1026	1ZK	Kaitaia	2k	1323	3ZM	Christchurch	2k
720	4YZ	Invercargill	20k		1ZN	Whangarei	2k	1332	1XI	Auckland	5k
747	3ZA	Kumara	2k	1035	2ZB	Wellington	20k	1341	2ZN	Nelson	2k
756	1YA	Auckland	20k	1044	4ZB	Dunedin	10k	1350	1ZC	Rotorua	2k
765	2ZK	Hastings	2.5k	1053	2ZP	New Plymouth	2k	1386	1ZT	Turangi	100
783	2YB	Wellington	20k	1080	1ZB	Auckland	10k	1413	1ZO	Tokoroa	2k
810	4YA	Dunedin	20k	1098	3ZB	Christchurch	10k				
819	1YZ	Paengaroa	10k	1116	2YX	Nelson	2k	1431	4XD	Dunedin	250
837	1YK	Kaitaia	2k	1134	4YQ	Queenstown	2k	1449	2YM	Palmerston North	2k
	1YX	Whangarei	2k	1143	1YW	Hamilton	2k	1458	3YW	Westport	2k
846	2ZD	Masterton	2k	1152	3ZC	Timaru	2k	1476	1XA	Auckland	5k
864	4ZA	Invercargill	10k	1161	2ZM	Wellington	2k	1485	3Z0	Twizel	100
882	1YC	Auckland	10k	1197	2ZW	Wanganui	2k	1494	1ZA	Taupo	2k
891	2XW	Wellington	5k	1206	4X0	Dunedin	2k	1512	1ZU	Taumarunui	1k
900	4YC	Dunedin	10k	1215	1ZE	Kaikohe	2k	1521	3YR	Reefton	100
918	3YZ	Kumara	10k	1242	1XX	Murapara	100	1539	2ZE	Blenheim	1k
927	2ZA	Palmerston North	2k		1XX	Whakatane	2k	1557	2ZH	Hawera	2k
945	2ZG	Gisborne	2k	1251	1ZM	Auckland	2k	1575	3XG	Christchurch	2k
							ELECT	RONICS	Australi	a, January, 1979	93

#### **AUSTRALIAN SHORT WAVE STATIONS**

The Australian Broadcasting Commission has shortwave broadcasting stations located in several states. These provide a service to distant sparsley populated areas of the commonwealth and territories.

The short-wave service transmits programs obtained as follows: VLI takes NSW regional programs; VLH relays 3AR; VLR relays 3LP; VLM and VLQ take Qld regional programs; VLW takes WA regional programs.

The frequencies on which these stations transmit are varied as necessary to obtain optimum results.

Call	Location	Watt
/LH	Melbourne	10
/LI	Sydney	2
/LM	Brisbane	10
/LQ	Brisbane	10
/LR	Melbourne	-12 10
/LW	Perth (two services	on -

two frequencies) 10k and 50k

#### **AUSTRALIAN TELEVISION STATIONS**

Area	Call	Channel Polarity	Area	Call	Channel Polarity	Location	Call	Channel Polarity
ACT			Northern To	erritory		South Austra	lia	
Canberra	ABC	3-V	Darwin	ABD	6-H	Adelaide	ABS	2-H
	CTC	7-V		NTD	8-H	Adelaide	ADS	7-H
			Alice Springs	ABAD	7-H		NWS	9-H
			Katherine	ABKD	7-H		SAS	10-H
New South	Wales		Tennant Creek	ABTD	9-H	Ceduna	ABCS	7-H
Sydney	ABN	2-H		7		Central East	ABRS	3-V
Cydiley	ATN	7-H				Leigh Creek	ABLCS	9-H
	TCN	9-H				Renmark-Loxton	RTS	5A-V
	TEN	10-H			1-	South East	ABGS	1-H
Bega-Cooma	ABSN	8-V	0				SES	8-H
Broken Hill	ABLN	2-V	Queensland			Spencer Gulf North	ABNS	1-V
	BKN	7-V	Brisbane	TVQ	0-H	\A/	GTS	4-V 7-H
Central Tablelands	ABCN	1-V	2.1024110	ABQ	2-H	Woomera	ABWS	/-H
	CBN	8-V		вто	7-H			
Central Western	4.5.041			QTQ	9-H			
Slopes	ABQN	5-V	Alpha	ABAQ	8-H			
Castan Vanana	CWN	6-V	Augathella	ABAAQ	11-H	Western Aust	tralia	
Grafton-Kempsey	ABDN NRN	2-H 11-H	Barcaldine	ABBQ	10-H	vvesterii Ausi	lialia	
Illawarra	WIN	4-H	Blackall	ABBLQ	9-H	Perth	ABW	2-H
illavvalla	ABWN	5A-H	Cairns	ABNQ	9-H		TVW	7-H
Manning River	ABTN	1-V	01 1 111	FNQ	10-H		STW	9-H
manning moon	ECN	8-V	Charleville	ABCEQ	9-H	Bunbury	BTW	3-H
Mungindi	ABMIN	10-H ·	Clermont	ABCTO	10-H		ABSW	5-H
Murrumbidgee	ABGN	7-H	Cloncurry Cunnamulla	ABCLQ	7-H 10-H	Carnarvon	ABCNW	7-H
	MTN	9-H				Central Agricultural	ABCW	4-H
Newcastle-Hunter	NBN	3-H	Darling Downs	ABDQ DDQ	3-H	Dampier	ABDW	10-H
	ABHN	5A-H	Dirranbandi	ABDIQ	10-H 7-V	Esperance	ABEW	10-H 6-H
Richmond-Tweed	ABRN	6-H	Emerald	ABEQ	11-H	Geraldton	ABGW GTW	11-H
	RTN	8-H	Goondiwindi	ABGQ	6-H	Kalgoorlie	ABKW	6-H
SW Slopes and	ABMN	0-H	Hughenden	ABHQ	9-H	Raigoonie	VEW	8-H
E Riverina	RVN	2-H	Julia Creek	ABJQ	10-H	Karratha	ABKAW	7-H
Upper Namoi	ABUN NEN	7-H 9-H	Longreach	ABLQ	6-H	Mt. Newman	ABW	7-H
	IVEIV	9-H	Mackay	ABMQ	4-H	Moora	ABMW	10-H
				MVQ	6-H	Morawa	ABCMW	8-H
Victoria			Mary Kathleen	ABMKQ	9-H	Norseman	ABNW	7-H
			Miles	ABMSQ	9-V	Port Hedland	ABPHW	7-H
Melbourne	ATV	0-H	Mitchell	ABMLQ	6-H	Roebourne	ABRBW	9-H
	ABV	2-H	Morven	ABMNQ	7-H	Southern Agricultural	ABAW	2-V
	HSV		Mount Isa	ABIQ	6-H		GSW	9-V
Dellana	GTV	9-H	Disk and	ITQ	8-H	Southern Cross		
Ballarat	ABRV	3-H	Richmond	ABRDQ	6-H	Bullfinch	ABSBW	9-H
Bendigo	BTV ABEV	6-H 1-V	Rockhampton	ABRQ RTQ	3-H 7-H			
Denaigo	BCV	8-V	Roma	ABRAQ	7-H			
Goulburn Valley	ABGV	3-V	St George	ABSGQ	8-H			
200.20 701107	GMV	6-V	Southern Downs	ABSQ	1-H	Tasmania		
Latrobe Valley	ABLV	4-H		SDQ	4-H	lasilidilid		
	GLV	10-H	Springsure	ABSEQ	9-H	Hobart	ABT	2-H
Mildura	ABMV	4-H	Townsville	ABTQ	3-H		TVT	6-H
	STV	8-H		TNQ	7-H	King Island	ABKT	11-H
Murray Valley	ABSV	2-V	Wide Bay	ABWQ	6-V	North Eastern		
Upper Murray	ABAV	1-H		SEQ	8-V	Tasmania	ABNT	3-H
7.0	AMV	4-H	Winton	ABWNQ	8-H	200	TNT	9-H

#### **AUSTRALIAN TRANSLATOR STATIONS**

Area	Parent Station	Channel Polarity	Area	Parent Station	Channel Polarity	Area		Channel Polarity
Australian Cap	oital Te	rritory	Tasmania			Mossman- Port Douglas	ARNO 4	0 V
Tuggeranong	CTC-7	10-V	Burnie	TNT-9	10-V	Fort Douglas	ABNQ-4	8-V 11-V
		10-0	burnie	ABNT-3	4-V	Nambour	FNQ-5A SEQ-1	10-H
New South V	Vales		Derby	TNT-9	11-H	Nebo	MVQ-6	8-H
Armidale	NEN-9	10-H	Lileah	TNT-9	6-V	North Cairns	ABNQ-9	4-H
	ABUN-7	4-H		ABNT-3	8-V		FNQ-10	5A-H
Batemans Bay-			Maydena	TVT-6	8-H	Toowomba	DDQ-10	5A-H
Moruya	ABWN-5		Queenstown-Zeehan	ABT-2	4-H	Townsville	TNQ-7	5A-H
	WIN-4	11-H		TVT-6	8-H		ABTQ-3	1-H
Bathurst	ABCN-1	6-V	Roseberry-	ADT 4	4.11	Whitsunday Islands/Shute Harbour	ABMQ-4	2-H
Bega (via Bateman's	CBN-8 WIN-11	11-V 6-H	Renison Bell (via Queenstown)	ABT-4 TVT-8	1-H 10-H	Islands/ Shute Harbour		
Bay-Moruya)	AA114-1.1	0-11	St Helens	ABNT-1	0-H	Victoria		
Bonalbo	ABRN-6	3-V	Strielens	TNT-11	7-H			
Bonaibo	RTN-8	5-V	St Marys-Fingal Valley		1-V	Alexandra	ABGV-3	5A-H
Bourke-Brewarrina	ABN-2	4-H	, , , , , , , , , , , , , , , , , , , ,	TNT-9	11-V	4	GMV-6	10-H
Cobar	ABN-2	2-V	Savage River-Luina	ABNT-2	4-H	Bright	AMV-4	11-H
100	CWN-6	10-V	(via Waratah)	TNT-10	7-H	Corryong/Khancoban	ABAV-1	9-H
Cooma	ABSN-8	· 0-M	Smithton	TNT-9	11-V	Filder (via Alexander)	AMV-4	10-H
	CTC-7	10-V	0 4 5	ABNT-3	4-V	Eildon (via Alexandra)	GMV-10	1-H 3-H
Deniliquin	GMV-6	10-V	South Launceston	ANBT-3	1-H	Myrtleford	ABGV-3	3-H 2-H
	ABGN-7	9-V		TNT-9	11-H	wyrucioid	AMV-4	9-H
Eden	ABSN-8	1-H	Cauchan	TNT-9	6-V	Nhill	BTV-6	7-V
Glen Innes	WIN-6 ABUN-7	3-H 0-H	Strahan (via Queenstown)	ABT-4	10-H		ABRV-3	9-V
Gien innes	NEN-9	3-H	Strathgordon	ABT-2	5-H	Orbost	ABLV-4	2-V
Gloucester	ABTN-1	6-H	Stratingordon	TVT-6	8-H		GLV-10	7-V
Gloucester	ECN-8	11-H	Swansea-Bicheno	TVT-6	8-H	Portland	ABRV-2	4-H
Goulburn	ABC-3	0-V	OWANISCA DICTIONS	ABT-2	4-H		BTV-6	11-H
Godibarri	CTC-7	10-V	Taroona	TVT-6	8-H	Swan Hill	BCV-8	11-V
Hay	ABGN-7	10-H	Waratah	ABNT-3	2-H	Warrnambool-		
	MTN-9	5A-H		TNT-9	10-H	Port Fairy	ABRV-3	2-V
Inverell	ABUN-7	2-H	Wynyard	TNT-9	5A-V		BTV-6	9-V
	NEN-9	10-H		ABNT-3	1-V			
Jerilderie	ABGN-7	11-H	Ourseland			South Austral	ia	
V 10 D 11	GMV-6	8-H	Queensland					2
Kandos-Rylstone	ABCN-1 CBN-8	0-V 10-V	Babinda	FNQ-10	6-V	Bordertown	ABS-2	2-V
Khancoban	AMV-10	7-H		ABNQ-9	1-V	Cowell	ABNS-1	6-V
Kyogle	ABRN-6	3-V	Blackwater Bluff	ABRQ-3	8-H	Keith	GTS-4 ABS-2	8-V 4-V
.,, - 3	RTN-3	5-V		RTQ-7	10-H	Port Lincoln	AD3-2	1
Lithgow	ABCN-1	5-V	Bowen	TNQ-7	1-H	(via Cowell)	ABNS-6	3-H
0 1-	CBN-8	6-V	0.1	ABTQ-3	5A-H	(Via Covveii)	GTS-8	5-H
Menindee	ABLN-2	9-V	Cardstone Village	TNQ-7	5-V			
Mudgee	CWN-6	9-V	Collinsville	ABMQ-4	8-H 11-H	Western Aust	ralia	
	ABQN-5	11-V	Cracow	MVQ-6 RTQ-7	5-H	Westelli Aust	ialia	
Murwillumbah	RTN-8	5-H	Dysart (via Goonyella-		9-H	Albany	ABAW-2	7-V
Nyngan	ABN-2	3-V ,	Moranbah)	MVQ-11	6-V		GSW-9	10-V
Portland-	40014	0.11	Gladstone	ABRQ-3	5-H	Kambalda	VEW-8	3-H
Wallerawang	ABCN-1 CBN-8	0-H 4-H	- C.G.G.G.G.G	RTQ-7	10-H		ABKW-6	5-H
Tamworth	NEN-9	0-H	Goonyella-Moranbah	MVQ-8	11-H	Katanning	ABW-2	4-V
Upper Hunter	ABHN-5	2-H	(via Nebo)			b	BTW-3	10-V
opportiumer	NBN-3	10-H	Gordonvale	FNQ-10	2-H	Koolyanobbing	ABSBW-9	
Walcha	NEN-9	1-H		ABNQ-9	0-H	Merredin	ABW-2	11-H
	ABUN-7	5-H	Gunpowder	ITQ-8	10-H	Mullewa Narrogin	ABGW-6 ABW-2	9-H 1-H
Wollongong	WIN-4	3-H	Gympie	SEQ-8	1-V	Newman	ABW-2	7-H
Young	RVN-2	6-H	Mareeba	ABWQ-6 FNQ-10	4-V 6-H	Pannawonica	ABW-2	11-H
			ividieeDd	ABNQ-9	1-H	Wagin	ABW-2	8-H
Northern Ter	ritory		Monto	ABWQ-6	1-V	, ragin	BTW-3	11-H
Warrego Mine	ABTD-9	10-H		SEQ-8	5-V	Wongan Hills	ABMW-1	
USTRALL	AN R	FPEA	TER STATIC	ONS				
					Channel	Area	Station	Channel
rea	Station	Channel Polarity	Area	Station	Polarity	Area	Station	Polarity
Western Aus	tralia		Paraburdoo	HTWR	11-H	Northern Terr	itory	
AACSIGIII WAS	CKWR	9-H	Newman	NEWR	9-H			1
Cockatoo Island	0.000					Groote Eylandt	GEMR	7-H
	CKWR	7-H	Ouganaland			All I I	00:15	
Cockatoo Island Koolan Island Mount Tom Price	CKWR HTWR	7-Н 7-Н	Queensland Weipa	WEQR	7-H	Nhulunbuy Yirkkala Mission	GOVR GOVR	11-H 9-H

## The Australian CB SCENE



## CRYSTALS, SYNTHESISERS AND THE PHASE-LOCKED LOOP — Part 2

As distinct from direct crystal control, or the synthesisers discussed in part 1 of this article, many modern CB transceivers use a phase-locked loop system to maintain them precisely on the allotted channels. Without getting too involved, this article seeks to explain what the term means.

#### by NEVILLE WILLIAMS

The phase-locked loop concept has been around for quite some time, certainly since the 1930s. More recently, it found wide application in the horizontal oscillator circuitry of television receivers, where the principle is used to lock the local oscillator to the incoming sync pulses. It is also fundamental to the design of automatic frequency control (AFC) circuitry in modern colour TV receivers and FM tuners.

Basically, a phase-locked loop — called PLL for short — is an electronic servo system which has the capability of producing an output which is frequency (and phase) locked to some external

reference signal.

In its simplest form, as illustrated in Fig. 2, a phase-locked loop involves three basic circuit elements. One is a voltage controlled oscillator, or VCO, whose output frequency is dependent not only on its own circuit constants but on an externally derived DC control voltage. Part of the output signal from the VCO is fed to a phase comparator or detector, which compares it with the incoming reference signal to produce resultants of one kind and another, including a "DC" component whose value reflects any difference between the frequencies being compared. After filtering to remove the original signal components, and possible amplification, the so-called DC component is fed to the VCO.

Assuming that the circuit constants have been suitably arranged, the control voltage will modify the output frequency of the VCO, so that it will lock to the incoming reference frequency. If the latter is absolutely fixed, so also will be the output from the VCO. If the

reference frequency varies, for any reason, the output from the VCO will vary with it, provided the time-constant of the control voltage circuitry is not excessively long. In short, the VCO will "track" the reference frequency.

A point to mention in passing is that, while a VCO will lock to a reference signal in terms of frequency, it tends to stabilise with a fixed phase displacement between output and reference


half that of the VCO output, meaning that the VCO could be locked to a frequency twice that of the original reference.

. Equally, it could conceivably be locked to four times the frequency or eight times the frequency.

As before, this would seem to be a rather pointless exercise but it provides an important step in the logic. Imagine that the frequency divider was switchable so that it could be set for ratios of 1:1, 2:1, 4:1 and 8:1; fairly obviously, the VCO could now be made to produce four different frequencies, all reference to a single source.

Interesting, but still not apparently relevant to the CB transceiver situation!

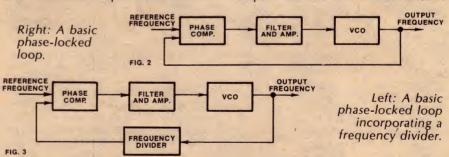The ratios of 2:1, 4:1 and 8:1 were chosen deliberately because they are simple ratios which have been used for



signals. It is not important in the present context but will explain why, in some circuitry, a phase difference is noted between the two.

To get back to Fig. 2, however, it will be apparent that a VCO could be locked to a crystal source selected for any CB transmit or receive function. The one obvious objection is that it would be a completely pointless exercise. If a crystal source had to be provided for each channel function, it might be as well be used directly!

Fig. 3 contains an important additional circuit function: a frequency divider in series with the feedback

Let's say that frequency divider was set for a ratio of 2:1. The frequency fed back to the phase comparator would be decades in conventional receivers and transmitters. In fact, up till not so many years ago, frequency division by other than simple ratios was regarded as rather impractical.

However, the emergence of digital logic technology has changed all that. It is now possible to arrange circuitry, usually in integrated circuit form, which will count up to any desired number of digits, then automatically reset and start counting all over again. In short, by producing one (reset) pulse after any selected integral number of digits, it can effectively divide by that number.

So, if one should wish to divide by 239, digital counting circuitry can be set up to do just that.

Why pick on 239? Because it provides

#### The Australian

#### CB SCENE

a handy example of what we mean.

If we set up digital circuitry to divide by 239 the output from a crystal oscillator set near 2MHz, it will divide its output down to 8366Hz, which is the top "C" note on a typical electronic organ. If we divide the same 2MHz (approx) by 253, we get 7903Hz—equivalent to "B". Divide it by 268 and we get 7460Hz, equivalent to B-flat, and so on down the entire octave.

That kind of complex division in-

That kind of complex division involves an integrated circuit especially interconnected internally to provide the integral ratios necessary to produce the notes in a musical octave. It could be described as a "dedicated" IC.

It is possible, however, to produce

It is possible, however, to produce integrated circuits which will provide a wide variety of division ratios in response to deliberate external manipulation — as, for example, by modifying external connections or voltages by means of a switch. Such an IC is commonly described as a "programmable divider".

Now refer back to Fig. 3 and, in place of the simple divider previously discussed imagine that we insert a programmable divider capable of being set for a variety of ratios no less odd looking (at first glance) but no less deliberate than those nominated for the production of a musical octave.

Fairly obviously, by settling on some appropriate (and fairly low) frequency for the reference, and by setting the programmable divider to a series of critically chosen ratios, the VCO can be made to deliver the range of frequencies required by a CB transceiver, all of them stabilised against the one common reference frequency — logically from a highly stable source.

The foregoing can be expressed in another way, for those who remember their school maths. The design task is to write down the required CB frequencies, determine the highest common factor (which becomes the reference frequency) and set the programmable divider for the relevant ratios.

What of the reference frequency source?

On the assumption that it has to be a relatively low figure, the most practical source is a crystal oscillator whose output is also divided down to the required figure. On this basis, Fig. 3 can be re-drawn as in Fig. 4 to incorporate the reference crystal oscillator/divider.

If the CB channel frequencies were all multiples of 10kHz and all 10kHz apart, the position would be delightfully simple. The crystal derived reference could be 10kHz and, with the programmable divider settable to 2700, 2701, 2702, etc, the VCO would produce frequencies of 27,000kHz, 27,010kHz,

# SIGNET CB RADIOS

OVERSEAS AUSTRALIA PTY LTD

#### **CB101 18 CHANNEL AM DELUXE**



☆ Electronic Channel Selector ☆ Squelch Control
☆ Public Address Control ☆ Volume Control ☆ Power
on-off Control ☆ R.F. Gain Control ☆ Delta Control ☆
Signal Power Meter ☆ Noise Blanker Control ☆
Automatic Noise Level Control ☆ Extension Speaker
Socket.

\$112.91

#### CB102 18 CHANNEL AM/SSB DELUXE



★ A.M. Control — 18 Channels ★ USB Control — 18 Channels ★ LSB Control — 18 Channels ★ Electronic Channel Selector ★ Squelch Control ★ Power on/off Control ★ Volume Control ★ R.F. Gain Control ★ Fine Tune Clarifier Control ★ Illuminated Signal Power Meter ★ Hi/Lo Tone Control ★ Noise Blanker Control ★ Public Address Control ★ C.B. Control Switch ★ Extension Speaker Socket.

\$213.92

#### INTRODUCTORY OFFER

\* A five foot fibreglass helical antenna complete with lead and plug will be supplied free of charge with each Signet CB purchased.



562 Spencer St., West Melbourne (03) 329 7888 1103 Dandenong Rd, East Malvern (03) 211 8122



#### The Australian CB SCENE

27,020kHz and so on.

But, while the official CB channels are 10kHz apart in most cases, they are not divisible by 10. with figures like 27.015mHz, 27.02MHz, 27.035MHz, etc, the highest common factor is five (or 5kHz) and some measure has to be taken in the design to accommodate this situation.

For example, the reference frequency might be reduced to 5kHz and the programmable divider switching arranged to select only the appropriate 23 or 40 (American) channels or 18 Australian channels.

Again, the PLL could be set up to produce frequencies 10kHz apart, referenced to 10kHz, but heterodyned up to 27.005kHz and so on by beating with a fixed crystal oscillator containing the odd 5kHz. In short, frequency synthesis (see part 1) in addition to the basic phase-locked loop.

In fact, a variety of schemes have been devised to cover this requirement. There is also the need, in receive mode, to provide a VCO output displaced from the channel frequency by a figure equal to the first intermediate frequency. Yet again, for SSB reception, a further increment of about 3kHz must be provided.

In some cases, these various requirements have been met by the provision of additional crystal oscillators to supplement the basic PLL by frequency synthesis. Even so, the need for two or three supplementary crystals is of little consequence when compared with the needs of alternative methods.

#### SPECIAL PURPOSE ICS

Not surprisingly, however, integrated circuit manufacturers have come up with custom-designed programmable ICs which offer their own in-built answers to the various problems. Referenced to a single crystal, some of these will produce the transmit frequency and the required receiver oscillator" frequencies for a doublechange multi-mode superhet automatically in response to inputs from the channel selector, mode and send/receive switches.

More than that, their "programming" can be rationalised to correspond with that necessary to operate a LED channel readout, and to respond to pulsed rather than hardwired input.

You find all this confusing?

So does just about everyone else who has not had occasion to work closely with modern multi-channel transceiver design!

REFERENCE CRYSTAL OSC. FREQUENCY PROGRAMMABLE DIVIDER FIG. 4

But, leaving aside these refinements and complications, you will hopefully have gained what we set out to impart an appreciation of how a voltage controlled oscillator can produce an array of precise frequencies, aided by a reference crystal, a phase-locked loop and a programmable divider.

BRISBANE

HIGHWAY NETWORK WITH PHILIPS UHF 320

Following an announcement made in Melbourne during mid-September, Philips have lost no time in giving effect to an ambitious plan: to set up a complete UHF CB monitoiring network along the New England and Hume highways linking Brisbane, Sydney and Melbourne.

Having just received the Australian design award for the UHF 320 CB transceiver, Philips-TMC announced that they would make 30 or more of the units available gratis, as a community service, to Truckers Radio Australia and Big Wheels stations along the highways, already operating on the 27MHz band. In fact, at the time of writing, 33 stations have been equipped.

Warwic Stanthorpe Glen Innes Kootingal Tamworth Murrurundi Scone Muswellbrook Singleton Waratah SYDNEY Camden. Mittagong 4 South Gundagal **Tumblong** Albury Wodonga Wodonga Benalla Glenrowan Euroa Violet Town Avenel Nagambie MELBOURNE

The main role of the stations is to assist and cooperate with professional drivers using the highways — a task which is often made difficult on 27MHz by noise and interference and by CB "idiot" behaviour. The new UHF FM equipment offers substantial relief from these problems, with an exceptional degree of speech clarity as a further bonus.

Wallan

Mr Graham Evans, National Director of Truckers Radio Australia, says that his organisation is keen to promote the exclusive use of UHF channel 40 (477.400MHz) for highway communication, primarily by professional drivers. However, TRA stations would cooperate with responsible private drivers on the highway channel, in respect to road conditions, directions and emergency situations.

"In return for that service on the highway, TRA will beg the indulgence of UHF users to leave channel 40 alone in the cities for the use of truckers".

"So we offer a service on the highway, and they give us a go in the city".

#### NOW AVAILABLE

#### **ELECTRONICS AUSTRALIA BINDERS**

These attractive binders finished in brown plastic with gold lettering will keep your back issues of Electronics Australia neat and tidy

Available from: Electronics Australia, 57 Regent St, Sydney. PRICE: \$4.50 or by mail order from Electronics Australia, P.O. Box 163, Beaconsfield 2014. PRICE \$5.50 NSW; \$6.50 other states.

## INCREDIBLE BUT TRUE

Near half price! WASP CB reduced to



#### SAVE \$60 THE CB BARGAIN OF THE YEAR!

Thousands of these advanced Wasp CB's from Dick Smith sold for \$129.50 - now look at the price. Hurry - this is your last chance to buy at this incredible bargain price. Next shipment must at least double (even treble) in price as a result of import duty and deteriorating exchange rate. HURRY IN FOR YOUR WASP NOW! Cat D-1520

#### **Huge savings on SIDEBAND sets**



#### HORNET MOBILE

The set with a sting reduced to a price that won't hurt!

LED readout, maximum legal power. Save an incredible \$100!

#### **SCORPION BASE**

Designed and built as a base station: 240 & 12 volt operation, large 'S' & power/SWR meters, LED readout: Save \$50.00 NOW!



#### PRICES SLASHED ON CB ACCESSO RUSH THESE - AT SUCH LOW, LOW PRICES THEY WON'T LAST LONG.

HURRY!

DELUXE ALTERNATOR FILTER

Ferrite core - for really tenacious alternator whines. Cat. A-7926 WAS \$9.50 SAVE \$3.00 NOW \$6:50

WHITE FLASH HELICAL ANTENNA

The famous 'top adjust' nelical attention state and plug. Cat D-4076 WAS \$29.00 \$19:50 The famous 'top adjust' helical antenna complete with base,

**GUTTER MOUNT ANTENNA** 

Simply clips on the rain gutter of any vehicle. Complete with lead & plug. Cat. D-4411 \$16:50

MAGNETIC BASE ANTENNA

Centre-loaded, stainless steel construction with strong magnetic base. Lead & plug included. Cat D-4412

WAS \$22.50 GAVE \$6.00 NOW \$ 16:50

CB/FM/BC ANTENNA

Three antennas in one! Locks down when not in use. All connecting cables and fittings supplied. Cat. D-4418

WAS \$32.50 SAVE \$3.00 NOW \$29:50

ELECTRIC CB/FM/BC ANTENNA

Similar to D-4418 above with the added convenience of electrical operation controlled from dashboard switch. Cat. D-4419 WAS \$65.00 SAVE \$15.55 NOW \$49:50 WHITE NIGHT TOP LOADED ANTENNA

Fibreglass antenna with exclusive 'Power Coil'. Complete with roof mount base, trunk tip mount, cable & plug. Cat. D-4452 WAS \$29.50 SAVE \$11.00 NOW\$18:50

MAGNETIC BASE

Uses a powerful base so no need to drill holes in car roof. Nylon gasket prevents scratching. Cat D-4622

WAS \$25.00 SAVE \$9.50 NOW \$15:50

ANTENNA MATCHBOX

Connect into antenna lead. By adjusting four knobs virtually all mismatch between antenna and rig can be eliminated. Cat..D-5512 WAS \$15.00 SAVE \$2.50 NOW \$12:50

**CB ANTENNA ELIMINATOR** 

Enables you to use your car radio airial for your CB and car Enables you to use your car radio Silve \$5.00 \$24:50 radio. Cat. D-5516 WAS \$29.50 SAVE \$5.00

SWR/POWER/FIELD STRENGTH METER

Get the best out of your rig by ensuring antenna is SWR'ed properly & transmitter is putting out maximum legal power. Cat Q-1352 WAS \$21.50 SAVE \$6.00 NOW \$15:50

27MHz TESTER

A must for CB servicemen & serious CBers. Measures SWR power, modulation, field strength, checks crystals too. WAS \$59.50 SAVE \$10.00 Cat. Q-1380

Mail Orders? Certainly! Add the following amounts for delivery: Order value \$5.00 -\$9.99 P & P \$1; \$10 - \$24.99 P & P \$2; \$25 - \$49.99 P & P \$3; \$50 - \$99.99 P & P \$4; \$100 or more P & P \$5.50



125 York Street, SYDNEY. Ph. 290-3377 147 Hume Hwy, CHULLORA. Ph. 642-8922 162 Pacific Hwy, GORE HILL. Ph. 439-5311 30 Grose Street, PARRAMATTA. Ph. 683-1133

399 Lonsdale Street, MELBOURNE. Ph. 67-9834 656 Bridge Road, RICHMOND. Ph. 42-1614 BRISBANE 166 Logan Road, BURANDA, Ph. 391-6233 ADFL AIDE 203 Wright Street, ADELAIDE. Ph. 212 1962

SHOPS OPEN 9AM to 5 30PM (Saturday 9AM 12 noon) BRISBANE 1.2 Hous earlier

Many lines available from the Dick Smith Electronics Centra

GRACE BROS

MAIL ORDERS P.O. Box 747, Crows Nest, N.S.W. 2065. Post and packing extra.

Dealers across Australia.

## RMATEUR RADIO

by Pierce Healy, VK2APQ

#### Wireless Institute educational service report

The Wireless Institute of Australia Youth Radio Service, incorporating the novice licence trial examination program, has been responsible for a large percentage of the successful candidates for an amateur licence.

The International Telecommunication Union, Radio Regulation 1-78, defines the amateur service as "-a service of self training, intercommunication and technical investigations carried out by amateurs; that is, persons interested in radio techniques solely with a personal aim and without pecuniary interest."

That definition certainly applies to the work associated with the WIA

education service.

Educational activities are organised within each state division of the WIA by Youth Radio Scheme committees, members of various school or college radio clubs, or amateur clubs who, as an extension of the clubs' activities, conduct classes for amateur licence candidates.

On the other hand, the WIA federal education committee, co-ordinated by Graeme Scott, VK3ZR, through its collaboration with the P&T radio branch officers, has been responsible for a number of improvements in the format and other aspects of amateur licence examinations; in particular, the preparation and issue of a syllabus for the novice licence.

A bank of multi-choice format questions for the novice examination, prepared in consultation with YRS state education officers, and based on the syllabus, was presented to the radio branch for use at examinations.

New South Wales appears to have the most intensified YRS activity, with 56 clubs registered during 1978. Of these, 26 provide novice licence training, 16 follow the YRS courses and participate in the certificate examination provided by them, and 12 provide general interest electronics where members construct simple electronic projects that provide almost instant satisfaction to

the builder. Seven clubs follow standard "Manual Arts" style courses designed by the teacher and run for a few periods each week. Pupils build graded projects, do theory study, and sit for school examinations in electronics, but find the YRS notes and other assistance helpful.

One club, at the Armidale High School, conducts a senior one-year course, with three periods a week, under the category "Other Approved Course". This course leads to the amateur operators limited certificate of

proficiency (AOLCP).

The situation in Victoria is not fully known. There are at least 22 clubs associated with YRS activity, but few

details have come to hand.

The Midland Zone of the Victorian Division of the WIA reports a number of classes in its area. At the Golden Square High School, Bendigo, 30 students attended novice classes, while another 14 elected to attend preliminary classes based on NSW YRS notes. These classes were conducted by Bob Lukeis, VK3BRL, with assistance from some parents and Bob's wife.

Another course at novice licence level was conducted at the Bendigo Technical College by Ken Slade,

VK3ZGS and Alec Wilson.

At the Echuca Technical College, George Loft, VK3AGM conducted a novice licence course and successful students at AONCP examinations went

on to study for the AOCP.

The Midland Zone will hold classes for the three levels of amateur licences during 1979. Enquiries should be directed to the secretary Bill Clark, VK3FY, High Street, Kangaroo Flat, Vic. 3555 or telephone (054) 47 7274.

In Northern Territory at the Casuarina High School, near Darwin, an active club operating under the call VK8CH has received a school commission grant of \$1087. The grant has been used to equip the station for demonstration and practical training towards the novice licence. The club is under the supervision of teacher David Boehm, VK8DB.

In the other states it is understood that educational activity is available at a number of flourishing clubs at various

centres.

During 1978, three amateur radio weekends were conducted by the NSW YRS, co-ordinated by Reverend Bro Cyril Quinlan, VK2ACQ, at the Mount St Mary's Conference Centre, Katoomba. Two nights accommodation and meals plus lectures on radio theory, propagation, and Morse code was provided for \$17 a person. Trial examinations at novice licence level were also conducted.

(Details of radio weekend January 1979 given elsewhere in these notes.)

Publications available for those interested in the novice licence are: "Manual of Questions and Answers" by Keith Howard, VK2AKX. This is a short course in radio for candidates for the AONCP and is available from the Westlakes Radio Club, PO Box 1, Teralba, NSW 2284. Price \$4.50 post

"1000 Questions for Novice Candidates", and "50 Basic Electronics Projects" — produced by the WIA NSW Division Education Service. Price \$3.00 and \$1.50 respectively post paid. Available from D. R. Wilson, PO Box 109, Toongabbie, NSW 2146. Cheques should be made out to - WIA Educa-

tion Service.

"Zero Beat", published quarterly, is the national magazine of the YRS, available on a subscription basis. It contains details of YRS activities, technical articles, and simple projects. The editor is Ken Hargreaves, VK2AKH, 52 Marlin Avenue, Floraville, NSW 2280. All correspondence should be directed to Ken.

Also available is a Self Study Kit for the novice. This kit contains the Manual of Questions and Answers; 1000 Questions; Learning Morse Code (book and two C60 cassette tapes) and

Radio clubs and other organisations, as well as individual amateur operators, are cordially invited to submit news and notes of their activities for inclusion in these columns. Photographs will be published when of sufficient general interest, and where space permits. All material should be sent to Pierce Healy at 69 Taylor Street, Bankstown 2200.

#### AMATEUR RADIO

other material. Price \$15.00. Available from D. R. Wilson.

The work done by those associated with the WIA education service is on a purely voluntary basis, the only charges made are to cover cost of materials,

postage, etc.

If you are interested in radio communication or electronics, the WIA education service provides the opportunity to expand your knowledge. Science teachers have found the YRS courses very helpful in the formation of clubs among interested students, as have the organisers of various youth groups.

For details of the WIA Education Service contact the secretary, WIA Division, in each state. In NSW the YRS state supervisor is Ken Hargreaves, VK2AKH, 52 Marlin Avenue, Floraville 2280.

Reference to the Australian Radio Club Directory published last month in these notes may provide details of a direct contact in your local area.

#### **GENEROUS GIFT TO YRS**

In October, 1978, a most generous gesture was made by Dick Smith Electronics. A large range of electronic and radio equipment consisting of surplus warehouse stock, samples, shop soiled returns, etc, including transceivers, multimeters, speakers, antennas, transformers and a large selection of assorted components, was donated to the WIA federal education section for sale and auction for the benefit of youth radio work throughout Australia.

The sale was conducted at Wireless Institute Centre, 14 Atchison Street, Crows Nest on Saturday, October 28, 1978 and yielded a gross amount exceeding \$3500. This will be shared among all divisions of the WIA.

There is no doubt that such a fine gesture will be appreciated by WIA members and will be the means of assisting many to become engaged a very worthwhile hobby — amateur radio.

#### AMATEUR RADIO WEEKEND

Following the success of study weekends held prior to the May, August and November P&T Dept examinations during 1978, the first of this year's pre-examination courses will take place over the Australia Day weekend, allowing an extra day for intensive study.

Again the venue will be the Mount St Mary's Education Centre at Katoomba, NSW, on the Great Western Highway opposite the police station. Being an ex-boarding school it is an ideal venue for a live-in study situation.

As well as providing the final brushup and evaluation for those attempting the full call exam in February, lectures will be available for novices and persons seeking an introduction to amateur radio.

Reverend Bro Cyril Quinlan, VK2ACQ, who was the instigator and convenor of these weekends has, due to pressure of work, requested the following to act as convenors: Les Dickenson, VK2NMY, Sel Carlyle, VK2NOK and Ken James, VK2NWK.

Date: 8 pm, Friday, January 26, 1979, to 3 pm Monday, January 29, 1979.

Courses: Full call — final brush up and lectures for February theory and Morse code examination.

Novice and beginners — introduction to radio and lectures on theory, introduction and Morse code practice, both at novice licence standard.

Fees: Adults — \$29.00; ladies not attending lectures — \$19.00; students age 11 years to secondary standard — \$19.00; children 10 years and under — \$12.00. Deposit \$5.00 per person (non-refundable).

Bookings: Katoomba Weekend. PO Box 52, Asquith, NSW 2078. Please make cheques payable to Katoomba Weekend.

There is a limit to the number of persons that can be accommodated; bookings will be on the first in basis, so book early.

When booking list any call signs held and the level of instruction required.

A limited number of private rooms are available with preference given to family groups. Other accommodation is in dormitories. Bring own bed linen or

sleeping bags; meals and everything else are supplied.

Any enquiries may be made to Sydney telephones — (02) 827 3589; 638 1687 or 47 3044 during evenings only.

#### VALE TREVOR EVANS VK2NS

The many Australian and overseas friends of Trevor Evans, VK2NS, will be sad to hear of his death at Bathurst, NSW, on Sunday, 29th October, 1978.

Born around the turn of the century at Blaney, NSW, he became interested in radio communication at a very early age and in 1912 he was experimenting with a spark transmitter and coherer receiver. He was licenced as an amateur in 1923 and until the day of his death was actively engaged in the many facets of amateur radio. As an immaculate CW and phone operator his "fist" and operating procedure was world renowned and an inspiration to all.

Many years ago Trevor specialised in accurate frequency measurements and was one of the pioneers in hand grinding crystals, having supplied these to

broadcasting stations.

In 1926, Trevor founded the Rag Chewers Club which functioned for many years to encourage and improve the standard of CW operation. He was member number 575 of the Old Old Timers Club and held the number one 50 years award.

In 1931, Trevor won the British Empire Radio Union's trophy in the in-



35 EILEEN ROAD, CLAYTON, VICTORIA, 546 5076. TELEX AA36004 (ALL MAIL TO:— P.O. BOX 42, SPRINGVALE, VIC. 3171)



With more than 36 years experience BRIGHT STAR can supply your Crystal needs.


ALSO AVAILABLE

Crystal Clock and Decade Counter

- ock de Counter Wideband Amplifier
- Wideband Amplifiers.
  Crystal Oscillators.
  Crystal Clock and Decade
- Counters, C-MOS, TTL.

  Pre Scalers to 250MHz,
  (See previous advertisements.)

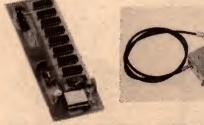See previous advertisements.)
 Send S.A.E. for new catalogue



HOSE & EQUIPMENT CO. PTY. LTD. SYDNEY. PHONE 666-8144

WESTEST ELECTRONICS, PERTH, 337 6392.

FRED HOE & SONS PTY. LTD. BRISBANE. PHONE 277 4311 ROGERS ELECTRONICS ADELAIDE. PHONE 42 6666

DILMOND INSTRUMENTS HOBART, PHONE 47 9077

augural contest which, in the presence of many of his associates in amateur radio, was presented to him in Sydney by the Lord Mayor, Alderman J. lackson.

Apart from radio, Trevor had many hobbies. During the 1930s he became interested in dirt track motor cycling. He also was an expert photographer. Model making was another hobby at which he excelled, constructing miniature blast furnaces for smelting iron ore, steam driven locomotives, turbines and stationary engines, also hot air and suction gas engines.

Well known and respected by all who knew him, for 55 years Trevor upheld the principles of the amateur radio operators code in a manner which should be an example to us all.

To his wife and family is extended deepest sympathy.

#### TV CHANNELS 0 & 5A

Strong objections by the WIA, and amateur licencees in general, to members of the Australian Federal Parliament in relation to proposed expansion of TV channel 5A, has brought heartening results.

In an address, opening the WIA Queensland division 1978 annual convention in Brisbane on October 16-17,

Mr David Jull, MP for Bowman, Qld, and secretary of the communications committee of Federal Parliament, made these comments, which were broadcast over WIA official stations -

"... Congratulations to the number of members of your association indeed the community who approached members of parliament, who wrote to the Minister and to members of my committee, to express their concern and in fact formed themselves into a very satisfactory and very hard hitting lobby group.

"I am pleased to announce that the decision for channel 5A to be used in metropolitan areas has been completely shelved and won't happen. Furthermore, an investigation is now underway by the department to eliminate those areas that are using channel 5A for translator facilities in some of the TV country areas.

"I believe that if it had not been for pressure of members of your association throughout Australia the decision to go ahead with channel 5A would have gone ahead and we would have been in all sorts of troubles and got ourselves into a ridiculous situation, certainly internationally.

"An announcement was made on Thursday of the first of the moves as far as TV stations are concerned. As you probably know, the original idea was to transfer Channel 0 in Melbourne and Channel 0 in Brisbane to Channel 10 but this would have caused problems in areas like Traralgon in Victoria and

Toowoomba in Queensland, because those areas are using Channel 10 and Channel 5A was seen as a very real alternative.

'However, on Friday it was announced that Channel 0 in Melbourne is already going to Channel 10 as soon as possible and I should think a similar announcement will be made here in Brisbane about the fate of Universal Telecasters as well. Both stations I understand are quite pleased about the change because that suits their network arrangements as well.

"I am sure that you are pleased with that news and once again congratulations for the work that has been done by your organisation."

Later in his address David Jull made these observations: "... and I think by the experience of Channel 5A you will probably realise as well, the amount of power and punch an organisation such as yours and your affiliated branches around Australia can have and, indeed, if there are any other areas of these particular operations that concern you, I would ask that you do submit your objections and so once again a concerted approach can be made to try to get some sensible and sane decisions to be made by the government.

#### **RADIO CLUB NEWS**

It is time again to plan your visit to the Central Coast of NSW for the Central Coast Amateur Radio Club's field

This will be held on Sunday, February



#### ICOM'S DIGITAL ALL SOLID STATE HF TRANSCEIVER

STATE OF THE ART TECHNOLOGY





ICOM's superior LSI technology takes the lead in Amateur HF. The extremely compact IC-701 delivers 100 watts output from a completely solid state, no tune (broad band design) final, on all modes and all bands, from 160-10 M. With single knob frequency selection and built-in dual VFO's, the LSI controlled IC-701 is the choice in computer compatible, multi-mode Amateur HF transceivers.

The IC-701's single frequency control knob puts fully synthesized instant tuning at a single finger tip. WIDE bandspread, with 100 Hz per division and 5 KHz per turn, is instantly co-ordinated between the smooth turning knob and the synthesizer's digital read-out with positively no time lag or backlash (no waiting for counter to update: less operator fatigue). And at the push of the electronic high speed tuning button, the synthesizer flies through megacycles at 10 KHz per step (500 KHz per turn).



Sydney Adelaide Gold Coast Canberra 681 3544 43 7981 32 2644 82 3581 Melbourne 836 8635 321 3047 43 6337 54 1035 Perth Hobart aunceston

The computer compatible IC-701 LSI chip provides input of incremental step or digit-by-digit programming data from an external source, such as the microprocessor controlled accessory which will also provide remote band selection and other functions.

Full band coverage of all six HF bands, and continuously variable bandwidth on filter widths for SSB, RTTY, and even SSTV, help to make the IC-701 the very best HF transceiver ever made. IC-701 includes two CW widths, all of this standard at no extra cost.

Sold complete with the high quality electret condenser base mic (SM-2), the IC-701 is loaded with many ICOM quality standard features. Standard in every IC-701 are two independently selectable, digitally synthesized VFO's at no extra cost. Also standard are a double-balanced schottky diode 1st mixer for excellent receiver IMD, and RF speech processor, separate drop times for voice and CW VOX, optionally continuous RIT, fast/slow AGC, efficient IF noise blanker, fast break-in CW, and full metering

Price \$1380 (AC power supply extra)

VICOM

68 Eastern Road **SOUTH MELBOURNE VIC 3205** PH. (03) 699.6700 Telex AA30566





#### DOES YOUR ANTENNA TURN IN THE WIND?

DOES YOUR CONTROL UNIT 'CUT-OUT' AFTER ONLY A FEW REVOLUTIONS?



... then step-up to a RELIABLE EMOTO ROTOR.

Bail Electronics are pleased to announce . . . ... an exciting range of ANTENNA ROTATORS by EMOTO ANTENNA Co. of Japan



EMOTO FEATURES

• ROBUST DESIGN

• HEAVY DUTY

STAINLESS

HARDWARE . 100v. SUPPLY TO MOTOR REDUCES VOLTAGE/POWER-LOSS

COMPARISON OF ROTOR BRAKE TORQUE FIGURES (kg./cm.) CDE model CD44 Torque 1,152 4,025 HAM-2 103 LBX 502 CXX 1,500 1102 MXX 10,000

We have been in the business long enough to we have been in the business single eliberations, who your requirements for a first class antenna rotor, and we have gone "over-board" for the EMOTO rangel There are many brands of antenna rotors, some of them completely unsuitable for the majority of amateur applications, and for this reason we do not stock them.

Most likely your present antenna rotor will turn your antenna and hold satisfactorlly, but it just will not hold it stationary under strong wind conditions; i.e. YOUR ROTATOR LACKS SUFFICIENT BRAKE TORQUE, the ability to hold the antenna still whilst a gale is blowing. HERE IS WHERE THE EMOTO SCORES.

Take a close look at the comparison figures

above. Then compare the prices of all the rotors and you will have to agree that the EMOTO 103 LBX, EMOTO 502 CXX and EMOTO 1102 MXX are the best value.

Finally, EMOTO ANTENNA CO., is not a new company. They have been making rotors for many years. Have no fears about this being a new and untried producti

#### Universal antenna couplers

Extremely important, especially with modern all-solid state transceivers, is the maintenance of a very low SWR to avoid destruction of costly high-power P.A. transistors. An antenna coupler enables precise adjustment with almost any antenna.



(S,W. or co-ax.)

HC 500A - 160-10m, up to 500w pep

(also available — not illustrated) **HC 2500** — 160-10m, up to 2.5kw pep HC -75 — 80-10m, up to 2.5kw pep HC -75 — 80-10m, up to 75w pep HC 250 — 80-10m, up to 200w pep FC 301 Yaesu — 160-10m, up to 500w pep FC 301 Yaesu — 160-10m, up to 500w pep

Our years of handling and specializing in this equipment have enabled us to build up a fund of knowledge and technical experience, backed by a comprehensive range of spare parts and service facilities. We don't just sell a set, our concern extends throughout the life of your equipment. Now an addition to YAESU'S range of measuring instruments . . .

Radio amateur equipment from B.E.S. also sold by -

World



Yaesu has now made an addition to their already well known range of measuring instruments, it is the QTR-24, a 24 hour World Clock. With a glance the time in any principal city or time zone can be simultaneously coordinated with local time on a 24 Hour basis. The QTR-24 is powered by a 1.5V dry cell, which has a normal life of approximately one year. No amateur or SWL station could be complete without one.

Contact us for details of other Yaesu equipment plus the accessories required to complete your station.

All equipment from Bail's carries a 90-day warranty and complete service back-up.

JAS 7879-1



## **ELECTRONIC**

FRED BAIL **VK3ABA** 

60 Shannon St., Box Hill North, Vic., 3129. Ph. (03) 89 2213

Yaesu Agents in Australia since 1963

Radio Communication Services, H. R. PRIDE, 26 Lockhart St., Ph 450 4379 Como, 6152 Ph. 21 7609 WILLIS TRADING CO., 429 Murray Street, Perth 6000
FARMERS RADIO PTY LTD., 20 Stanley St., Plympton 5036
G. T. ELECTRONICS, 131 Westbury Rd., South Launceston 7200 Ph. 293 2155 Ph. 44 4773 Ph. 44 5000 J. P. ELECTRONICS 64 Wentworth St, Launceston 7200. 34 6912 PRINS RADIO, 123 Argyle Street, Hobart 7000

N.S.W. Aviation Tooling, STEPHEN KUHL, 104 Robey St., Mascot 2020

Amateur & Novice Comm. Supplies, W.E. BRODIE, 23 Dalray Street, Ph. 667 1650 Seven Hills 2147
DIGITRONICS, 186 Parry St., Newcastle West 2302
RIVERCOM, Sid Ward, 9 Copland St., Wagga Wagga 2650
H. C. BARLOW, 92 Charles St., Aitkenvale, Townsville 4814 Ph. 624 2691 69 2040 21 2125 79 8179

MITCHELL RADIO CO., 59 Albion Rd., Albion 4010 ACT QUICKTRONIC, Jim Bland, Shop 11, Altree Crt., Phillip 2606

57 6830

81 2824

#### AMATEUR RADIO

18, 1979 at the Gosford Showground.

Amateurs, their families and friends, are invited to what has become the largest event associated with amateur radio in Australia.

Full program details next month.

GOLD COAST AMATEUR RADIO SOCIETY: An overall plan for a GCARS emergency network has been accepted by the Queensland police and State Emergency Service organisation who were very impressed with it.

All amateurs from Kingscliffe (Nth NSW) to Beenleigh along the Gold Coast areas will be notified of an emergency channel, whether they are GCARS members or not, and will be asked to participate in exercises.

It is anticipated that a separate search and rescue communication unit will be formed within the existing plan, to cater for minor emergencies.

Gold Coast visitors are invited to attend GCARS meetings, held every second Friday of the month at the State Education Centre, Cnr Laycock Street and Gold Coast Highway, Surfers Paradise.

#### WAGGA AMATEUR RADIO CLUB:

Recently a large WIECN exercise was held by WARC members in conjunction with a Handicapped Persons Radio Appeal Day via the local broadcast station. WICEN's role entailed handling over 1000 messages during a 12 hour period.

A base was set up at the broadcast station centre and information was continuously passed to six WICEN mobile units strategically positioned throughout the city of Wagga. WICEN members helped to make the event most successful and, at the same time,

#### THE WIRELESS INSTITUTE OF AUSTRALIA

New South Wales Division

14 Atchison Street, Crows Nest, N.S.W. 2065 Telephone: 43 5796

#### WOULD YOU LIKE TO JOIN THE RANKS of AMATEUR RADIO ENTHUSIASTS?

The Institute conducts Courses for the A.O.C.P. or L.A.O.C.P. with the benefit of expert guidance throughout your studies.

PERSONAL CLASSES for 1979 will commence on Tuesday, February 6, at 6 p.m. at Crows Nest, and will continue for three terms to December in readiness for the February 1980 examinations. CORRESPONDENCE COURSES may be commenced at any time.


For further information, write to:

#### THE COURSE SUPERVISOR, W.I.A.

14 Atchison Street, CROWS NEST, N.S.W. 2065
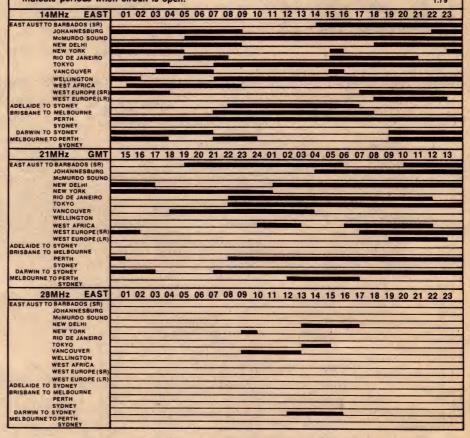
#### IONOSPHERIC PREDICTIONS FOR JANUARY

Reproduced below are radio propagation graphs based on information supplied by the lonospheric Prediction Service Division of the Department of Science. The graphs are based on the limits set by the MUF (Maximum Usable Frequency) and the ALF (Absorption Limiting Frequency). Black bands indicate periods when circuit is open.



provided the opportunity for members to handle high density traffic.

During the past six months, members of the Wagga Rescue Club otained and reconditioned a heavy duty 23 metre high radio tower for WICEN's HF and VHF antennas. The tower, combined with an excellent operating console and telephone, indicates the high level of liaison between the Wagga Rescue Club and WICEN. A similar level of liaison exists between WICEN and Regional Headquarters of the SES—with whom WICEN is heavily involved during river floods.

Anyone wishing to join the WARC 1979 training classes for the full call (AOCP) or novice (AONCP) licence are invited to write to the secretary WARC, PO Box 71, Kooringal, Wagga, NSW.

GEELONG AMATEUR RADIO CLUB: The "Sleepy Hollow" 10 metre award has been initiated by a group of novice licencees in Geelong. Sleepy Hollow is the local pet name for Geelong.

The basic award is a series of prints of Geelong in 1857. Two more prints in the series can be obtained by working the required number of contacts and applying for the Citizen and Overlander endorsements.

To obtain the basic award it is necessary to have five contacts with chapter members, two of which must be charter members. The Citizen endorsement requires 15 contacts and four of these must be charter members. The Overlander endorsement requires 30 contacts and six of these must be charter members.

The chapter meets on 28.530MHz at 2300GMT and again two hours later on 28.480MHz.

Chapter awards manager is John Weston, VK3NRW, who can be contacted on 10 or 15 metres or via PO Box 520, Geelong, Vic. 3220.

ILLAWARRA AMATEUR RADIO SOCIETY: Insurance money to cover the loss and damage of moonbounce equipment and buildings at Dapto, NSW, has been paid. Quotes have been called for the removal and installation of the dish antenna at a new site.

Details of a microstrip line type radiator as used in the Parkes radio telescope at 408MHz have been obtained. If the relocation of the antenna is successful a 432MHz version will be made as it will give better illumination of the dish than the crossed dipoles that have been used.

The moonbounce transmitter has been reassembled by Lyle Patison, VK2ALU and is being modified and checked.

Meetings of the IARS are held on the second Monday of each month at 7.30 pm in the Wollongong Town Hall meeting room. Visitors welcome.



#### YAESU aerial tuners with power & SWR meters

By use of a tuning unit, available as an accessory, the output impedance of most high frequency transceivers can be accurately matched irrespective of the type of antenna used.

Two YAESU antenna tuners, models FC-301 and FC-901, were tested recently. These are designed as matching accessories for the Yaesu FT-301 and FT-901 transceivers. However, both are suitable for use with other types.

Both use virtually the same circuit, the only electrical difference being in the value of one minor component. The major difference is physical, the FC-301 being smaller than the FC-901, and having a recessed front panel.

Both units have the same front panel layout, consisting of two meters and six control knobs. One meter displays SWR on two ranges, one for power outputs up to 25W and one for powers above 25W. The second meter indicates forward power on three ranges; 25W, 250W, and 500W, and also carries an "SWR Set" mark. The six controls are; Power & SWR, Antenna Select, SWR Set, Tune, Band, and Load.


The Antenna Select switch has four positions; any one of three coaxial antenna connectors, or a single wire antenna terminal, all on the back panel. The Band Select switch has eight positions; direct, 160L, 160H, 80, 40, 20, 15 and 10 (metres). The "L" and "H" indicate the lower and higher sections of the 160 metre band. The direct position allows the antenna to be fed direct to the transceiver, bypassing the tuning unit but retaining the SWR and power metering facilities.

metering facilities.

Basically, the operation is that the output of the transceiver is fed through an SWR and power bridge to the junction of two 300pF ganged variable capacitors, in parallel with an inductance which is tapped for each band setting, and then coupled to the antenna through a variable 430pF (loading) capacitor.

Checks were made on 3.5MHz and 7MHz using halfwave dipole antennas, and on 14MHz, 21MHz and 28MHz using a three element Yagi tri-band antenna. All used coaxial feeders and had good centre-band SWR figures. Using the tuning unit it was possible improve this to a 1 to 1 SWR on any portion of any band.

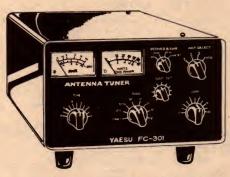A more exacting test involved a single wire, inverted "V" aerial, 53 metres long, with an apex 15 metres high. The tuning unit enabled the transceiver to be loaded to give close to



maximum output on all bands, including 1.8MHz, on which some good contacts were made. Several shorter random lengths of wire were fed and loaded for 7MHz and higher bands.

The most severe test involved a 2.5 metre long, centre loaded whip antenna originally tuned for mobile operation when mounted on the rear bumper bar of a station sedan vehicle. Used as a vertical antenna about two metres above ground it presented an extremely high SWR to the transceiver. However, coupled through the tuning unit it was a very effective antenna, producing a readability five, strength six report from Helsinki, in Finland, on 14MHz.

Yes, the units achieved their design purpose without any difficult or critical adjustments and are considered quite effective. They are of solid construction

and the components appear to be of good quality.

Although not affecting the performance of the units, here are two suggestions for worthwhile improvements. It seems that, with digital readout tuning now almost commonplace, and the emphasis on frequency allocations, the legend associated with control knobs and switches should read lower band edge frequency rather than metre bands.

Also desirable is a facility to enable all four antenna connections to be positively earthed when the tuning unit is not in use. This would provide protection from lightning strikes or the build-up of high static charges, particularly for solid state front end devices, and elimite the need to disconnect antennas as a safety precaution when the station is unattended.

The units are supplied with an eight page manual containing instructions, circuit diagram, and a photograph of the interior layout. There is also a coaxial cable connector to connect the tuning unit to the transceiver.

A section in the manual strongly recommends the procedure to be followed when matching antennas. It also points out that, although the correct impedance will be presented to the output of the transmitter, the tuning unit will have no effect on losses due to miss matches at the antenna or feeder line losses between the tuning unit and antenna.

The unis under review were supplied by Dick Smith Electronics Pty Ltd. (PJH-VK2APQ)

#### AMATEUR BALUN FROM SCALAR DISTRIBUTORS

Scalar Distributors Pty Ltd announce the availability of a substantially made commercial balun suitable for amateur use on all bands from 2MHz to 40MHz. Called the "W2AU Balun", it is manufactured by the Microwave Filter Co Inc, of U.S.A.

The balun is designed to replace the centre insulator in a dipole antenna. It is fitted with three stainless steel eyelets, two of which are used to terminate the two halves of the antenna. The third eyelet, at the top of the package, can be used to support the balun, and the aerial, for inverted "V" configurations.

As well as the balun, the unit contains a lightning arrester to assist the discharge of lightning and static electrici-

ty. It is fitted with an SO239 socket on the underside, is weatherproofed, and designed to withstand a 290kg (650lb) antenna pull. It weights only 184g (6.50z), and measures 38mm (1.5in) in diamter and 150mm (6in) long.

Two versions of the balun are available. The model K1:1 gives a 1 to 1 ratio and is designed to couple 50 or 75 ohm coax to a 50 or 75 ohm balanced load. The model K4:1 gives a 4 to 1 ratio and is designed to couple 50 or 75 ohm coax to 200 or 300 ohm balanced loads. Power rating is 1kW.

Price of either model is \$34.50, including sales tax. Further details from Scalar Distributors Pty Ltd, 18 Shelly Avenue, Kilsyth, Victoria, 3137, or 20 The Strand, Penshurst, NSW 2222.

## NEW YEAR TIME IS NEW GEAR TIME

Don't dilly dally pally - the longer you put it off the more it'll cost you



FT-101E

World's most popular transceiver! Get yours today, they'll never be cheaper! Cat. D-2860...\$975.00 (or from \$6.75 weekly)



Incredible matching linear amp. Full 1.2kW really stirs the DX. Team it with a 101E or 901D for a real signal.

Cat D-2546...\$585.00 (or from \$4.00 weekly)

Did you make a new year's resolution to work VHF - DX? Here's your chance! Take the hassle out of satellite work

Complete kit for both OSCAR 7 and 8 full instructions. OKK SMITH ELECTHONIS CO. OSCARTRAK SATELLITE LOCATOR KIT

Cat. K-3480

**EXCLUSIVE TO** DICK SMITH

Dick Smith's Oscar Tables Full basic details on OSCAR, prediction tables, standard orbits and tracking details. The most comprehensive brochure ever

assembled on OSCAR. Totally practical. Cat. B-3482

Morse

Economy key - value Cat. D-7105 Quality key - precision built Cat. D7101

Hi-Mound deluxe key Cat. D-7104 \$29.50 Electronic keyer kit Cat. K-3470 \$37.50 paddle only Cat. D-7103 \$17.50 Morse code trainer kit - includes oscillator key extra Cat. K-3472 \$5.90

[built up unit Cat. D-7110 \$7.90] Morse code cassettes - teach yourself - set of Cat. D-7106 only \$7.90

FANTASTIC OFFER

ARRL Handbook 1978 EDITION VED TO S

An absolute must for every amateur. Cat. B-2218

Accessories

Shinwa 500W L.P. filter Cat. D-7080

Viking 5kW L.P. filter Cat. D-7086 \$37.50 Type 101 rugged coax relay Cat. D-5210

\$44.50 small egg insulators Cat. D-5300 large egg insulators Cat. D-5302

> EASY TERMS ON ALL **ITEMS OVER \$111.00** ON 10% DEPOSIT.\*

\$1.20

#### HF Equipment We are YAESU distributors

FT-901D, FL2100B sold Cat. D-9050 usually \$3.95

PVC dust cover with each FRG-7, FRG-7000, FT-101E, 🗡 🛠

FRG-7 HF receiver Cat. D-2850 \$395.00 FRG-7000 deluxe HF receiver Cat. D-2848 \$695.00

Shortwave antenna kit Cat. K-3490 FT-301 S/S 200W transceiver Cat. D-2870 Huge Reduction SAVE \$100.00! \$895.00 FP-301 AC power supply Cat. D-2872

\$195.00 FC-301 antenna tuner Cat. D-2896 \$249.00 FT-901D ultimate transceiver Cat. D-2854 \$1375.00

FC-901 new antenna tuner Cat. D-2855 \$289.00

FT-7 Incredibly popular novice/mobile rig. Cat. D-2866 \$535.00 FL-110 200W linear Cat. D-2884 \$255.00

CPU-2500K 25 watts, keyboard mic, 4 memories & scanner. Cat D-2889 \$575.00

FT-227R 2M synthesized. Cat. D-2890

\$395.00 FT-227 RA with up /down scanner. Cat. D-2891 \$445.00 FTV-250 2m transverter Cat. D-2894

\$339.00 Quartz 16 2m FM transceiver Cat. D3009 incredibly, only \$169.50 TR-2200 Cat. D-3210 \$189.00

TR-7200 Cat. D-3215 \$199.50 TV-502 2m transverter Cat. D-3502

now only \$245.00 YC-500S 500MHz counter Cat. D-2892

MAIL ORDERS? Certainly! Postage & packing extra. ······

#### plete with control box and power supply. \$149.00 rotator and control box only Cat. D-5000 \$133.00

Heavy duty FU-400 antenna rotator com-

#### ANTENNAS

Incredibly popular mobile antennas RSE-M-2 gutter grip Cat. D-4100 \$32.50 RSE-2A 2m ¼wave stub Cat. D-4102 \$10.95

RSL-145 6m/2m combined whip Cat. D-4104 \$23.95 RSL-3.5 80m mobile whip Cat. D-4110

RSL-7 40m mobile whip Cat. D-4112 \$19.95

RSL-14 20m mobile whip Cat. D-4114 \$20.95

RSL-28 10m mobile whip Cat. D-4118

SYDNEY 125 York Street, SYDNEY. Ph. 290-3377

147 Hume Hwy, CHULLORA. Ph. 642-8922

162 Pacific Hwy, GORE HILL. Ph. 439-5311

30 Grose Street, PARRAMATTA. Ph. 683-1133

RSL-21 15m mobile whip Cat. D-4116 \$20.95 \$20.95

#### HY-GAIN

18AVT 80-10m trapped vertical

Cat. D-4302 \$135.00 TH3JR 3 element triband beam

Cat. D-4304 \$199.00 TH3MK3 large 3 element beam

Cat. D-4306 \$299.00

TH6DXX 6 element thunderbird Cat. D-4308 \$399.00 BN86 balun Cat. D-4300 \$19.50

(only available with a Hi-Gain antenna purchase)

2 metre beams also available WILSON

System 1 tribander Cat. D-4330 \$350.00 System 2 tribander Cat. D-4332 \$269.00 BN-50A Balun, Cat. D-4334 \$19.95 BL-50A Rak balun, Cat. D-5310 \$27.50 \$\$9.00

Balun kit. Cat. D-5350

399 Lonsdale Street, MELBOURNE. Ph. 67-9834

656 Bridge Road, RICHMOND. Ph. 42-1614 BRISBANE 166 Logan Road, BURANDA. Ph. 391-6233 ADELAIDE 203 Wright Street, ADELAIDE. Ph. 212-1962

SHOPS OPEN 9AM to 5.30PM (Saturday 9AM - 12 noon) BRISBANE 1/2 Hour earlier

ANY TERMS OFFERED ARE TO APPROVED APPLICANTS ONLY

Many lines available from the

MAIL ORDERS P.O. Box 747, Crows Nest, N.S.W. 2065. Post and packing extra.

# SHORTWAY SCENE



# More frequencies and restricted power predicted

Various countries are putting forward ideas to be presented at the World Administration Radio Conference (WARC), to be held in Geneva this year. The Conference will determine the allocation and control of frequencies, including the short-wave bands.

There have already been proposals to increase the size of many of the existing short-wave bands to allow for more frequencies for international broadcasting. One idea, which has not been approved by third world countries, is the use of the present 60-metre tropical band for international broadcasting. The use of this band would be a point of concern for short-wave listeners world-wide, as the lower-powered African and Latin American stations could be lost if high-powered international stations used the frequencies between 4750 and 5060kHz.

At the same time there have been moves afoot to give international stations a maximum power output so that super-powered transmitters on short-wave would be banned. Radio Canada is putting forward the suggestion that 250kW be the maximum power allowed for international broadcasting, as they believe that this power, with its limitations, would force stations to improve their aerial systems and give a better beam and concentrated signal on target areas. This would of course reduce interference to other transmissions, not only to those adjacent to the frequency but also those using the same channel.

Radio listeners in Australia and New Zealand have been making submissions to the various government departments that will be attending the Geneva Conference, and it is known that radio amateurs are also concerned of the possibility of in-roads into the

frequencies they have been allocated in the past.

The frequency plan put forward by most countries seems to be consistent with the idea that all the present shortwave bands should be increased to double their present size, and a new frequency band be opened around 13600-14000kHz. The expansion of the bands would not include the present 13 and 11-metre bands, which appear to be sufficient for the frequencies being used during the maximum sunspot period.

### **BROADCASTS TO AUSTRALIA**

Over 30 countries have special transmissions to Australia every day, and this short summary only includes information about stations which have changed frequency for our summer reception period. During our summer evenings, signals on the higher frequencies reach their peak. Many stations are now using the 16 and 13-metre bands to serve this area more effectively during the period of high sunspot activity.

AUSTRIA: The Austrian Radio at Vienna has three transmissions to this area: 0400-0600GMT on 17770kHz, 0700-0900 on 17720kHz and 0900-1300 on 21715kHz. Additional coverage is noted at 0600GMT on 21470 and 21555kHz, and both these signals are well received at the moment. The English broadcasts are at 0430 and 0830, and the 30 minute program is called "Report from Austria".

CANADA: Radio Canada provides a secondary coverage to Australia in several transmissions. The broadcast 2130-2200GMT on 15150, 15325 and 17820kHz has been well received, with the additional frequency of 11945kHz providing fair reception. During our afternoons the 30 minute program at 0300GMT is noted on 9535 and 11845kHz, while it is repeated at 0400GMT on 9535kHz.

**DENMARK:** Radio Denmark has a daily transmission to Australia 0900-1000GMT on 15165kHz. The station is now using this frequency for all its broadcasts, having dropped the experimental transmissions on 6175 and 9710kHz.

GREECE: Athens continues to be well received with its program of Greek and English 0900-0905GMT on 9655 and 15160kHz. Transmission for our morning reception is received 2100-2150GMT on 6140, 9655 and 9760kHz. A further transmission in Greek is broadcast 2200-2250GMT on 9655kHz. GERMANY: Deutsche Welle, in its English broadcast to Australia, has added the new frequency of 21680kHz for the transmission 0930-1030GMT. The other frequencies carrying this program are 9650, 11850, 15275, 17780, 17800 and 21540 kHz. The new channel of 21680kHz is being well received. The morning broadcast in English 2100-2200 is on two frequencies: 7130 and 9765kHz.

ISRAEL: Jerusalem uses several frequencies for our afternoon reception in English 0500-0515, followed by a broadcast in French to 0530GMT. Three frequencies — 11655, 17855 and 21495kHz — are used, with the former being the best received. The latest schedule from the Israel Broadcasting Authority gives details of two further English broadcasts: 1200-1230GMT on 11655, 15405, 15530, 17685 and 21495kHz; 2000-2030 on 9009, 9425, 9815, 11655 and 17685kHz.

**SWEDEN:** Radio Sweden is now using 21690kHz for its English broadcast to Australia and New Zealand 1100-1130GMT. This frequency replaces 15125kHz. The single sideband transmission to this area, which is a relay of the Swedish home program 0500-0830GMT, continues to be received on 21550kHz.

SWITZERLAND: Swiss Radio International is the new name for the overseas service of the Swiss Broadcasting Corporation, Berne. Two English transmissions are broadcast to Australia each day. The broadcasts are 0700-0730 and 0900-0930GMT on 9560, 11780, 15305 and 21520kHz. The balance of the transmission includes Italian at

Notes from readers should be sent to Arthur Cushen, 212 Earn Street, Invercargill, NZ. All times are GMT. Add 8 hours for WAST, 10 hours for EAST and 12 hours for NZT. In areas observing daylight time it is necessary to add one hour.



# ARLEC DMM 10

### **Features**

- Large %" (9.5.mm) LED Numerals
- Automatic Decimal Point
- 3 Digit 0-999 Display
- Instantaneous Readout
- Zero Locked
- 7 MEGOHM Input Impedance
- 12 Measuring Ranges
- Over-range Indication
- Overload Protected
- 1% Accuracy

### Supplied complete with:

- 1. Rechargeable Nicad Batteries
- 2. Combined AC Adaptor & Battery Charger
- 3. Connector for charging from auto battery
- 4. Test Prods
- 5. Operating instructions
- 6. 12 month guarantee

A Heavy Duty Carrying Case is available as an optional extra.

SEE THEM AT YOUR LOCAL ELECTRONICS STORE OR THE A+R ELECTRONICS BRANCH IN YOUR STATE.



A+R ELECTRONICS

A MEMBER OF THE A & R-SOAHAR ELECTRONICS GROUP

30 Lexton Road, Box Hill, Victoria

\_\_\_\_\_\_\_\_\_\_

### SHORTWAVE SCENE

0730, French 0800 and German 0830GMT.

**USA:** The Voice of America has two daily transmissions to the South Pacific: from 1100-1400GMT on 5955 and 9730kHz; and from 2200-2400GMT on 15290, 17820, 21610 and 26095kHz.

USSR: The Radio Moscow World Service has now been extended to 19 hours a day from 0400 to 2300GMT. The balance of the day is devoted to a special transmission to North America. English news and commentary is broadcast every hour on the hour, with news headlines on the half hour.

**VATICAN:** The Vatican Radio is using 15120kHz for our summer reception period and this frequency carries the English broadcast 2210-2225GMT. Two other frequencies — 9615 and 11705kHz — also carry this special transmission to Australia.

### **AFRICAN SIGNALS**

Signals from Africa in the 60-metre band are best received at dawn during September and March, and these signals should again be heard in about a month's time. This review is a listing of observations at our own location, together with items provided by Peter Bunn of Melbourne in "DX Time," on Radio Australia.

MAURITIUS: Forest Side is noted on 4850kHz, closing at 1830GMT. The station has also been noted with "Saturday Special" in English, closing at 1900GMT, the normal sign-off time for Saturdays.

**SEYCHELLES:** The Far East Broadcasting Association has been heard on 15405kHz with a program in Farsi to 0345GMT and then a program in Arabic

then a program in Arabic. **SWAZILAND:** Trans World Radio has been noted on two frequencies with a Portuguese program on 4790kHz at 1830GMT and a gospel program in German on 4760kHz at the same time.

### **NEW VOA OUTLETS**

The Voice of America has added another frequency to the 11-metre band with a broadcast to the Far East on 25990kHz from 2200GMT. The broadcast to Australia and New Zealand in English has also undergone a frequency change. The transmissions are now 1100-1400GMT on 5955 and 9730kHz from Dixon, 2200-2400GMT on 21610 and 26095kHz from Dixon, and 15290 and 17820kHz from the Philippines relay base.

The latest VOA schedule also shows that the 11-metre band is being used by the Greenville transmitter on 26040kHz from 1600-2000GMT. This transmission is beamed to Africa using the power of 50kW. At 1100GMT, the VOA is using some new channels to the Far East, including 15245kHz 1100-1330GMT, while 17840kHz is used 2200-2400GMT from the Delano transmitters in California.

### LISTENING BRIEFS ASIA

**ISRAEL:** Jerusalem, in its special transmission to Australia with English 0500-0515GMT, now uses three frequencies: 11655, 17855 and 21495kHz.

PAKISTAN: Radio Pakistan has recently introduced a short news bulletin in English at 1005GMT as part of their World Service to Europe. The transmission is carried in Urdu for the rest of the program 0700-1100GMT on 17665 and 21625kHz. A full news bulletin in English is broadcast at 1100GMT on the same frequencies. The transmission to Europe, heard during our mornings 1915-2145GMT, is received on 9465 and 11677kHz.

**SAUDI ARABIA:** The Riyadh transmitter has been observed on 15060kHz by John Mainland of Wellington, NZ. Broadcasts are in Arabic and noted at 0730 and 1800GMT. This frequency is also used by Radio Peking, while some sideband interference has been noted from these two stations to the BBC on 15070kHz.



### WIA and WARC '79

One of the main functions of the Wireless Institute of Australia, according to many people, is to represent amateur radio nationally and internationally. This is quite apart from the various membership services, including the monthly journal, available to members.

The WIA does represent Australian amateur radio. Officers of the Institute have spent countless hours of their own time negotiating better conditions for amateurs with the Posts & Telecommunications Department. Unfortunate-

ly this is not enough. Why?

Amateur radio in Australia is one of the many services governed by the Wireless Telegraphy Act and Regulations. A very large number of the Regulations stem from international radio regulations adopted by the member countries of the International Telecommunications Union. Australia is one of the 154 member countries of the ITU.

About once in every 20 years the ITU holds a general administrative conference to revise the international radio regulations relating to all the world-wide allocations in the frequency spectrum and various associated matters. The next conference, WARC '79, is to

be held in Geneva in 1979.

At WARC'59, the amateurs of Australia were so concerned about the amateur service that, through the WIA, they lobbied for and were successful in obtaining amateur observer status on the Australian delegation. This amateur was the late John Moyle, VK2JU. His attendance highlighted the belief that amateurs must always be present at the vitally important conferences and, of course, the International Amateur Radio Union (of which Australia through the WIA is a member) is best geared to cover the general interests of amateurs. His report also highlighted the need for an amateur to be part of the Australian delegation and consequently the WIA established a fund shortly afterwards to enable this amateur participation to occur in the future.

WARC '79 is a 10 week conference. Leading up to this, each country's Government must make plans and prepare a brief for the delegation. Australia has been involved with this

for two years and the amateur service is one of the Committees forming part of the Planning Group. As part of the preparations for WARC '79 a meeting of Governments' technical experts (CCIR) will occur in Geneva later this year. Australia will participate.

Ministerial assurances have been given that an amateur representative will be included in the Australian

delegations.

Simultaneously a tremendous amount of preparatory work has been carried out by the IARU. Once again Australia has been involved through the WIA. This preparatory work is aimed at amateurs throughout the world influencing their Governments, through amateur societies, to ensure as uniform and strong a voice as possible is heard from amateur radio. This is vital both now and throughout WARC '79 to ensure that commercial and other interests do not take away any of our frequencies and privileges without the strongest possible fight.

It is sadly true that all these efforts cost money. Members of the WIA have met the brunt of the financial burden but in comparison with America, Japan and Europe we are comparatively small

in numbers.

Additional funds are essential if the radio amateurs of Australia are to assure themselves that no losses occur to our amateur service by default. Amateurs and others can help in either or both of two ways: By sending a donation to the ITU fund, and/or by joinging the WIA.

Donations should be sent by crossed cheque, money order or postal order made out to "W.I.A." and sent to P.O. Box 150, Toorak, Victoria 3142.

P. B. Dodd, Secretary, Wireless Institute of Australia, Toorak, Victoria.

### Film striping

In the October issue of Electronics Australia on pages 50 & 51 there appears an article "Electronic eraser for mag film and tape". In the bottom right corner of page 51 a little item appears i.e., "Where can I get film striped".

We are manufacturers of film striping equipment and are in the film striping business. We are the original and the

major company in the film striper manufacturing business and also the major film stripers in Australia. We cater for film laboratories, camera stores throughout Australia, government departments, schools, industry and the public. Our charges are in accordance.

I thought I would like to bring the foregoing to your attention as there are many people in Australia and the Pacific and in overseas countries whom we cater for in addition to those residing in Sydney and surrounds and in NSW country towns who require a service they can trust and require the best in performance.

Our prices are (retail): Std & Super 8mm single track: 3 cents per foot with a minimum of 100 feet. Cost of balance stripe is additional. We stripe both double and single perforated 16mm film. We also lay in stripe on 8mm and 16mm prints. We will be only too happy to supply details to those interested.

I trust the above is of interest to you and your readers.

E. K. De Cean (Gp Capt RAAF Rtd) 3-S Sound Stripe Services 10 Glenwood Avenue Beaumaris, Victoria 3193.

### **Apprentices**

I read with interest the article in your September issue concerning the apprentice at station 3DB, and decided to let you know that STW 9/6KY Perth also has an apprentice scheme in operation. In 1978 we had two apprentices in Stage 4 and two apprentices in Stage 3, and we intend to continue again this year with a further apprentices. Our current Stage 4 apprentices will complete their formal training at the end of 1979 and their efforts until now are a credit to them.

The apprentices attend the Mount Lawley Technical College and are training with the Radio and TV Servicing Trades. Our recruiting has been by selection from the Pre-apprenticeship Courses held at that college.

I hope that this is of interest to you

and your readers. Bob Penno

Asst Chief Engineers, STW9 Tuart Hill, WA

# **New Products**

# Trio CS-1570 Dual Trace 30MHz Oscilloscope

While it looks very similar to other dual trace oscilloscopes in the Trio range, the top-of-the-line CS-1570 is a considerably upgraded and more complex unit. The CS-1570 has a bandwidth from dc to 30MHz and a maximum sensitivity of 5mV/cm.

Dimensions of the CS-1570 are 277 x 204 x 440mm (W x H x D) and mass is 8.5kg. The unit has a large carrying handle which also functions as a tilting bail for convenient viewing.

Vertical deflection sensitivity is adjustable in ten ranges in a 1-2-5 sequence from 5mV/cm to 5V/cm, with continuous variation being available via a small knob concentric with each channel's attenuator. Input impedance is one megohm shunted by 22 picofarads. Rise-time of the vertical deflection amplifiers is 11.7 nanoseconds with overshoot less than 3%.

Maximum input signal to either channel is 600 volts peak-peak or 300V (dc + ac peak). Each channel input is controlled by a three-position switch which provides dc or ac coupling or grounds the input. Crosstalk between channels is quoted as 66dB at 1kHz, although the test conditions are not stated.

Twenty timebase ranges, in a 1-2-5 sequence, give sweep speeds ranging from 0.5 seconds to 0.2 microseconds per division (one division equals one centimetre). Continuous adjustment is again provided in the form of a concentric vernier knob.

As with other Trio oscilloscopes, the timebase can be switched off to give X-Y operation, with the CH2 signal being the horizontal component.

Comprehensive timebase triggering facilities are provided on the CS-1570 with four switches and one knob. Triggering can be on the positive or negative slope of waveforms and low or high frequency filtering can be employed. The timebase can be triggered from channel 1 or channel 2.

There are switches to select the display mode, which can be either channel 1 or 2 or both (dual trace) or the sum or difference of both channels. The "Add" mode is particularly handy for checking phase differences (or propagation times) of two different waveforms. In fact, it is the only

method of accurate comparison of waveforms at fast sweep speeds, because the CS-1570 cannot be switched to the alternate trace mode at the whim of the user. The unit changes automatically from chopped trace to alternate trace for sweep speeds above (and including) 0.5 milliseconds per division

For calibration of the sweep speed and vertical amplifier sensitivity a reference 1kHz 0.5V peak-peak section of general test methods and applications for the oscilloscope.

Optional accessories for the CS-1570 oscilloscope are a pair of PC-28 probes. These may be switched from 10:1 attenuation to direct connection by disconnecting the probe tip and reinserting after rotating through 180 degrees. Input impedance in the direct mode is one megohm shunted by 120pF or less, while in the 10:1 mode it is 10 megohms shunted by 18pF or less. Maximum input is 500V peak-peak.

We found the oscilloscope easy to

We found the oscilloscope easy to use and the sync and triggering facilities particularly good. The tube gives bright and sharp displays, although by comparison with a com-

The Trio CS-1570 features comprehensive sync and triggering facilities and has a mesh-type PDA tube. The vertical channels have delay lines to enable the risetimes of pulses to be viewed.



waveform is provided. The amplitude of the waveform is accurate to within  $\pm 1\%$  while the frequency accuracy is  $\pm 3\%$ .

The oscilloscope employs a 130mm diameter tube with a mesh type PDA (post deflection acceleration) electrode. The accelerating potential is 4kV overall, which is provided by a high frequency inverter. Apart from the tube, all the circuitry is solid state, with 10 ICs and a large number of discrete semiconductors.

A comprehensive manual is supplied with the instrument. Not only does it include full details of the circuitry and its adjustment, but it also has a large peting model (of lesser bandwidth) the display focus and brightness was not as good with pulse waveforms, which require very fast trace writing speeds.

The probes are a little awkward to use in practice and we have a preference for those that are switchable between direct and 10:1

Our overall impression of the CS-1570 is that for the facilities it offers, it represents good value for money. Further information can be obtained from the distributors for Trio test equipment, Parameters Pty Ltd, 68 Alexander Street, Crows Nest, NSW 2065 (L.D.S.)

### **B&K Model E-200D RF Signal Generator**

This middle of the road RF signal generator fills a gap between the very expensive laboratory models and those which are little more than toys. The B&K Model E-200D should meet a need for a quality instrument at a reasonable price.

The B & K Model E-200D RF Signal Generator promises to fill a gap between the top line laboratory-grade signal generators and the very simple ones. By "simple" we mean those which are basically a calibrated oscillator, with usually only a token attenuator which could not be seriously

calibrated for output.

The E-200D is housed in a neat metal cabinet with ligh khaki painted ends and bottom. An L-shaped piece covered with black vinyl is removable and forms the top and back panels. The front panel is finished in matt black with white engraving. Dimensions are 322mm wide x 180mm high x 170mm deep, plus knobs. Shipping weight is given as approximately 14 pounds, which is a bit less than 6.5kg.

Frequency coverage of 100kHz to 54MHz is achieved on fundamental, in five bands. These are 100kHz to 370kHz, 370kHz to 1400kHz, 1.4MHz to 5.1MHz, 5.1MHz to 16MHz, and 16MHz to 54MHz. Two extra ranges are added covering 32MHz to 108MHz, using the second harmonic, and 64MHz to 216MHz, using the fourth harmonic. Frequency calibration checks can be made at 1MHz and 100kHz points from a crystal oscillator. The heterodyne principle is used, the beat note coming from a small loudspeaker mounted behind the main dial scale.

RF output attenuation is achieved by seven slider switches, five giving 20dB each, one 10dB and one 6dB, giving 96 dB in all. Further fine attenuation is available with a rotary attenuator, calibrations being read off the meter up to 10dB. RF output levels of down to 0.5uV, corresponding to -106dB, and up to 126mV, corresponding to +2dB, are available when properly terminated with the cable provided. In practice, these levels can be exceeded by a useful amount in each direction without the benefit of calibration.

The carrier generated may be used unmodulated but provision is made to amplitude modulate at approximately 400Hz with an internal audio oscillator. The RF generated may also be modulated from an external source, while the output of the 400Hz internal audio is also accessible from the front panel. Modulation depth is adjustable, with up to 50% indicated on the meter. Modulation up to 100% is available, but external means would be needed to measure values above 50%.

Frequency accuracy is quoted as +1.5% of the highest frequency on any given band, usable to  $\pm 0.1\%$  with crystal calibrator. The dial scale cursor

is adjustable to enable accurate frequency setting at any calibrator point.

Calibrated RF output accuracy is quoted as ±1dB from 100kHz to 54MHz. No figures are given for the two higher ranges as harmonics are used and calibrations would not be valid.

A large metal dial 128mm in diameter carries the seven scales, alternately in black and red. Although the seven scales occupy most of the available space, it is uncluttered and easy to read. A 6:1 planetary drive between the tuning knob and the dial gives a smooth action and allows easy and accurate set-

An instruction manual is included which gives the circuit of the unit, together with a full description. Operating instructions are clearly set panel and this results in quite floppy controls.

To cure this problem it would be necessary to fit a second bush to the front panel, as well as fitting a flexible coupling between the sub-assembly and the front panel. This would add a little to the cost but I think that it would be worthwhile.

Still on the subject of mechanics, two other improvements would seem to me to be worth while. For ease of operation it would be nice to have some sort of prop so that the front panel can be inclined for better access to the controls. A carrying handle would also be a welcome addition. Perhaps these latter points may be a matter of individual choice; to be sure they do not affect the basic performance of the instru-

Having made a check on the question of RF leakage, with the facilities available, I was impressed with the performance of the attenuators. It may be that higher priced units would be somewhat better down in the sub-



out and easy to follow. Also, suggested methods of using the generator are given, including methods of receiver alignment where such is not available for the particular receiver to be aligned. Suggestions are also given for the alignment of FM receivers and television receivers.

I found the instrument easy and convenient to use, but some of the mechanical aspects seem to have suffered due to cost cutting. The knobs are of the spring-loaded push-on type which fit a standard half-flat shaft. These do the job but they are inclined to be a bit floppy when compared with knobs which are secured with a good grub screw. Also, the range switch and fine attenuator shafts originate from internal sub-assemblies. These shafts pass through clearance holes in the front microvolt region, but I am of the opinion that for most practical purposes, the readings could be relied upon.

To sum up, at the price of \$345 including sales tax and \$299 without sales tax, this should be a worthwhile generator for professional and amatuer use where the ultimate is not required.

The E-200D was submitted for review by B&K distributors Paramaters Pty Ltd, 68 Alexander Street, Crows Nest, NSW 2065. Further information may be obtained from the above address, or by phone on 439 3288 in Sydney, or 90 7444 in Melbourne. (ILP).

Order your copy now of the "ELECTRONICS AUSTRALIA" PROJECTS & CIRCUITS NO. 2 \$3.00 plus 60c p & p **Electronics Australia** Box 163, Beaconsfield, NSW 2014

## ECIAL PURCHASES



### GARRARD Model SL65B

RECORD CHANGER AT LESS THAN \$35.00 1/3 LIST PRICE

(RECOMMENDED RETAIL PRICE \$110.00) SUPPLIED WITH SHURE M75-6s MAGNETIC CARTRIDGE AND DIAMOND STYLUS

Also available with ceramic cartridge and \$30 All changers new in original cartons Send S.A.E for full specifications

A precision automatic and manual record-playing unit fitted with Garrard Synchro-Lab4 pole shielded motor to provide constant speed conditions for the 10½ inch aluminium turntable. The low resonance tubular pickup arm is counter-balanced with a resiliently mounted weight to permit light sensitive tracking, and the slide-in cartridge carrier enables styles inspection and the interchange or replacement of cartridges to be carried out simply and quickly. Fine stylus force adjustment and bias compensation are both calibrated for accurately setting the arm to give optimum playing conditions for the chosen cartridge.

The fluid-damped level-type cue and pause control ensures gentle lowering of the pickup to the surface of the record. A short spindle is supplied for single record play records. Precision engineering is reflected in the styling of the SL65B, which is elegantly finished in black and silver.

POST AND PACKING EXTRA NSW \$3.75

Send SAE for details Vic., SA & Qld \$5.75 Tas., WA & NT \$7.00 (Reg. post \$2.00 extra)

BASE & PERSPEX COVER FOR GARRARD OF B.S.R. UNITS \$29.50 EXTRA PLUS FREIGHT

### NEW IMPORTED HOKUTONE 12" HI-FI SPEAKERS

These 12" speakers have a frequency range to 5000 cycles with a resonant frequency of 30 cycles. Max. power 30 watts. Post & packing NSW \$2.50. Interstate \$3.50.

\$17.50

### **NEW GOODMAN-FOSTER 3-WAY** 4 SPEAKER HI-FI SYSTEM

\$39.00 PER KIT

Frequency Range 45 to 22,000 cycles. Power rating 25 watts. RMS Imp-8ohms. Supplied in kit form (less cabinet) each kit comprises two English Goodman 8" bass units. Foster 5" mid range. Foster 1" dome tweeter crossover components. Ocodensers and inductance innabond, speaker fabric and plans of cabinet. Cabinet

dimensions 23" x 13" x 10". CABINETS AVAILABLE.

Post & packing extra: NSW \$2.70; VIC, SA, QLD \$4.70; WA \$5.70. (REGISTERED POST \$2.00 EXTRA IF REQUIRED) cabinets available.

### NEW MAGNAVOX — MV50 — 50 WATT SPEAKER SYSTEMS As featured in Feb. 1976 issue of Electronics Today

Complete kit of parts (less cabinet) comprising Magnavox 10-40 10" bass unit. 625 mid range 6" two XJ3 dome tweeters, crossover network, innabond, speaker silk and plans of cabinet.

> \$87.00 PER KIT

Freight extra per rail or air freight. Cabinet available. 830 System also available.

### NEW STANDARD B.S.R. C129 RECORD CHANGERS \$25.00

LESS THAN 1/2 LIST PRICE

Fully automatic turntable plays up to six records fully automatically and single records automatically and single records automatically or manually required. 11" turntable. Cue & pause control. Record speeds 33 1/3, 45 and 78 rev/min. Finished in black with silver trim. Player and changer spindles supplied. Fitted with ceramic cartridge. Post & packing extra NSW \$2.70; Vic., Qld.. SA \$3.70; WA \$4.70 (registered post \$2 extra if

Spare cartridge and stylus for above \$3.50 (list price \$10.00)




Incl. spare cartridge and stylus

B.S.R. STEREO PLAYER MODEL LESS THAN ½ PRICE
P128B \$39.00 WITH SHURE
M75CS MAGNETIC CARTRIDGE
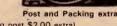
#### PROFESSIONAL SERIES

Auto or manual operation 3 speed, 11½" diecast turntable 4 pole shielded motor. Slide-in cartridge carrier. Counter-balanced pick-up arm. Fine stylus force adjustment & bias compensation. Damped lever type cue & pause control. Diamond stylus

NSW \$3.75, VIC. SA & QLD \$5.75, Tas. WA & NT \$7.00 (reg post \$2.00 extra)



#### GARRARD M.82 \$60.00

TRANSCRIPTION CHANGER

Supplied with Pickering Cartridge with Diamond Stylus. Post & Packing (reg post \$2.00 extra), NSW \$3.60, Vic., SA, Qld \$4.74, Tas. \$5.50, WA & NT \$7.00.



245 PARRAMATTA RD, HABERFIELD 2045. PHONES 798-7145, 798-6507.

### **New Products**

### LCD calculators

A new series of advanced pocket calculators featuring liquid-crystal displays, compact size and long battery life, has been released by Toshiba Australia Pty Ltd. They cover the needs of a wide variety of users from students, housewives and office staff up to business executives and scientists.



Smallest in the range are the slim-line Model LC-850M and the thin creditsize Model LC-581. Battery life on these is 2,000 hours continuous operation. Two other models incorporate digital watches with an alarm; one of these has a calendar and stopwatch facility as well.

The scientific calculator is ideal for engineers, mathematicians and advanced students. It offers 39 functions, and a 12-digit readout.

For the business executive, the electronic "brain" model includes 30 independent alphanumeric memories for names, dates, telephone numbers and similar constantly-used data.

### AC wiring detector



Instantaneous non-contact indication of AC mains wiring is provided by the E-Z Scan Detector, a hand held battery powered device. Indication is via six LEDs, the number lit indicating the proximity of the wiring. Typical detection range is 20cm for 240V AC wiring, allowing detection of domestic wiring in walls, etc. It can also be used to find breaks in appliance cords and buried radiant heaters. From University Graham Instruments and most leading wholesalers.

### **New Products**

### 153cm screen TV




National Panasonic has released "Cinema-Vision", a compact one-piece projection colour TV system with a 153cm diagonal screen, UHF/VHF tuner and remote control. The projection system uses three tubes and a fold-out mirror, to give a picture three times brighter than a movie theatre image.

The CinemaVision comes complete with a 26-function infra-red remote control. It also has the ability to replay video tapes using either PAL or NTSC

formats.


Enquiries to National Panasonic (Australia) Pty Ltd, PO Box 278, Kensington, NSW 2033, or National dealers.

### **DC-DC** converter

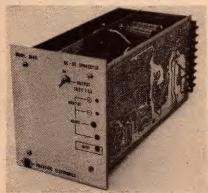

The latest DC-DC converter in Scientific Electronics' range has all of the features of the existing 96D model, but now provides two independent and isolated output rails each capable of delivering 60W. The new model 96DB will operate over a wide DC input voltage range without changing any voltage links or taps. It has high efficiency, good regulation, overload and short-circuit protection. Further information from Scientific Electronics, 48 Barry St, Bayswater, Victoria 3153.

### Digital thermometer

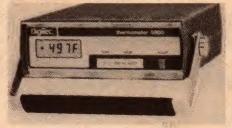

The latest additions to the DigiTec range of portable digital thermometers are the 5900 series, which offer thermocouple and RTD sensors, readout in either Celsius or Fahrenheit, and either LCD or LED display. Resolution of the series is 1 degree C or F. Optional analog output is available on all models, to allow strip chart recording of temperature trends.

Models are available offering compatibility with J, T, E or K type thermocouples, or PT100 platinum sensors.

For further information contact NIC Instrument Co, Matthews Avenue, Airport West, Victoria 3042.


### Power opto-coupler

opto-coupler, the COP-008, designed for power switching in such applications as machine tool controls, computer peripherals, heating controls

and lamp drivers. The device can perform zero-voltage switching and is capable of controlling up to 8A in 380V circuits.

Available from Instant Component Service, which has branches in most states.

### Solid state relay

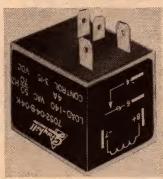

The Grayhill 4 amp Mini Cube solid state relay is now available with terminations compatible with standard relay sockets, allowing direct plug-in interchangeability. The solid state relay measures 25 x 30 x 25mm and switches from 0.1 to 4A at 120V or 240V AC. No additional heatsinking is required for operation at rated loading.

Further details from Acme Engineering Co, 2-18 Canterbury Rd, Kilsyth, Victoria.

VIDEO TECHNICS

THE CAROUSEL CENTER, SHOP 17 & 18, 530 OXFORD ST., BONDI JUNCTION. P.O. BOX 50, BONDI ROAD, BONDI 2026, NSW 2022. TEL: 387 2555. 3RD FLOOR, EQUITABLE LIFE BUILDING, 301 CORONATION DRIVE, BRISBANE 4064. PH. 36 1257.

### 3 HOURS VCR VIEWING



3 hours continuous recording/playback. 1-2-3 operation simplicity. Video head and azimuth recording system: key to perfect picture reproduction. The ingenious yet simple "M" loading system, low 35 watts power consumption.

### VIDEO EQUIPMENT -

Sony, Akai and JVC Colour and BW Portopacks. We have several BW Portopacks traded on colour sets. Also agents for JVC, National, Sony and Nec Umatic equipment. All formats and brands colour and BW recorders, editors, generators and blank video tapes available. New and used equipment. Trade and terms.

Specials. Also transfers from Super 8 film to video tape.

### **VIDEO MOVIES**

### FULL LENGTH FEATURES — MANY TITLES AVAILABLE AUSTRALIA WIDE


These movies suitable for all video players including U-matic, Philips, Grundig One, and two-hour machines, Betamax and VH(S).

Movies available in all classifications from G to R rating.

We require dealers and franchises in all states.
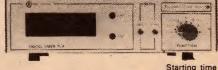
### SPECIAL CLOCK TIMERS


Can be set to switch equipment up to 4 days ahead.



accurate to a second

\$195 + P.P

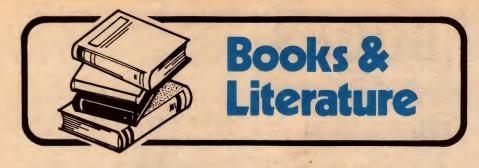FRANCHISEES REQUIRED FOR S.A., W.A., VICTORIA AND TASMANIA



### New ARRL handbook

THE RADIO AMATEUR'S HANDBOOK, by the Headquarters Staff of the American Radio Relay League, Fifty Sixth Edition, 1979. Soft covers, 208 x 275mm, 538pp, many diagrams and pictures.

The latest yearly edition of the "Handbook" has arrived somewhat earlier than usual. And that's not all. It comes in a new format, with somewhat larger pages, having three columns instead of two. The new format is in keeping with that adopted for QST since about January, 1976. Using it has meant that the entire book has been laid out anew. Also much of the text has been revised or rewritten.

Other changes involve some rearrangement of the chapter subjects. The chapter on Amplitude Modulation and Double-Sideband Phone has been dropped and in its place a chapter on the new technique of Narrow-Band Voice Modulation has been added. This new chapter gives a good idea of this new breakthrough method, which promises to conserve bandwidth and so allow about twice the number of channels compared with the now normal SSB mode.

Another change is a negative one, in that the popular chapter listing vacuum tubes and semiconductors has been dropped. Presumably the reason for this would be to prevent the new handbook from becoming larger than the publishers wished. Also, it could be reasonably assumed that the publishers took the view that the information was already available quite readily from other sources.

Along with the many other changes to the handbook, the page numbering has been changed, from starightforward numbering to the system where each page is identified by the chapter number and the page number of that chapter. This latter system can have some advantages and I found it quite acceptable and convenient to use.

The larger format makes the book easier to handle and due to the fact that this format is more efficient, the publishers have wisely adopted a slightly larger type face. This naturally makes it easier to read. In the copy which I had for review, there were a couple of large ink blotches, one each on pages

7-16 and 6-44. But this was an early copy from a preliminary run, and hopefully we can expect that this fault will be rectified for copies coming off the press later on.

For readers not familiar with the chapter headings to be expected from this ARRL publication, here is a list. 1. Amateur Radio; 2. Electrical Laws and Circuits; 3. Radio Design Technique and Language; 4. Solid-State Fundamentals; 5. AC Operated Power Supplies; 6. HF-Transmitting; 8. Receiving Systems; 9. VHF and UHF Receiving Techniques; 10.Mobile, Portable and Emergency Equipment; 11. Code Transmission; 12. Single-Sideband Transmission; 13. Frequency Modulation and Repeaters; 14. Narrow-Band Voice Modulation; 15. Interference with other Services; 16. Test Equipment and Measurements; 17. Construction Practices and Data Tables; 18. Wave Propagation; 19. Transmission Lines; 20. Antennas for High Frequency; 21. VHF and UHF Antennas; 22. Operating a Station.

If you do not have a recent copy of the ARRL Handbook, then this new edition is a must. If on the other hand, you do have a recent copy, then you may like to have a look before you invest in this one.

Our review copy came from Dick Smith Electronics. They quote the price as \$16.95 and say that copies should be available about the middle of January. Copies should also be available from other technical booksellers. (I,L,P,)

### Waveform generator

110 WAVEFORM GENERATOR PROJECTS For The Home Constructor, by R. M. Marston. Stiff paper covers, 136 pages 217mm x 138mm, illustrated mainly by circuits. Published 1978 by Newnes Technical Books, London. Price in Australia \$8,50.

Before the advent of solid-state devices, an author would have been hard put to it indeed to find anything like this number of variations on the one theme. But how different things are now.

In this book, R. M. Marston offers 13 pages of basic sine wave generators, with about as many circuits, 40 pages of triangle, ramp and sawtooth

generators, followed by 11 pages of multi-waveform generators.

Then follows a chapter on special waveform generators, another on waveform modulation and two appendices: one showing integrated circuit connections and the other charts to extend the usefulness of the basic circuits.

Designed around transistors and ICs, the various designs have all been checked out, according to the author, and should therefore perform for anyone capable of working from a schematic and a brief circuit explanation. In fact, it looks like a good one for the experimenter who enjoys lashing up and checking out circuit ideas.

Our copy came from Butterworths, 586 Pacific Highway, Chatswood, NSW 2067. Tel. (02) 412 3444. (W.N.W.)

### **Drawing text**

ELECTRICAL AND ELECTRONIC ENGINEERING DRAWING by T. Baitch. Published by McGraw-Hill Pty Ltd, Roseville East, NSW. Hard covers, 277 pages 215mm x 185mm, illustrated by diagrams and photographs.

Theodore Baitch is an electrical design engineer with lecturing experience at the Sydney technical College and the New South Wales Institute of Technology. He has written this book primarily as a text book for the subject, "Drawing", in electrical and electronic certificate, diploma and degree courses.

The International System of Units (SI) is used throughout the book and the drafting standards used are the Australian Standards AS1100, AS1102 and AS1103 as well as the International Electrotechnical Commission (IEC) Standards 113 and 117.

The book is structured into 60 chapters and deals with all forms of electrical and electronic drafting, schematic diagrams, wiring diagrams, printed circuit boards, electrical reticulation, etc. The electrical and electronic draftsman also needs a knowledge of other aspects of drafting — isometric and orthagonal projection, screw threads and fasteners, welding representation, etc. These subjects, and more, are covered in the text.

The text of the book is written in clear, easily read language and printed in a clean typeface. To match the text, the numerous illustrations are of a high standard and well reproduced.

In short, this book should be of great value not only to electrical and electronic course students, but also anyone in other drafting fields who may need to learn about electrical and electronic drawing.

The review copy came from the publisher, but copies should be available from the larger book stores. (R.F.)

### Steam-age RADAR

ELECTRONIC RADAR FUNDAMENTALS, by the US Department of the Navy and Army. Previously published as Radar Electronics — Fundamentals. Published by Coles Publishing Co, Toronto, Canada. Stiff paper covers, 474 pages, 215 x 135mm, many illustrations and diagrams. Recommended retail price \$8.75.

No date is given for the original publication of this book. Judging by the contents, however, it would appear to be just after the Second World War. The first four pages give a brief resume of the principles of RADAR, with the rest of the book occupied with fairly detailed explanations of electrical fundamentals.

There are sections concerned with vacuum tubes, power supply circuits, amplifiers and oscillators, cathode-ray tubes, transmission lines, waveguides, cavity resonators and ultra-high frequency generators (including klystrons and magnetrons), and finally antennas. The book concludes with a glossary of terms and an index.

No mention is made of any of the modern electronic advances, such as semiconductors, integrated circuits and computers. It would appear that this volume would be of most interest to the historian rather than the keen student of electronics. The sole section of the book concerned with RADAR is very limited. (D.W.E.)

### Television DX

LONG DISTANCE TELEVISION RECEPTION (TV-DX) FOR THE ENTHUSIAST, by Roger W. Bunney. Bernard Babani (Publishing) Ltd, London, 1978. Soft covers, 111 x 181mm, many illustrations. Price in UK £1.45.

The author of this new book on TV-DX is a regular columnist on the subject, writing in the British magazine "Television". His book is basically an updated and expanded version of an earlier booklet published by that magazine, which ran to three editions.

Intended as an introduction to the subject, the book begins with details of world TV systems and standards, including channel frequencies. Then it discusses relevant aspects of propagation, followed by sections on the requirements of TV-DX in terms of the receiver and the antenna system. The approach taken is very practical, with details given for a variety of receiver "add-ons" and modifications such as IF preamps, masthead amplifiers and adjacent channel traps.

Although written primarily for the British reader, much of the material should be of interest and value to local enthusiasts.

The review copy came direct from the publisher, but copies should arrive here soon. (J.R.)

# BOOKS

Just some of the books from the biggest range of radio and electronics books in Australia.

If the book you require is not listed below, it can be ordered from us.

	Can be oro-ted from us.	-
NEW — NEW — NEW	The Z-80 Microcomputer Handbook	
Latest editions of some of the most popular books on	(William Barden, Jr)	\$11.95
subject:	Computer Hobbyists (Neil Graham)	\$11.75
	2.95 Using the 6800 Microprocessor (Elmer Poe)	\$8.95
RSGB Handbook (New Edition) Volume 2 \$18	8.90 Beginner's Guide to Microprocessors	
Reference Data for Radio Engineers (New Edition) I.T.T	0.50 (Charles M. Gilmore)	\$7.95
Radio Handbook (William Orr) 20th	Computers (David L. Heiserman)	\$8.50
How to Build Proximity Detectors and	6.50 Getting Acquainted with Microcomputers	011.05
	6.75 (Lou Frenzel)	\$11.95
6800 Programming for Logic Design	Interfacing and Programming	\$14.25
(Adam Osborne)	DBUG: An 8080 Interpretive Debugger (Titus & Titus)	\$7.00
(Adam Osborne)	2.55 How to Program Microcomputers (William	
New Books:	Barden, Jr.)	\$12.70
Master OP-AMP Applications Handbook	American Radio Relay Leagu	ue l
(Harry W. Fox)	Hints and Kinks for the Radio Amateur	\$7.20
Woodruff)	3.75 The Radio Amateur's VHF Manual	\$7.20
Oscar, — Amateur Radio Satellites \$14 Understanding Sound, Video and Film	4.30 ARRL Antenna Handbook	\$8.80
Recording (Michael Overman) \$8	Understanding Amateur Radio The Radio Amateur's License Manual .	\$8.80 \$6.20
Master OP-ĀMP Applications Handbook (Harry W. Fox)	A Course in Radio Fundamentals	\$7.20
Shortwave Listener's Guide (Charles H.	the Radio Amateur	\$7.20
Woodruff)	FM & Repeater for the Radio Amateur	\$7.20
Accessories (John Sunier) \$14	4.00 Single Sideband for the Radio Amateur Ham Radio Operating Guide	\$7.20 \$7.20
The Complete Handbook of Public Address Sound Systems (F. Alton Everest) \$11	1.30 Electronic Data Book	\$7.20
Understanding and Using Modern Signal	Learning to Work with Integrated	\$12.80
Generators (Charles M. Gilmore) \$5 Microphones — How they Work and How	9.75 Circuits	\$4.00
	7.95 Getting to Know Oscar From the Ground	\$6.20
How to Build and Use Electronic Devices without Frustration, Panic, Mountains of	Howard W. Sams Publication	ns:
Money or an Engineering Degree (Stuart	Video Tape Recorders (Harry Kybett)	\$13.50
	5.00 Modern Recording Techniques (Robert E. Runstein)	\$14.80
How to Repair Musical Instrument Amplifiers (Byron Wels)	8.50 Electric Guitar Amplifier Handbook (Jack	
Amplifiers (Byron Wels) 4	8.50 Electric Guitar Amplifier Handbook (Jack Darr)	\$1,4.80
Amplifiers (Byron Wels) 4	8.50 Electric Guitar Amplifier Handbook (Jack Darr) Other Titles:	\$1,4.80
Amplifiers (Byron Wels) ,	8.50 Electric Guitar Amplifier Handbook (Jack Darr)  Other Titles:  Newnes Radio and Electronics Engineer's	
Amplifiers (Byron Wels) ,	8.50 Electric Guitar Amplifier Handbook (Jack Darr)  Other Titles:  Newnes Radio and Electronics Engineer's Pocket Book 15th Edition Understanding Sound and Video Recording	\$7.25
Amplifiers (Byron Wels) ,  Master Handbook of 1001 Practical Electronic Circuits (Ed. Kendall Webster Sessions) (TAB)	8.50 Electric Guitar Amplifier Handbook (Jack Darr)  Other Titles:  Newnes Radio and Electronics Engineer's Pocket Book 15th Edition  Understanding Sound and Video Recording (Overman)	
Amplifiers (Byron Wels) .  Master Handbook of 1001 Practical Electronic Circuits (Ed. Kendall Webster Sessions) (TAB) .  Build Your Own Working Robot (David L. Heiserman)	8.50 Electric Guitar Amplifier Handbook (Jack Darr)  Other Titles:  Newnes Radio and Electronics Engineer's Pocket Book 15th Edition Understanding Sound and Video Recording (Overman)  The Amateur Radio Vertical Antenna Handbook	\$7.25
Amplifiers (Byron Wels) ,  Master Handbook of 1001 Practical Electronic Circuits (Ed. Kendall Webster Sessions) (TAB)	8.50 Electric Guitar Amplifier Handbook (Jack Darr)  Other Titles:  Newnes Radio and Electronics Engineer's Pocket Book 15th Edition Understanding Sound and Video Recording (Overman) The Amateur Radio Vertical Antenna Handbook Integrated Circuit Pocket Book (R. G.	\$7.25 \$4.95
Amplifiers (Byron Wels) ,  Master Handbook of 1001 Practical Electronic Circuits (Ed. Kendall Webster Sessions) (TAB)	8.50 Electric Guitar Amplifier Handbook (Jack Darr)  Other Titles:  Newnes Radio and Electronics Engineer's Pocket Book 15th Edition Understanding Sound and Video Recording (Overman) The Amateur Radio Vertical Antenna Handbook Integrated Circuit Pocket Book (R. G. Hibberd) Transistor Pocket Book (R. G. Hibberd)	\$7.25 \$4.95 \$7.90 \$9.50 \$9.50
Amplifiers (Byron Wels)	8.50 Electric Guitar Amplifier Handbook (Jack Darr)  Other Titles:  Newnes Radio and Electronics Engineer's Pocket Book 15th Edition Understanding Sound and Video Recording (Overman) The Amateur Radio Vertical Antenna Handbook Integrated Circuit Pocket Book (R. G. Hibberd) Transistor Pocket Book (R. G. Hibberd) Colour Television Theory (Hutson)	\$7.25 \$4.95 \$7.90 \$9.50 \$9.50 \$15.40
Amplifiers (Byron Wels)  Master Handbook of 1001 Practical Electronic Circuits (Ed. Kendall Webster Sessions) (TAB)  Build Your Own Working Robot (David L. Heiserman)  The ABC Book of Hi-Fi/Audio Projects (George deLucenay Leon)  IC Function Locator — 4-way Index, Reference. Identification & Selection Guide to Thousands of ICs produced by over 40 Manufacturers (Ken Tracton) Home Brew HF/VHF Antenna Handbook (Williamd Hood)  Security Electronics (John E.	8.50 Electric Guitar Amplifier Handbook (Jack Darr)  Other Titles:  Newnes Radio and Electronics Engineer's Pocket Book 15th Edition Understanding Sound and Video Recording (Overman) The Amateur Radio Vertical Antenna Handbook Integrated Circuit Pocket Book (R. G. Hibberd) Transistor Pocket Book (R. G. Hibberd) Colour Television Theory (Hutson) MOS Digital IC's (G. Flynn)  MOS Digital Tenergy — For Radio	\$7.25 \$4.95 \$7.90 \$9.50 \$9.50
Amplifiers (Byron Wels)	8.50 Electric Guitar Amplifier Handbook (Jack Darr)  Other Titles:  Newnes Radio and Electronics Engineer's Pocket Book 15th Edition Understanding Sound and Video Recording (Overman) The Amateur Radio Vertical Antenna Handbook Integrated Circuit Pocket Book (R. G. Hibberd) Transistor Pocket Book (R. G. Hibberd) Tolour Television Theory (Hutson) MOS Digital IC's (G. Flynn)  Wind/Solar Energy — For Radio Communications and Low Power	\$7.25 \$4.95 \$7.90 \$9.50 \$9.50 \$15.40
Amplifiers (Byron Wels)  Master Handbook of 1001 Practical Electronic Circuits (Ed. Kendall Webster Sessions) (TAB)  Build Your Own Working Robot (David L. Heiserman)  The ABC Book of Hi-Fi/Audio Projects (George deLucenay Leon)  IC Function Locator — 4-way Index, Reference. Identification & Selection Guide to Thousands of ICs produced by over 40 Manufacturers (Ken Tracton) Home Brew HF/VHF Antenna Handbook (Williamd Hood)  Security Electronics (John E. Cunningham)  IC OP-AMP Cookbook (Walter C. Jung)  TTL Cookbook (Lancaster)	8.50 Electric Guitar Amplifier Handbook (Jack Darr)  Other Titles:  8.50 Newnes Radio and Electronics Engineer's Pocket Book 15th Edition Understanding Sound and Video Recording (Overman)  The Amateur Radio Vertical Antenna Handbook Integrated Circuit Pocket Book (R. G. Hibberd)  7.95 Hibberd)  7.95 Colour Television Theory (Hutson)  MOS Digital IC's (G. Flynn)  Wind/Solar Energy — For Radio Communications and Low Power Electronic/Electric Applications (E. Noll)	\$7.25 \$4.95 \$7.90 \$9.50 \$9.50 \$15.40
Amplifiers (Byron Wels)	8.50 Electric Guitar Amplifier Handbook (Jack Darr)  Other Titles:  8.50 Newnes Radio and Electronics Engineer's Pocket Book 15th Edition Understanding Sound and Video Recording (Overman)  The Amateur Radio Vertical Antenna Handbook Integrated Circuit Pocket Book (R. G. Hibberd)  Transistor Pocket Book (R. G. Hibberd)  Colour Television Theory (Hutson) MOS Digital IC's (G. Flynn)  Wind/Solar Energy — For Radio Communications and Low Power Electronic/Electric Applications (E. Noll)  Sound System Engineering (Don & Carolyn	\$7.25 \$4.95 \$7.90 \$9.50 \$9.50 \$15.40 \$8.60
Amplifiers (Byron Wels)	8.50 Electric Guitar Amplifier Handbook (Jack Darr)  Other Titles:  8.50 Newnes Radio and Electronics Engineer's Pocket Book 15th Edition Understanding Sound and Video Recording (Overman)  The Amateur Radio Vertical Antenna Handbook Integrated Circuit Pocket Book (R. G. Hibberd)  7.95 Hibberd) Transistor Pocket Book (R. G. Hibberd)  Colour Television Theory (Hutson) MOS Digital IC's (G. Flynn)  Wind/Solar Energy — For Radio Communications and Low Power Electronic/Electric Applications (E. Noll)  6.60 Sound System Engineering (Don & Carolyn Davis)  73 Dipole and Long-Wire Antennas	\$7.25 \$4.95 \$7.90 \$9.50 \$9.50 \$15.40 \$8.60 \$11.30 \$26.95
Amplifiers (Byron Wels)	8.50 Electric Guitar Amplifier Handbook (Jack Darr)  Other Titles:  Newnes Radio and Electronics Engineer's Pocket Book 15th Edition Understanding Sound and Video Recording (Overman) The Amateur Radio Vertical Antenna Handbook Integrated Circuit Pocket Book (R. G. Hibberd) Transistor Pocket Book (R. G. Hibberd) Colour Television Theory (Hutson) MOS Digital IC's (G. Flynn) Wind/Solar Energy — For Radio Communications and Low Power Electronic/Electric Applications (E. Noll) Sound System Engineering (Don & Carolyn Davis) 73 Dipole and Long-Wire Antennas (Edward M. Noll)	\$7.25 \$4.95 \$7.90 \$9.50 \$9.50 \$15.40 \$8.60
Amplifiers (Byron Wels) Master Handbook of 1001 Practical Electronic Circuits (Ed. Kendall Webster Sessions) (TAB)  Build Your Own Working Robot (David L. Heiserman) The ABC Book of Hi-Fi/Audio Projects (George deLucenay Leon) IC Function Locator — 4-way Index, Reference. Identification & Selection Guide to Thousands of ICs produced by over 40 Manufacturers (Ken Tracton) Home Brew HF/VHF Antenna Handbook (Williamd Hood) Security Electronics (John E. Cunningham) IC OP-AMP Cookbook (Walter C. Jung) ITL Cookbook (Lancaster) TV Typewriter Cookbook (Lancaster) TV Typewriter Cookbook (Lancaster) The Cheap Video Cookbook (Lancaster) CMOS Cookbook (Lancaster) Active Filter Cookbook (Lancaster) S2	8.50 Electric Guitar Amplifier Handbook (Jack Darr)  Other Titles:  8.50 Newnes Radio and Electronics Engineer's Pocket Book 15th Edition Understanding Sound and Video Recording (Overman)  The Amateur Radio Vertical Antenna Handbook Integrated Circuit Pocket Book (R. G. Hibberd)  7.95 Hibberd) Transistor Pocket Book (R. G. Hibberd)  7.95 MOS Digital IC's (G. Flynn) MOS Digital IC's (G. Flynn)  Wind/Solar Energy — For Radio Communications and Low Power Electronic/Electric Applications (E. Noll)  6.60 Sound System Engineering (Don & Carolyn Davis)  73 Dipole and Long-Wire Antennas (Edward M. Noll)  73 Vertical, Beam and Triangle Antennas (Noll)	\$7.25 \$4.95 \$7.90 \$9.50 \$9.50 \$15.40 \$8.60 \$11.30 \$26.95
Amplifiers (Byron Wels)	8.50 Electric Guitar Amplifier Handbook (Jack Darr)  Other Titles:  8.50 Newnes Radio and Electronics Engineer's Pocket Book 15th Edition Understanding Sound and Video Recording (Overman) The Amateur Radio Vertical Antenna Handbook Integrated Circuit Pocket Book (R. G. Hibberd) Transistor Pocket Book (R. G. Hibberd) Colour Television Theory (Hutson) MOS Digital IC's (G. Flynn) Wind/Solar Energy — For Radio Communications and Low Power Electronic/Electric Applications (E. Noll) Sound System Engineering (Don & Carolyn Davis) 73 Dipole and Long-Wire Antennas (Edward M. Noll) 73 Vertical, Beam and Triangle Antennas (Noll) Basic Television — Principles and	\$7.25 \$4.95 \$7.90 \$9.50 \$9.50 \$15.40 \$8.60 \$111.30 \$26.95 \$7.80
Amplifiers (Byron Wels) Master Handbook of 1001 Practical Electronic Circuits (Ed. Kendall Webster Sessions) (TAB) Build Your Own Working Robot (David L Heiserman) The ABC Book of Hi-Fi/Audio Projects (George deLucenay Leon) IC Function Locator — 4-way Index, Reference. Identification & Selection Guide to Thousands of ICs produced by over 40 Manufacturers (Ken Tracton) Home Brew HF/VHF Antenna Handbook (Williamd Hood) Security Electronics (John E. Cunningham) IC OP-AMP Cookbook (Walter C. Jung) TTL Cookbook (Lancaster) TV Typewriter Cookbook (Lancaster) TV Typewriter Cookbook (Lancaster) TCMOS Cookbook (Lancaster) S1 TCMOS Cookbook (Lancaster) TC Timer Cookbook (Lancaster) S2 Transistor Specifications Manual — 8th Edition S3 Transistor Specifications Manual — 8th	8.50 Electric Guitar Amplifier Handbook (Jack Darr)  Other Titles:  Newnes Radio and Electronics Engineer's Pocket Book 15th Edition Understanding Sound and Video Recording (Overman)  The Amateur Radio Vertical Antenna Handbook Integrated Circuit Pocket Book (R. G. Hibberd)  Colour Television Theory (Hutson)  MOS Digital IC's (G. Flynn)  Wind/Solar Energy — For Radio Communications and Low Power Electronic/Electric Applications (E. Noll)  Sound System Engineering (Don & Carolyn Davis)  73 Dipole and Long-Wire Antennas (Edward M. Noll)  73 Vertical, Beam and Triangle Antennas (Noll)  Basic Television — Principles and Servicing — 4th Edn. (Barnard Grob)  New Edition — Soft Cover	\$7.25 \$4.95 \$7.90 \$9.50 \$9.50 \$15.40 \$8.60 \$111.30 \$26.95 \$7.80
Amplifiers (Byron Wels)	8.50 Electric Guitar Amplifier Handbook (Jack Darr)  Other Titles:  8.50 Newnes Radio and Electronics Engineer's Pocket Book 15th Edition Understanding Sound and Video Recording (Overman)  The Amateur Radio Vertical Antenna Handbook Integrated Circuit Pocket Book (R. G. Hibberd)  7.95 Hibberd) Transistor Pocket Book (R. G. Hibberd)  7.95 MOS Digital IC's (G. Flynn) MOS Digital IC's (G. Flynn)  Wind/Solar Energy — For Radio Communications and Low Power Electronic/Electric Applications (E. Noll)  6.60 Sound System Engineering (Don & Carolyn Davis)  73 Dipole and Long-Wire Antennas (Edward M. Noll)  73 Vertical, Beam and Triangle Antennas (Noll)  89.90 Servicing — 4th Edn. (Barnard Grob) New Edition — Soft Cover Basic Electronics — 4th Edition (Bernard	\$7.25 \$4.95 \$7.90 \$9.50 \$9.50 \$15.40 \$8.60 \$11.30 \$26.95 \$7.80 \$7.50
Amplifiers (Byron Wels)	8.50 Electric Guitar Amplifier Handbook (Jack Darr)  Other Titles:  Newnes Radio and Electronics Engineer's Pocket Book 15th Edition Understanding Sound and Video Recording (Overman)  The Amateur Radio Vertical Antenna Handbook Integrated Circuit Pocket Book (R. G. Hibberd)  Colour Television Theory (Hutson)  MOS Digital IC's (G. Flynn)  Wind/Solar Energy — For Radio Communications and Low Power Electronic/Electric Applications (E. Noll)  Sound System Engineering (Don & Carolyn Davis)  73 Dipole and Long-Wire Antennas (Edward M. Noll)  73 Vertical, Beam and Triangle Antennas (Noll)  Basic Television — Principles and Servicing — 4th Edn. (Barnard Grob)  New Edition — Soft Cover  Basic Electronics — 4th Edition (Bernard Grob)  Better Shortwave Reception — New 4th	\$7.25 \$4.95 \$7.90 \$9.50 \$9.50 \$15.40 \$8.60 \$11.30 \$26.95 \$7.80 \$7.50
Amplifiers (Byron Wels)  Master Handbook of 1001 Practical Electronic Circuits (Ed. Kendall Webster Sessions) (TAB)  Build Your Own Working Robot (David L. Heiserman)  The ABC Book of Hi-Fi/Audio Projects (George deLucenay Leon)  IC Function Locator — 4-way Index, Reference, Identification & Selection Guide to Thousands of ICs produced by over 40 Manufacturers (Ken Tracton) Home Brew HF/VHF Antenna Handbook (Williamd Hood) Security Electronics (John E. Cunningham)  IC OP-AMP Cookbook (Walter C. Jung) TTL Cookbook (Lancaster)  TV Typewriter Cookbook (Walter C. Jung) TTL Cookbook (Lancaster)  RTL Cookbook (Lancaster)  The Cheap Video Cookbook (Lancaster)  ST Tomyers Ocokbook (Lancaster)  ST Transistor Specifications Manual — 8th Edition  Transistor Substitution Handbook International Transistor Selector (T.D. Towers) 2nd Edition  Master Tube Substitution Handbook (Tab Books)	8.50 Electric Guitar Amplifier Handbook (Jack Darr)  Other Titles:  Newnes Radio and Electronics Engineer's Pocket Book 15th Edition Understanding Sound and Video Recording (Overman) The Amateur Radio Vertical Antenna Handbook Integrated Circuit Pocket Book (R. G. Hibberd) Transistor Pocket Book (R. G. Hibberd) Transistor Pocket Book (R. G. Hibberd) Toolour Television Theory (Hutson) MOS Digital IC's (G. Flynn) Wind/Solar Energy — For Radio Communications and Low Power Electronic/Electric Applications (E. Noll)  2.75 Noll)  3.73 Dipole and Long-Wire Antennas (Edward M. Noll)  3.74 Vertical, Beam and Triangle Antennas (Noll)  Basic Television — Principles and Servicing — 4th Edn. (Barnard Grob) New Edition — Soft Cover Basic Electronics — 4th Edition (Bernard Grob) Better Shortwave Reception — New 4th Edition (William I. Orr & Stuart D.	\$7.25 \$4.95 \$7.90 \$9.50 \$9.50 \$15.40 \$8.60 \$11.30 \$26.95 \$7.80 \$7.50
Amplifiers (Byron Wels) Master Handbook of 1001 Practical Electronic Circuits (Ed. Kendall Webster Sessions) (TAB) Build Your Own Working Robot (David L. Heiserman) The ABC Book of Hi-Fi/Audio Projects (George deLucenay Leon) IC Function Locator — 4-way Index, Reference. Identification & Selection Guide to Thousands of ICs produced by over 40 Manufacturers (Ken Tracton) Home Brew HF/VHF Antenna Handbook (Williamd Hood) Scurrity Electronics (John E. Cunningham) IC OP-AMP Cookbook (Walter C. Jung) TTL Cookbook (Lancaster) TV Typewriter Cookbook (Lancaster) TV Typewriter Cookbook (Lancaster) TC MOS Cookbook (Lancaster) The Cheap Video Cookbook (Lancaster) IC Timer Cookbook (Jung) Transistor Specifications Manual — 8th Edition Transistor Substitution Handbook International Transistor Selector (T.D. Towers) 2nd Edition Master Tube Substitution Handbook (Tab Books) Australian Electrical Wiring Theory and	8.50 Electric Guitar Amplifier Handbook (Jack Darr)  Other Titles:  Newnes Radio and Electronics Engineer's Pocket Book 15th Edition Understanding Sound and Video Recording (Overman) The Amateur Radio Vertical Antenna Handbook Integrated Circuit Pocket Book (R. G. Hibberd) Transistor Pocket Book (R. G. Hibberd) Colour Television Theory (Hutson) MOS Digital IC's (G. Flynn)  Wind/Solar Energy — For Radio Communications and Low Power Electronic/Electric Applications (E. Noll) Sound System Engineering (Don & Carolyn Davis)  73 Dipole and Long-Wire Antennas (Edward M. Noll) 73 Vertical, Beam and Triangle Antennas (Noll) Basic Television — Principles and Servicing — 4th Edn. (Barnard Grob) New Edition — Soft Cover Basic Electronics — 4th Edition (Bernard Grob) Better Shortwave Reception — New 4th Edition (William I. Orr & Stuart D. Cowan) Simple Low-Cost Wire Antennas (William	\$7.25 \$4.95 \$7.90 \$9.50 \$9.50 \$15.40 \$8.60 \$11.30 \$26.95 \$7.80 \$7.50 \$18.75 \$19.35
Amplifiers (Byron Wels) Master Handbook of 1001 Practical Electronic Circuits (Ed. Kendall Webster Sessions) (TAB)  Build Your Own Working Robot (David L Heiserman) The ABC Book of Hi-Fi/Audio Projects (George deLucenay Leon) IC Function Locator — 4-way Index, Reference, Identification & Selection Guide to Thousands of ICs produced by over 40 Manufacturers (Ken Tracton) Home Brew HF/VHF Antenna Handbook (Williamd Hood) Security Electronics (John E. Cunningham) IC OP-AMP Cookbook (Walter C. Jung) TTL Cookbook (Lancaster) TV Typewriter Cookbook (Lancaster) TV Typewriter Cookbook (Lancaster) The Cheap Video Cookbook (Lancaster) The Cheap Video Cookbook (Lancaster) IC Timer Cookbook (Jung) Transistor Specifications Manual — 8th Edition Transistor Substitution Handbook International Transistor Selector (T.D. Towers) 2nd Edition Master Tube Substitution Handbook (Tab Books) Australian Electrical Wiring Theory and Practice (Pethebridge & Williams)  \$1	8.50 Electric Guitar Amplifier Handbook (Jack Darr)  Other Titles:  Newnes Radio and Electronics Engineer's Pocket Book 15th Edition Understanding Sound and Video Recording (Overman) The Amateur Radio Vertical Antenna Handbook Integrated Circuit Pocket Book (R. G. Hibberd) Transistor Pocket Book (R. G. Hibberd) Transistor Pocket Book (R. G. Hibberd) Transistor Pocket Book (R. G. Hibberd) Toour Television Theory (Hutson) MOS Digital IC's (G. Flynn) Wind/Solar Energy — For Radio Communications and Low Power Electronic/Electric Applications (E. Noll) Sound System Engineering (Don & Carolyn Davis) 73 Dipole and Long-Wire Antennas (Roll) Basic Television — Principles and Servicing — 4th Edn. (Barnard Grob) New Edition — Soft Cover Basic Electronics — 4th Edition (Bernard Grob) Better Shortwave Reception — New 4th Edition (William I. Orr & Stuart D. Cowan) Simple Low-Cost Wire Antennas (William I. Orr & Stuart D. Cowan)	\$7.25 \$4.95 \$7.90 \$9.50 \$15.40 \$8.60 \$11.30 \$26.95 \$7.80 \$7.50 \$18.75 \$19.35
Amplifiers (Byron Wels) Master Handbook of 1001 Practical Electronic Circuits (Ed. Kendall Webster Sessions) (TAB)  Build Your Own Working Robot (David L. Heiserman) The ABC Book of Hi-Fi/Audio Projects (George deLucenay Leon) IC Function Locator — 4-way Index, Reference, Identification & Selection Guide to Thousands of ICs produced by over 40 Manufacturers (Ken Tracton) Home Brew HF/VHF Antenna Handbook (Williamd Hood) Security Electronics (John E. Cunningham) IC OP-AMP Cookbook (Walter C. Jung) TTL Cookbook (Lancaster) TV Typewriter Cookbook (Lancaster) TV Typewriter Cookbook (Lancaster) The Cheap Video Cookbook (Lancaster) CMOS Cookbook (Lancaster) IC Timer Cookbook (Jung) Transistor Specifications Manual — 8th Edition Transistor Substitution Handbook International Transistor Selector (T.D. Towers) 2nd Edition Master Tube Substitution Handbook (Tab Books) Australian Electrical Wiring Theory and Practice (Pethebridge & Williams)  Microcomputers/Microprocessors	8.50 Electric Guitar Amplifier Handbook (Jack Darr)  Other Titles:  Newnes Radio and Electronics Engineer's Pocket Book 15th Edition Understanding Sound and Video Recording (Overman)  The Amateur Radio Vertical Antenna Handbook Integrated Circuit Pocket Book (R. G. Hibberd)  Transistor Pocket Book (R. G. Hibberd)  Colour Television Theory (Hutson)  MOS Digital IC's (G. Flynn)  Wind/Solar Energy — For Radio Communications and Low Power Electronic/Electric Applications (E. Noll)  Sound System Engineering (Don & Carolyn Davis)  73 Dipole and Long-Wire Antennas (Edward M. Noll)  73 Vertical, Beam and Triangle Antennas (Noll)  Basic Television — Principles and Servicing — 4th Edn. (Barnard Grob)  New Edition — Soft Cover  Basic Electronics — 4th Edition (Bernard Grob)  Better Shortwave Reception — New 4th Edition (William I. Orr & Stuart D. Cowan)  1.45 Sirier & William I.	\$7.25 \$4.95 \$7.90 \$9.50 \$9.50 \$15.40 \$8.60 \$11.30 \$26.95 \$7.80 \$7.50 \$18.75 \$19.35
Amplifiers (Byron Wels) Master Handbook of 1001 Practical Electronic Circuits (Ed. Kendall Webster Sessions) (TAB)  Build Your Own Working Robot (David L. Heiserman) The ABC Book of Hi-Fi/Audio Projects (George deLucenay Leon) IC Function Locator — 4-way Index, Reference, Identification & Selection Guide to Thousands of ICs produced by over 40 Manufacturers (Ken Tracton) Home Brew HF/VHF Antenna Handbook (Williamd Hood) Security Electronics (John E. Cunningham) IC OP-AMP Cookbook (Walter C. Jung) TTL Cookbook (Lancaster) TV Typewriter Cookbook (Lancaster) TV Typewriter Cookbook (Lancaster) The Cheap Video Cookbook (Lancaster) CMOS Cookbook (Lancaster) IC Timer Cookbook (Jung) Transistor Specifications Manual — 8th Edition Transistor Substitution Handbook International Transistor Selector (T.D. Towers) 2nd Edition Master Tube Substitution Handbook (Tab Books) Australian Electrical Wiring Theory and Practice (Pethebridge & Williams)  Microcomputers/Microprocessors Books:	8.50 Electric Guitar Amplifier Handbook (Jack Darr)  Other Titles:  Newnes Radio and Electronics Engineer's Pocket Book 15th Edition Understanding Sound and Video Recording (Overman) The Amateur Radio Vertical Antenna Handbook Integrated Circuit Pocket Book (R. G. Hibberd) Transistor Pocket Book (R. G. Hibberd) Transistor Pocket Book (R. G. Hibberd) Toolour Television Theory (Hutson) MOS Digital IC's (G. Flynn) Wind/Solar Energy — For Radio Communications and Low Power Electronic/Electric Applications (E. Noll) Sound System Engineering (Don & Carolyn Davis) 73 Dipole and Long-Wire Antennas (Roll) Basic Television — Principles and Servicing — 4th Edn. (Barnard Grob) New Edition — Soft Cover Basic Electronics — 4th Edition (Bernard Grob) Better Shortwave Reception — New 4th Edition (William I. Orr & Stuart D. Cowan) VHF Handbook for Radio Amateurs (Herbert S. Brier & William I. Orr) \$7.00	\$7.25 \$4.95 \$7.90 \$9.50 \$9.50 \$15.40 \$8.60 \$11.30 \$26.95 \$7.80 \$7.50 \$18.75 \$19.35
Amplifiers (Byron Wels) Master Handbook of 1001 Practical Electronic Circuits (Ed. Kendall Webster Sessions) (TAB) Build Your Own Working Robot (David L. Heiserman) The ABC Book of Hi-Fi/Audio Projects (George deLucenay Leon) IC Function Locator — 4-way Index, Reference. Identification & Selection Guide to Thousands of ICs produced by over 40 Manufacturers (Ken Tracton) Home Brew HF/VHF Antenna Handbook (Williamd Hood) Security Electronics (John E. Cunningham) IC OP-AMP Cookbook (Walter C. Jung) TTL Cookbook (Lancaster) TV Typewriter Cookbook (Lancaster) TN Typewriter Cookbook (Lancaster) The Cheap Video Cookbook (Lancaster) IC Timer Cookbook (Lancaster) IC Timer Cookbook (Lancaster) IC Timer Cookbook (Lancaster) S1: CTimer Cookbook (Lancaster) S2: IC Timer Cookbook (Lancaster) S2: IC Timer Cookbook (Lancaster) S3: Transistor Substitution Handbook S3: S4: S4: S5: Master Tube Substitution Handbook (Tab Books) Australian Electrical Wiring Theory and Practice (Pethebridge & Williams)  Microcomputers/Microprocessors Books: Programming Microprocessors (M. W. McMurran)	8.50 Electric Guitar Amplifier Handbook (Jack Darr)  Other Titles:  Newnes Radio and Electronics Engineer's Pocket Book 15th Edition  Understanding Sound and Video Recording (Overman)  The Amateur Radio Vertical Antenna Handbook Integrated Circuit Pocket Book (R. G. Hibberd)  Colour Television Theory (Hutson)  MOS Digital IC's (G. Flynn)  MOS Digital IC's (G. Flynn)  Wind/Solar Energy — For Radio Communications and Low Power Electronic/Electric Applications (E. Noll)  Sound System Engineering (Don & Carolyn Davis)  73 Dipole and Long-Wire Antennas (Edward M. Noll)  Basic Television — Principles and Servicing — 4th Edn. (Barnard Grob)  New Edition — Soft Cover  Basic Electronics — 4th Edition (Bernard Grob)  New Edition — Soft Cover  Basic Electronics — 4th Edition (Bernard Grob)  Setter Shortwave Reception — New 4th Edition (William I. Orr & Stuart D. Cowan)  VHF Handbook for Radio Amateurs (Herbert S. Brier & William I. Orr)  Seam Antenna Handbook — New 5th Edition (William I. Orr)	\$7.25 \$4.95 \$7.90 \$9.50 \$9.50 \$15.40 \$8.60 \$11.30 \$26.95 \$7.80 \$7.50 \$18.75 \$19.35
Amplifiers (Byron Wels) Master Handbook of 1001 Practical Electronic Circuits (Ed. Kendall Webster Sessions) (TAB)  Build Your Own Working Robot (David L. Heiserman) The ABC Book of Hi-Fi/Audio Projects (George deLucenay Leon) IC Function Locator — 4-way Index, Reference. Identification & Selection Guide to Thousands of ICs produced by over 40 Manufacturers (Ken Tracton) Home Brew HF/VHF Antenna Handbook (Williamd Hood) Scurrity Electronics (John E. Cunningham) IC OP-AMP Cookbook (Walter C. Jung) TTL Cookbook (Lancaster) TV Typewriter Cookbook (Lancaster) RTL Cookbook (Lancaster) TV Typewriter Cookbook (Lancaster) S17 CMOS Cookbook (Lancaster) IS Transistor Substitution Handbook International Transistor Selector (T.D. Towers) 2nd Edition Transistor Substitution Handbook (Tab Books) Australian Electrical Wiring Theory and Practice (Pethebridge & Williams)  Microcomputers/Microprocessors Books: Programming Microprocessors (M. W. McMurran) Microcomputer (Waite & Pardee)  \$1	8.50 Electric Guitar Amplifier Handbook (Jack Darr)  Other Titles:  Newnes Radio and Electronics Engineer's Pocket Book 15th Edition Understanding Sound and Video Recording (Overman) The Amateur Radio Vertical Antenna Handbook Integrated Circuit Pocket Book (R. G. Hibberd) Colour Television Theory (Hutson) MOS Digital IC's (G. Flynn) Unid/Solar Energy — For Radio Communications and Low Power Electronic/Electric Applications (E. Noll) Sound System Engineering (Don & Carolyn Davis) 73 Dipole and Long-Wire Antennas (Roll) Basic Television — Principles and Servicing — 4th Edn. (Barnard Grob) New Edition — Soft Cover Basic Electronics — 4th Edition (Bernard Grob) Better Shortwave Reception — New 4th Edition (William I. Orr & Stuart D. Cowan) VHF Handbook for Radio Amateurs (Herbert S. Brier & William I. Orr) \$7.00 Beam Antenna Handbook — New 5th	\$7.25 \$4.95 \$7.90 \$9.50 \$9.50 \$15.40 \$8.60 \$11.30 \$26.95 \$7.80 \$7.50 \$18.75 \$19.35 \$5.85
Amplifiers (Byron Wels) Master Handbook of 1001 Practical Electronic Circuits (Ed. Kendall Webster Sessions) (TAB) Build Your Own Working Robot (David L. Heiserman) The ABC Book of Hi-Fi/Audio Projects (George deLucenay Leon) IC Function Locator — 4-way Index, Reference, Identification & Selection Guide to Thousands of ICs produced by over 40 Manufacturers (Ken Tracton) Home Brew HF/VHF Antenna Handbook (Williamd Hood) Security Electronics (John E. Cunningham) IC OP-AMP Cookbook (Walter C. Jung) TTL Cookbook (Lancaster) TV Typewriter Cookbook (Lancaster) TV Typewriter Cookbook (Lancaster) TRTL Cookbook (Lancaster) TPHC Cheap Video Cookbook (Lancaster) IC Timer Cookbook (Lancaster) IC Timer Cookbook (Lancaster) IC Timer Cookbook (Jung) Transistor Specifications Manual — 8th Edition Transistor Substitution Handbook International Transistor Selector (T.D. Towers) 2nd Edition Master Tube Substitution Handbook (Tab Books)  Muster Tube Substitution Handbook (Tab Books)  Muster Tube Substitution Handbook (Tab Books)  Microcomputers/Microprocessors  Books:  Programming Microprocessors (M. W. McMurran) Microcomputer Primer (Waite & Pardee) How to Buy and Use Minicomputers and	8.50 Electric Guitar Amplifier Handbook (Jack Darr)  Other Titles:  Newnes Radio and Electronics Engineer's Pocket Book 15th Edition Understanding Sound and Video Recording (Overman) The Amateur Radio Vertical Antenna Handbook Integrated Circuit Pocket Book (R. G. Hibberd) Transistor Pocket Book (R. G. Hibberd) Transistor Pocket Book (R. G. Hibberd) Transistor Pocket Book (R. G. Hibberd) Toolour Television Theory (Hutson) MOS Digital IC's (G. Flynn) Wind/Solar Energy — For Radio Communications and Low Power Electronic/Electric Applications (E. Noll) Sound System Engineering (Don & Carolyn Davis) T3 Dipole and Long-Wire Antennas (Roll) Basic Television — Principles and Servicing — 4th Edn. (Barnard Grob) New Edition — Soft Cover Basic Electronics — 4th Edition (Bernard Grob) Better Shortwave Reception — New 4th Edition (William I. Orr & Stuart D. Cowan)  Simple Low-Cost Wire Antennas (William I. Orr & Stuart D. Cowan)  VHF Handbook for Radio Amateurs (Herbert S. Brier & William I. Orr) S7.00 Beam Antenna Handbook — New 5th Edition (William I. Orr) All About Cubical Quad Antennas — 2nd	\$7.25 \$4.95 \$7.90 \$9.50 \$15.40 \$8.60 \$11.30 \$26.95 \$7.80 \$7.50 \$18.75 \$19.35 \$5.85
Amplifiers (Byron Wels)  Master Handbook of 1001 Practical Electronic Circuits (Ed. Kendall Webster Sessions) (TAB)  Build Your Own Working Robot (David L. Heiserman)  The ABC Book of Hi-Fi/Audio Projects (George deLucenay Leon)  IC Function Locator — 4-way Index, Reference. Identification & Selection Guide to Thousands of ICs produced by over 40 Manufacturers (Ken Tracton) Home Brew HF/VHF Antenna Handbook (Williamd Hood)  Scurrity Electronics (John E. Cunningham)  IC OP-AMP Cookbook (Walter C. Jung) TTL Cookbook (Lancaster)  TV Typewriter Cookbook (Lancaster)  TV Typewriter Cookbook (Lancaster)  TRL Cookbook (Lancaster)  The Cheap Video Cookbook (Lancaster)  IC Timer Cookbook (Jung)  Transistor Substitution Handbook International Transistor Selector (T.D. Towers) 2nd Edition  Master Tube Substitution Handbook (Tab Books)  Australian Electrical Wiring Theory and Practice (Pethebridge & Williams)  Microcomputers/Microprocessors  Books:  Programming Microprocessors (M. W. McMurran)  Microcomputers Primer (Waite & Pardee) How to Buy and Use Minicomputers and Microcomputers (W. Barden, Jr.)  \$1	8.50 Electric Guitar Amplifier Handbook (Jack Darr)  Other Titles:  Newnes Radio and Electronics Engineer's Pocket Book 15th Edition Understanding Sound and Video Recording (Overman) The Amateur Radio Vertical Antenna Handbook Integrated Circuit Pocket Book (R. G. Hibberd) Colour Television Theory (Hutson) MOS Digital IC's (G. Flynn) MO	\$7.25 \$4.95 \$7.90 \$9.50 \$9.50 \$15.40 \$8.60 \$11.30 \$26.95 \$7.80 \$7.50 \$18.75 \$19.35 \$5.85 \$5.85

### McGILL'S AUTHORISED NEWSAGENCY PTY LTD

187 Elizabeth Street, Melbourne

Phone: 60 1475-6-7

### **Notes & Errata**

NEW GAME PROGRAMS FOR YOUR 2650 (December 1978. File No. 8/M/32): The hexadecimal listings of the programs given in this article did not reproduce with full clarity. To assist readers who found difficulty in feeding the programs into their system, we reproduce a new and (hopefully) clearer set of listings below.

LIFE: HEX LISTING

0000 76 40 75 FF 04 F9 C8 27 12 1A 7D 3B 25 12 1A 78 @C1@ 3B 1E 3B 1C 12 9A @4 @5 59 1B @7 3B 13 12 1A Ø4 0 C20 05 F9 C9 0B 1B 32 24 ØD 3B ØF 04 ØA 3B 2B Ø C3Ø 3B ØØ ØB 7B 14 14 FB 7D 17 77 10 05 08 3B 71 Ø C40 6F 74 40 3B 6B 50 1A 04 74 40 1B 0.3 76 40 14 75 Ø C5Ø 72 76 4Ø 3B 58 10 17 1B 1C 77 18 05 ØØ Ø6 Ø8 Ø C60 1A 7D 12 14 3B 4C 3B 48 12 14 DØ 51 FA 78 3B 40 01 75 Ø C7 Ø 45 7 F 18 17 Ø5 Ø1 3F ØE B6 Ø4 3A 3F ØC 39 0 080 3F 0C 5A E4 1.0 OC FR 50 E4 47 1C @D 8A E4 4E 98 Ø C9 Ø 6F 3F ØC 39 05 46 20 CD 4E EE 59 7B 0.5 FF 3F 0C Ø CAØ 26 96 98 97 00 D3 3F ac 5A E4 20 13 22 E4 4F 18 18 ØD 98 3F C CBC 22 E4 ØA 10 E4 6D ØC 39 85 Ø1 45 FC D3 FA 3F 2E F4 65 @ CC@ A5 Ø1 1B 5D 7 D Ø3 CD 03 1 B ØF 04 Ø CDØ 2E 1B Ø2 67 0.1 ØC. 39 FA 4B Ø3 CD 2E F4 F5 03 ØCE® 3F 9E Ø5 FF BC ØC A1 E5 BC ØC 26 CA 3F ac. 06 00 08 @ CFØ 07 ØD 2E F4 aa 9 A 02 15 DA CA ØA DØ FB 77 F5 98 ØDØØ Ø3 6E A5 04 06 1.0 98 06 85 Ø4 1B 10 FR ag 07 77 65 ØDIØ Ø8 ØD 2E F4 77 10 C2 52 10 D2 1A Ø4 04 20 1B ec Ø D2Ø 02 04 4F 3F 39 FA 65 Ø3 E5 90 ac. 3F EA 014 @ D3@ ØD 3B FI ØD OF. EF E5 9 99 04 45 ØA 1B 78 91 24 Ø D4Ø 30 3F ØC 39 ØD ØE 00 EE Ø6 09 99 ØE E5 86 Ø1 E6 @ D5@ 99 02 06 00 A5 ØA E5 09 19 72 02 24 30 3F ac Ø D6Ø 39 01 24 30 3F ØC 39 1F ØC 7B 3B ØB 07 9 C2 82 Ø D7Ø FB 7 D C2 3B 02 82 17 3F ØC 5A E4 30 79 1A E4 39 0 D80 19 75 C3 3F ØC 39 Ø3 44 ØF 17 3F ac 39 3B CC 5B Ø D9 Ø ØE ED Ø5 ØC E4 ØØ ØE BØ 1 C 05 15 ØF E4 1A F8 05 Ø DAØ 1B E4 37 1 A F2 Ø5 21 E4 4C IA EC Ø5 27 1 B E8 05 ØDBØ 04 06 Ø4 ØD 4E F4 CE 4F 34 ØE 6F 30 CD 6E FØ 5 A Ø5 ØDCØ 02 06 04 59 6E FF 07 ØЗ 85 Ø3 3B 33 2F 08 50 Ø DDØ 50 C8 2A 3B 14 A5 03 3B 27 Ø8 22 C8 22 3B ØA ØD ØDEØ 2E F4 77 10 C1 07 3B ØA Ø8 1B 13 Ø8 CA 10 ØE DØ 03 ØDFØ CB ØB 44 CF 6E 20 FB 02 07 Ø3 17 81 21 48 20 C8 79 ØEØØ 7A C8 06 Ø3 ØD 2E FØ 44 55 88 70 CS 6E FØ 50 44 ØEIØ ØD 6E 55 88 65 CS 63 85 ØЗ FA 69 A5 ØC Ø E 2 Ø 17 Ø1 00 01 FB ØE 75 10 F5 03 18 04 3B 52 1 B 04 Ø E3Ø Ø8 4D C8 49 75 10 3F ØD E9 77 10 08 88 64 63 88 Ø E 4 Ø 62 E4 Ø4 18 10 E4 Ø3 18 Ø5 Ø1 1A Ø5 18 01 1 A Ø E5Ø 04 66 01 25 80 DI 5B 4C 75 Ø1 44 10 03 C2 ØE 6E Ø E6Ø FØ CD 6E FØ 77 01 75 CE 6E FØ 10 10 F5 03 9 C ØD @ E7 Ø DF E5 3F 90 ØD C9 04 FØ Ø5 ØD 4E CD 6F 30 59 78 ØE8Ø 77 10 02 1C ØE A8 Ø6 ØØ 75 10 05 01 8D ØE EE E5 @ E9 Ø 64 98 ØA Ø5 Ø1 8 D ØE EF CD ØE EF 05 ØØ CD ØE EE ØEAØ ac ØE ED A4 01 CC ØE ED E4 ØØ 1C ØC E8 1F AF C FRO 3F ØE B6 1F ØD AF ØD 2E BF E4 ØØ 3F 14 39 1 B Ø ECØ 75 ØD ØA 22 4C 49 46 45 22 ØD ØA ØØ 2Ø 3D 20 32 ØEDØ 35 36 47 2E 00 20 3C 3Ø 35 53 00 20 3C 31 35 53 ØEEØ ØØ 20 3C 32 30 53 00 20 30 32

ROTATE: HEX LISTING

0440 06 FF 3F 05 64 05 08 07 F5 1B 00 12 9A 06 D9 Ø45@ DB 79 1B 71 Ø6 31 66 80 F6 03 18 ØA 26 FF F6 Ø46Ø 18 Ø2 66 8Ø FF CA 6C 26 52 ØF 3F 46 04 18 0470 62 DB 60 07 ØF 1F Ø4 B5 3F 05 44 06 ØF 3F 02 86 @48@ 3F E4 58 1 C Ø5 03 E4 0D 18 ØD 3F 04 0490 3B 30 98 1 A 06 19 18 64 Ø3 C2 3B 26 18 76 Ø 4AØ 3B 22 3B 20 07 ØF Ø6 21 3F Ø5 64 A5 01 95 18 49 C3 85 95 Ø4BØ 02 67 06 40 ØE 25 76 E2 18 7A 60 10 05 79 F6 03 Ø4CØ 56 1F 04 14 F6 ØC 14 ØE 65 BB CS 13 ØE Ø 4DØ 65 BC CE 65 BB ØE 65 B8 CE 65 BC ØE 65 B7 CE 65 Ø4EØ B8 Ø4 4E CE 65 B7 17 E4 5A 1C Ø5 58 E4 41 1 A Ø4FØ E4 50 19 ØE 06 10 B7 EE 45 Ø4 5A 79 18 9 B 22 3F 06 0500 Ø2 B4 17 28 3F Ø5 64 3F Ø2 86 3B 5A 58 79 02 0510 C3 04 20 3F 02 B4 3F Ø2 86 3B 4C 58 79 02 A3 9A Ø52Ø Ø2 Ø3 A2 E4 Øl 18 Ø8 E4 Ø4 18 Ø4 Ø6 19 1B 56 ØE 0530 65 B7 C8 07 ØF B7 65 CE 65 B7 Ø4 44 CF 65 B7 Ø7 Ø54Ø ØF 1F 04 B2 06 Ø1 ØE 25 B3 14 3F 92 B4 F6 Ø3 98 0550 75 3F 00 8A 18 70 3B 6C 06 34 3B Ø8 3F 02 69 3B 0560 03 1F Ø4 40 ØE 25 6D 14 3F 77 Ø2 B4 18 ØA 50 52 0570 45 53 53 20 41 4E 59 20 4B 45 59 00 aa ØA 52 4F 0580 54 41 54 45 3A 2Ø ØØ ØA 57 48 41 54 3F 00 43 20 0590 41 4E 43 45 4C 00 ØA 45 58 43 48 4E 47 41 45 3A Ø5AØ 20 00 0A 59 4F 55 20 54 4F 4F 4B 20 00 20 4D 4F 05B0 56 45 53 ØA ØØ ØD ØA 4D 4E 48 41 4B 50 49 44 43 Ø5CØ 45 4A 4F 46 4C

MUSIC: HEX LISTING

04A0 04 00 0C A5 56 1E 05 58 C2 44 70 24 70 C1 51 51 04B0 51 81 51 77 10 83 C3 86 00 75 11 46 OF D2 OF. 65 ØE 25 BC Ø6 FF 0 4C0 BC C3 E5 ØØ 18 Ø5 DØ D3 D2 F9 7B CADO 75 01 84 80 87 00 86 00 CB 22 CA 1F 77 10 87 44 Ø 4EØ 86 01 9A Ø6 87 ØE 86 ØØ 1A 7A ØD 85 56 77 01 GAFG 76 7B 09 AA 06 40 04 Ø8 1B 31 28 00 F9 5A AB 0.500 78 93 07 80 8B 76 8.4 73 9A Ø6 87 ØE 86 ØØ 1A 7 A 0510 53 13 53 B5 01 98 18 Ø1 CØ 03 47 03 9F 05 1F CØ 0520 Ca Ca 93 12 24 40 92 13 77 11 AB 50 AA 4D 9A 05 0.530 93 07 80 18 AF FO 46 44 Ø1 4C 04 FC 64 18 93 8F 0.540 Ø4 FC 8E 0.4 FB 75 11 ØB ØE ØA ØB 87 Ø2 86 00 0550 06 CA 03 1F 0.4 AØ 06 B6 77 10 E4 FF 1 C 00 22 09 0 560 F5 87 86 00 9A 01 AF 87 ØE 86 ØØ 8 A 06 1A 7A 74 40 75 0570 Ø1 86 92 04 FA AE Ø4 FQ 87 1E 86 aa 87 0.580 ØE 86 aa 1 A FQ 6E A6 74 02 1F 05 45 75 FF 3F 02 Ø 590 DB ØC 2A 98 Ø6 ØA 23 04 09 20 1B 04 CA 1D C9 1A CE 05 CD Ø5 56 3F 0.5A0 57 Ø2 DB 77 Ø8 ØC Ø4 2A 1 C 04 1F Ø4 AØ Ø5 Ø 5BØ AØ CE Ø4 FA CD 04 F9 D4 02 FC 11 2F 1E 97 0.5C0 28 3E 69 37 2F 42 74 4D 17 57 22 60 9C 05D0 72 00 79 FS

YANKEE DOODLE: HEX LISTING

Ø5D4 8Ø 8Ø Ø8 43 08 80 08 43 08 80 08 Ø5EØ Ø8 8Ø Ø8 47 Ø8 8Ø 08 43 08 80 08 Ø SFØ 08 80 08 3A Ø8 80 Ø8 43 Ø8 80 Ø8 Ø8 80 0600 08 80 08 47 08 80 14 43 08 80 08 Ø8 80 3A 42 08 0610 08 80 08 43 08 80 08 43 as 80 08 45 as 80 as 47 08 Ø8 0620 Ø8 8Ø 48 08 80 47 08 80 08 45 08 80 08 43 0630 08 80 08 42 Ø8 8Ø Ø8 3A Ø8 80 08 40 08 80 08 42 0640 Ø8 80 10 43 ØC 80 10 43 10 80 08 40 10 80 08 42 0650 02 80 08 40 08 80 08 3A Ø8 80 08 40 08 80 98 42 08 80 10 43 10 80 Ø8 80 0660 ЗА 10 Ø8 40 02 80 08 3A Ø8 8Ø 1Ø 37 1Ø 8Ø 1Ø Ø2 8Ø Ø8 4Ø Ø8 8Ø Ø8 0670 08 80 08 38 10 80 3A Ø8 0680 10 80 08 42 3A Ø8 8Ø as 40 0690 08 80 08 42 08 80 08 43 08 80 08 40 08 80 08 34 Ø6AØ Ø8 8Ø Ø8 43 Ø8 8Ø Ø8 42 Ø8 8Ø Ø8 45 Ø8 8Ø 10 43 Ø6BØ ØC 8Ø 1Ø 43 8Ø 8Ø Ø2 FF

BACH: HEX LISTING

06B8 80 80 06 43 06 45 04 47 06C0 04 4A 04 48 04 48 04 50 04 4A 04 4A 04 53 04 52 43 47 04 04 45 04 47 04 40 Ø6EØ Ø4 48 Ø4 47 45 @4 43 Ø4 3A 04 04 43 43 18 4A 47 ØC 48 Ø6FØ ØC 8Ø 13 47 ØC 4A @C 4A 13 48 ec 0,700 06 80 06 80 13 13 4A PC 47 06 45 03 ØC 45 18 ØC 47 43 ØC 8@ 02 80 Ø6 43 06 04 4A 04 48 04 48 04 53 04 4A 04 47 Ø4 4A 0720 04 47 04 50 04 4A 0730 04 52 04 53 04 43 04 45 84 47 04 40 04 4A 04 48 47 04 45 04 43 Ø4 3A 0740 04 43 04 42 @750 04 43 84 47 04 4A 04 53 Ø4 4A 04 47 04 43 0760 04 49 18 4A 06 80 02 30 03 80 06 43 06 0770 04 4A 04 43 04 43 04 50 04 4A 04 4A 04 06 43 06 45 53 94 04 53 04 4A 04 47 04 43 04 45 04 04 47 40 0790 04 48 04 47 04 45 04 43 04 3A 04 07AØ 8Ø 8Ø Ø2 FF

TRS-80 BIORHYTHMS (November 1978, File No. 8/M/31): A number of errors have been found in the program listing, caused by faulty printing of the original listing from which it was prepared. The corrections are:

Line 400 should begin with V=0, not Y=0.

Line 499 should begin: P.T. (10), "HERE COME . . . Line 520 should begin: F.X=325 TO 327 S.2:

Line 545 should read P.A.709, B: P.A.739, "BIRTHDATE ="; G; H; J: GOS.800

Line 600 should begin O=14:

Line 475: note that the third section reads Q = I + (7-Q):

CAR BURGLAR ALARM (November 1976. File No. 3/AU/16): Some readers have reported a problem involving spontaneous arming of the circuit when other electrical devices, such as the starter, are operated. Others have reported a tendency for the alarm circuit to re-trigger after automatic horn shutdown.

Both are due to spikes or noise on the battery line being fed into the appropriate sections of the circuit. Two modifications are suggested. For the first problem the 100k resistor between pins 2 and 4 of A1 is changed to two 47k resistors and the junction connected to a tantalum capacitor, which connects to chassis. The same junction connects to a diode, the cathode end of which connects to pin 4.

For the second problem the line between pin 3 of B1 (Continued opposite)

# INFORMATION CENTRE

MORSE CODE DECODER: I have recently read in a U.S. magazine an article on the construction of a decoder that automatically decodes Morse code signals and displays them alphanumerically. I would like to know whether your magazine would be interested in this idea as a project. I would also like to know whether you have published articles on radio control of models.

• The possibility of a Morse code decoder has occurred to us and one staff member has gone so far as to work out a likely way to approach the problem, both technically and in terms of available components. However, the design would involve a fair amount of work and, at present, pressure of more popular projects prevents the necessary time being available. As the staff member put it, "Keep your fingers crossed — but don't hold your breath!"

We have described a few model control circuits in the past, but these are now quite dated. A problem here is that the subject is as much, or more, one of mechanical hardware as it is of electronic circuitry.

DIP OSCILLATOR: I would like to request that you run a project for a dip oscillator. While many circuits of dip oscillators have been published in the past I have yet to see a project which included high level calibration, FET oscillator and a very precise dip at a very precise frequency.

Accessories would also be needed to use with the dipper. This would include use as resonating antennas, as an RF oscillator for the alignment of tuned circuits and other varied uses.

You may ask why I require a project such as this. The simple explanation is "calibration". The dial must be calibrated to within 0.1% as a maximum, any less degree of accuracy the instrument would be useless. I place this thought in your capable hands, with the suggestion that a range of 0.5 to 30MHz would be desirable. (L.T., Duffy, ACT).

• A tall order indeed! To obtain the order of accuracy laid down would require very precise hand-spread ranges, calling for a large number of coils to cover from say 0.5 to 30MHz. Having done this, in the case of a home made dipper, the problem of providing an accurately calibrated scale is a difficult one to solve. If a builder has all the facilities to accurately calibrate a scale then well and good. However, in most cases, readers would want a ready

made scale so that they could just drop it into position. Unfortunately, such a scale would not give the required accuracy because of spreads in tolerances of components, leading to variations in calibration points.


As if that is not enough! Basically, and by its very nature, a dip oscillator is not a very precise instrument. Where circuits have to be coupled for dipping, a certain amount of error is introduced by the amount of coupling, the accuracy of setting and reading of the dia scale. The popular dipper is normally used to give an approximate measurement, which may be followed up later by more accurate methods. However, we agree that it may be worth while taking a look at the possibility of describing a new dipper.


PERSONAL COMPUTER: I am very interested in buying a minicomputer for personal use. Do you know of any minicomputers on the market, either in kit form or built up, that do not operate in hexadecimal but in BASIC? I am interested in one like your Mini Scamp, which does not need an expensive terminal to go with it. But I also want one which can be expanded. (D.S.L., Beaumaris, Vic.)

To a certain extent you are asking for the impossible. By their very nature, high level languages like BASIC require the flexibility of interaction which can only be provided by a full-keyboard type terminal; it is not really feasible to program a system running BASIC using only a set of front-panel switches.

The cheapest way of getting a personal computer which is programmed in BASIC is probably to buy one of the low cost integrated systems like the Tandy TRS-80 (Tandy Electronics) or the Apple (Computerland), which have a video terminal built into the computer. At present this type of system will cost you around \$800-\$1000, but lower cost systems will be available before long.

### NOTES & ERRATA contd.

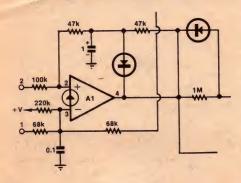

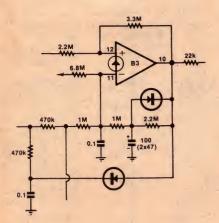

and pin 10 of B3 is modified. A diode is connected between the (lower) 470k resistor and pin 10, with the cathode towards the resistor. From the junction a 0.1uF capacitor connects to chassis.

If you are unable to complete an "Electronics Australia" project because you missed out on your regular issue, we can usually provide emergency assistance on the following basis:

PHOTOSTAT COPIES: \$2 per project, or \$2 per part where a project spreads over multiple Issues. Requests can be handled more speedily if projects are positively identified, and if not accompanied by technical queries.

METALWORK DYELINES: Available for most projects at \$2 each, showing dimensions, holes, cutouts, etc., but no wiring details.

PRINTED BOARD PATTERNS: Dyeline transparencies, actual size but of limited contrast: \$2. Specify positive or negative. We do not sell PC boards.

PROJECT QUERIES: Members of our technical staff are NOT available to discuss individual projects, either in person at our office or by telephone.

REPLIES BY POST: Limited to advice concerning projects published within the past two years. Charge \$2. We cannot provide lengthy

answers, undertake special research or discuss design changes.

BACK NUMBERS: Available only until our stocks are exhausted. Within three months of publication, face value. Four months and older, if available, \$2. Post and packing 60c per issue

OTHER QUERIES: Technical queries outside the scope of "Replies by Post" may be submitted without fee, for reply in the magazine, at the discretion of the Editor.

COMMERCIAL, SURPLUS EQUIPMENT: No information can be supplied.

COMPONENTS: We do not deal in electronic components. Prices, specifications, etc., should be sought from advertisers or agents.

REMITTANCES: Must be negotiable in Australia and made payable to "Electronics Australia". Where the exact charge may be indoubt, we recommend submitting an open cheque endorsed with a suitable limitation.

ADDRESS: All requests to the Assistant Editor, "Electronics Australia", Box 163, Beaconsfield, 2014.

### 2650 SYSTEM USERS!



This 175mm 33-1/3rpm record provides 11 useful programs for small computer systems based on the Signetics 2650 microprocessor. You feed them into your system via a normal cassette interface ("Kansas City" standard).

The programs include hex input and listing routines, block move and search, tape measure and verifier, a disassembler, 300-baud binary dump and loader, and two amusing games for relaxation. All load in via Signetics' PIPBUG.

The EA-Philips 2650 System Software Record is available from the Electronics Australia office for \$2.50, or \$3.00 posted anywhere in Australia from EA, P.O. Box 163, Beaconsfield, NSW 2014.

# Marketplace

### FOR SALE

IN WA: For EA Project boards, Robert P. Nederpelt Electronics, (09) 279 4716.

REVOX A700 2 Track — 3 speed with Remote Control. Near new. \$1800 ono. S. White, 35 Bank Street, South Melbourne. 690 2344 (bus.), 489 9139 (AH).

PAPER TAPE READER. Siemens Model 108A 30 Char/Sec. Excellent condition \$65. Ken Ryan, PO Box 50 Croydon, NSW 2132. Phone (02) 799 3000

**TRANSFORMERS!** 240-110V and 240-24V up to 1.5kva very cheap. PO Box 85 Rozelle 2039 or 827 3778.

TEAC A7300 2 Track 7½/15 Professional Recorder. New condition. \$1500 onc. S. White, 35 Bank Street, South Melbourne. 690 2344 (bus.), 489 9139 (AH).



FREE SAMPLE LED against 20c SAE
To see is to buy. Best value in LED
in Aust. No brag just fact. Quality.
17c ea. \$12 a 100, \$110 a 1000, 40c P&P
5mm red well diffused wide viewing angle.
Clips 3c each all quantities. Diggerman
Electronics. Box 33, Coramba, NSW 2466.

12" SST Tube \$10. PSV Teletype \$10 62 B. Murphy Rad \$60. Chart Rec. from \$20. Audio OSC \$35. Tape Rec. \$60. Trans. 240-110 \$30. Jack Field \$15 Pro. Tape Deck suit conversion \$250. Studio 20 Sales, 31 3383 367 Bourke St. Darlinghurst 2010.

AUSTRALIAN RADIO DX CLUB, the national group for people interested in long distance (DX) radio reception and monitoring as a hobby. The monthly bulletin "Australian DX News" is a primary source of DX information for Electronics Australia's "Shortwave Scene" and covers shortwave broadcast, medium wave and utility listening, Write for details, enclosing a 30c stamp to ARDXC, PO Box 67 Highett, Victoria 3190 or PO Box 79 Narrabeen, NSW 2101.

VALVES BRAND NEW, 65c each, 6DQ6A, 6GV8, 6GW8, 6JW8, 6U9, 6X9, 6Y9, 6DX8, 6DT6, 6ES8, most other types avail, except 6AL3, 6BL8, 6CM5, type 1S2 30c each, plus post or COD, PHILIPS PM5509 Pal TV pattern Gen, cost over \$800, sell for \$375. Tweed TV, 6 Machinery Dr. Tweed Heads (075) 36 1983.

\$275. FRG-7. Receiver as new condition. R. Dell. War Veterans' Home. Yass 2582.

RIBBON CABLE — 10 way 0.1in centres 0.6mm solid core ideal PCB interconnections — 69c/mtr + 80 c pp. SAE for sample and bulkrates. JATRONICS, PO Box 31 Engadine 2233.

SPEAKER BOXES. Hand-made, excellent acoustically. Write: Sherwood Electronics, PO Sherbrooke 3789.

VIDEO TAPE, 2 inch 2600ft, \$5 each, Ampec erase head with rollers \$15: all good cond. Vacuum Pumps, rotary with pulley whl, Edwds 1550, .005 mm \$55. Merc. diff, small glass Vitrasil C36-127, with Merc., \$80. Paladm., leak detector Edwds, LT4A, with head \$45. Marconi Q meter TF329G, 50kHz-50MHz, (turret) \$55. Marconi Audio Wave Analyser TF455D/1 (hetro dyne), both good cond. with hardbooks. Recorders, pen, toldos, lamp, all with rolls, write list. Disc Cutter with Gramp amp and head, buyer turntable, \$75. S. Dekker Box 437, Gawler, \$A 5118.

"OLDER HI-FI GEAR UPDATED. We can restore your valve or solid state equipment to as new condition, or modify it to improve its performance, possibly up to current state of the art! Allen Wright Electronics, 13 Wentworth Ave. Sydney. Ph. 233 4833.

DISPLAY ADVERTISEMENTS IN MARKETPLACE are available in sizes from a minimum of 2cm x 1 col rated at \$11 per col cm.
CLASSIFIED RATES \$2 per line per insertion payable in advance. Minimum two lines.


CLOSING DATE is six weeks prior to the on-sale date. Issues are on sale the first Monday of each

ADDRESS all classified orders, copy, enquiries, etc., to: The Advertising Manager, ELECTRONICS Australia, Box 162, Beaconsfield 2014.
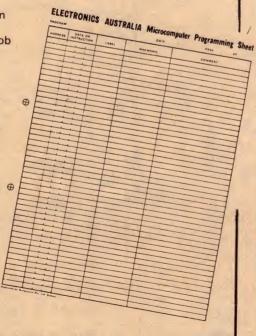
# If you program microprocessors, these sheets are for you

Writing microprocessor programs on blank or plain ruled paper is messy and time consuming. To make the job easier, Electronics Australia has produced these custom-designed programming sheets for use with virtually any microprocessor system. The sheets feature columns for a 4-digit address, up to six digits of instruction code or data, labels, mnemonics, and comments. There is space for 46 lines per sheet, and the sheets are provided with space for program title, date and sheet number. They are also punched for filing in a standard ring binder. All for less than 5 cents per sheet, posted!

PRICED AT \$2.00 FOR 50 SHEETS (plus 40c for postage anywhere in Australia)



Available only from Electronics Australia, 57 Regent St., Sydney (P.O. Box 163, Beaconsfield, NSW 2014)

### **OUR LATEST HANDBOOK PROJECTS &** CIRCUITS

**NUMBER TWO** 



### 27 DO-IT-YOURSELF PROJECTS FROM **ELECTRONICS AUSTRALIA**

You can't afford to miss out on this exciting new book from "Electronics Australia". Here are just a few of the projects it contains: remote TV headphones, multi-band vertical aerial, roulette wheel, radar burglar alarm, model train control, voice-operated relay, transistor tester, water level alarm ... plus many more. Get your copy now!

Available from:

"Electronics Australia", 57 Regent St, Sydney. PRICE \$3.00 OR by mail order from "Electronics Australia", PO Box 163, Beaconsfield, 2014. PRICE \$3.60.

# TELEVISION REPLACEMENTS

REAR 139 UNION ROAD, SURREY HILLS, 3127 PHONE: 89 1019

### WHERE THE TELEVISION TECHNICIANS MEET.

### GOLDRING ESTOH STEREO MAGNETIC CARTRIDGE

FS70S Output Channel Separation Compliance Channel Balance Tip Mass Tracking Weight

Tracking Angle

Stylus

Weight

Frequence Response 15 HZ - 25,000 HZ 9 M.V. @ 5 cm./sec. 20 D.B. 10 x 10 - 6 cm./dyne within 1.5 D.B. @ 1,000 HZ 0.8 milligrams 1 — 2.5 grams 15° Conical Diamond 5 grams



### INSTRUMENT CASE

The T.V.R.1 is an attractive, versatile moulded case which is suitable for housing a wide range of electronic equipment such as:

Power Supplies Signal Generators Digital Clocks Amplifiers, Tuners, etc. Overall dimensions:

51/2 x 51/8 x 23/4 Colours: Blue-Grey, White, Green, Black, Red.



only \$3.22

### A & R MULTI-TAP TRANSFORMERS

2155 TRANSFORMER 240V to 1.0, 1.2, 2.0, 2.2, 2.4, 3.1, 3.2, 4.1, 5.1, 5.5, 6.3, 6.5, 7.5, 8.5, 8.7, 9.5, 12.6, 15.0 Volts at 1 Amp maximum. Great value at only \$7.65. For a great choice of voltages, see all the A & R multi-

tap transformers at Television Replacements!



Introducing, the amazing, remarkable, the TM/13 Hills UHF/CB beam antenna

### BASIC SPECIFICATIONS ELECTRICAL

Nominal Impedance .... 50 ohms Power Handling Cap . . . . 5 Watts Input Termination . . . . . Co-Axial 13.1 Bandwidth . . . . . . . . . . . . . . . . . 10% Forward Gain . 15db (Ref. Dipole)

ONLY \$28.75

Also a great range of television aerials ALL PRICES INCLUDE SALES TAX.



136 VICTORIA RD MARRICKVILLE, NSW 2204

# **ELECTRONICS CENTRE**

### SUPER SPECIAL

12V 1.2AH RECHARGEABLE BATTERIES (2 SEPARATE 6V BATTERIES FOR SERIES CONNECTION)



PP NSW — \$1.75 INTERSTATE — \$2.50

COMPLETE WITH 240V AC PLUG-PAK BATTERY CHARGER, INCLUDING DIODES: 6V 1.2AH RECHARGEABLE BATTERIES \$4.95 EA PP NSW 80c. INTERSTATE \$1.20 THE ABOVE GEL-CELL BATTERIES ARE IN FULLY SEALED, HIGH IMPACT MOULDED CASES 318in x 78in x 2in

RED ROTATING **DISTRESS BEACON** REDUCED TO CLEAR

6V

12 VDC

240 VAC

\$7.75

\$14.75

IN A CAR, TRUCK OR BOAT EMERGENCY. THIS COULD SAVE

Used by bushfire brigades and civil defence organisations. Discos. NB. 240VAC model is supplied with transformer and rectifier, but no case for

P.P. NSW 90c, interstate \$1.60.

### **BRAND NEW 1-C**

UA301. UA741. UA723. UA709. 7450. 7451. 7490. 10 FOR \$2.50. 555. 10 FOR \$3.00. LM382 4 FOR \$6.00. P.P. NSW 75c. INTERSTATE \$1.25.

### 1 MA. FSD PANEL METER



38 M/M SQ. V-U SCALE, \$1.35 EA. 2 FOR \$2.00, P.P. NSW 80c, INTERSTATE \$1.25.

### RRAND NEW **TRANSISTORS**

All top quality, clearly marked, guaranteed.

BC549, BC558, BC547, BC177, 2N4248, 2N4250, AY1110, TT638A, TT1002.

10 for \$1.75. BC639/640, 10 for \$2.75. BD135/136, 10 for \$3.95. 2N3055, 10 for \$6.75. 2SD200-BU205, 4 for \$7.00. BUX80, 4 for \$19.00.

P.P. NSW 75c, interstate \$1.25.

#### MORILE TROLLEY IDEAL FOR COMPUTER STAND



Brand new in cartons. On 4 heavy duty castors. 101 uses. sq section mat black steel finish 23%"H 23" L 16".

\$23.50

P.P. NSW, \$2.00. INTERSTATE \$3.50.

3 WATT WIRE WOUND



250HM POTS. SINGLE 75c EA. 10 for \$6.00. TANDEM \$1.50 EA. 10 for \$12.00. P.P. NSW 80c. INTERSTATE

### VERNIER DIAL S

46 M/M, 70 M/M, 100 M/M. DIA. 8.1

\$2.95 EA.

### GOLD PLATED

14 DIL. LOW PROFILE 1 — SOCKETS, 10 FOR \$2.26, P.P. 75c.

### A1 QUALITY **FIBREGLASS** P-C BOARD

oz. 1/16" thick, single-sided super smooth surface. 22½" x 456". 10 for \$6.00. P.P. NSW \$1.50. INTERSTATE \$2.75. 14%" x 13" \$2.50 EA. P.P. 80c OR 5 FOR \$10.00. P.P. NSW \$1.50. INTERSTATE \$2.75.

### CERAMIC INSULATORS

Egg. 1¼"x'⁄4", 10 for \$3.99, P.P. NSW 90c, interstate \$1.50. High power stand-off, 4" long flange dia. 3½", \$3.50, P.P. NSW 90c, interstate

Feed-through 31/2" x 11/4", \$1.50. P.P. NSW 75c, interstate \$1.25.

### SERVICE

Moderate charges — Repairs guaranteed. Radios, Tape Recorders, Cassettes. Amps.

HEAD

BOOM-MIC



\$9.95


With remote footswitch, plugs, cables, quality guaranteed. Both hands are free. Hearing not effected. P.P. \$1.50.

# Electronics is going digital. This book can help YOU go right along with it:

Electronic equipment now plays an important role in almost every field of human endeayour. And every day, more and more electronic equipment is "going digital".

Even professional engineers and technicians find it hard to keep pace. In order to understand new developments, you need a good grounding in basic digital conmcepts, and An Introduction to Digital Electronics can give you that grounding. Tens of thousands of people engineers, technicians, students and hobbyists - have used the first and second editions of this book to find out what the digital revolution is all about.

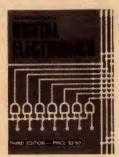The new third edition has been updated and expanded, to make it of even greater value. The author is Jamieson Rowe, Editor of "Electronics Australia" magazine, a qualified engineer and experienced technical writer.



### **ONLY \$3.50**

(PLUS PACKAGE AND POSTAGE)

### Here are the chapter headings:

- 1. Signals, circuits and logic
- 2. Basic logic elements
- 3. Logic circuit "families"
- 4. Logic convention and laws
- 5. Logic design: theory6. Logic design: practice
- Numbers, data & codes
- 8. The flipflop family
- 9. Flipflops in registers
- 10. Flipflops in counters

- 11. Encoding and decoding
- 12. Basic readout devices
- 13. Multiplexing
- 14. Binary arithmetic
- 15. Arithmetic circuits
- 16. Timing & Control 17. Memory: RAMs

  - 18. ROMs & PROMs
- 19. CCD's & magnetic bubbles Glossary of terms

Available from "Electronics Australia", 57 Regent St, Sydney. PRICE \$3.50 OR by mail order from "Electronics Australia", PO Box 163, Beaconsfield 2014. PRICE \$4.10.



Subscription Rates \$18.00 per year within Australia. \$A21.00 per year

Make sure you receive every copy of the magazine by ordering it from your newsagent or the publisher For publisher subscriptions post this coupon, with your remittance, to Electronics Australia Subscription Dept., John Fairfax & Sons Ltd, GPO Box 506, Sydney, 2001 Subscription will start with first available

Postcode									E	no	ele	)5(	ed	is	3					fe	or					y	ea	rs
Address						ċ										 												
Name	•	. !	•	•	٠	•	•	•	 •	•	•	•	•	•	•	 		•	•									

### **ADVERTISING** INDEX

A & R Soanar	8, 108
ASP Microcomputers	76
Academy of Sound Recording Engineers	31
Ace Radio	119
Acoustic Research Australia	26
All Electronic Components	58
Ampex Australia Pty Ltd	IFC
Amtex Electronics	40
Audiosound	86
Auditec Australia	52
Audio Telex Communications Pty Ltd	15
BWD Electronics Pty Ltd	
Bail Electronic Services	103
Bright Star Crystals	101
Cash-More Sound Systems Pty Ltd	32
Cema (Distributors) Pty Ltd	47
Classic Radio	112
Convoy International Pty Ltd	28
Deitch Bros	72
Dick Smith Electronic Group 7, 20,	
54, 55, 9	
Diggerman Electronics	1.18
Direct Disposal Trading Co.	68
E. D. & E. Sales Pty Ltd	58
E & M Electronics	83
Electrocraft Pty Ltd	76
Electronic & Semi Conductor	
Disposals	81
Electronic Agencies	64
Ellistronics	52
Enson Equipment	73
Hagemeyer (Aust.)	ОВС
Hurtle Webster Pty Ltd	65
Lanthur Electronics	46
Linear Electronics	71
McGills Newsagency	115
Marconi School of Wireless	.73
National Panasonic (Australia) Pty Ltd	IBC
Non-Linear Systems (Australia) Pty Ltd Paris Radio Electronics	24
Pennywise Peripherals	84
Philips	85
RCS Radio	12, 48
Radio Despatch Service	25
Radio Parts Group	71
Rod Irving Electronics	97 79
Roysten Electronics	
School of Audio Engineering	33
Sontron Instruments	85
Soundring Distributors	32
Stotts Technical College	
	23
Superscope (A'asia) Pty Ltd	34
Fandy International Electronics	62
Tasman Electronics	33
Television Replacement	
Service Pty Ltd	119
The Byte Shop	85
/icom International 2	4, 102
/idio Technics	113
Varburton Franki Ltd	2
Vireless Institute of Australia	
Australia	104



**Technics** rfectionists erfectionists.

In 1970 Technics introduced the ultimate turntable drive method . . . the direct-drive principle. In developing phases our first direct-drive turntable was succeeded Both feature a pitch control of by a whole family of them. A major innovation was the quartz phaselocked servo electronics featured in the SP10 MK2, enabling great speed accuracy to be attained  $(\pm 0.002\%)$ . Its enormous torque and super fast start/stop action make it the choice of top broadcasting stations both in Australia and the rest of the world. Two newly released Technics models—the SL1300 MK2 and SL1400 MK2 (automatic and semi-automatic respectively) are totally quartz controlled drive turntables. You won't find any belts, gears or idlers in these. But

you will find our lowest wow and flutter ever (0.025% WRMS) and inaudible rumble (-73dB DIN B).

 $\pm 9.9\%$  on normal turntable speeds that can be obtained simply by the push of a button.

The pitch chosen is displayed in digital form by a LED readout. All controls are located on the front panel of the turntables and can be operated even with the dust cover down.

Technics MK2 series of turntables are just a few components in the new Pro. Series from Technics. Reliable as they are precise.



For a National Technics catalogue, please write to: National Technics Advisory Service, P.O. Box 49, Kensington, N.S.W. 2033

# THE JVC QUARTZ-LOCKED TURNTABLE.

First we invented it. Now we've made it more precise than ever.

The turntable evolution comes full swing with the introduction of the new Quartz turntable series. We introduced the first quartz-controlled turntable in 1974, and we've been improving our designs ever since. Including:

### Super Servo Frequency Generator


To detect minute variations in platter speed, and send corrective information to the electronic circuit controlling turntable rotation, it provides near-perfect speed accuracy And, our Super Servo is factory-set for years of accurate, dependable use.

### **Direct Drive DC Servomotor**

For quick-start/stop and high-torque operation. Our powerful motor drive system and its companion speedmonitoring circuits reduce wow-andflutter and speed drift nearly to the vanishing point.
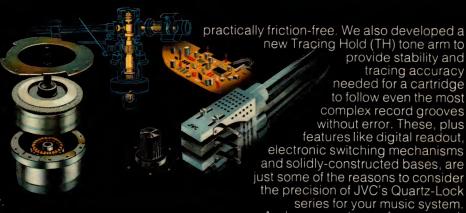
### Gimbal Support and TH Tone Arm

Our exclusive unipivot gimbal support holds the tone arm firmly, yet is





tracing accuracy needed for a cartridge to follow even the most complex record grooves without error. These, plus features like digital readout, electronic switching mechanisms and solidly-constructed bases, are just some of the reasons to consider the precision of JVC's Quartz-Lock series for your music system. And you can choose from manual, semi-automatic or totally-automatic models—JVC's most comprehensive turntable line ever. See them at your JVC dealer soon.

For details on all JVC Hi-Fi Equipment write to the JVC Advisory Service. Post Office Box 307. North Ryde, N.S.W. 2113



provide stability and

the right choice

